

# Bipolar Junction Transistor (BJT)

---

1. Introduction to the BJT ✓
2. Principles of Operation of the BJT ✓
3. Analysis of the BJT ✓
4. Large Signal Model of the BJT ←
5. Operating Point of BJT Circuits
6. Signal Amplification in Amplifiers
7. Small Signal (Simplified Hybrid- $\pi$ ) Model of the BJT
8. Full Hybrid- $\pi$  Model

## 4. Large Signal Model of the BJT

For the npn BJT in the forward active region of operation:


- Collector current  $i_C = I_S e^{v_{BE}/V_T}$  (3.7)

where  $I_S = qA \frac{D_n}{w_B} \frac{n_i^2}{N_{AB}}$  (3.8)

- Base current  $i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$  (3.13)

- $i_C = \beta i_B$  (3.14)

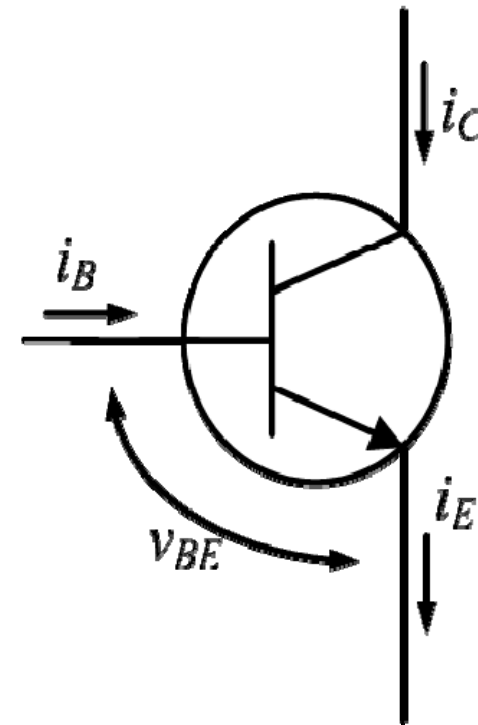
where  $\beta = \frac{D_n}{D_p} \frac{L_p}{w_B} \frac{N_{DE}}{N_{AB}}$  (3.11)


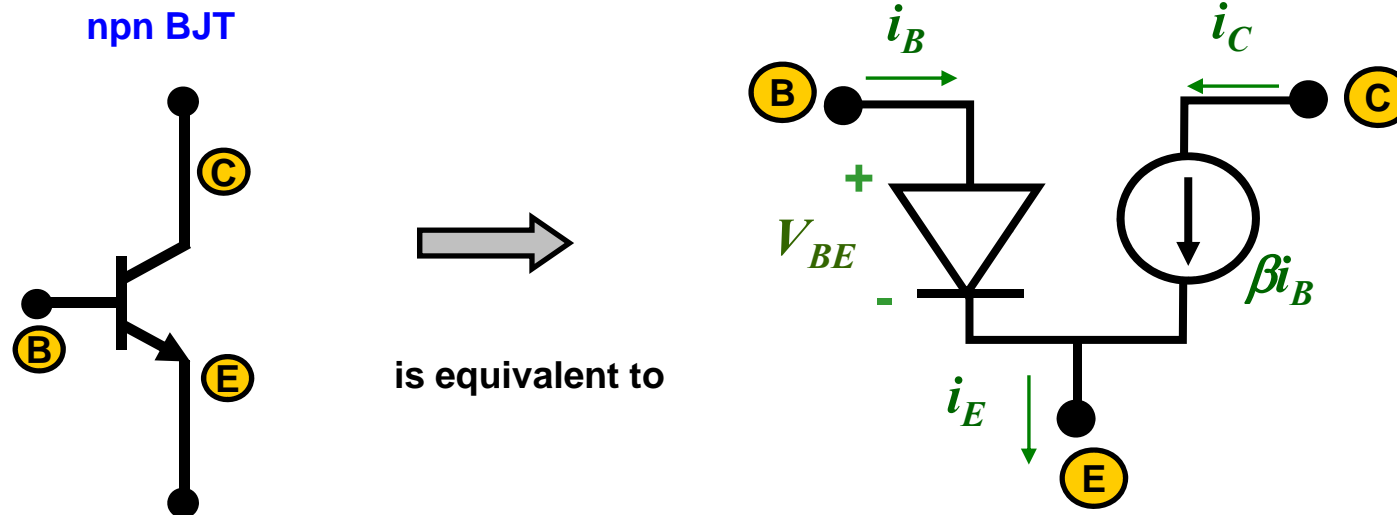
## 4.1 npn BJT


In forward active operation, we model the npn BJT using the following equivalent circuit :

- $i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$  (3.13)  $\Rightarrow$  diode.
- $i_C = \beta i_B$  (3.15)  $\Rightarrow$  dependent current source



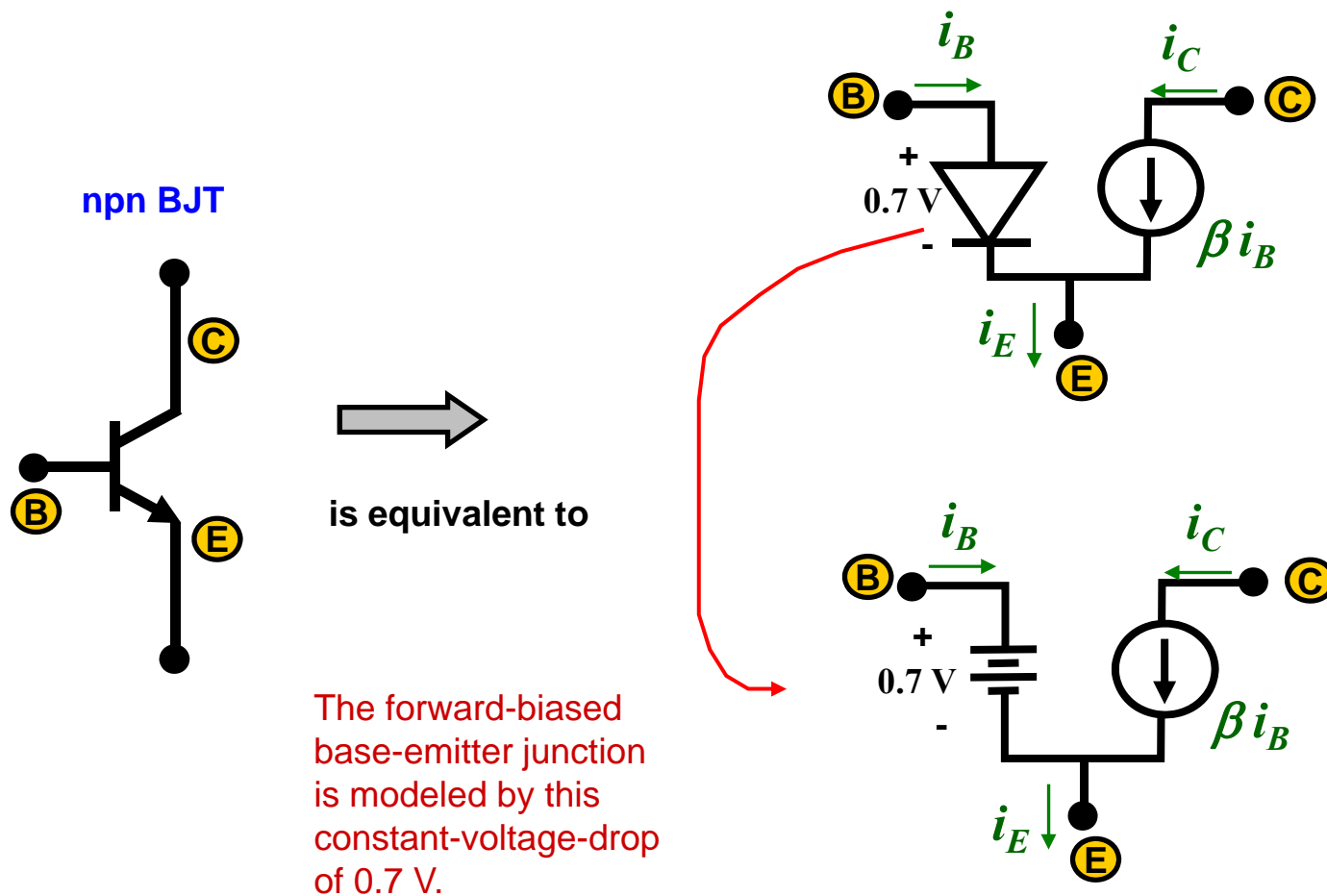
## 4.1 npn BJT

- The forward biased p-n base-emitter junction of the npn bjt has a voltage drop of  $\sim 0.7$  V.



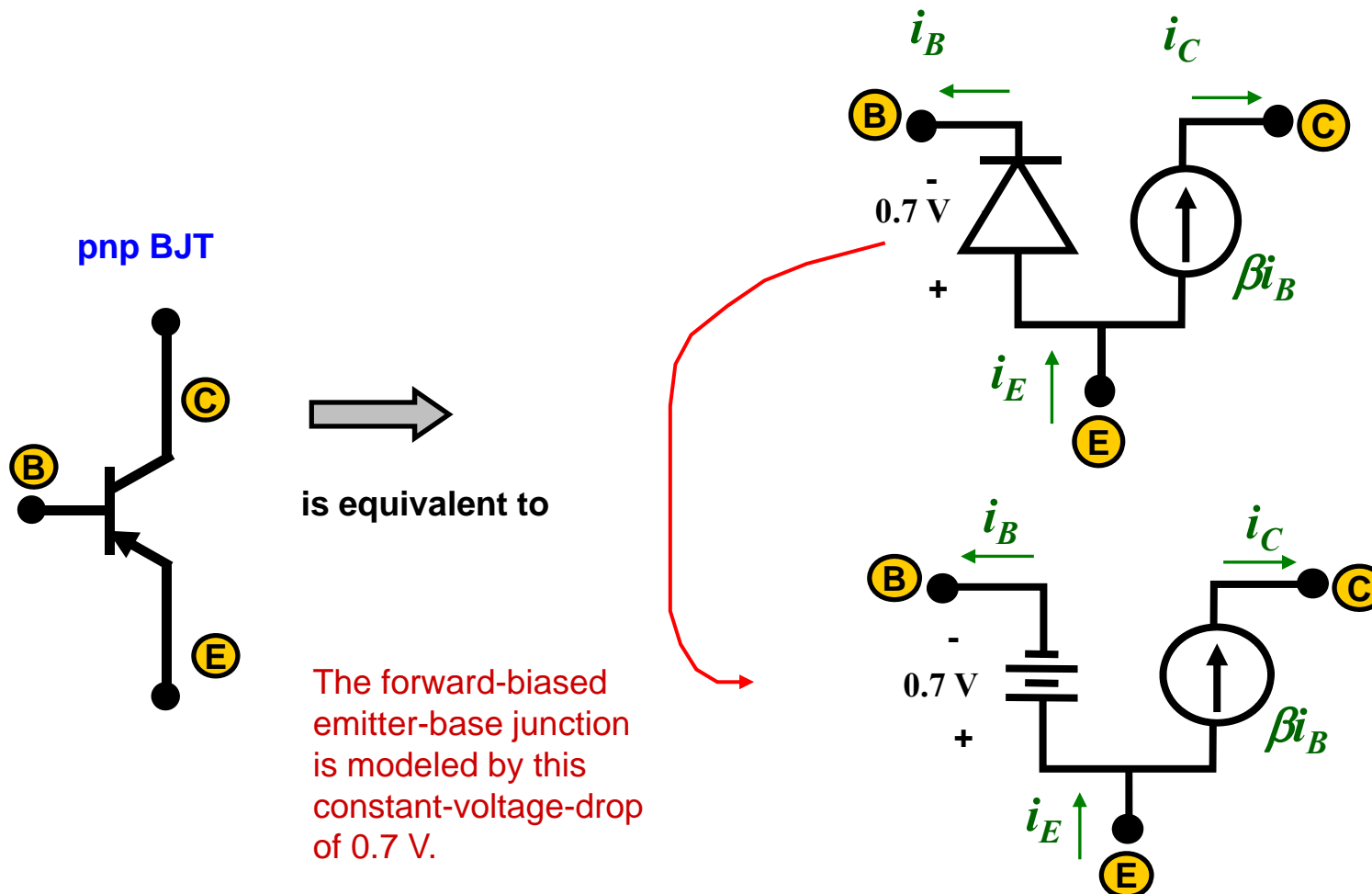
## 4.2 pnp BJT

- Equivalent circuit model of the pnp bipolar junction transistor :
- The polarities of the voltages, and the directions of the currents, are opposite to those of the npn bjt.




# Bipolar Junction Transistor (BJT)

---

1. Introduction to the BJT
2. Principles of Operation of the BJT
3. Analysis of the BJT
4. Large Signal Model of the BJT
5. Operating Point of BJT Circuits 
6. Signal Amplification in Amplifiers
7. Small Signal (Simplified Hybrid- $\pi$ ) Model of the BJT
8. Full Hybrid- $\pi$  Model

## 5. Operating Point of a BJT circuit

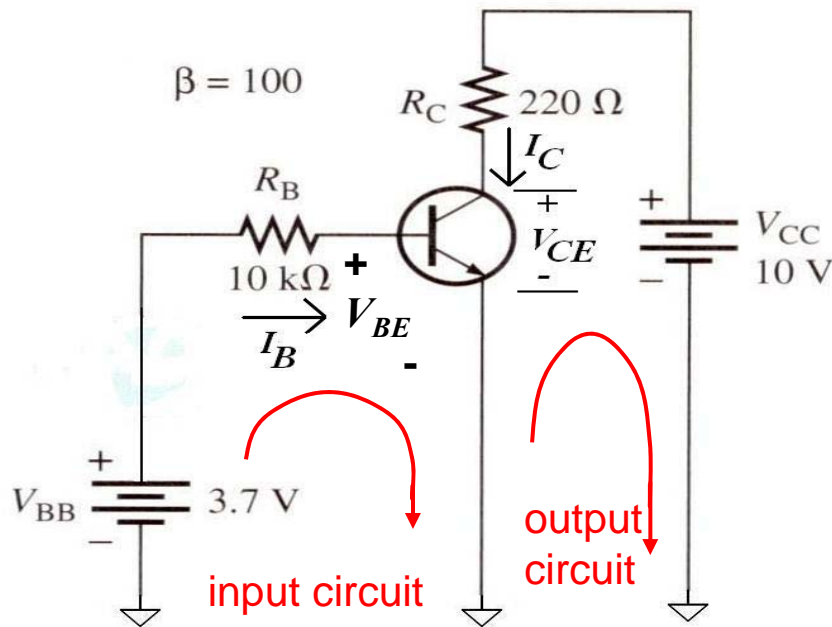

Assume that  $V_{BE} = 0.7 \text{ V}$



▪ Input circuit, KVL : 
$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{(3.7 - 0.7) \text{ V}}{10 \text{ k}\Omega} = 0.3 \text{ mA} = 300 \mu\text{A}. \quad (3.17)$$

▪ Output circuit, KVL : 
$$V_{CC} = I_C R_C + V_{CE} \quad (3.18)$$

Symbol for d.c. values (example):

$I_B$   
 capital letter      capital subscript

## 5. Operating Point of a BJT circuit

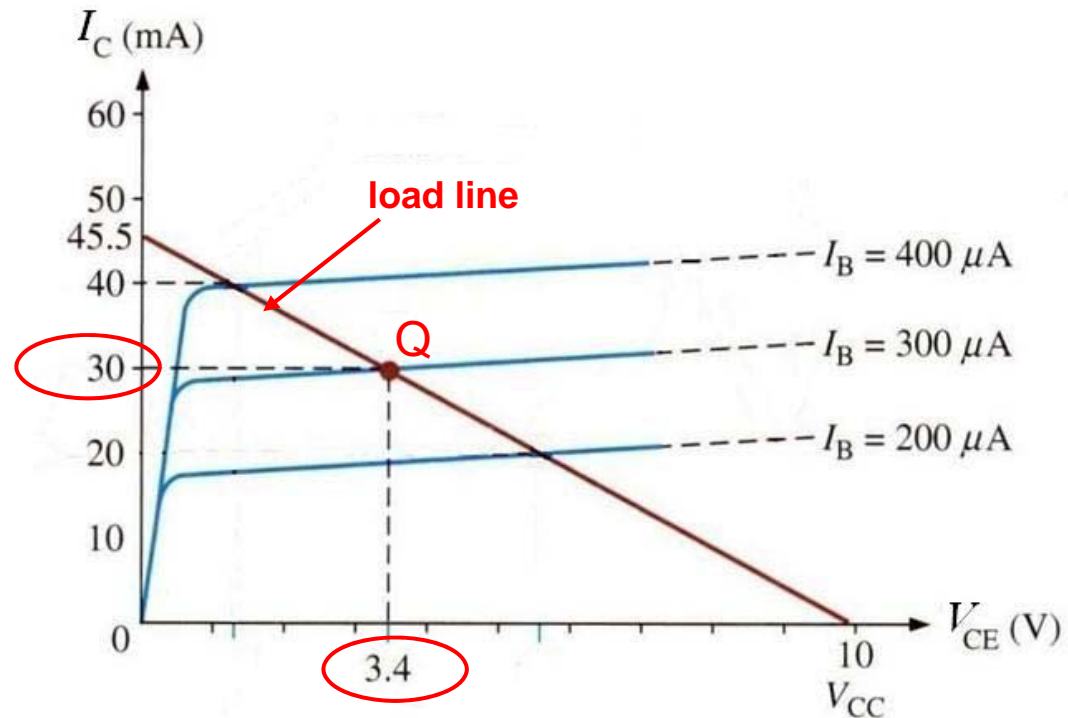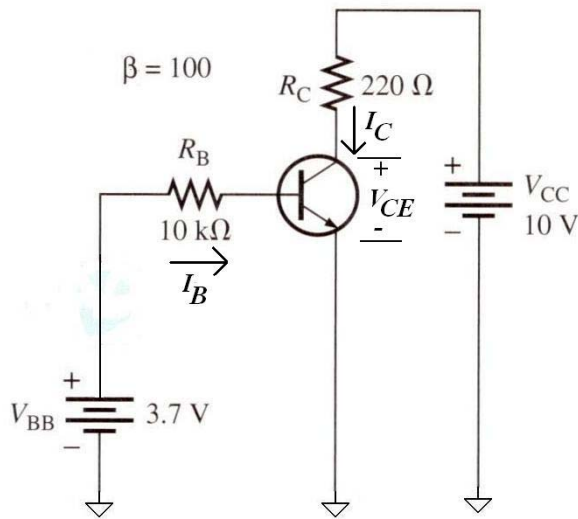


- By re-writing eqn (3.18), we have 
$$I_C = \frac{V_{CC} - V_{CE}}{R_C} \quad (3.19)$$
- At the operating point "Q",  $I_C = 30$  mA,  $V_{CE} = 3.4$  V.



# Calculation of Operating Point of BJT Circuits
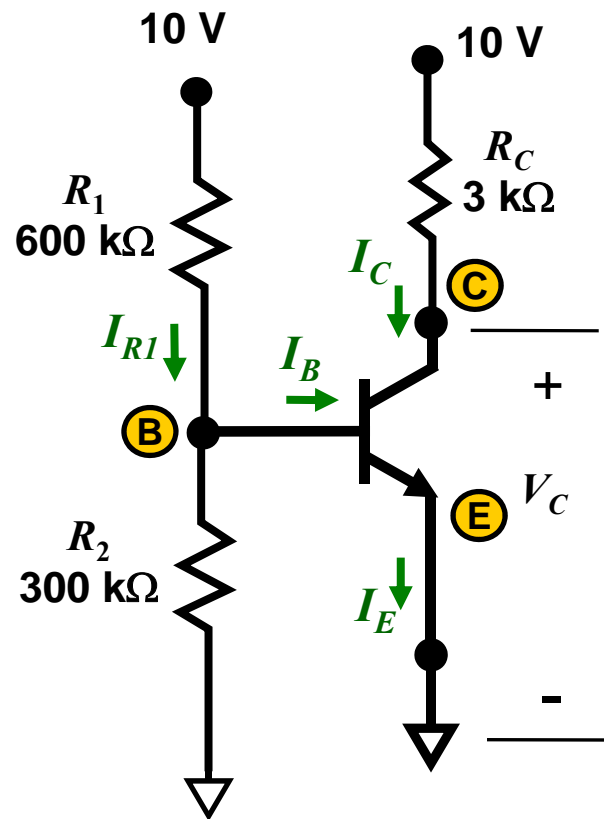
## Example 1 (Thevenin equivalent method).


Find the currents  $I_C$ ,  $I_B$ , and  $I_E$ , and the voltage  $V_C$  using an appropriate large signal model for the BJT, assuming that it is operating in the forward active region and has the parameter  $\beta = 100$ .



# Calculation of Operating Point of BJT Circuits
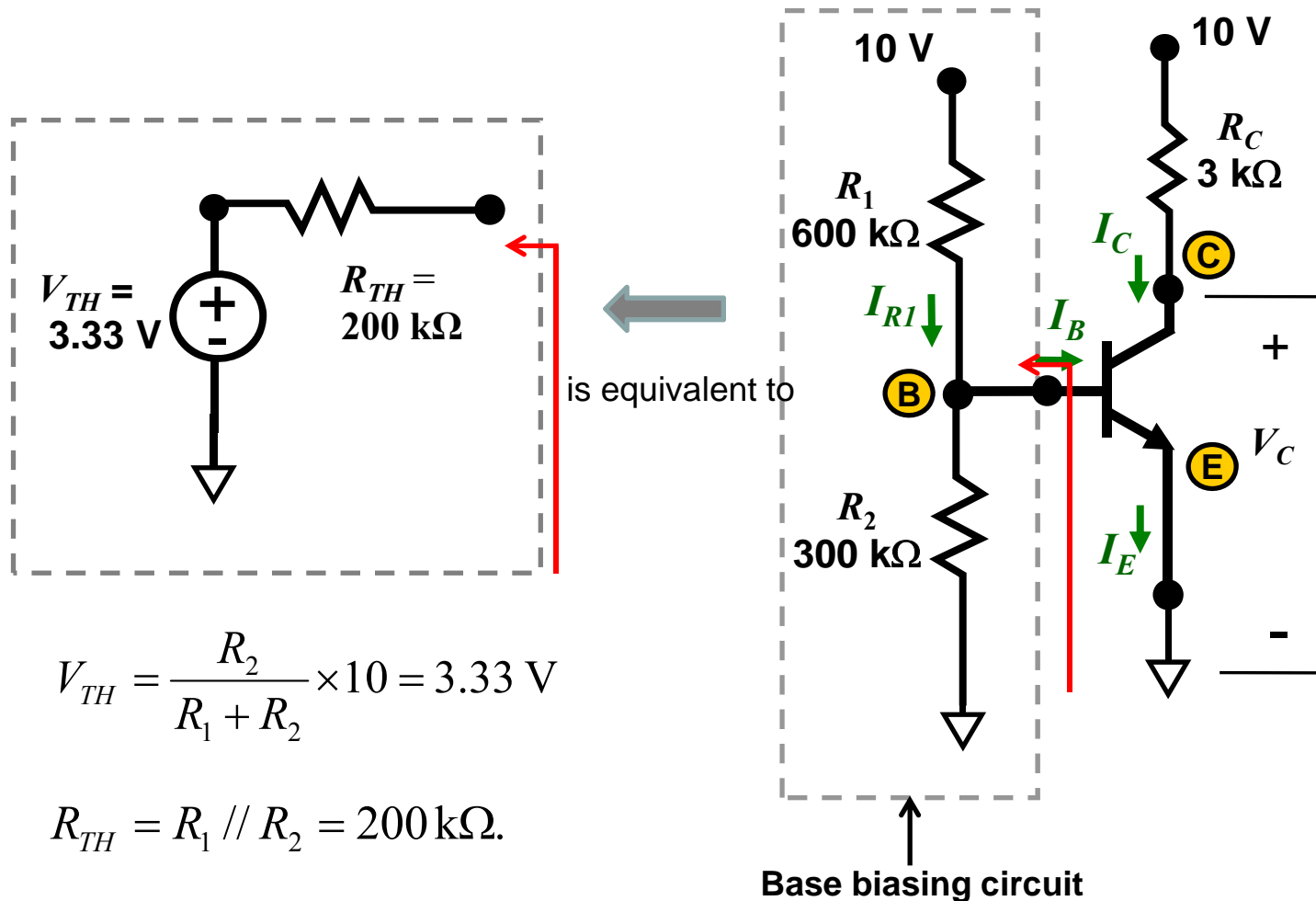
## Example 1 (Thevenin equivalent method) (contd.)

- First, we obtain the Thevenin's Equivalent Circuit of the base-biasing circuit, shown in the dashed grey box:




$$V_{TH} = \frac{R_2}{R_1 + R_2} \times 10 = 3.33 \text{ V}$$

$$R_{TH} = R_1 // R_2 = 200 \text{ k}\Omega.$$

# Calculation of Operating Point of BJT Circuits

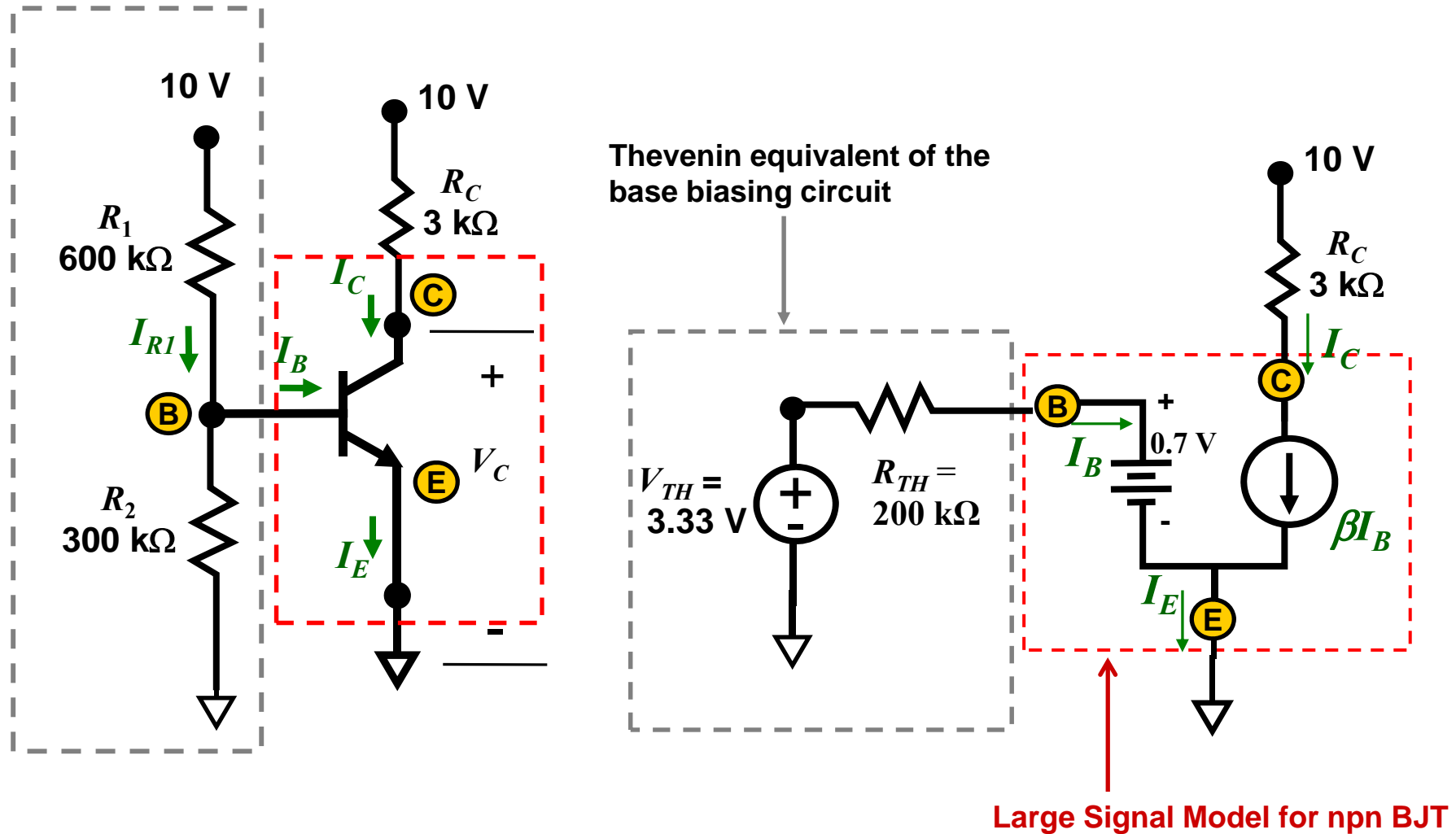
## Example 1 (Thevenin equivalent method) (contd.)

- Next, we replace the npn BJT with its large signal model.



# Calculation of Operating Point of BJT Circuits
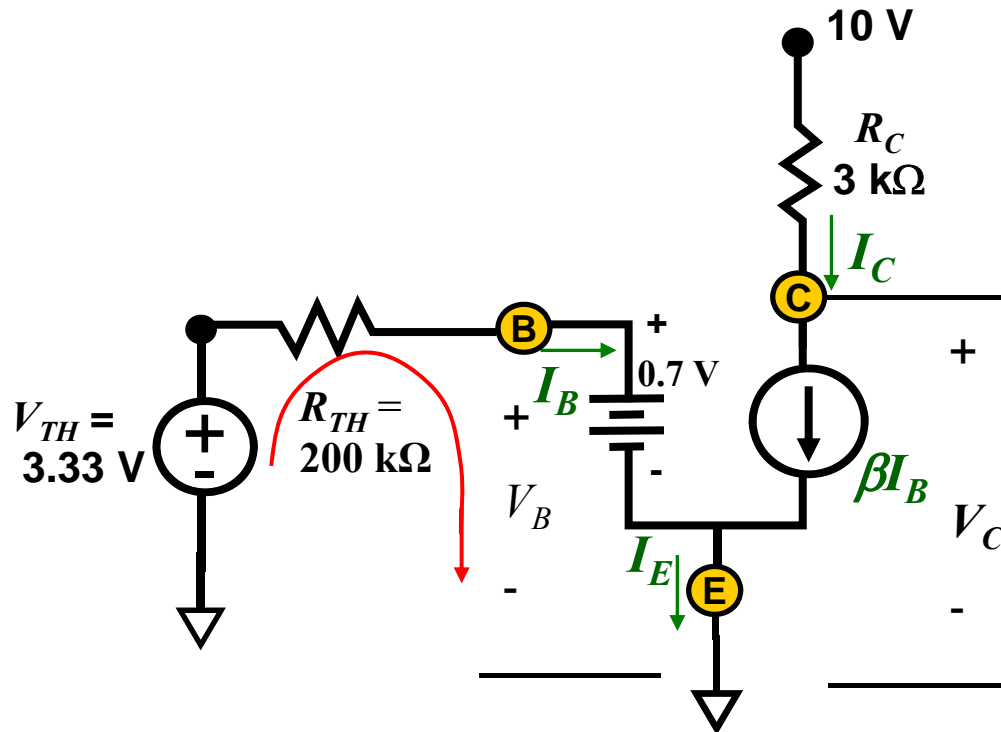
## Example 1 (Thevenin equivalent method) (contd.)



$$I_B = \frac{3.33 \text{ V} - 0.7 \text{ V}}{200 \text{ k}\Omega} = 0.0132 \text{ mA.}$$

$$I_C = \beta I_B = 100 \times 0.0132 \text{ mA} = 1.32 \text{ mA.}$$

$$I_E = (\beta + 1)I_B = 101 \times 0.0132 \text{ mA} = 1.33 \text{ mA.}$$

$$V_C = 10 \text{ V} - 3 \text{ k}\Omega \times (1.32 \text{ mA}) = 6.04 \text{ V.}$$

Check: Base voltage,  $V_B = V_{BE} = 0.7 \text{ V}$ .


Base-collector voltage  $V_{BC} = V_B - V_C = 0.7 \text{ V} - 6.04 \text{ V} = -5.34 \text{ V}$ ,

Since the base-emitter pn junction is forward biased, and the base-collector pn junction is reverse biased, the npn BJT is in operating in the forward active region.

# Calculation of Operating Point of BJT Circuits

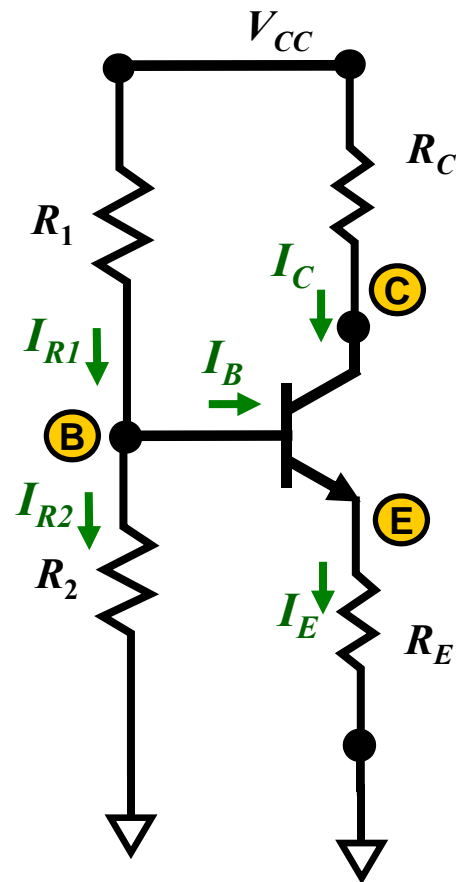
## Example 2 (Voltage divider method).

The circuit on the left has a  $V_{CC} = 20\text{ V}$ ,  $R_C = 5\text{ k}\Omega$ ,  $R_E = 1\text{ k}\Omega$ ,  $R_1 = 20\text{ k}\Omega$ , and  $R_2 = 3\text{ k}\Omega$ . The value of  $\beta$  for the BJT is 100. Determine the values of  $I_C$  and  $I_B$ .



# Operating Point of a BJT Circuit (Voltage Divider)

## Example 2 (Voltage divider method).

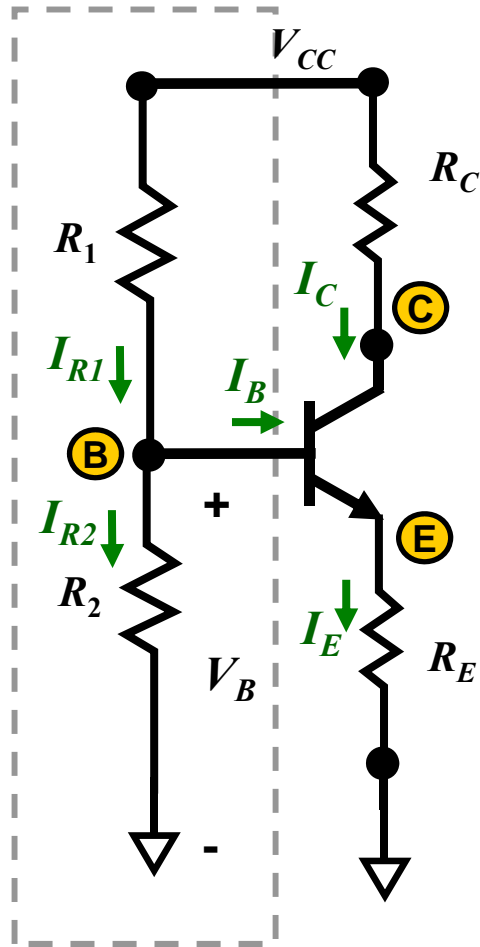


**Given :**  $V_{CC} = 20 \text{ V}$ ,  $R_C = 5 \text{ k}\Omega$ ,  $R_E = 1 \text{ k}\Omega$ ,  $R_1 = 20 \text{ k}\Omega$ , and  $R_2 = 3 \text{ k}\Omega$ .

- **Assuming** that  $I_B$  is small compared to  $I_{R1}$  and  $I_{R2}$ , we apply the voltage division rule to obtain

$$I_{R1} \approx I_{R2} \approx \frac{V_{CC}}{R_1 + R_2} = \frac{20 \text{ V}}{20 \text{ k}\Omega + 3 \text{ k}\Omega} = 0.87 \text{ mA}$$

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{3 \text{ k}\Omega}{(20 + 3) \text{ k}\Omega} 20 \text{ V} = 2.61 \text{ V}$$
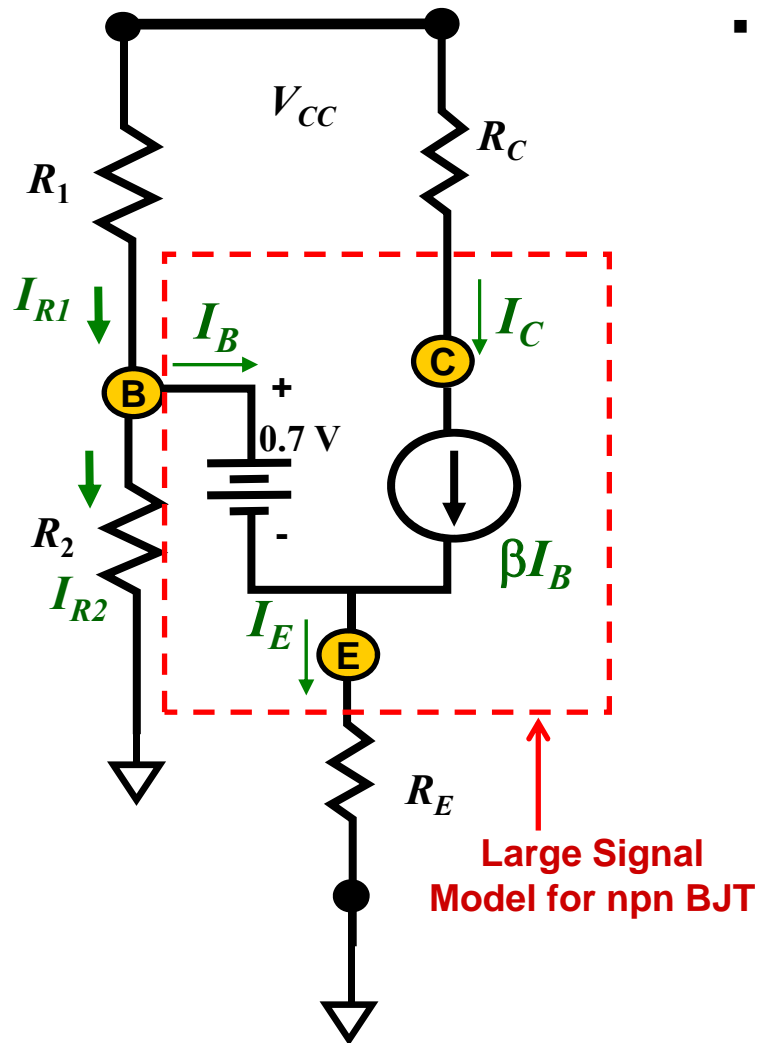
# Operating Point of a BJT Circuit (Voltage Divider)



- Replace the npn BJT with its large signal model.

$$V_E = V_B - 0.7 \text{ V} = 2.61 - 0.7 = 1.91 \text{ V.}$$

$$\text{Thus, } I_E = V_E / 1\text{k}\Omega = 1.91 \text{ mA.}$$

$$I_C = [\beta / (\beta + 1)] I_E = [100/101] \times 1.91 \text{ mA} = \mathbf{1.89 \text{ mA.}}$$


$$I_B = I_C / \beta = \mathbf{0.0189 \text{ mA} = 18.9 \mu\text{A}}$$

Check :  $I_B$  (0.0189 mA), is indeed much smaller than  $I_{R1}$  and  $I_{R2}$  (0.87 mA). Assumption is valid.

Note: If  $I_B$  is not small compared to the currents flowing through  $R_1$  and  $R_2$ , the voltage divider rule cannot be applied.

We would then to use the Thevenin's equivalent method.
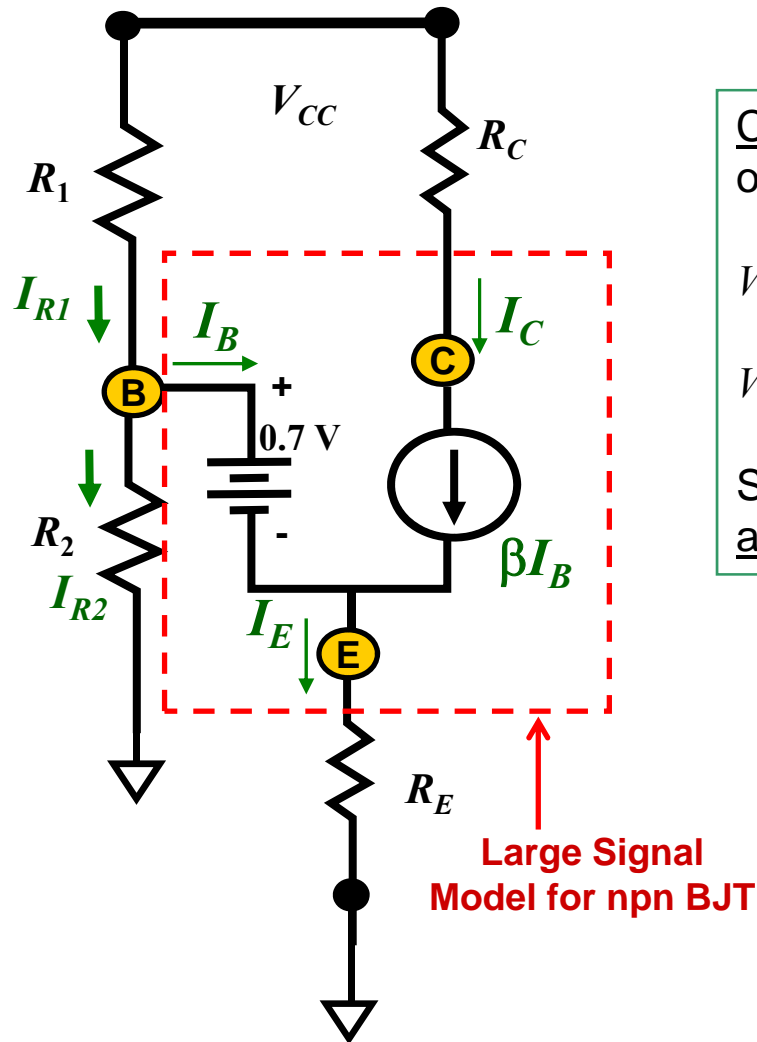
# Operating Point of a BJT Circuit (Voltage Divider)



Check that the BJT is in the forward-active region of operation :

$$V_C = V_{CC} - I_C R_C = 20 - 1.89 \text{ mA} \times 5 \text{ k}\Omega = 10.55 \text{ V.}$$

$$V_{BC} = V_B - V_C = 2.61 - 10.55 = -7.94 \text{ V.}$$

Since  $V_{BC} < 0$  and  $V_{BE} > 0$ , the BJT is in the forward active region of operation.




# Bipolar Junction Transistor (BJT)

---

1. Introduction to the BJT
2. Principles of Operation of the BJT
3. Analysis of the BJT
4. Large Signal Model of the BJT
5. Calculation of Operating Point of BJT Circuits ✓
6. Signal Amplification in Amplifiers ←
7. Small Signal (Simplified Hybrid- $\pi$ ) Model of the BJT
8. Full Hybrid- $\pi$  Model



## 6. Signal Amplification in Amplifiers

---

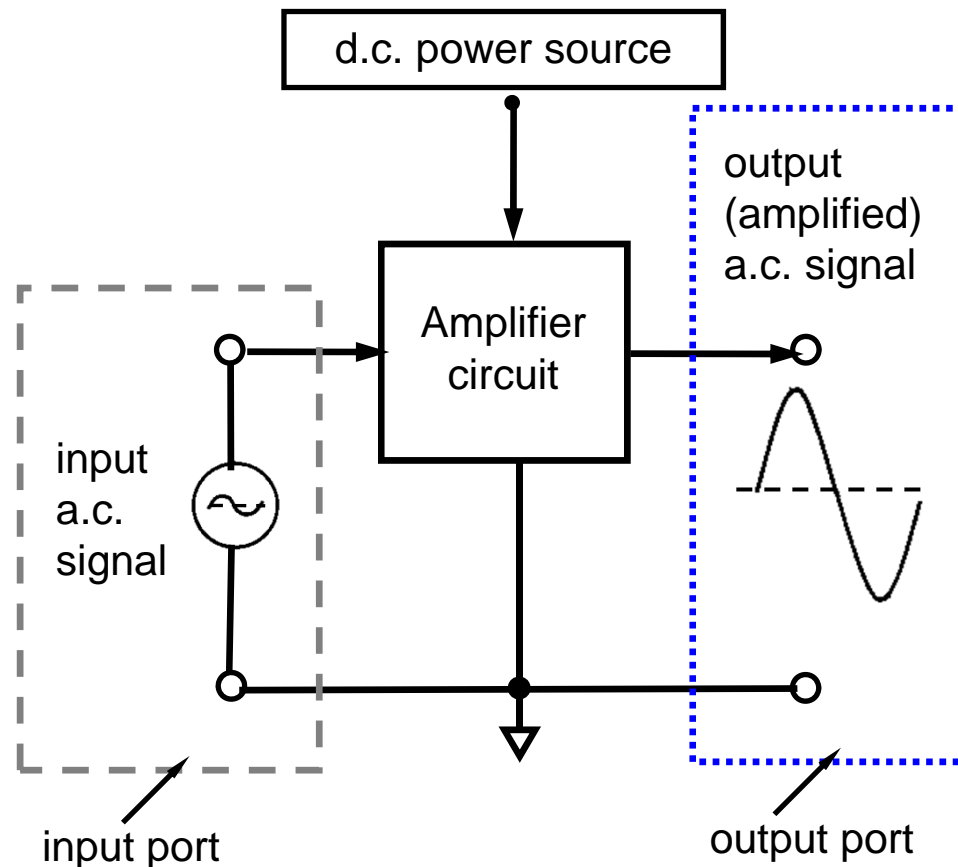

- The d.c. source supplies power to the amplifier, while the a.c. signal is applied to the input port .
- The transistor in the amplifier circuit acts as a control device, which controls the flow of power from the d.c. source, to produce an enhanced a.c. signal at the output port .
- The output a.c. signal is of the same waveform as the input a.c. signal, but is of larger amplitude (in current, voltage, or power).

# Signal Amplification in amplifiers

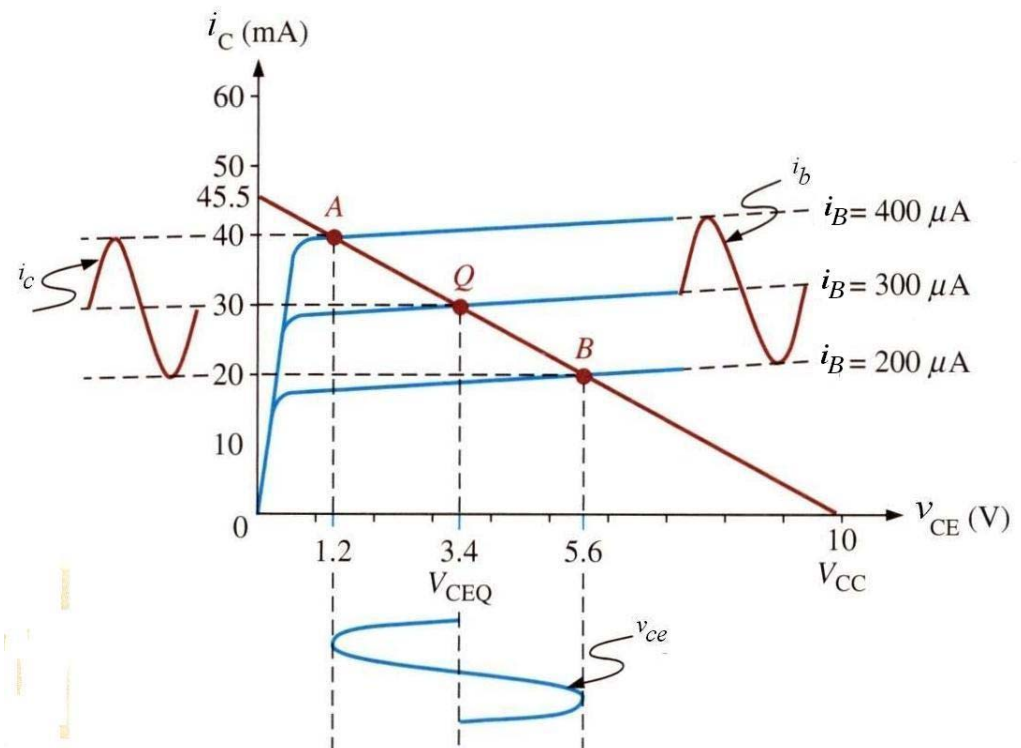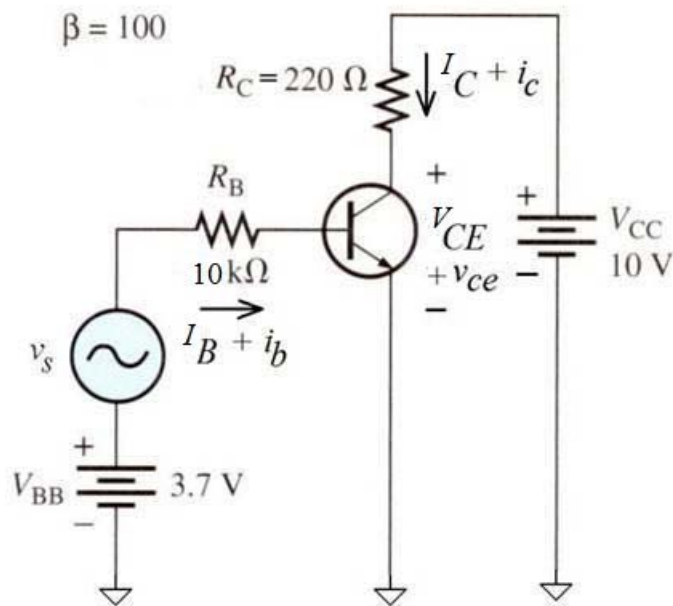

## Notations :


D.C. quantities, e.g.,  $I_B$  : capital letter, capital subscript.

Small signal A.C. quantities, e.g.,  $i_b$  : lower case letter, lower case subscript.

Total (instantaneous) quantities, e.g.,  $i_B$  : lower case letter, capital subscript



Example :  $i_B = I_B + i_b$

# Signal Amplification in amplifiers

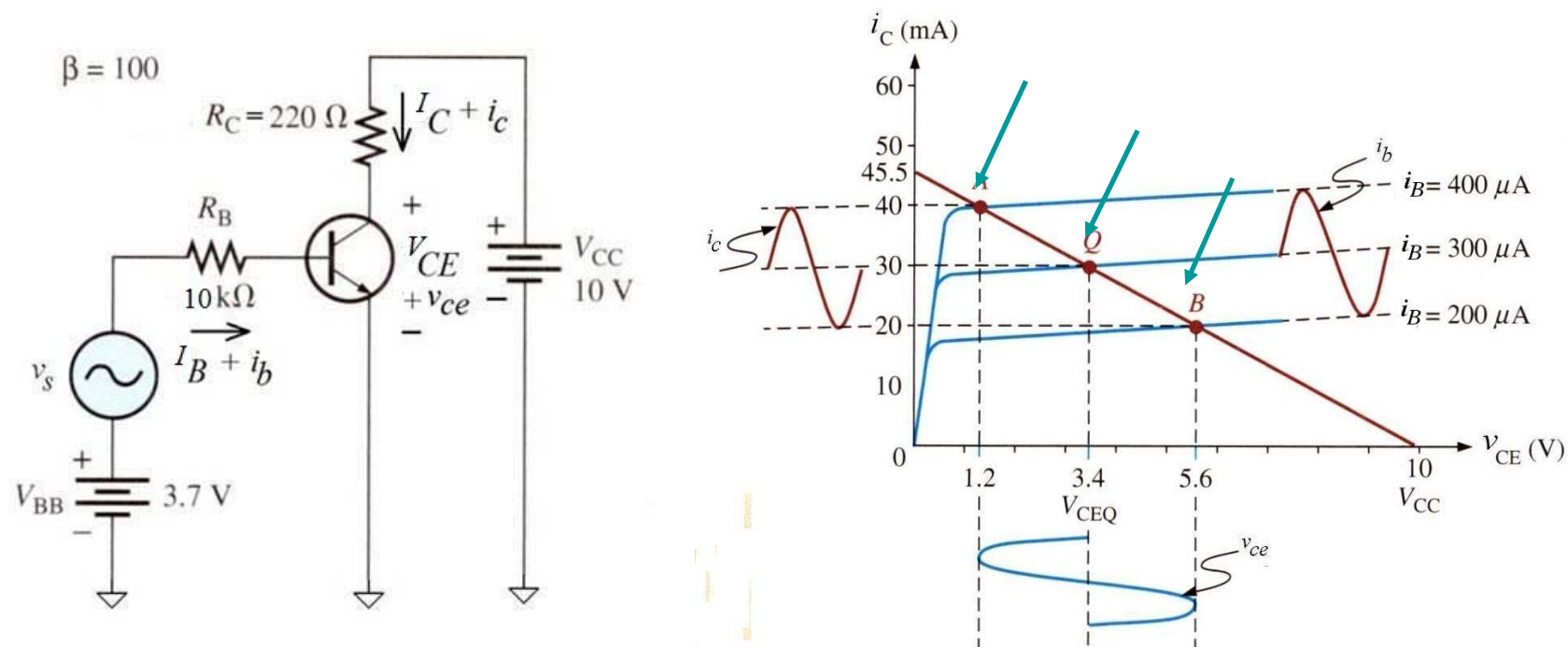

- When  $i_b = 0\text{ }\mu\text{A}$ ,  $i_B = I_B + i_b = 300\text{ }\mu\text{A}$ ,  $i_C = 30\text{ mA}$ , and  $v_{CE} = 3.4\text{ V}$ . (Point Q)
- When  $i_b = 100\text{ }\mu\text{A}$ ,  $i_B = I_B + i_b = 300\text{ }\mu\text{A} + 100\text{ }\mu\text{A} = 400\text{ }\mu\text{A}$ .  
 $i_C = 40\text{ mA}$ , and  $v_{CE} = 1.2\text{ V}$ . (Point A)
- When  $i_b = -100\text{ }\mu\text{A}$ ,  $i_B = 300\text{ }\mu\text{A} - 100\text{ }\mu\text{A} = 200\text{ }\mu\text{A}$ ,  
 $i_C = 20\text{ mA}$ , and  $v_{CE} = 5.6\text{ V}$ . (Point B)

# Signal Amplification in amplifiers

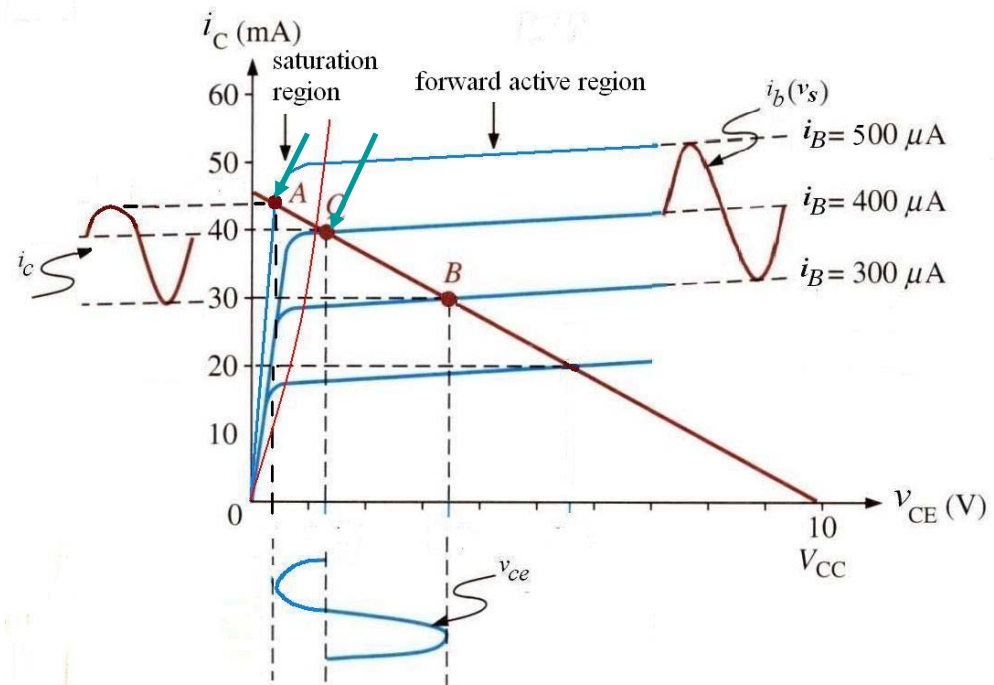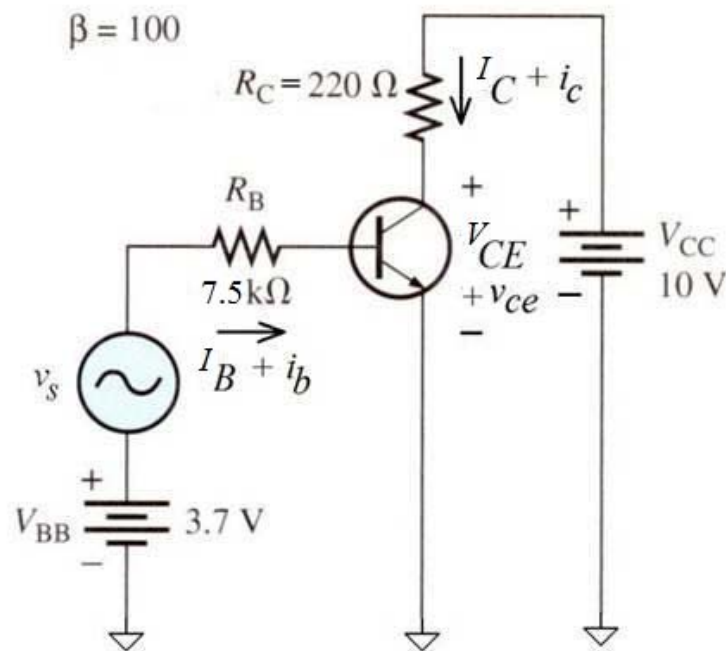


- D.C. base current  $I_B = (V_{BB} - V_{BE}) / R_B = 400 \mu\text{A}$ . Operating point at “Q”
- When  $i_b = 100 \mu\text{A}$ ,  $i_B = I_B + i_b = 500 \mu\text{A}$ ,

The intersection point between the load line and the BJT characteristics move to point “A”, where the BJT is no longer operating in the forward active region.

- The a.c. signal waveforms of  $i_c$  and  $v_{ce}$  are distorted.

# Signal Amplification in amplifiers

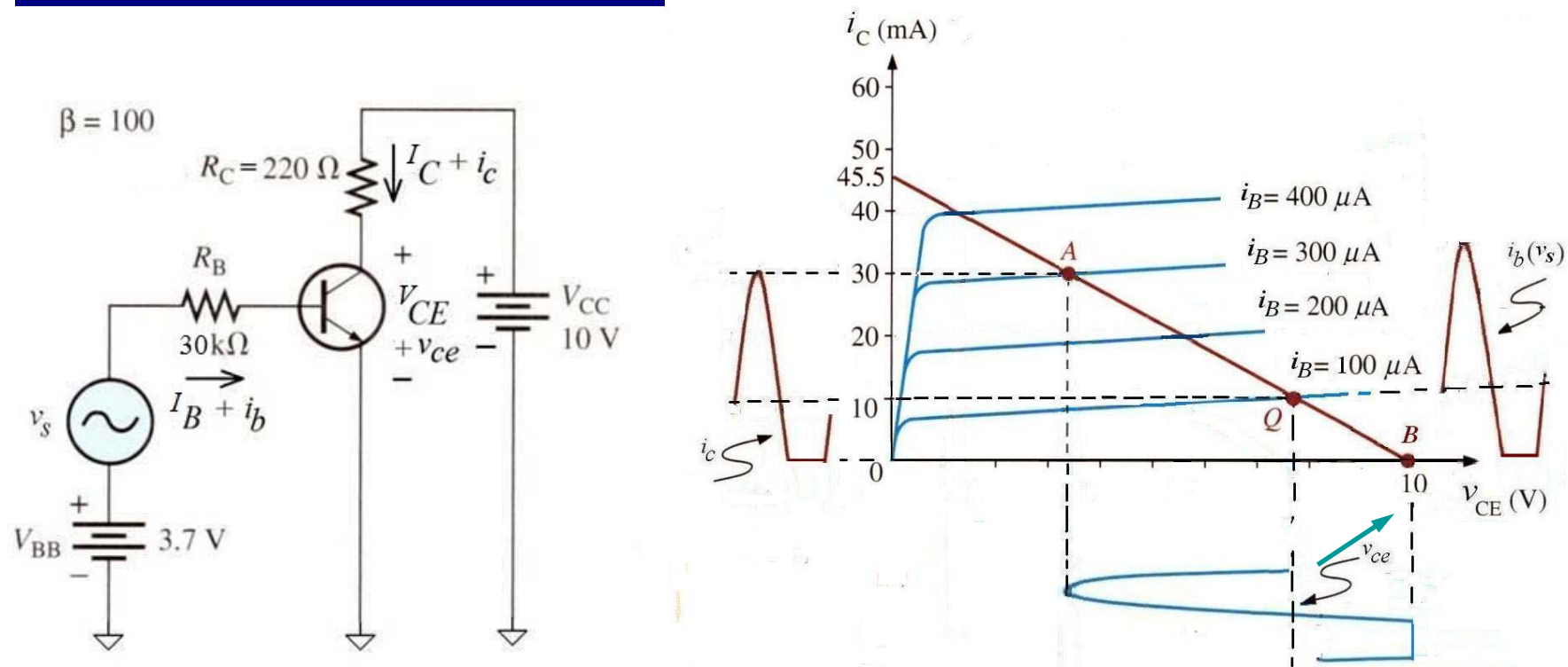

- D.C. base current  $I_B = (V_{BB} - V_{BE}) / R_B = 100\text{ }\mu\text{A}$ . Operating point at "Q"
- Assume that the amplitude of the a.c. base current  $i_b$  is  $200\text{ }\mu\text{A}$ .
- At some point during part of the negative half-cycle of the a.c. base current, the intersection point between the load line and the BJT characteristics is at point "B"
- The waveform of  $i_C$  is clipped as it cannot be negative.
- Similarly, the waveform of  $v_{CE}$  is clipped at  $10\text{ V}$  as it cannot exceed the power supply voltage.


# Bipolar Junction Transistor (BJT)

---

1. Introduction to the BJT
2. Principles of Operation of the BJT
3. Analysis of the BJT
4. Large Signal Model of the BJT
5. Calculation of Operating Point of BJT Circuits
6. Signal Amplification in Amplifiers ✓
7. Small Signal (Simplified Hybrid- $\pi$ ) Model of the BJT ←
8. Full Hybrid- $\pi$  Model
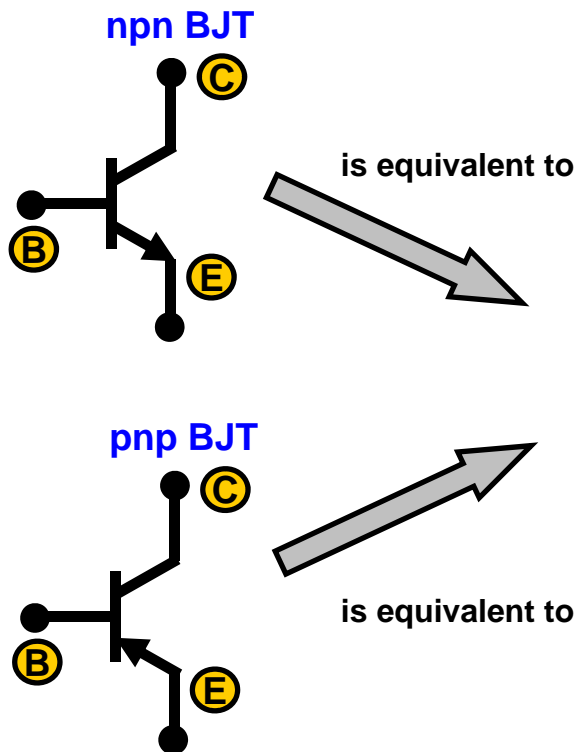
## 7. Small Signal (Simplified Hybrid- $\pi$ ) Model of the BJT


- To develop a small signal model of the BJT under **forward active region of operation**.
- We seek linear relationships among the **small signal a.c. components** of the base current, the collector current, the base-emitter voltage and the collector-emitter voltage.



$$i_C = i_C(v_{BE}, v_{CE})$$

$$\Delta i_C \approx [\partial i_C / \partial v_{BE}] \Delta v_{BE} + [\partial i_C / \partial v_{CE}] \Delta v_{CE}$$
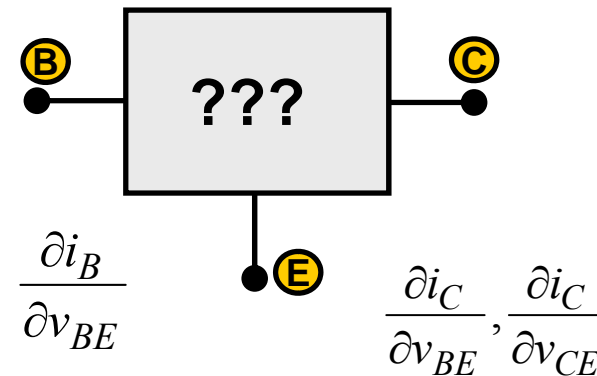
$$i_c = [\partial i_C / \partial v_{BE}] v_{be} + [\partial i_C / \partial v_{CE}] v_{ce}$$





# Transconductance $g_m$

---

- It has been shown previously\* that the collector current,  $i_C = I_S e^{v_{BE}/V_T}$
- At the d.c. operating point, the d.c. collector current,  $I_C = I_S e^{V_{BE}/V_T}$
- A linear relationship of small variations of the collector current,  $\Delta i_C$ , and the emitter-base voltage  $\Delta v_{BE}$ , around the d.c. operating point can be found by linearizing the  $I$ - $V$  characteristic.
- We approximate a small change in  $i_C$  with respect to a small change in  $v_{BE}$ , by the derivative of  $i_C$  with respect to  $v_{BE}$ :

$$\left. \frac{\Delta i_C}{\Delta v_{BE}} \right|_{V_{BE}} \approx \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{V_{BE}} = \left. \frac{i_c}{v_{be}} \right|_{v_{be} \rightarrow 0} = \frac{I_S e^{V_{BE}/V_T}}{V_T} = \frac{I_C}{V_T} \quad (3.20)$$

\* Refer to slide 3.22, eqn (3.12).

# Transconductance $g_m$

---

- Transconductance  $g_m = \frac{I_C}{V_T}$  (3.21)

where the value of  $I_C$  is calculated at the d.c. operating point.

- The transconductance models a small change in the collector current,  $i_c$ , caused by a small change in the base-emitter voltage,  $v_{be}$ .

Change in Collector current.      Change in Base-Emitter voltage.

↓                                      ↓

$$i_c = g_m v_{be}$$

(3.22)

# Input Resistance $r_\pi$

---

- It has been shown previously\* that the base current,  $i_B = \frac{I_S}{\beta} e^{v_{BE}/V_T}$
- At the d.c. operating point, the d.c. base current,  $I_B = \frac{I_S}{\beta} e^{V_{BE}/V_T}$
- We approximate a small change in  $i_B$  with respect to a small change in  $v_{BE}$ , by the derivative of  $i_C$  with respect to  $v_{BE}$ :

$$\left. \frac{\Delta i_B}{\Delta v_{BE}} \right|_{V_{BE}} \approx \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{V_{BE}} = \left. \frac{i_b}{v_{be}} \right|_{v_{be} \rightarrow 0} = \frac{I_S e^{V_{BE}/V_T}}{\beta V_T} = \frac{I_C}{\beta V_T} = g_\pi \quad (3.23)$$

\* Refer to slide 3.22, eqn (3.13).

# Input Resistance $r_\pi$

---

- Taking reciprocal of  $g_\pi$ , we have, the following equation :

$$r_\pi = \frac{1}{g_\pi} = \frac{\beta V_T}{I_C} = \frac{\beta}{g_m} \quad (3.24)$$

- Hence,

$$\beta = g_m r_\pi \quad (3.25)$$


- We use  $r_\pi$  to model the relationship between small signal values of  $v_{be}$  and  $i_b$  of the base-emitter pn junction of the BJT.

$$\begin{array}{cc} \text{Change in} & \text{Change in} \\ \text{Base-Emitter} & \text{Base} \\ \text{voltage.} & \text{current.} \\ \downarrow & \downarrow \\ v_{be} = r_\pi i_b \end{array} \quad (3.26)$$

- Combining eqns (3.25) and (3.26),


$$i_c = g_m v_{be} = g_m r_\pi i_b = \beta i_b \quad (3.27)$$
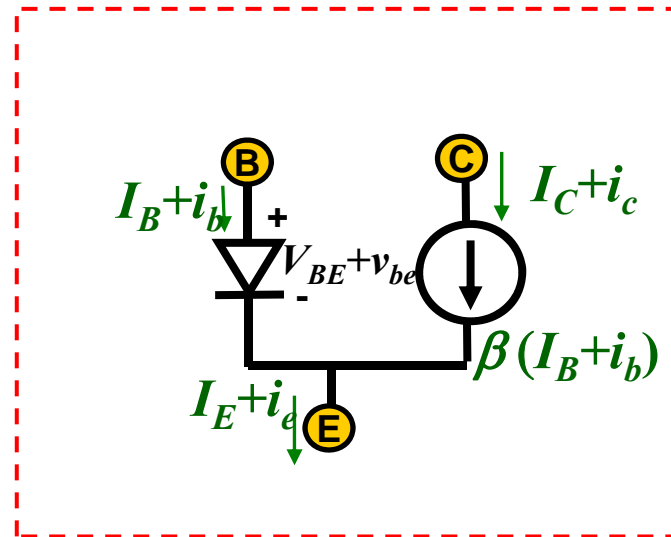
## Small-Signal (Simplified Hybrid- $\pi$ ) Equivalent Circuit of the BJT




Large-Signal Equivalent  
Circuit of the BJT

becomes

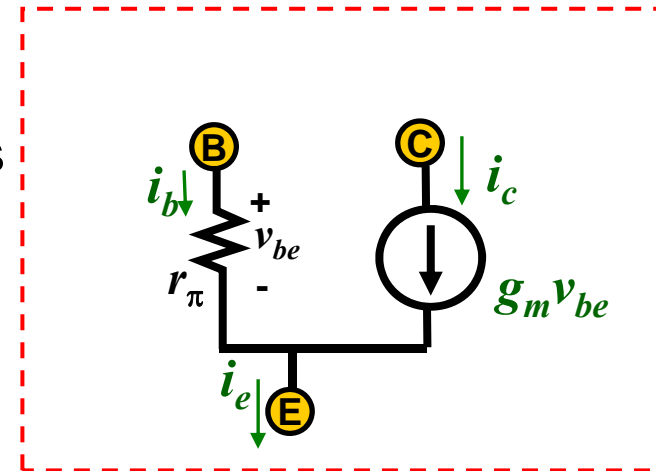


or

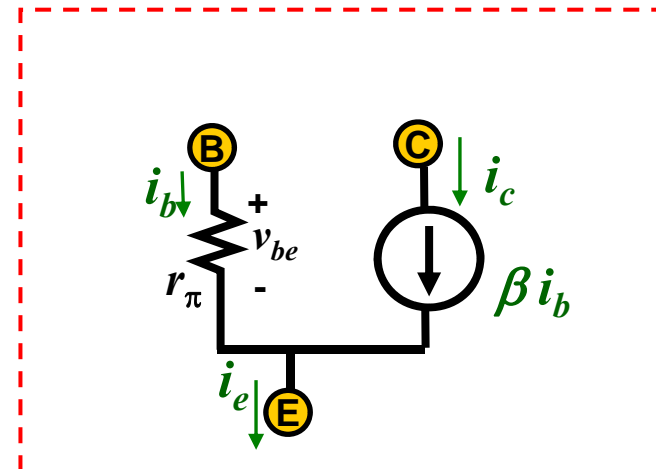


Small-Signal (Simplified  
Hybrid- $\pi$ ) Equivalent Circuits  
of the BJT
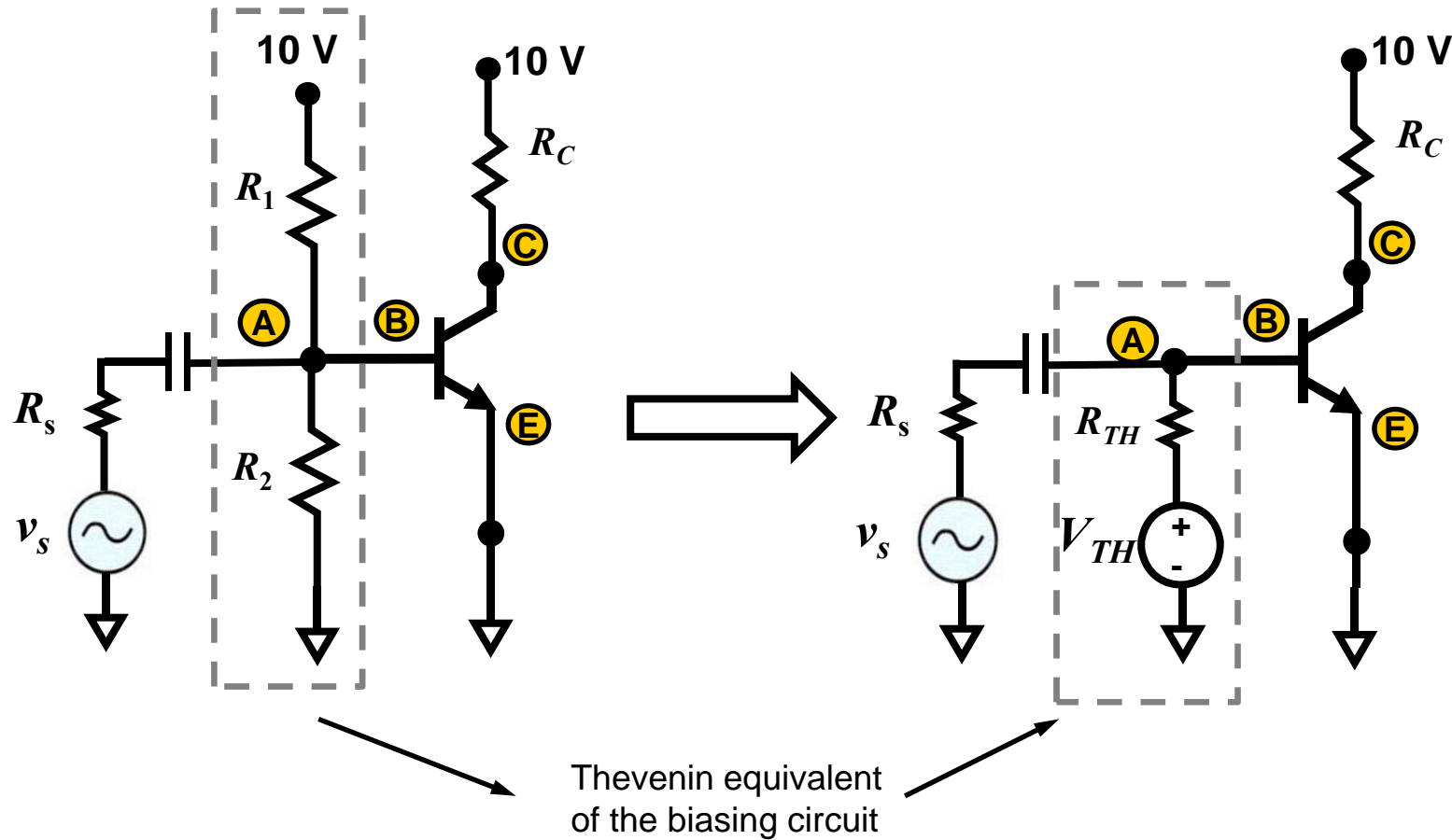
# Small-Signal Equivalent Circuit of a BJT Amplifier Circuit


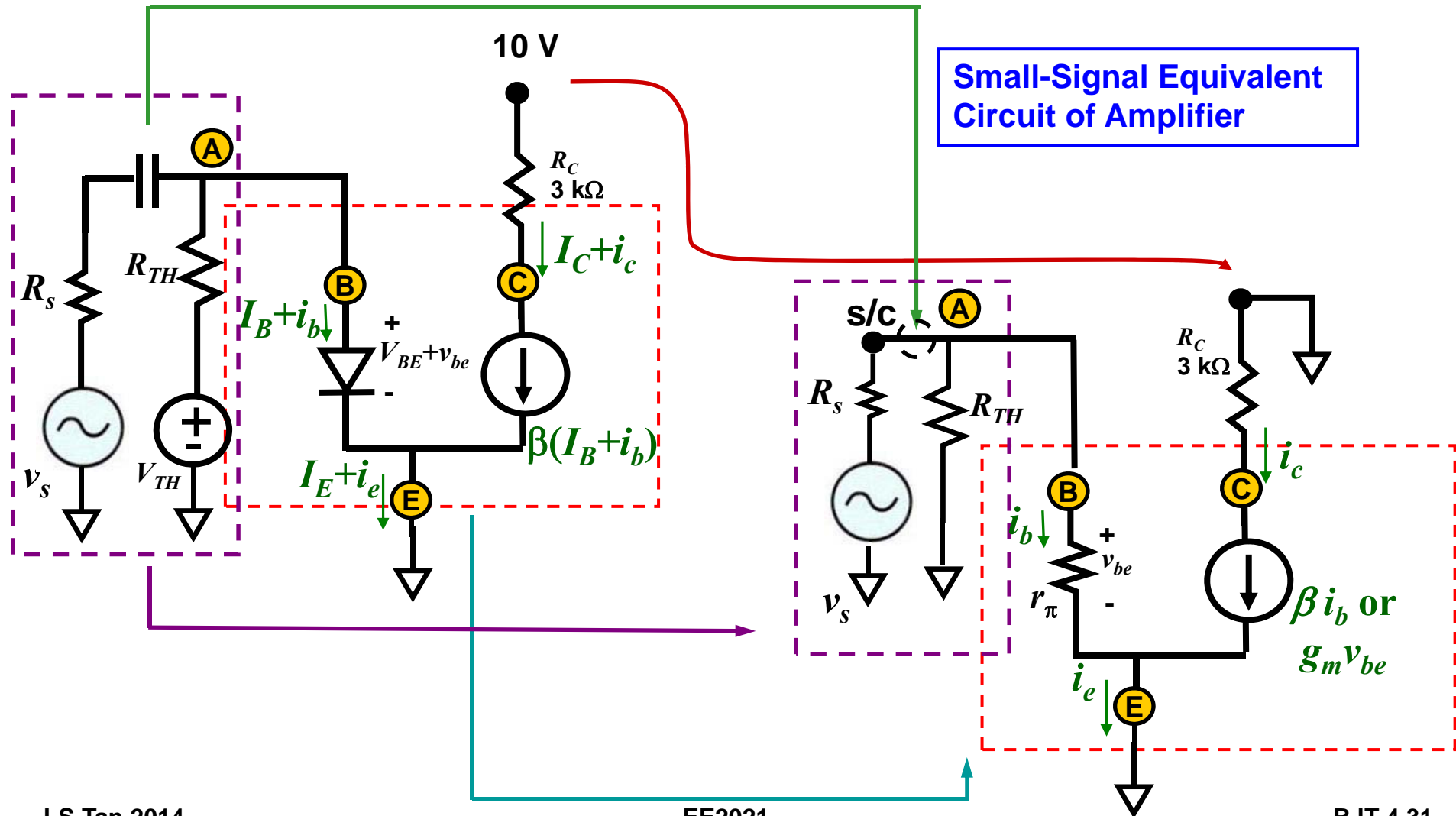
# Small-Signal Equivalent Circuit of a BJT Amplifier Circuit

Large-Signal Equivalent  
Circuit of Amplifier



# Bipolar Junction Transistor (BJT)


---

1. Introduction to the BJT
2. Principles of Operation of the BJT
3. Analysis of the BJT
4. Large Signal Model of the BJT
5. Calculation of Operating Point of BJT Circuits
6. Signal Amplification in Amplifiers
7. Small Signal (Simplified Hybrid- $\pi$ ) Model of the BJT ✓
8. Full Hybrid- $\pi$  Model ←




## 8. Full Hybrid- $\pi$ Model of the BJT

### A simple Hybrid- $\pi$ Model

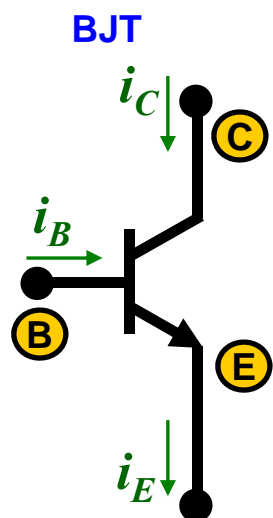


Replace the BJT  
by this Hybrid- $\pi$   
Model for Small-  
Signal Analysis

Current-Controlled Version

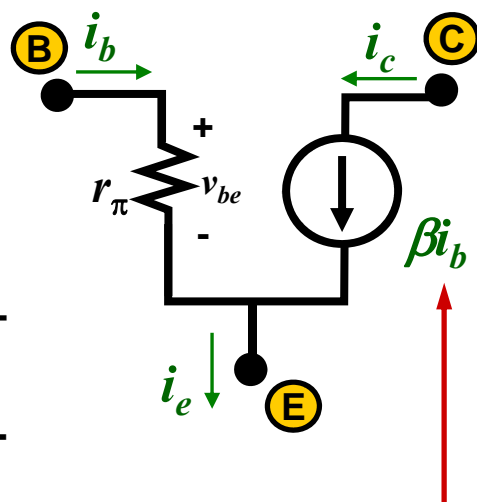


The value of  $i_c$  is  $\beta$  times  $i_b$ .  
A current-dependent  
current source is  
used here.

Voltage-Controlled Version

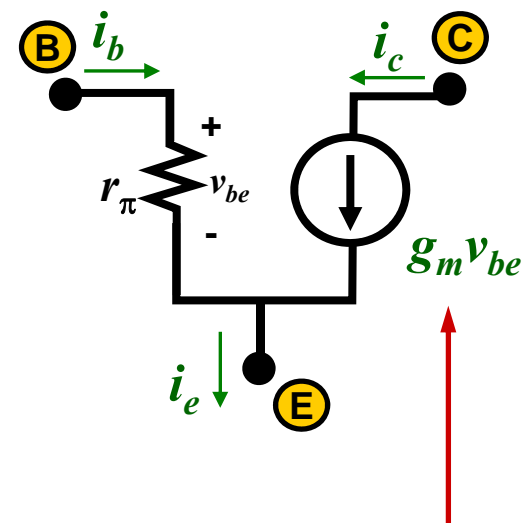

The value of  $i_c$  is  
dependent on  $v_{be}$ . A  
voltage-dependent  
current source is  
used here.


# Output Resistance $r_o$

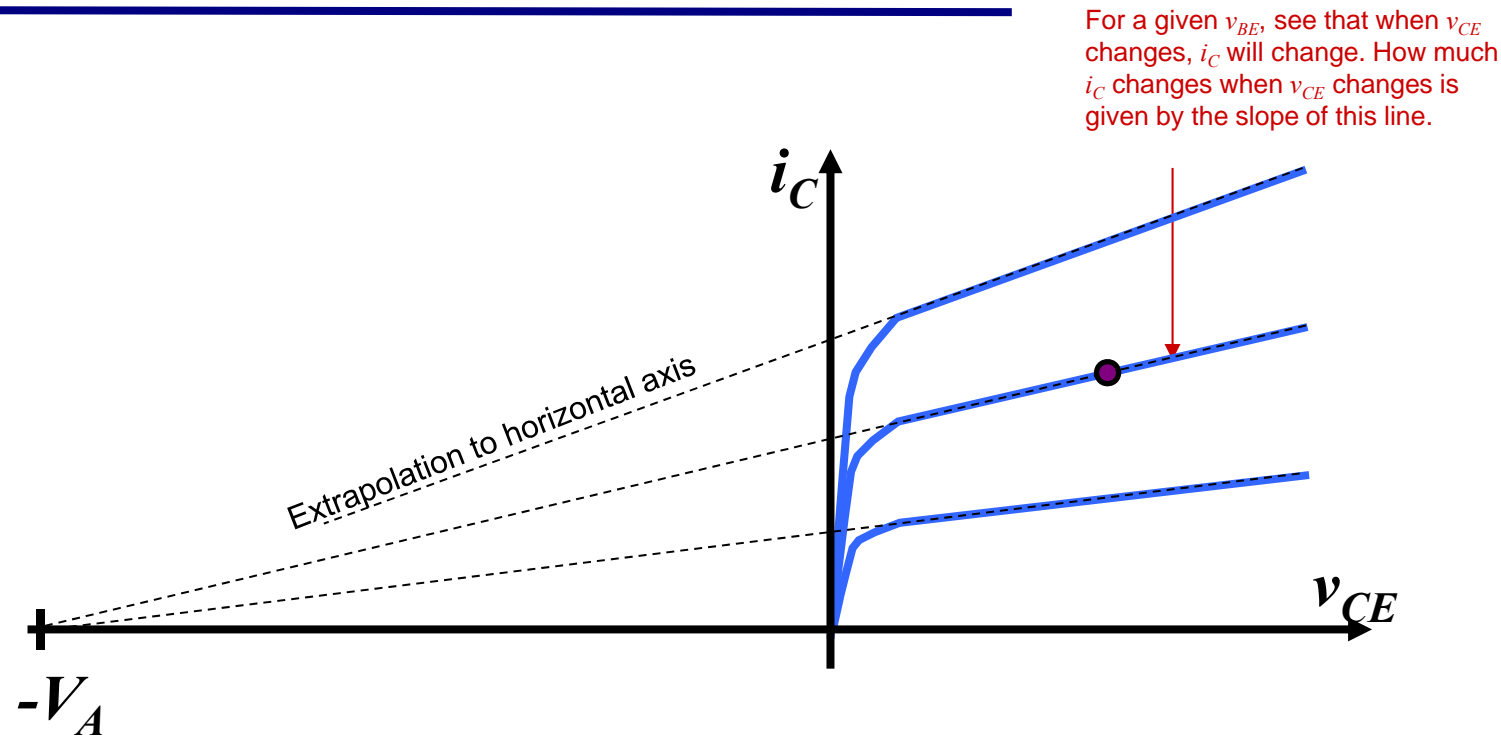

- From eqn (3.16) we have,  $i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$
- Output resistance,  $r_o = \frac{1}{g_o} = \frac{V_A}{I_C}$  (3.28)
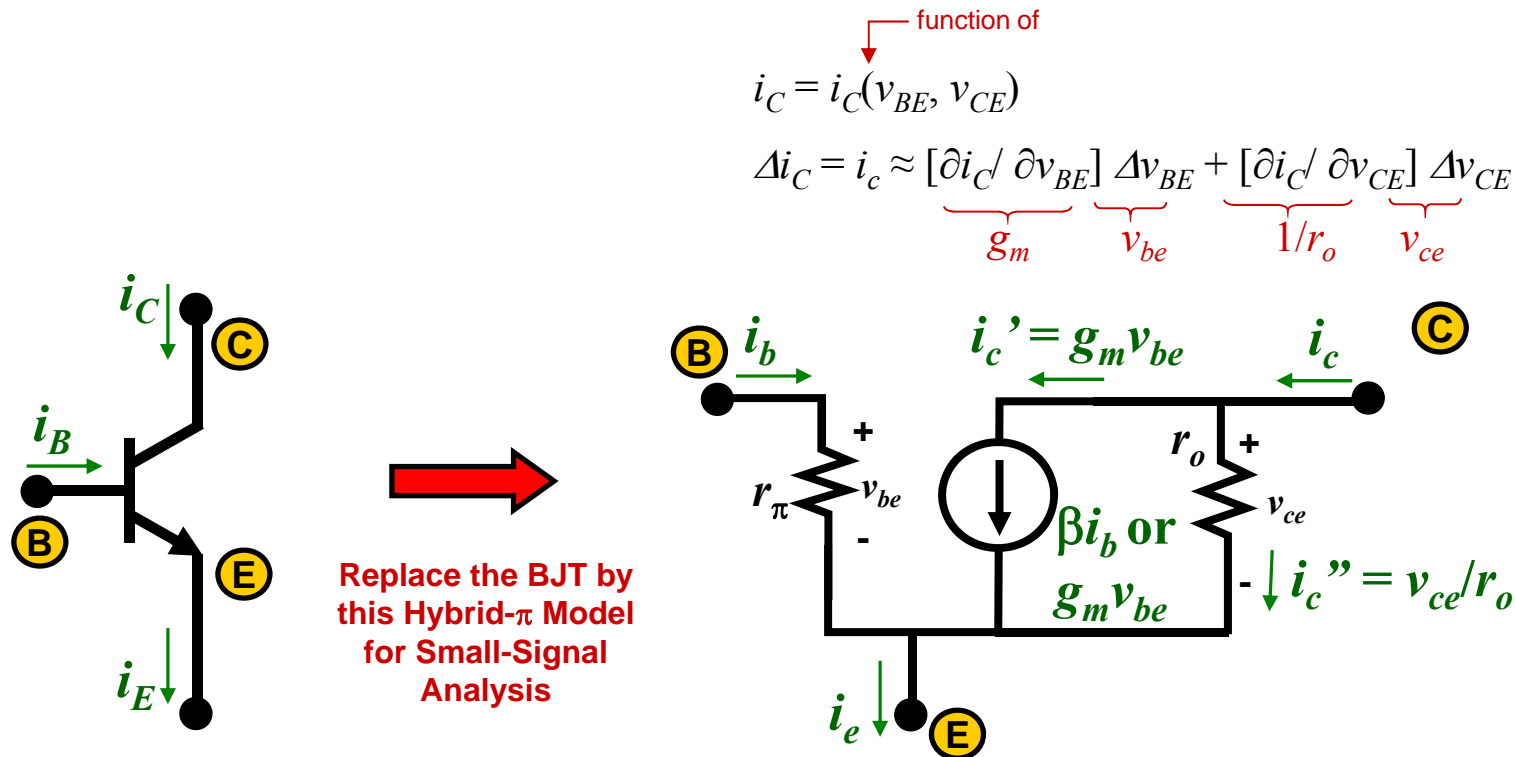
# Hybrid- $\pi$ Model with Output Resistance

- To model the increase in  $i_C$  with an increase in  $v_{CE}$ , a resistance  $r_o$  is included between nodes C and E in the Hybrid- $\pi$  Model.




- See that  $i_c$  is given by  $i_c = [g_m v_{be} + (v_{ce}/r_o)]$  or  $[\beta i_b + (v_{ce}/r_o)]$

This term accounts for the dependence of  $i_c$  on  $v_{ce}$ .

Note: In EE2021, you can assume that  $r_o$  is infinite by default. However, if the Early voltage  $V_A$  is given, then  $r_o$  should be calculated and employed in the Small-Signal Analysis.
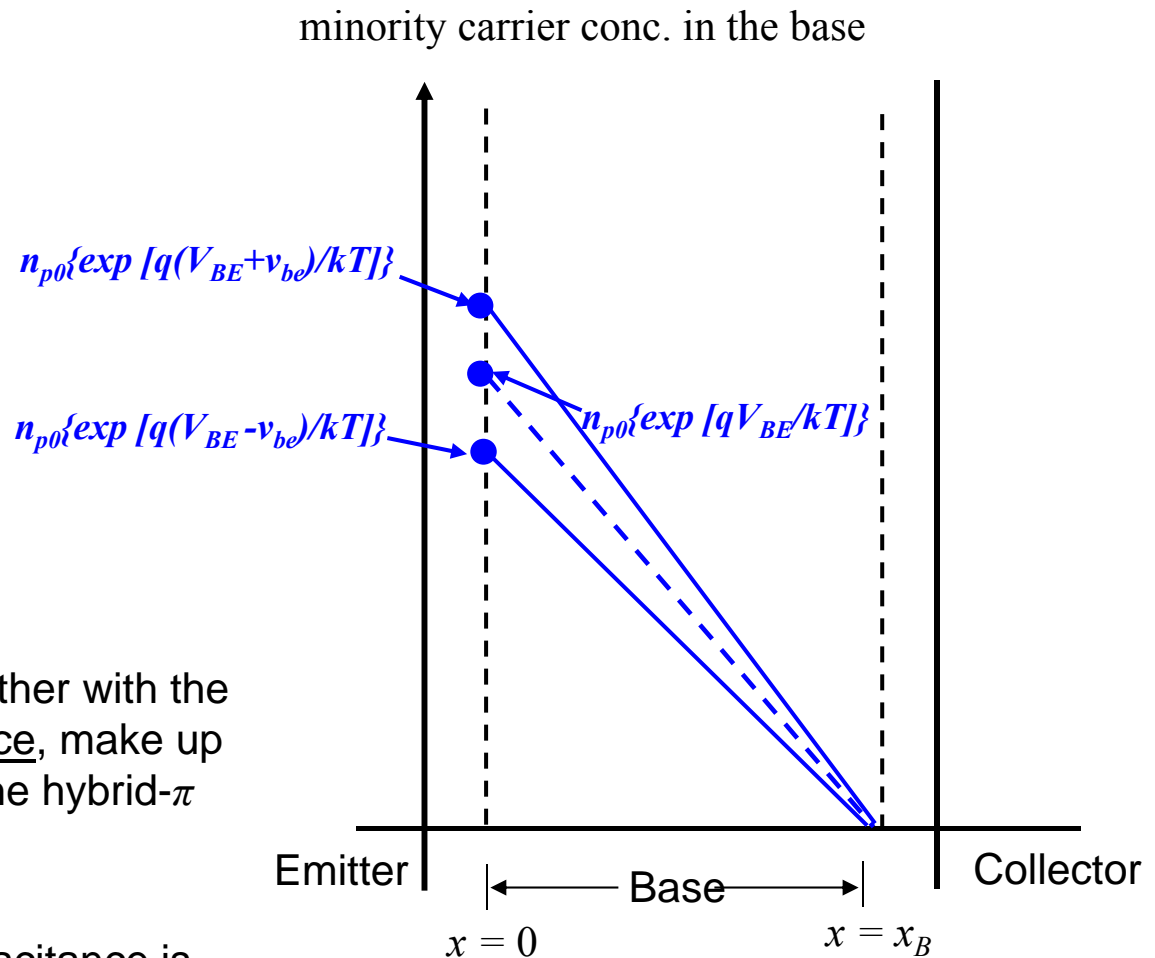
# Capacitances in the BJT


- When a small signal  $v_{be}$  is superimposed on the base-emitter (d.c.) forward bias  $V_{BE}$ , the concentration of the minority carriers at the base edge of the SCR is changed slightly.
- This results in a small change of the minority carrier charge in the base of the transistor, hence giving rise to a diffusion capacitance.
- This diffusion capacitance, together with the emitter-base junction capacitance, make up the input capacitance  $c_\pi$  in full the hybrid- $\pi$  model of the bipolar transistor.
- The collector-base junction capacitance is denoted as  $c_\mu$  in the hybrid- $\pi$  model.



Note that  $v_{be}$  also causes a change in charge in the emitter. However, in the bjt, the minority carrier conc. in the emitter is much less than that in the base, and so this component of the diffusion capacitance is negligible.
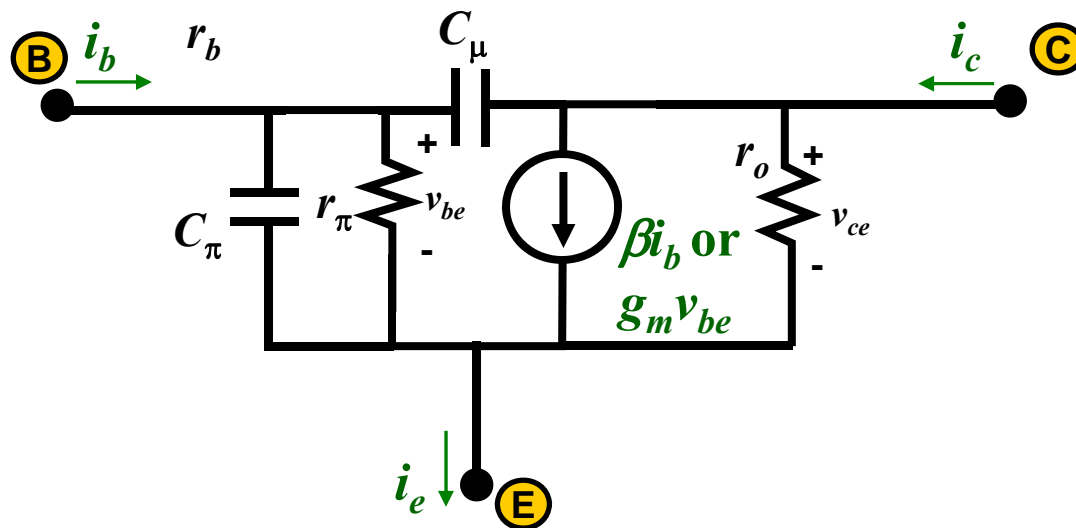
# Full Hybrid- $\pi$ Model at High Frequency

- BJTs have capacitances associated with pn junctions and with charge storage.
- At high frequencies, two parasitic capacitors have to be included:  $C_\mu$  and  $C_\pi$ .



Note: We introduce the existence of these capacitances  $C_\mu$  and  $C_\pi$  here, and their inclusion in the Hybrid- $\pi$  Model is only necessary when frequency response is discussed. We will ignore these capacitances (in the pF range) for low frequency signals.