

# EE2021

# Devices and Circuits

---

**Two-Port Network,  
Single Transistor Amplifiers -  
CE, CS, CB, CG**

# Lecture Outline


---

- **2-Port Network (Voltage and Transconductance)**

Important parameters that characterize 2-port;

- **Single Transistor Amplifiers,**  
CE/CS, CB/CG.
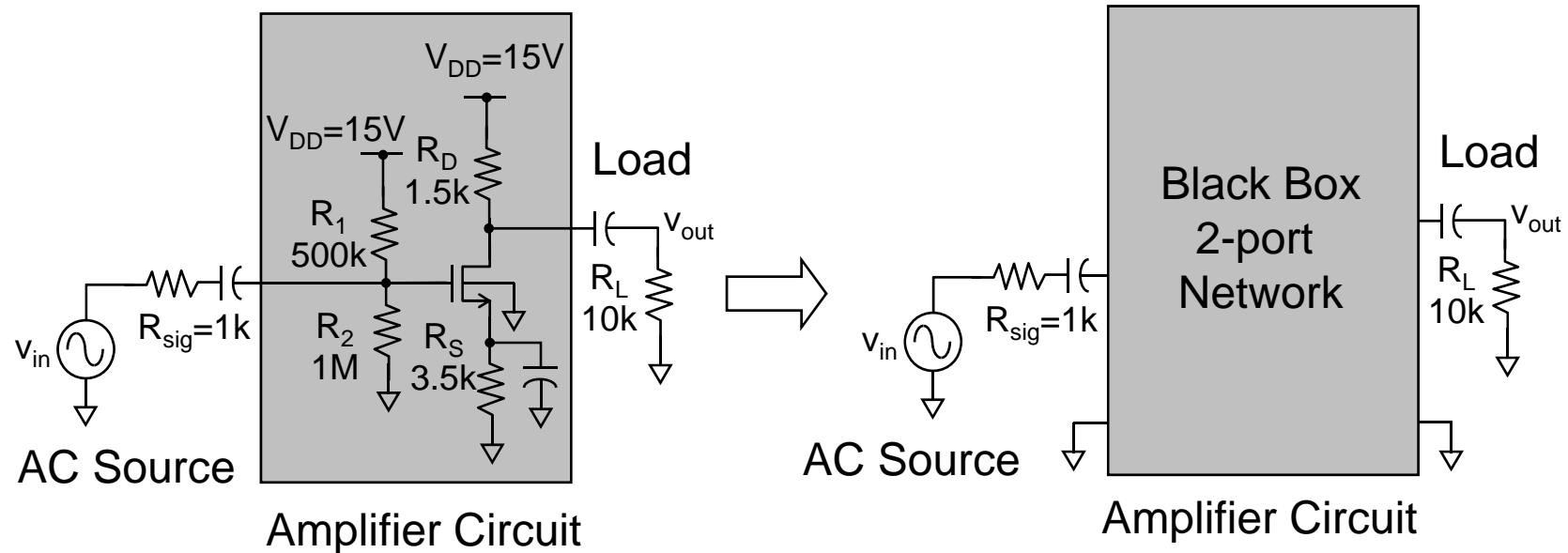
# Modeling Amplifier Circuit using 2-Port Network



Can we fully characterize the complicated amplifier circuit using simple black box (2-port network) with limited set of parameters?

For example, similar to a complicated linear network replaced by Thevenin Equivalent with only one Thevenin Voltage source and one Thevenin equivalent resistor, i.e. only 2 parameters.


# Analogy of Two-Port Network to Investment Scheme

---




- We are only interested in the relationship between output and input
- We don't care about what happens in between

# Why Use 2-port Network?


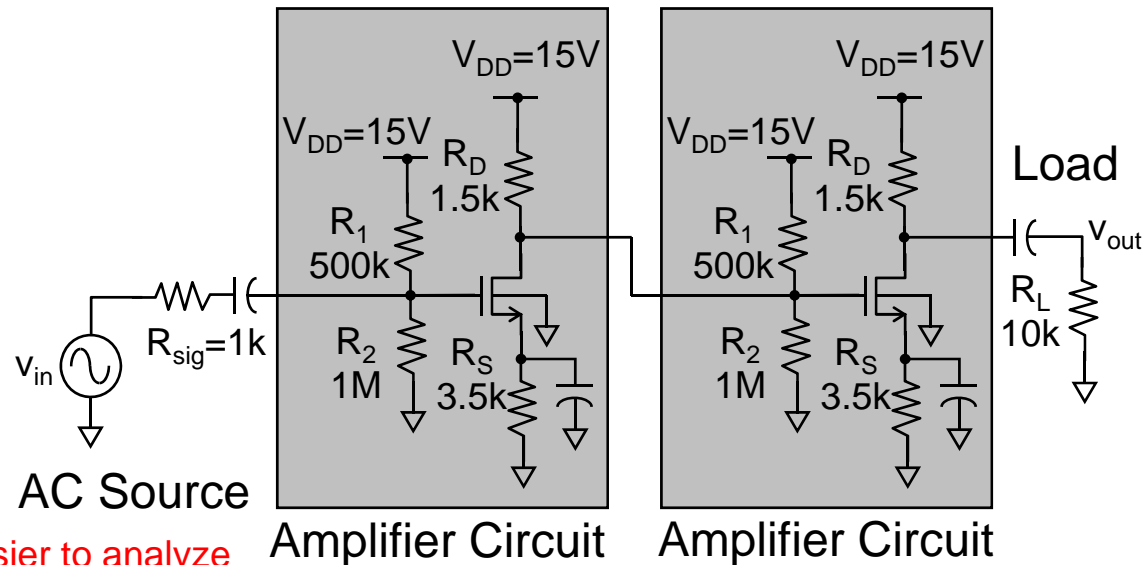


Easier to analyze complicated circuit (e.g., multi-stage amplifier) as each amplifier is simplified to its equivalent 2-port network.





Similar concept as Thevenin equivalent or Norton equivalent.

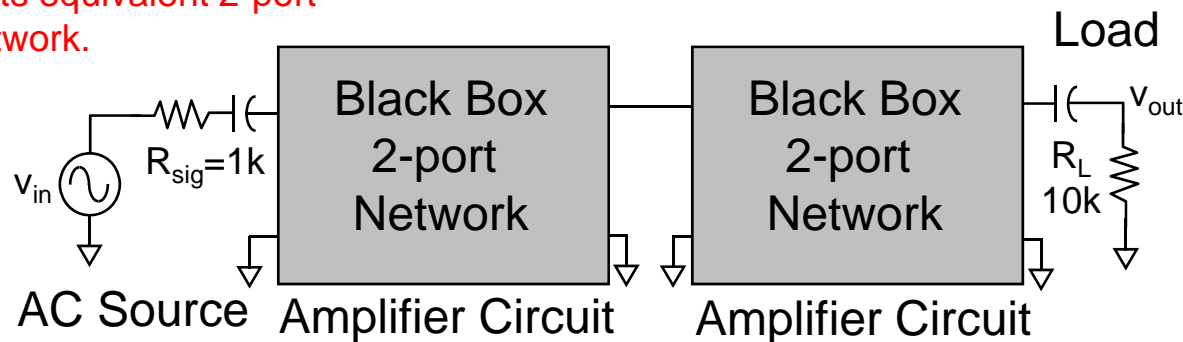

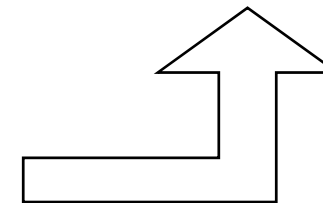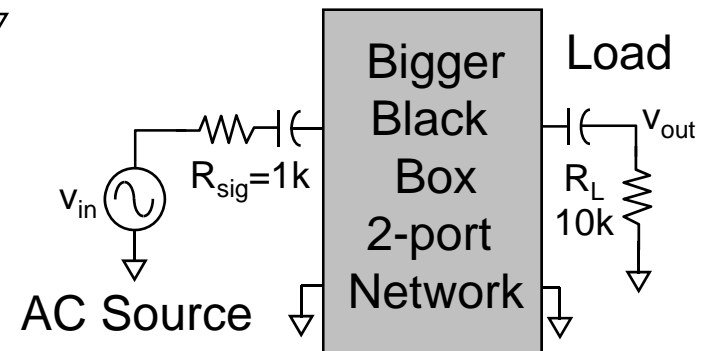Cascaded 2-port networks can be combined into a bigger 2-port network.




# Different 2-Port Amplifier Models

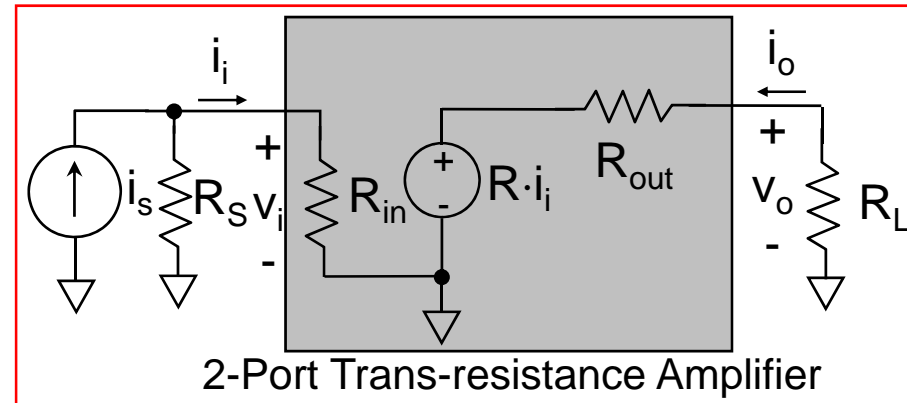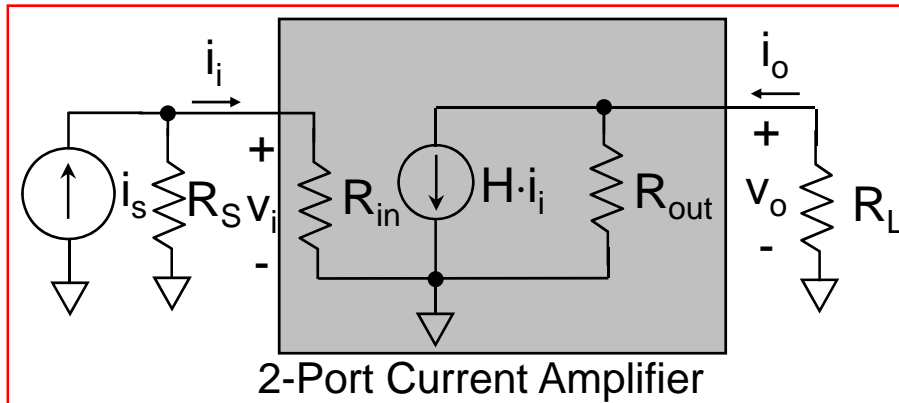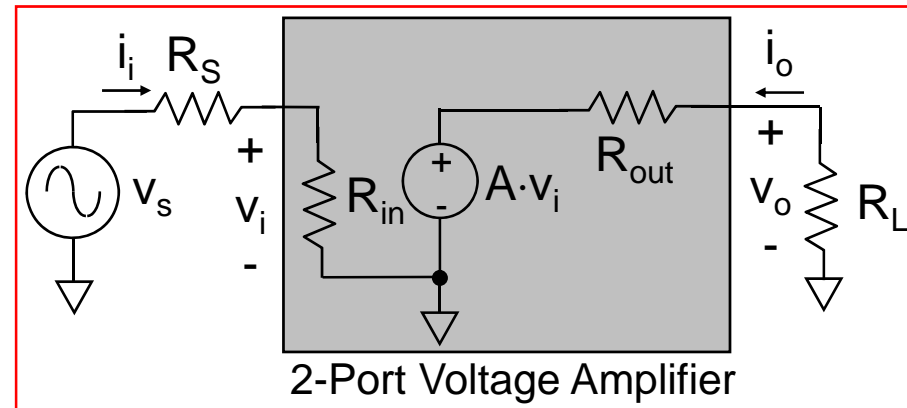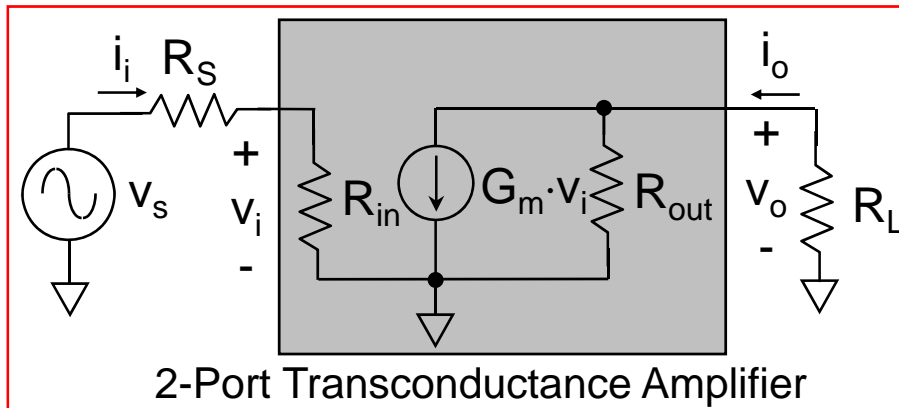

- They all can be used to represent same amplifier circuit.
- Same concept as Thevenin equivalent versus Norton equivalent.
- In some scenario, it is easier to consider the amplifier as 2-port transconductance amplifier to simplify the analysis. In some cases, it is easier to consider the amplifier as 2-port voltage amplifier to simplify the analysis. Same reasoning applies to 2-port current and trans-resistance amplifier.
- In this module, only 2-port transconductance and 2-port voltage amplifiers are considered as they simplify the analysis. (Based on experience from circuit designers)
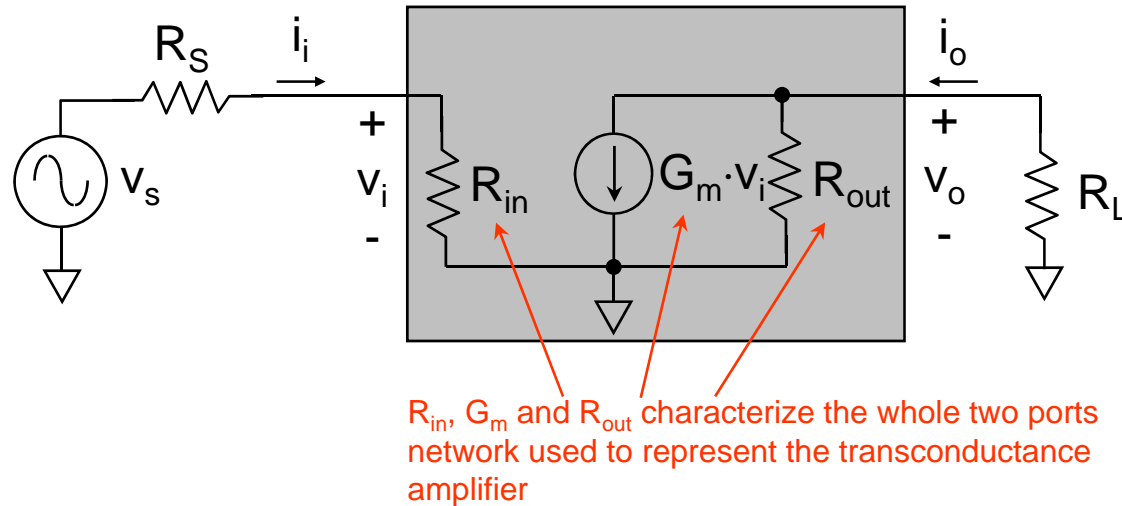
# Two Port Network – Transconductance Amplifier






- After converting amplifier circuit to 2-ports network, it is easier to cascade multiple of them together and analyze (Refer to 6A-5)

## Characteristic:


- High input resistance ( $R_{in}$ )
- High output resistance ( $R_{out}$ )
- Transconductance amplifier (Voltage-to-current :  $G_m v_i$ )
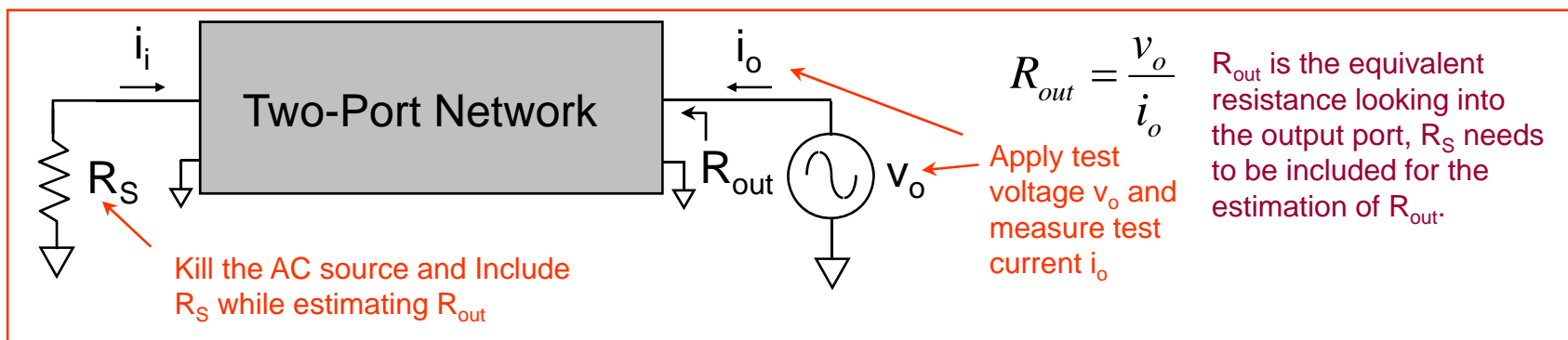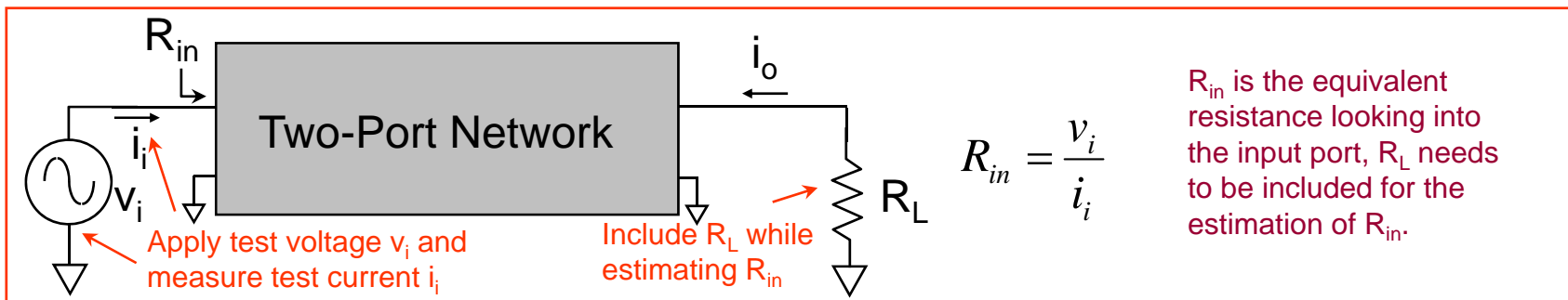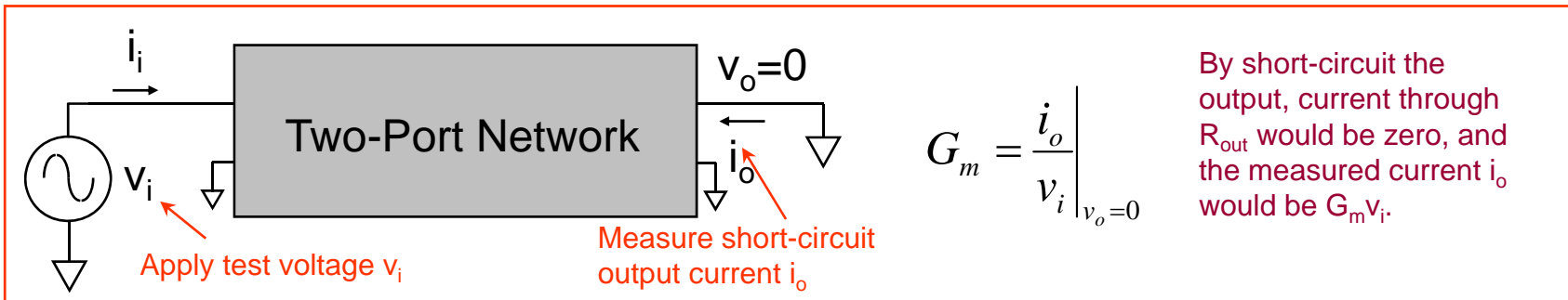
# Transconductance Amplifier – Parameter Characterizations






# Equivalent Resistance

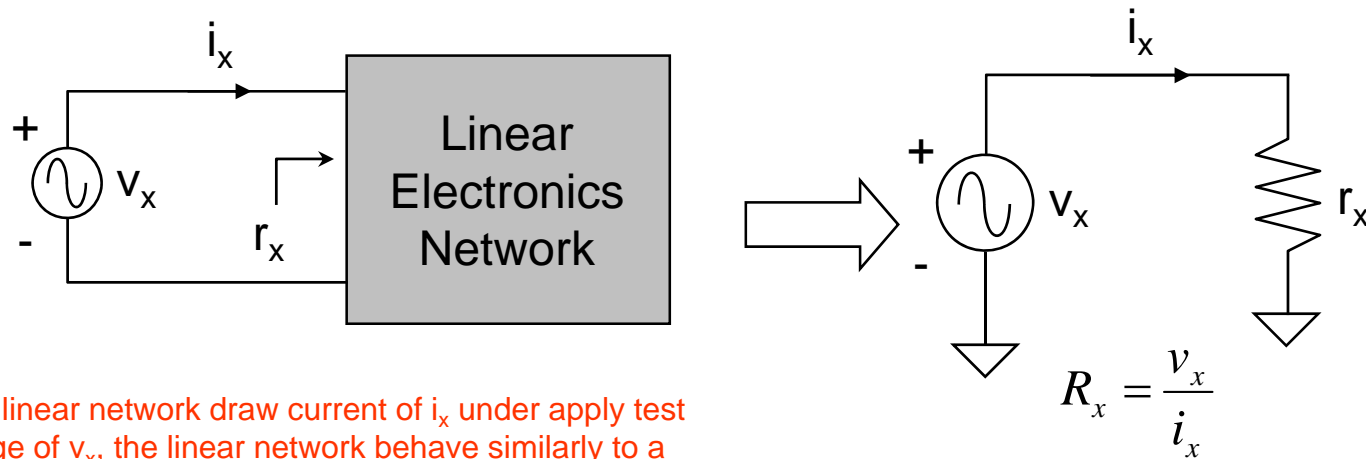

If the linear network draw current of  $i_x$  under apply test voltage of  $v_x$ , the linear network behave similarly to a simple resistor  $R_x$  obeying the Ohm's law

- Similar concept as Thevenin equivalent
- For a complicated **LINEAR** network, the current-voltage relationship can be modeled as a simple equivalent resistor

# Two-Port Network – Voltage Amplifier



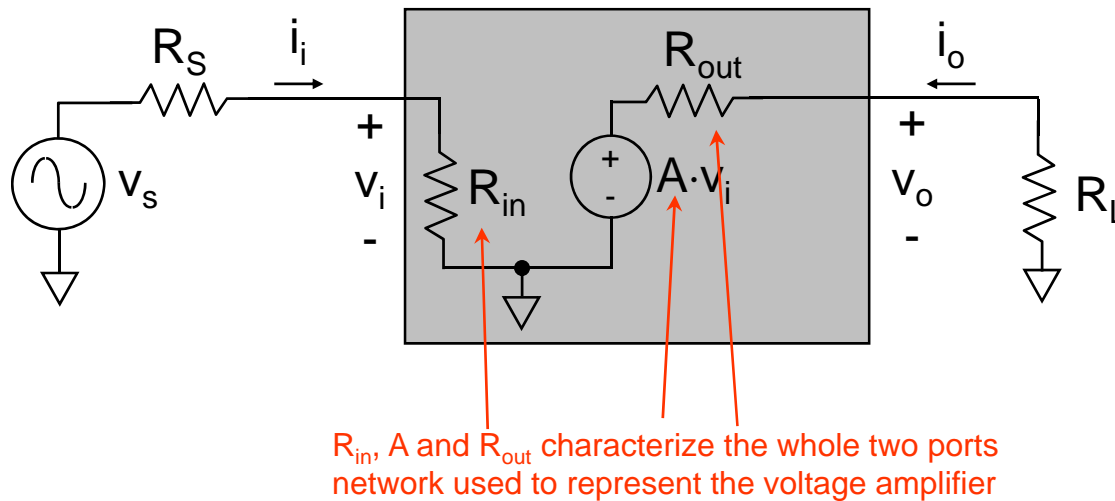


- After converting amplifier circuit to 2-port network, it is easier to cascade multiple of them together and analyze (Refer to 6A-5)


## Characteristics:

- High input resistance ( $R_{in}$ )
- Low output resistance ( $R_{out}$ )
- Voltage amplifier ( $A$ )

# Two-Port Network – Voltage Amplifier

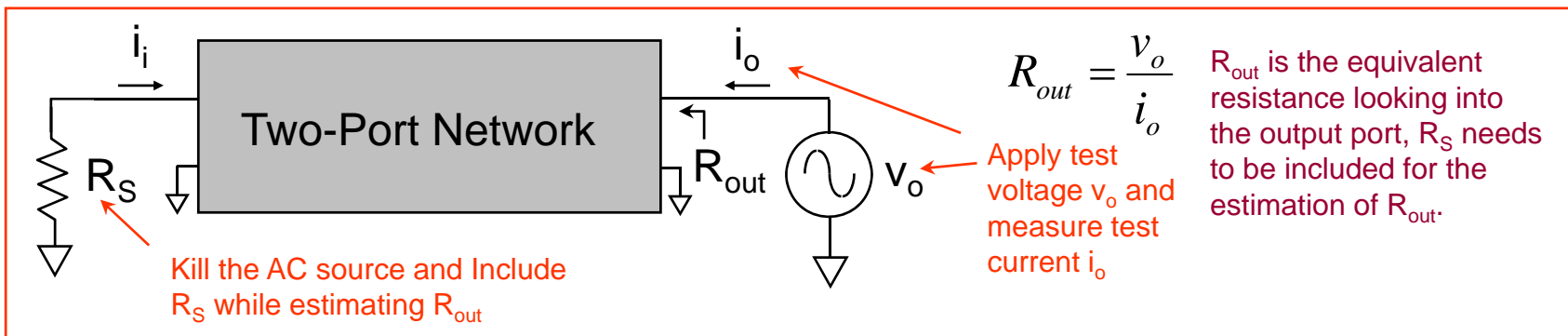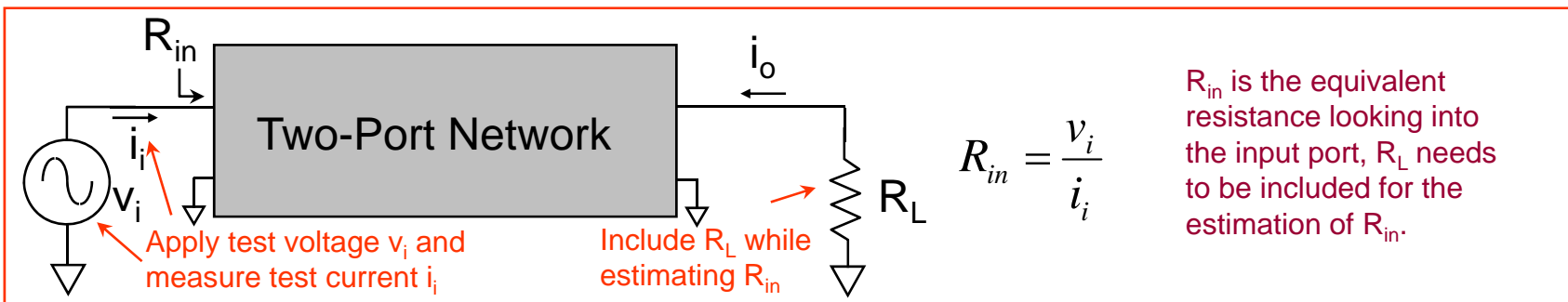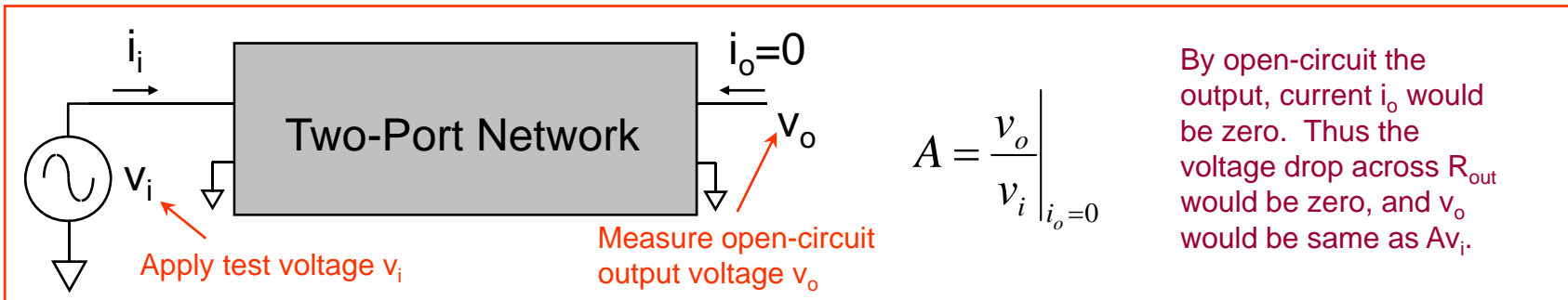

# Example on Cascade Two-Port

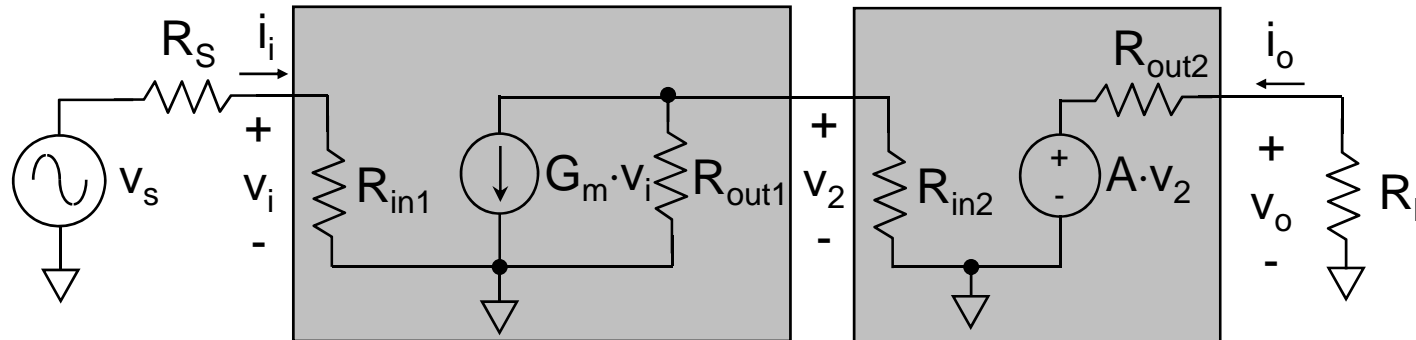

$$v_i = \frac{R_{in1}}{R_{in1} + R_s} \times v_s$$

$$v_2 = -G_m v_i \times (R_{out1} // R_{in2})$$

$$= -G_m \times \frac{R_{in1}}{R_{in1} + R_s} \times v_s \times (R_{out1} // R_{in2})$$

$$v_o = A v_2 \times \frac{R_L}{R_{out2} + R_L}$$


$$= \frac{A R_L}{R_{out2} + R_L} \left[ -G_m \times \frac{R_{in1}}{R_{in1} + R_s} \times v_s \times (R_{out1} // R_{in2}) \right]$$

$$\text{Gain} = \frac{v_o}{v_s} = \underbrace{-\frac{R_{in1}}{R_{in1} + R_s}}_{1^{\text{st}}} \times \underbrace{G_m (R_{out1} // R_{in2})}_{2^{\text{nd}}} \times \underbrace{A \times \frac{R_L}{R_{out2} + R_L}}_{3^{\text{rd}}} = \frac{v_i}{v_s} \times \frac{v_2}{v_i} \times \frac{v_o}{v_2}$$

In amplifier design,


- How should you choose  $R_{in1}$  with respect to  $R_s$ ?
- How should you choose  $R_{out2}$  with respect to  $R_L$ ?
- Why?
- What if the source and load are antenna or equipment with long coaxial cable?

# How to Treat Capacitors?








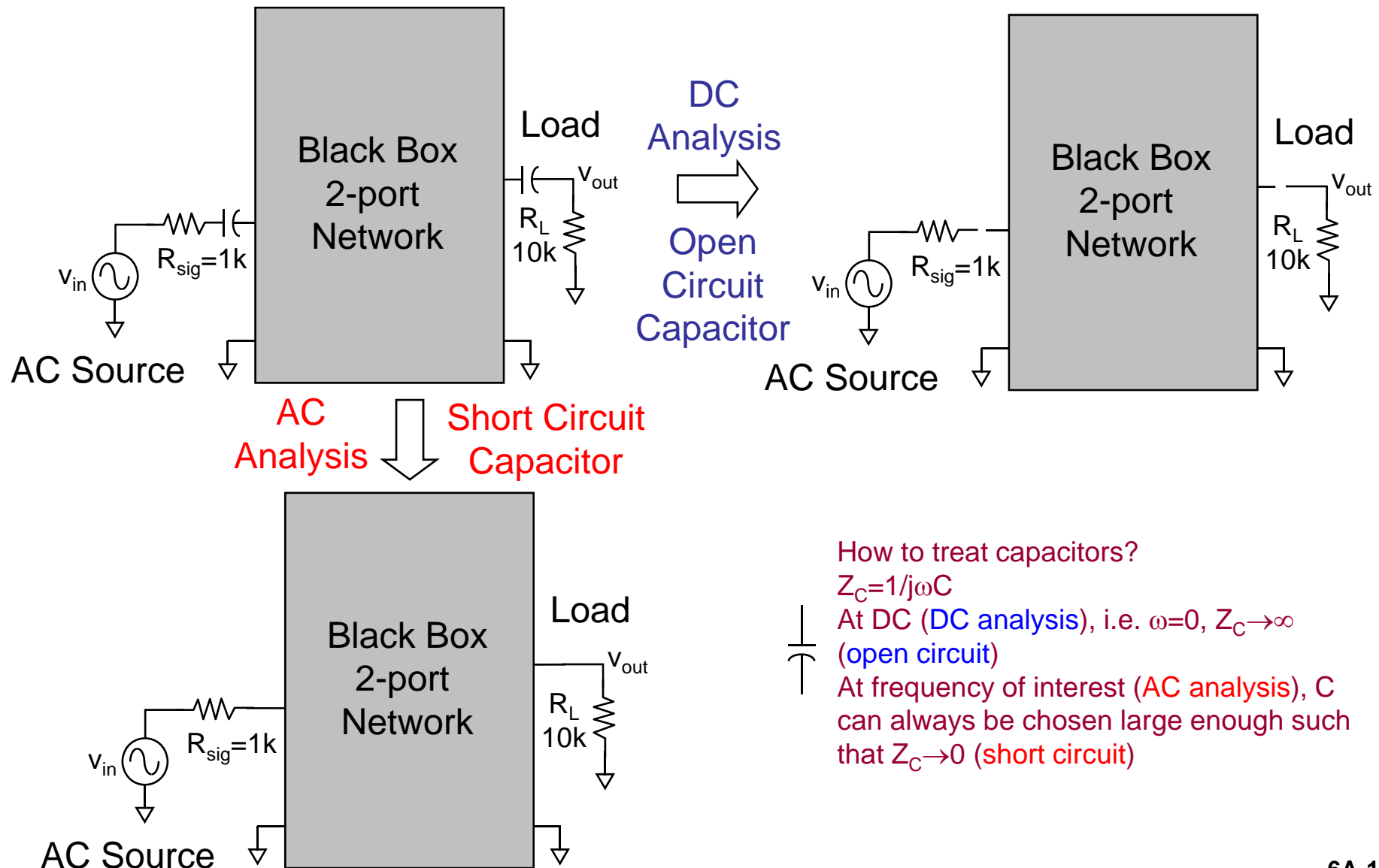


# Steps for Circuit Analysis


---

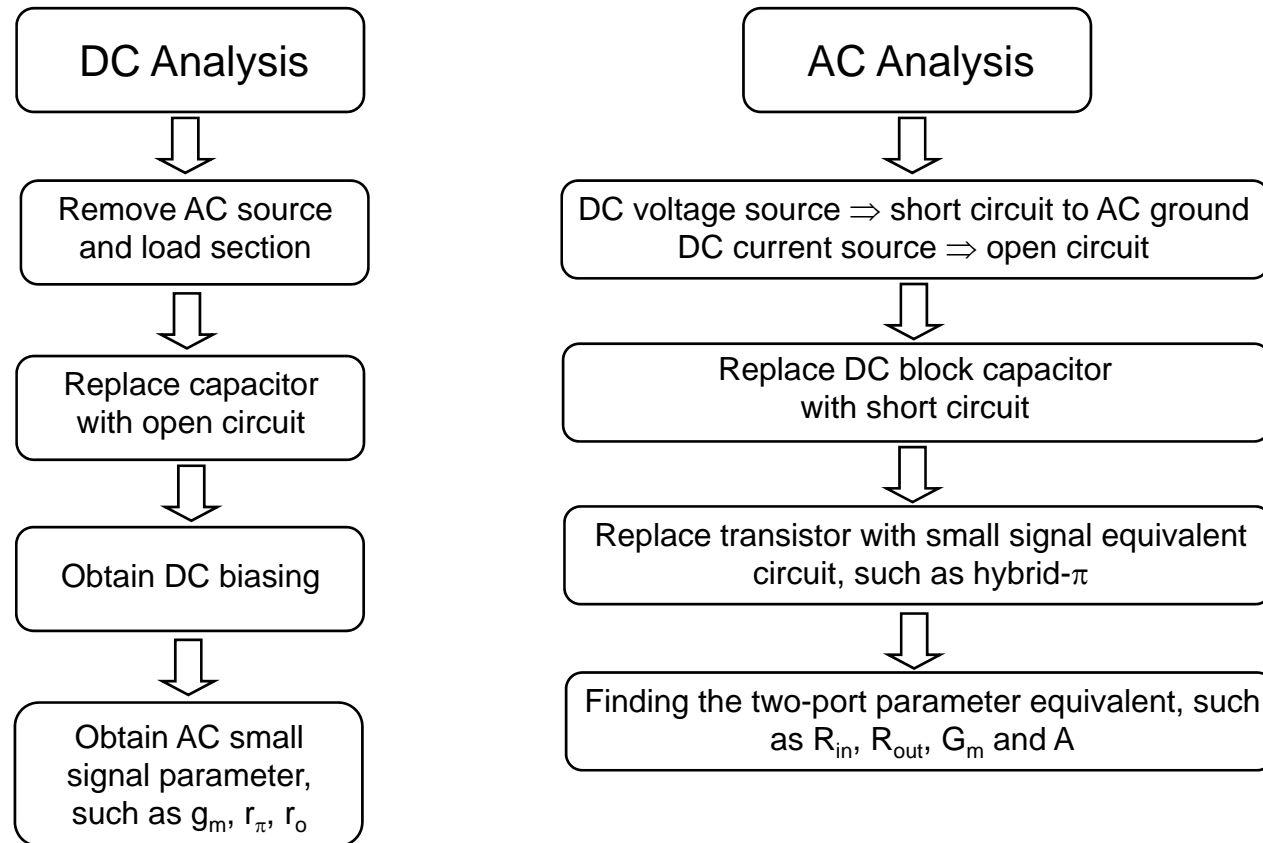

# 8 Amplifier Configurations
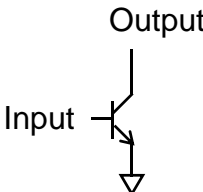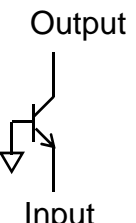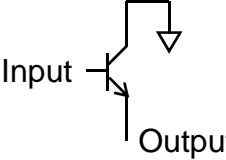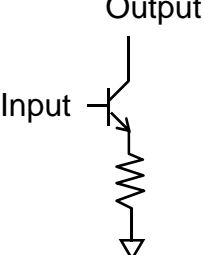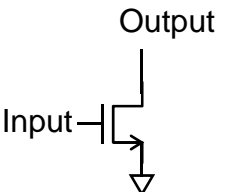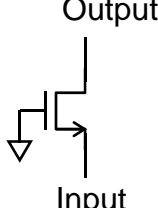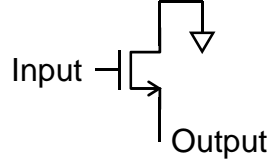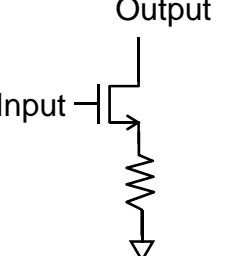
|   |  |   |   |
|---|--|---|---|
|  <p>Input – Base<br/>Output – Collector<br/>Neither – Emitter<br/>⇒ CE</p> |  <p>Input – Emitter<br/>Output – Collector<br/>Neither – Base<br/>⇒ CB</p> |  <p>Input – Base<br/>Output – Emitter<br/>Neither – Collector<br/>⇒ CC</p> |  <p>Input – Base<br/>Output – Collector<br/>Neither – Emitter<br/>(with resistor)<br/>⇒ CE with degeneration</p> |
|  <p>Input – Gate<br/>Output – Drain<br/>Neither – Source<br/>⇒ CS</p>     |  <p>Input – Source<br/>Output – Drain<br/>Neither – Gate<br/>⇒ CG</p>     |  <p>Input – Gate<br/>Output – Source<br/>Neither – Drain<br/>⇒ CD</p>     |  <p>Input – Gate<br/>Output – Drain<br/>Neither – Source<br/>(with resistor)<br/>⇒ CS with degeneration</p>     |

# Common Emitter (CE) Amplifier

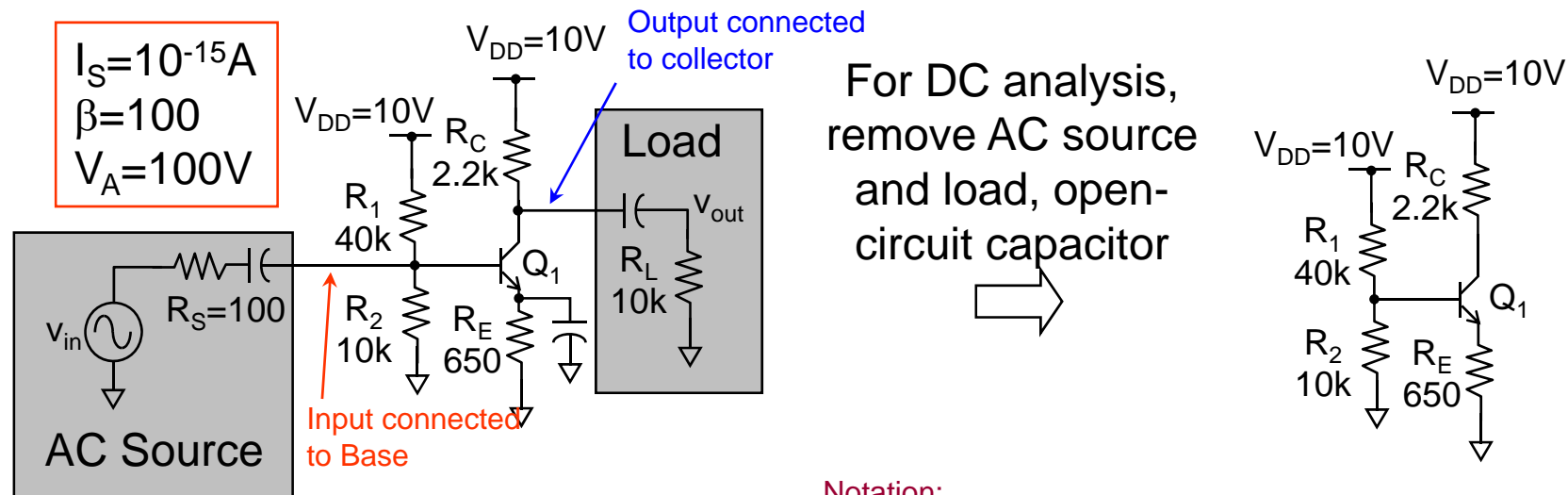

For DC analysis,  
remove AC source  
and load, open-  
circuit capacitor

Notation:

$V_{B,Q1}$ : Base voltage of  $Q_1$


$V_{E,Q1}$ : Emitter voltage of  $Q_1$

$V_{C,Q1}$ : Collector voltage of  $Q_1$

- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- Input** connected to **Base**, **output** connected to **Collector**, **Emitter** connected to neither input nor output  $\Rightarrow$  **Common Emitter (CE)**
- DC Analysis refer to "BJT Lecture Notes" slide 29



# DC Analysis for CE Amplifier

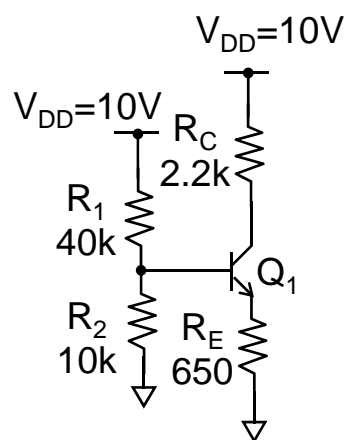

$$\begin{aligned} I_S &= 10^{-15} \text{ A} \\ \beta &= 100 \\ V_A &= 100 \text{ V} \end{aligned}$$

Determine DC biasing

Assume  $I_{B,Q1} \ll I_{R1}, I_{R2}$

$\Rightarrow$  voltage divider method

$$V_{B,Q1} = \frac{10k}{40k + 10k} \times 10 = 2V$$

$$V_{E,Q1} = 2V - 0.7V = 1.3V$$

$$I_{C,Q1} \approx I_{E,Q1} = \frac{1.3V}{650} = 2mA$$

$$I_{B,Q1} \approx 20\mu A$$

$$I_{R1} \approx I_{R2} \approx 200\mu A \gg I_{B,Q1}$$


Determine AC small signal parameter

$$g_m = \frac{I_C}{V_T} = 80mA/V$$


$$r_\pi = \frac{\beta}{g_m} = 1.25k\Omega$$

$$r_o = \frac{V_A}{I_C} = 50k\Omega$$


# Common Emitter (CE)

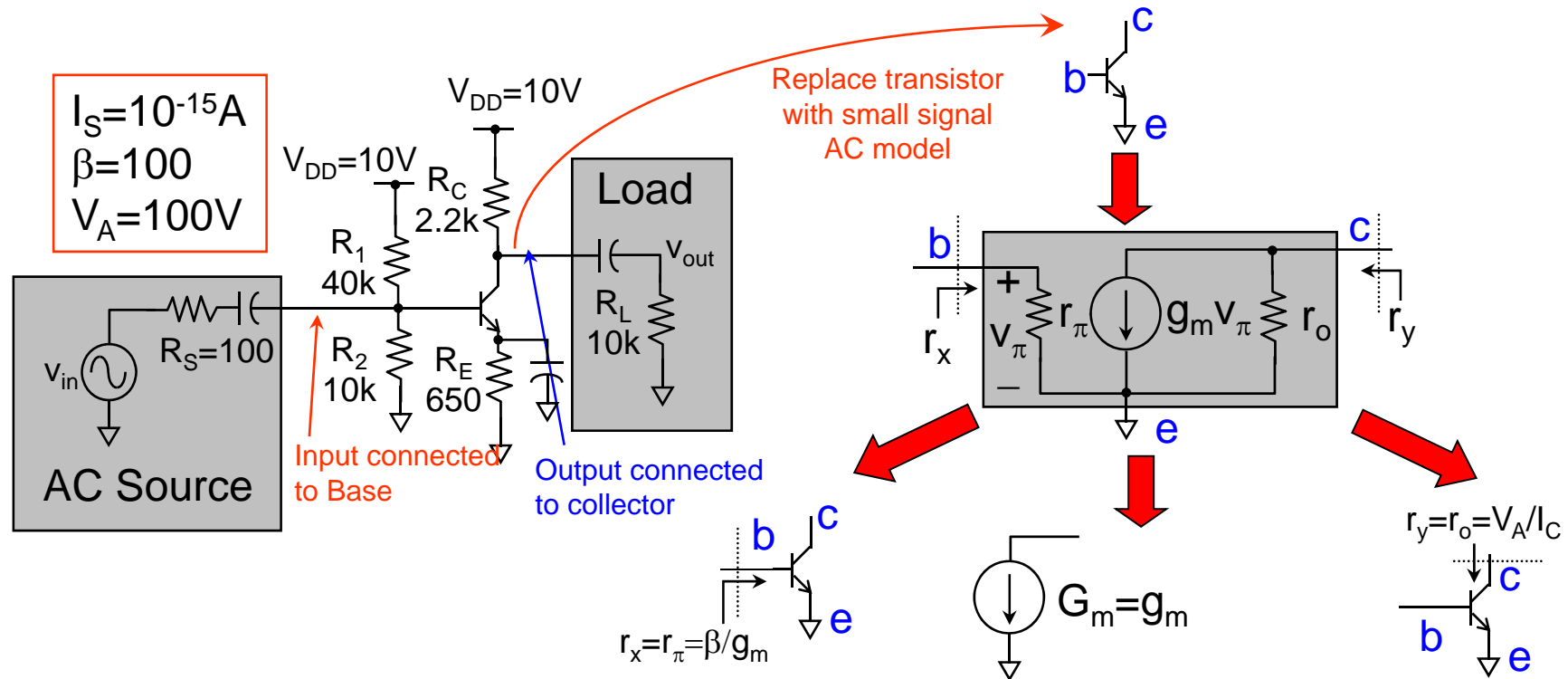

# AC Analysis for CE

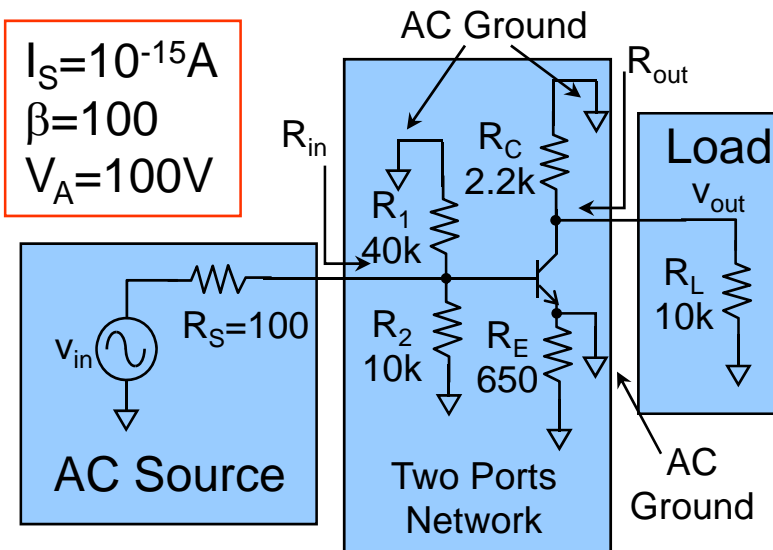

2-port Transconductance Amplifier

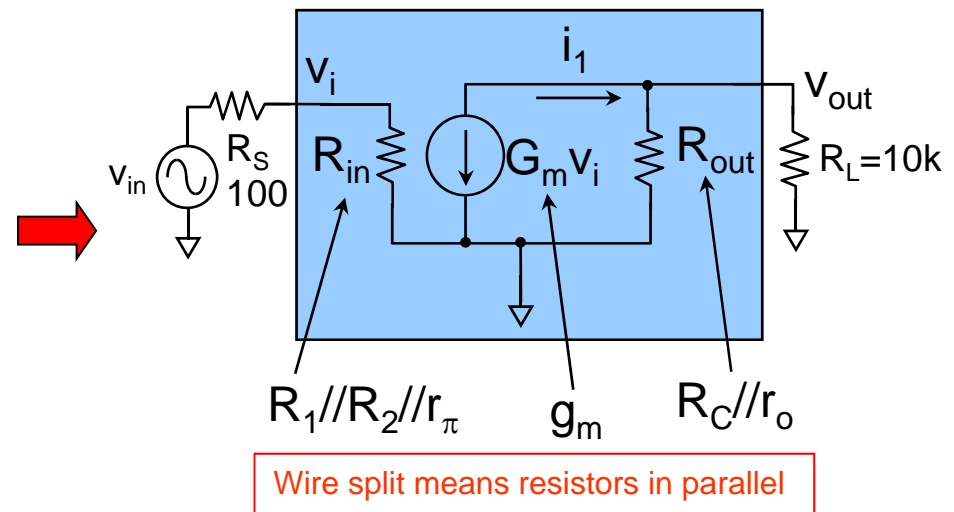

$g_m = 80 \text{mA/V}$   
 $r_\pi = 1.25 \text{k}$   
 $r_o = 50 \text{k}$


$$v_i = \frac{R_{in}}{R_S + R_{in}} v_{in} = \frac{R_1 // R_2 // r_\pi}{R_S + R_1 // R_2 // r_\pi} v_{in} \approx v_{in}$$

$$i_1 = -g_m v_i \approx -g_m v_{in}$$

$$v_{out} = i_1 \times [R_{out} // R_L] = i_1 \times [(R_C // r_o) // R_L] = -g_m (R_C // r_o // R_L) v_{in}$$

$$\Rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_m (R_C // r_o // R_L) = -144.3$$

# Common Source (CS) Amplifier

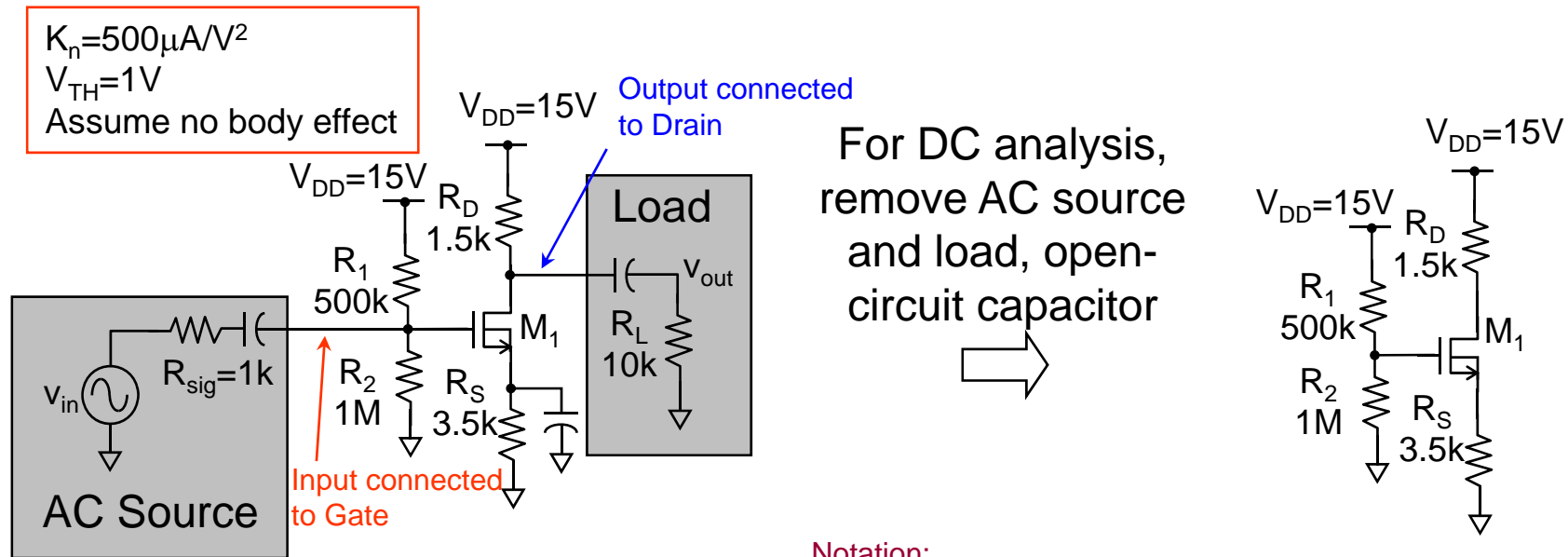


Notation:

$V_{G,M1}$ : Drain voltage of  $M_1$   
 $V_{S,M1}$ : Source voltage of  $M_1$   
 $V_{D,M1}$ : Drain voltage of  $M_1$   
 $V_{B,M1}$ : Body voltage of  $M_1$

- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- Input** connected to **Gate**, **output** connected to **Drain**, **Source** connected to neither input nor output  $\Rightarrow$  **Common Source (CS)**
- DC Analysis refer to “MOSFET Lecture Notes” slide 29

# DC Analysis for CS Amplifier

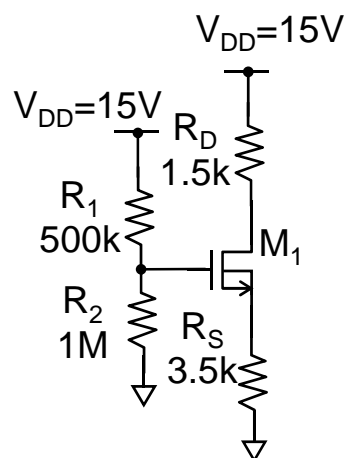

$K_n = 500 \mu\text{A}/\text{V}^2$   
 $V_{TH} = 1\text{V}$   
 Assume no body effect

## Determine DC biasing

$$V_{G,M1} = \frac{1\text{M}}{500\text{k} + 1\text{M}} \times 15 = 10\text{V}$$

*Square Law :*

$$\begin{aligned}
 I_{D,M1} &= K_n (V_{GS} - V_{TH})^2 \\
 &= K_n (V_{G,M1} - V_{S,M1} - V_{TH})^2 \\
 &= 500 \mu (9 - V_{S,M1})^2 \dots (1)
 \end{aligned}$$

*Ohm's Law :*

$$I_{D,M1} = I_{S,M1} = \frac{V_{S,M1}}{R_S} = \frac{V_{S,M1}}{3.5\text{k}} \dots (2)$$

$$\Rightarrow \frac{V_{S,M1}}{3.5\text{k}} = 500 \mu (9 - V_{S,M1})^2$$

$$1.75V_{S,M1}^2 - 32.5V_{S,M1} + 141.75 = 0$$

$$\Rightarrow V_{S,M1} = 6.94 \text{ or } 11.63$$

$$11.63 > V_{G,M1} \Rightarrow \text{invalid}$$

$$I_{D,M1} = 2\text{mA}$$

$$V_{DS} = V_{DD} - I_{D,M1} R_D - V_{S,M1} = 5.06$$

$$V_{GS} - V_{TH} = 2.06$$

$$\Rightarrow V_{DS} > V_{GS} - V_{TH} \quad \text{Device operates at saturation region}$$


## Determine AC small signal parameter

$$g_m = 2\sqrt{K_n I_{D,M1}} = 2\text{mA}/\text{V}$$

$$r_o = \frac{1}{\lambda I_{D,M1}} = \infty$$

Need to check for device operation region to ensure Square Law formula can be applied.

# Common Source (CS)

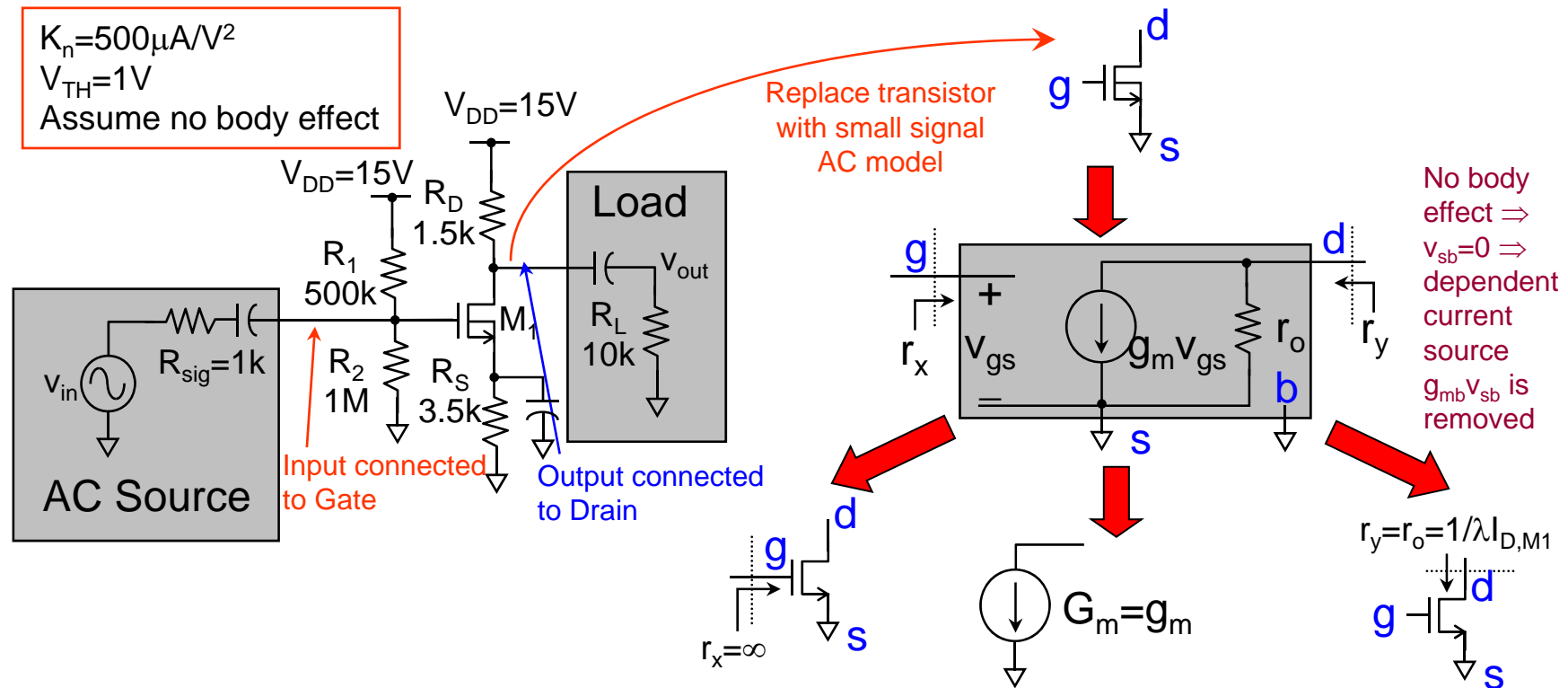

## Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the gate ( $r_x$ ) is open circuit. **No need to rederive.**

## Important Result:

For CS,  $G_m$  is directly given by  $g_m$ . **No need to rederive.**



## Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the drain ( $r_y$ ) is directly given by  $r_o$ . **No need to rederive.**

# AC Analysis for CS

$$K_n = 500 \mu\text{A}/\text{V}^2$$

$$V_{TH} = 1\text{V}$$

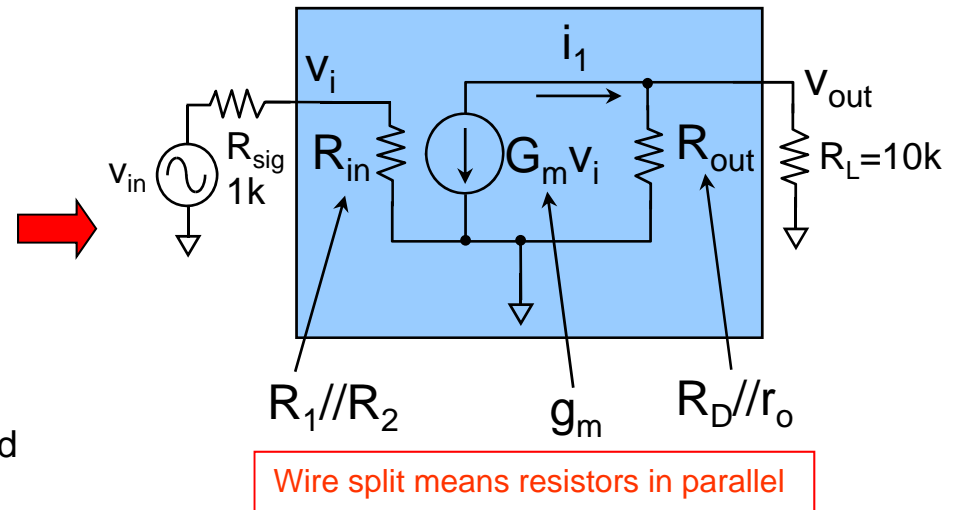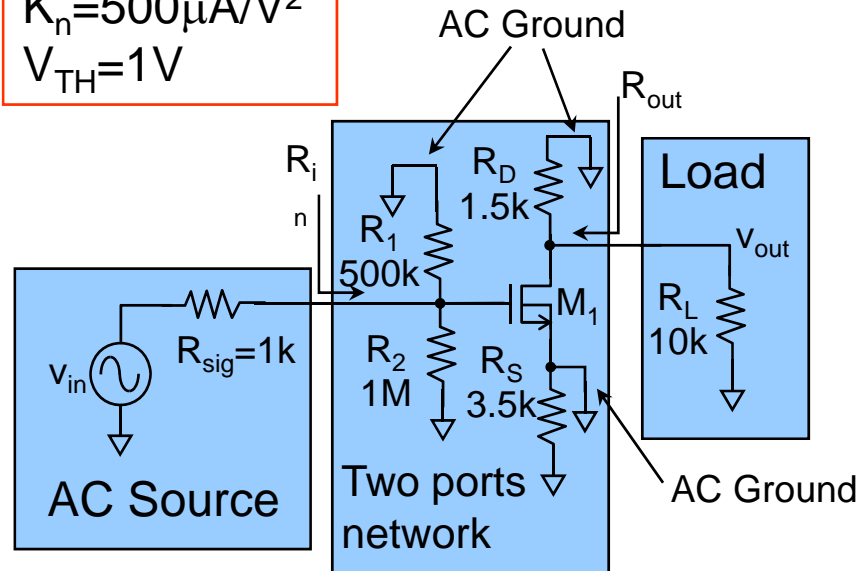

$$g_m = 2\text{mA}/\text{V}$$

$$r_o = \infty$$

$$v_i = \frac{R_{in}}{R_{sig} + R_{in}} v_{in} = \frac{R_1 // R_2}{R_{sig} + R_1 // R_2} v_{in} \approx v_{in}$$

$$i_1 = -g_m v_i \approx -g_m v_{in}$$

$$v_{out} = i_1 \times [R_{out} // R_L] = i_1 \times [(R_D // r_o) // R_L] = -g_m (R_D // r_o // R_L) v_{in}$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = -g_m (R_D // r_o // R_L) = -2.61$$

# Characteristic of CE/CS


---

- High input resistance
- High output resistance
- Medium gain
- Polarity inversion, i.e.  $v_{out}$  and  $v_{in}$  has opposite sign
- The higher the  $G_m$  and the total output resistance, the higher the gain ( $A_V$ )
- BJT provides larger  $g_m$  than MOS


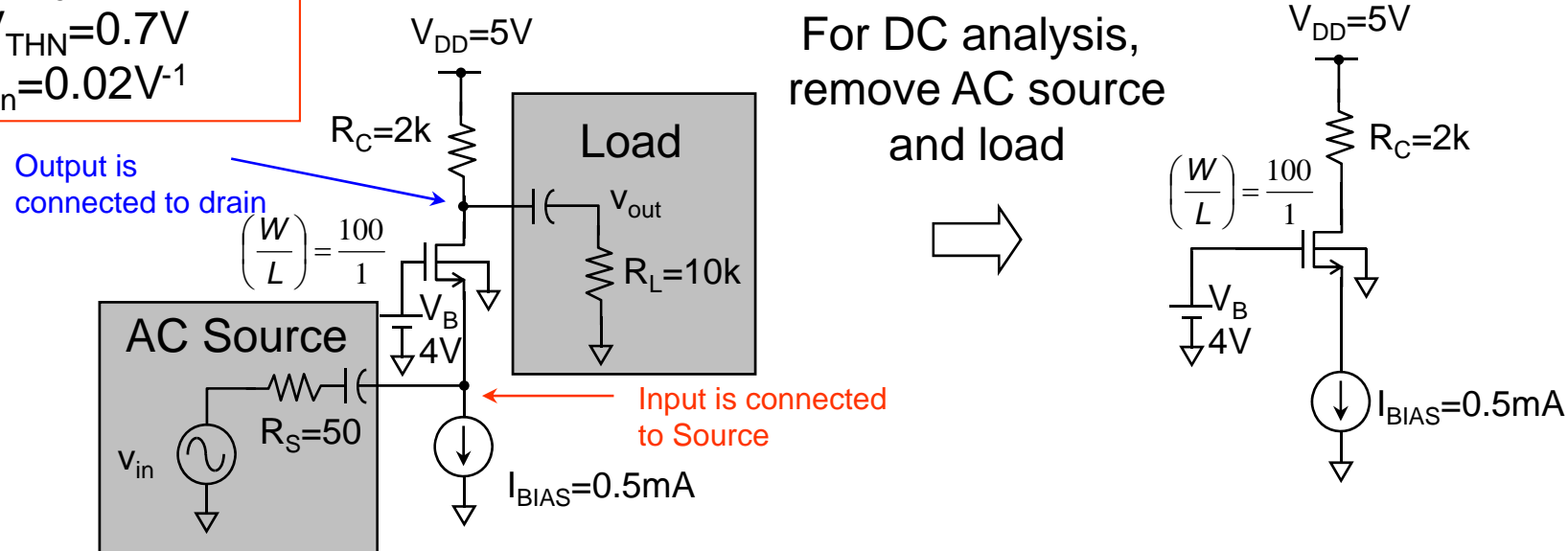
# Common Gate (CG)


$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A/V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$



- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- Input** connected to **Source**, **output** connected to **Drain**, **Gate** connected to neither input nor output  $\Rightarrow$  **Common Gate (CG)**
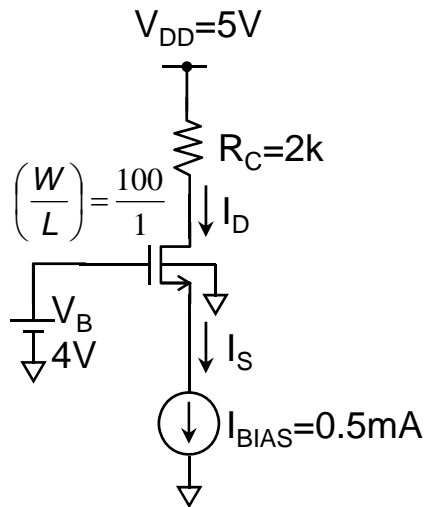
# DC Analysis for CG

- Remove source/load section when doing DC analysis



$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A}/\text{V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$

Determine DC biasing

$$I_D = I_S = I_{BIAS} = 0.5\text{mA}$$

$$\left(\frac{W}{L}\right) = \frac{100}{1}$$

Good approximation, no  
need to go through detailed  
calculations

Determine AC  
small signal parameter

$$\begin{aligned}g_m &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \\ &= 2.83\text{mA}/\text{V}\end{aligned}$$

$$g_{mb} \approx -\frac{g_m}{4} = -0.71\text{mA}/\text{V}$$


$$r_i = \infty$$

$$r_o = \frac{1}{\lambda_n I_D} = 100\text{k}\Omega$$


Diagram illustrating the AC equivalent circuit for a common-emitter amplifier. The left side shows the full circuit with an AC source  $v_{in}$ , resistor  $R_S=50$ , a DC voltage source  $V_{DD}=5V$ , collector resistor  $R_C=2k$ , load resistor  $R_L=10k$ , and a DC current source  $I_{BIAS}=0.5mA$ . The right side shows the AC equivalent circuit where DC sources are replaced by AC grounds. Annotations include: "DC Voltage Source  $\rightarrow$  AC Ground" (twice), "DC Block Capacitor  $\rightarrow$  AC Short Circuit" (twice), and "DC Current Source  $\rightarrow$  AC Open Circuit". A large arrow points from the full circuit to the AC equivalent circuit.

- 6A-27**

# AC Analysis for CG

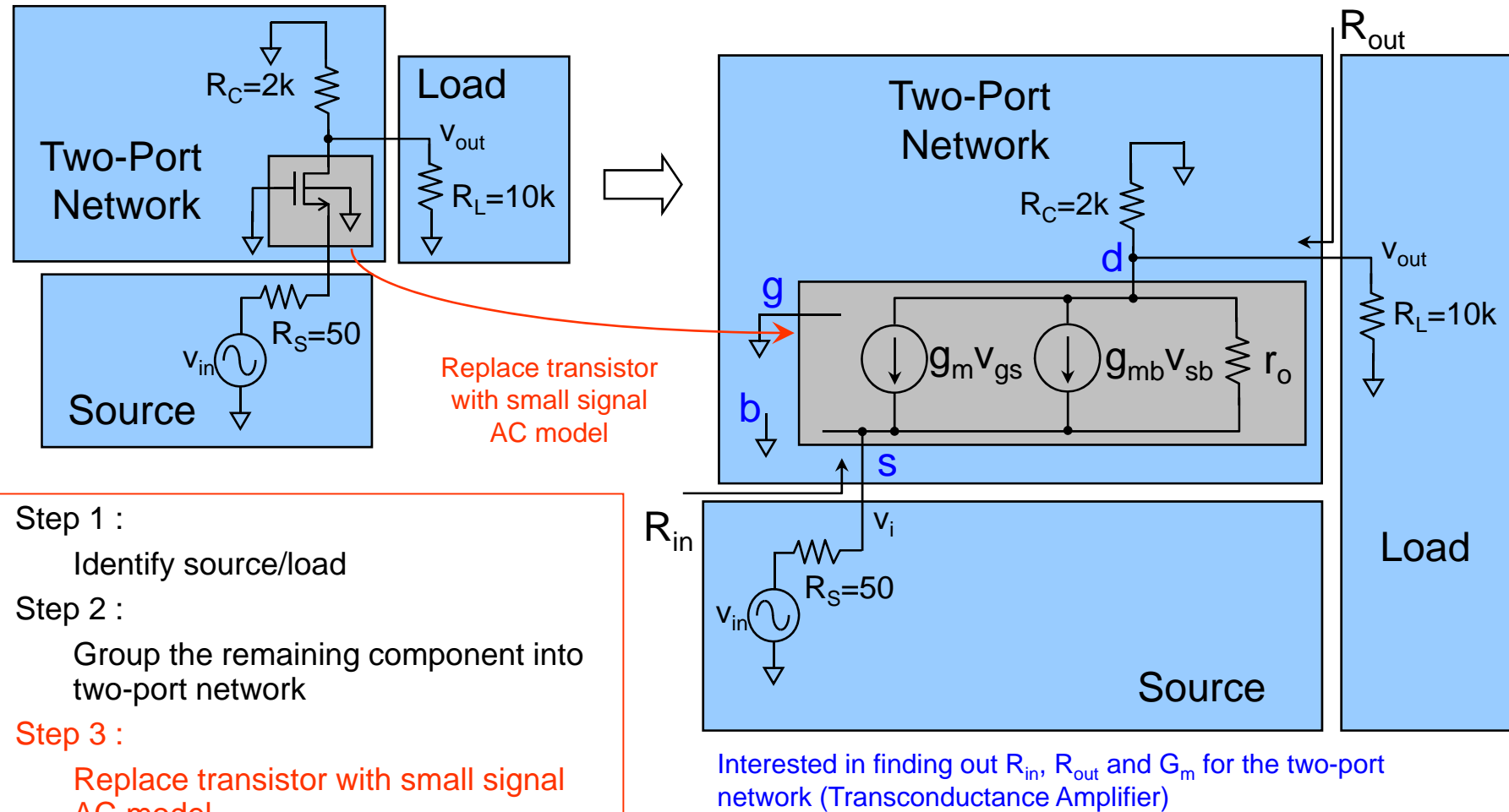

# CG – Two-Port Network ( $G_m$ )

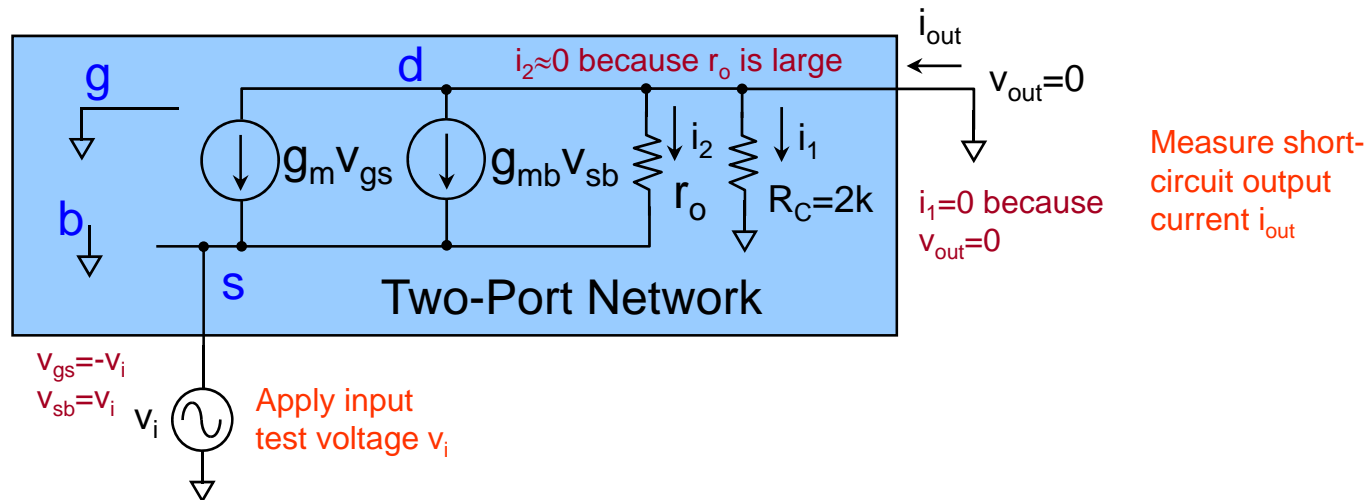


**Important Result :**  
Transconductance ( $G_m$ )  
for CG is just  $-(g_m - g_{mb})$

$$i_{out} \Big|_{v_{out}=0} = g_m v_{gs} + g_{mb} v_{sb} + \cancel{i_2} \approx -(g_m - g_{mb}) v_i$$

$$G_m = \frac{i_{out}}{v_i} \Big|_{v_{out}=0} \approx -(g_m - g_{mb}) = -3.54 \text{ mA/V}$$

# CG – Two-Port Network ( $R_{in}$ )

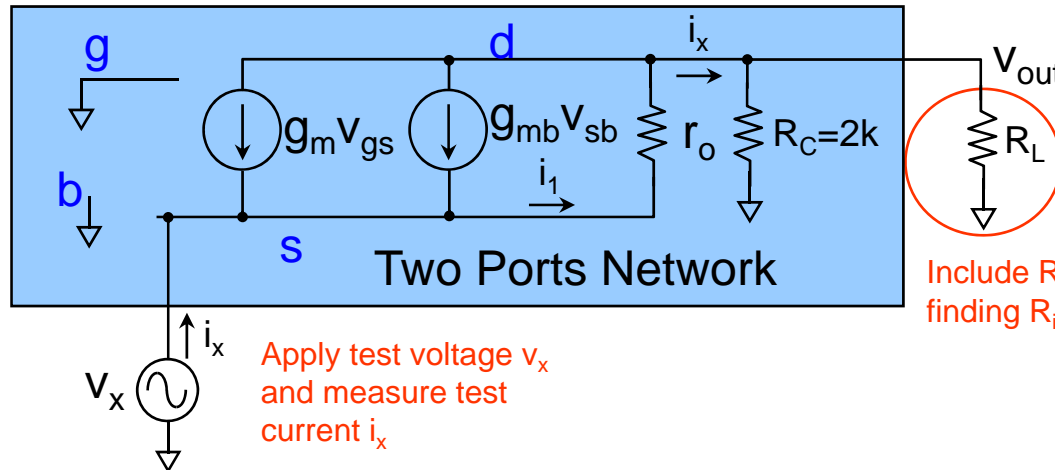

$$v_{gs} = -v_x \quad v_{sb} = v_x$$

$$i_1 = \frac{v_x - v_{out}}{r_o}$$

Include  $R_L$  when finding  $R_{in}$

Apply test voltage  $v_x$  and measure test current  $i_x$

$$\begin{cases} i_x = -g_m v_{gs} - g_{mb} v_{sb} + i_1 \\ = (g_m - g_{mb}) v_x + \frac{v_x - v_{out}}{r_o} \\ v_{out} = i_x (R_C // R_L) \end{cases}$$

Eliminate  $v_{out}$  and keep  $v_x$  and  $i_x$


$$\Rightarrow i_x = (g_m - g_{mb}) v_x + \frac{v_x}{r_o} - i_x \frac{(R_C // R_L)}{r_o}$$

$$\Rightarrow R_{in} = \frac{1 + \frac{(R_C // R_L)}{r_o}}{(g_m - g_{mb}) + \frac{1}{r_o}}$$

$$\approx \frac{1}{g_m - g_{mb}} \cdot \frac{r_o + (R_C // R_L)}{r_o}$$

$$g_m - g_{mb} \gg 1/r_o$$

# CG – Two-Port Network ( $R_{in}$ )

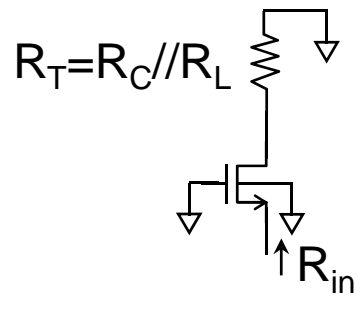

$$R_{in} \approx \frac{1}{g_m - g_{mb}} \cdot \frac{r_o + R_T}{r_o}$$

$$\approx \frac{1}{g_m - g_{mb}} \quad [If \ R_T \ll r_o]$$

## Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the source ( $R_{in}$ ) is directly given by the formula. **No need to rederive.**

Example :


$$R_C = 2k \quad R_L = 10k \quad r_o = 100k$$

$$\Rightarrow R_T = (R_C // R_L) \ll r_o$$

$$\Rightarrow R_{in} = \frac{1}{g_m - g_{mb}} = 282$$

- If  $R_C // R_L$  is negligible compared to  $r_o$ , the input resistance ( $R_{in}$ ) reduced to the inverse of the transconductance  $[1/(g_m - g_{mb})]$

# CG – Two-Port Network ( $R_{out}$ )

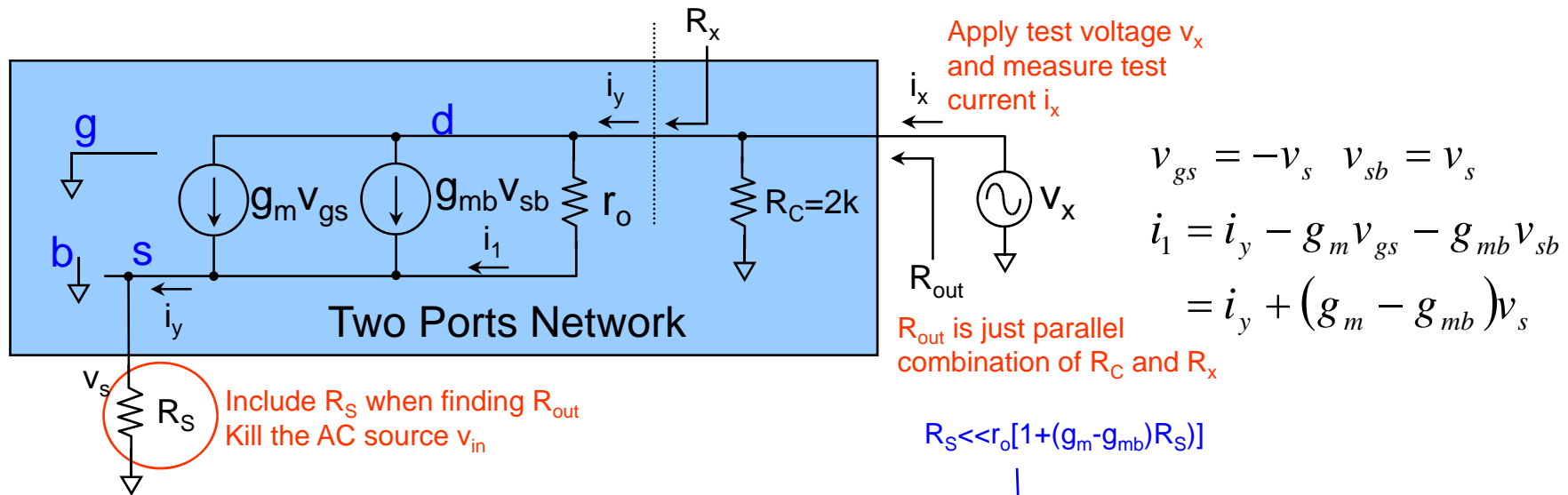

$$R_x = \frac{v_x}{i_y}$$

Eliminate  $v_s$  and keep  $v_x$  and  $i_y$

$$\begin{cases} v_s = i_y R_S \\ v_x = v_s + i_1 r_o \\ = v_s + [i_y + (g_m - g_{mb}) v_s] r_o \end{cases}$$

$$\Rightarrow v_x = i_y R_S + i_y r_o + i_y (g_m - g_{mb}) R_S r_o$$


$$\Rightarrow R_x = \frac{v_x}{i_y} = R_S + r_o [1 + (g_m - g_{mb}) R_S]$$

$$R_{out} = R_C \parallel R_x$$

$$\approx R_C \parallel \{r_o [1 + (g_m - g_{mb}) R_S]\} \approx R_C$$



# CG – Two-Port Network ( $R_{out}$ )

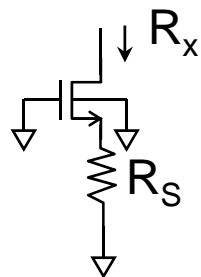

$$R_x \approx r_o [1 + (g_m - g_{mb}) R_S]$$

## Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the drain ( $R_x$ ) is directly given by the formula. **No need to rederive.**

Example :

$$R_S = 50 \quad r_o = 100k$$

$$g_m = 2.83m \quad g_{mb} = -0.71m$$

$$\Rightarrow R_x \approx 118k \gg R_C$$

$$\Rightarrow R_{out} \approx R_C = 2k$$


- Source side resistor help boost up the output resistance of the transistor ( $R_x$ )

# CG – Important Results

1

**Important Result :**  
Transconductance ( $G_m$ )  
for CG is just  $-(g_m - g_{mb})$


2

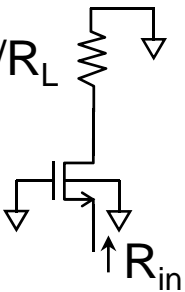

$$R_{in} \approx \frac{1}{g_m - g_{mb}} \cdot \frac{r_o + R_T}{r_o}$$


$$\approx \frac{1}{g_m - g_{mb}} \quad [If \ R_T \ll r_o]$$

3

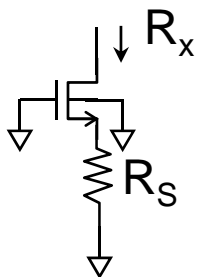


$$R_x \approx r_o [1 + (g_m - g_{mb}) R_S]$$

# CG – Two-Port Network

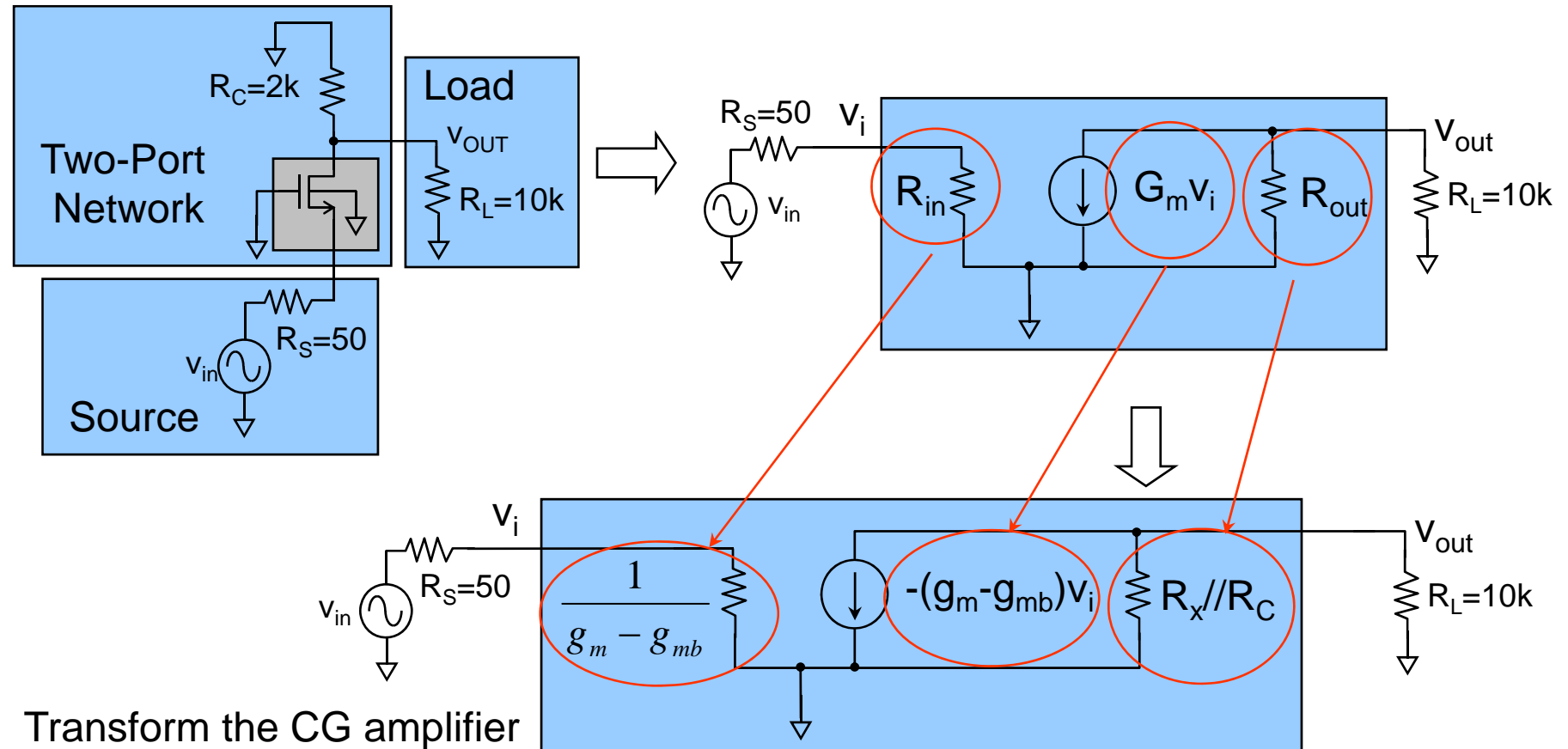

Transform the CG amplifier  
into **two-port**  
**transconductance amplifier**

# CG – Two-Port Network ( $A_V$ )

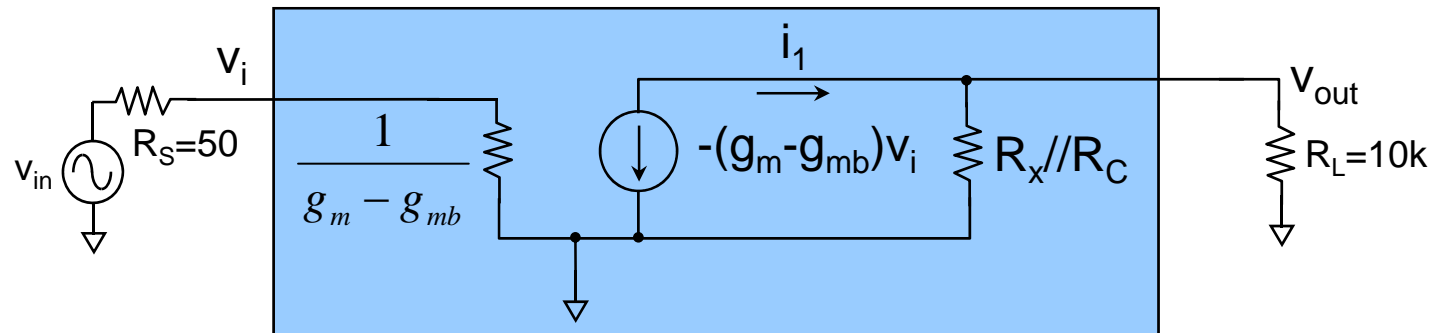

$$v_i = v_{in} \times \frac{R_{in}}{R_S + R_{in}}$$

$$R_{in} = \frac{1}{g_m - g_{mb}}$$

$$i_1 = -[-(g_m - g_{mb})v_i] \\ = (g_m - g_{mb})v_i$$

$$v_{out} = i_1 \times [(R_x // R_C) // R_L]$$


$$\approx (g_m - g_{mb}) \times v_i \times (R_C // R_L)$$

$R_x$  is too big

$$\approx (g_m - g_{mb}) \times \left( v_{in} \times \frac{R_{in}}{R_S + R_{in}} \right) \times (R_C // R_L)$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_S + R_{in}} (g_m - g_{mb}) (R_C // R_L)$$


# Common Base (CB)

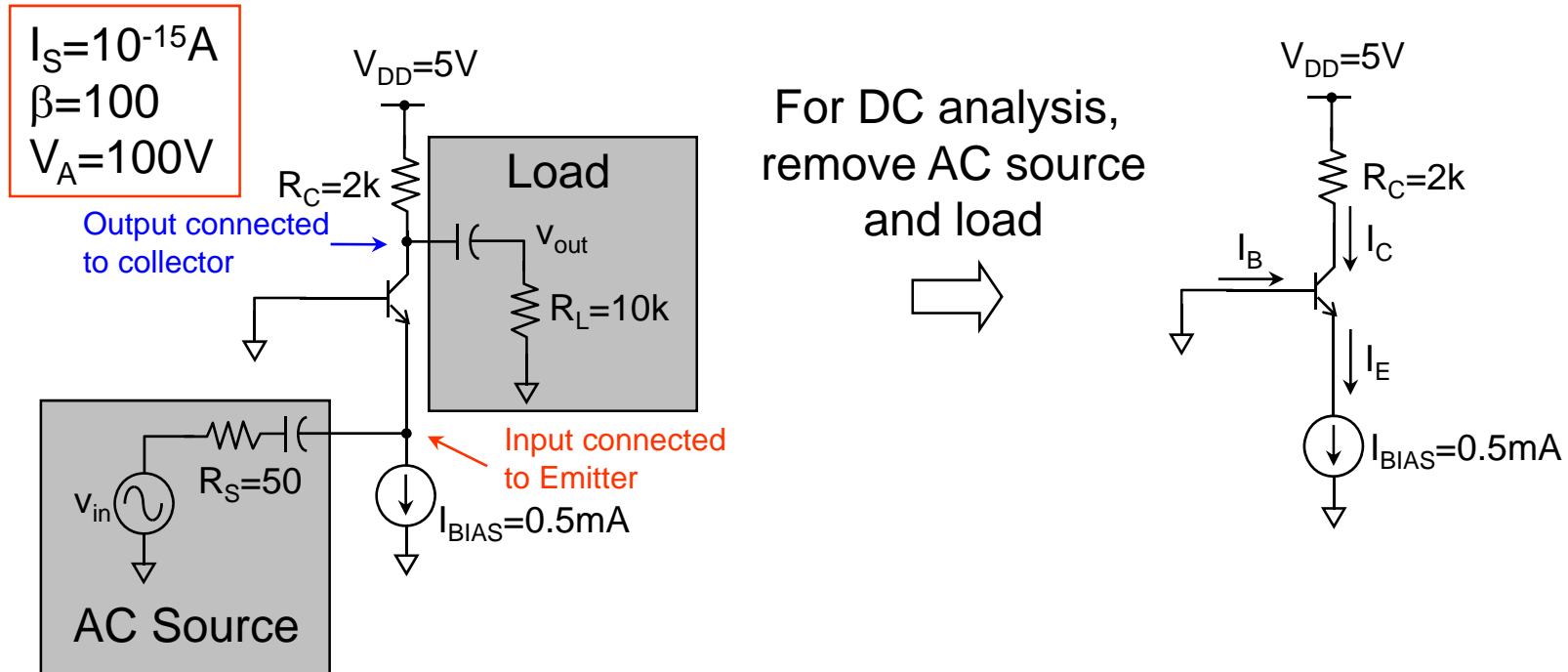

- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- Input** connected to **Emitter**, **output** connected to **Collector**, **Base** connected to neither input nor output  $\Rightarrow$  **Common Base (CB)**
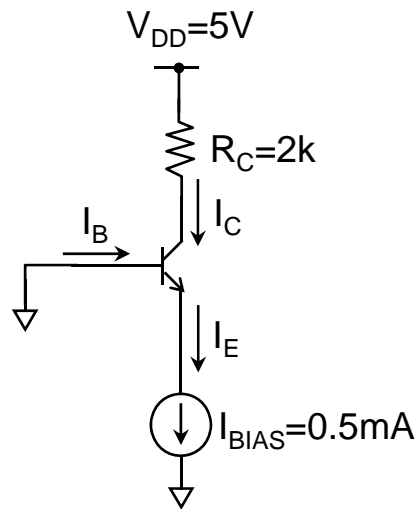
# DC Analysis for CB (Self Reading)

- Remove AC source/load section when doing DC analysis



$$\begin{aligned} I_S &= 10^{-15} \text{A} \\ \beta &= 100 \\ V_A &= 100 \text{V} \end{aligned}$$

Determine DC biasing

$$V_T = \frac{kT}{q} = 26 \text{mV}$$

$$I_E = I_{\text{BIAS}} = 0.5 \text{mA}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = 0.495 \text{mA}$$

$$I_B = \frac{I_C}{\beta} = 4.95 \mu\text{A}$$


Determine AC small signal parameter

$$g_m = \frac{I_C}{V_T} = 19 \text{mA/V}$$


$$r_\pi = \frac{\beta}{g_m} = 5.26 \text{k}\Omega$$

$$r_o = \frac{V_A}{I_C} = 202 \text{k}\Omega$$

# AC Analysis for CB (Self Reading)

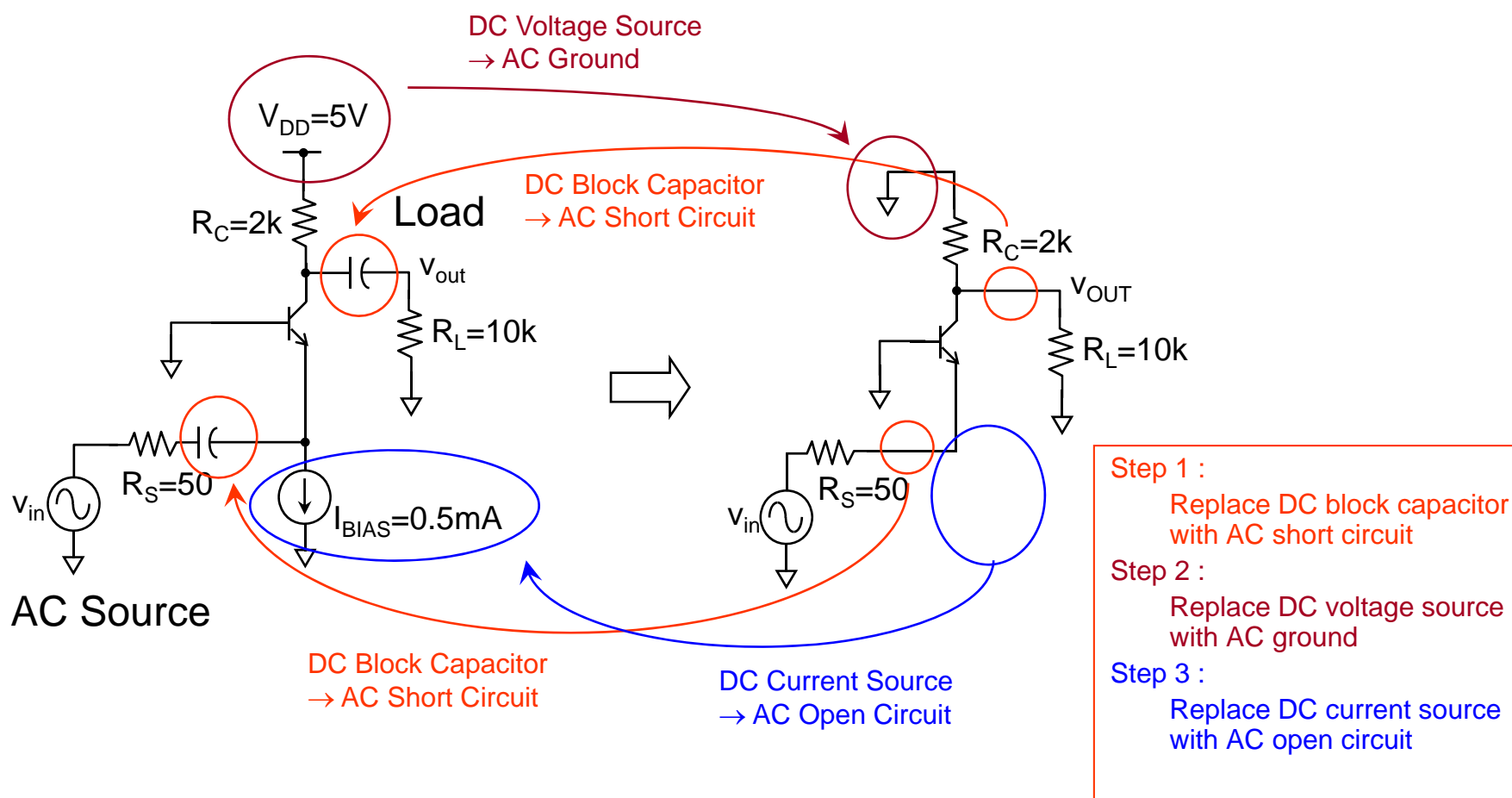


# AC Analysis for CB (Self Reading)

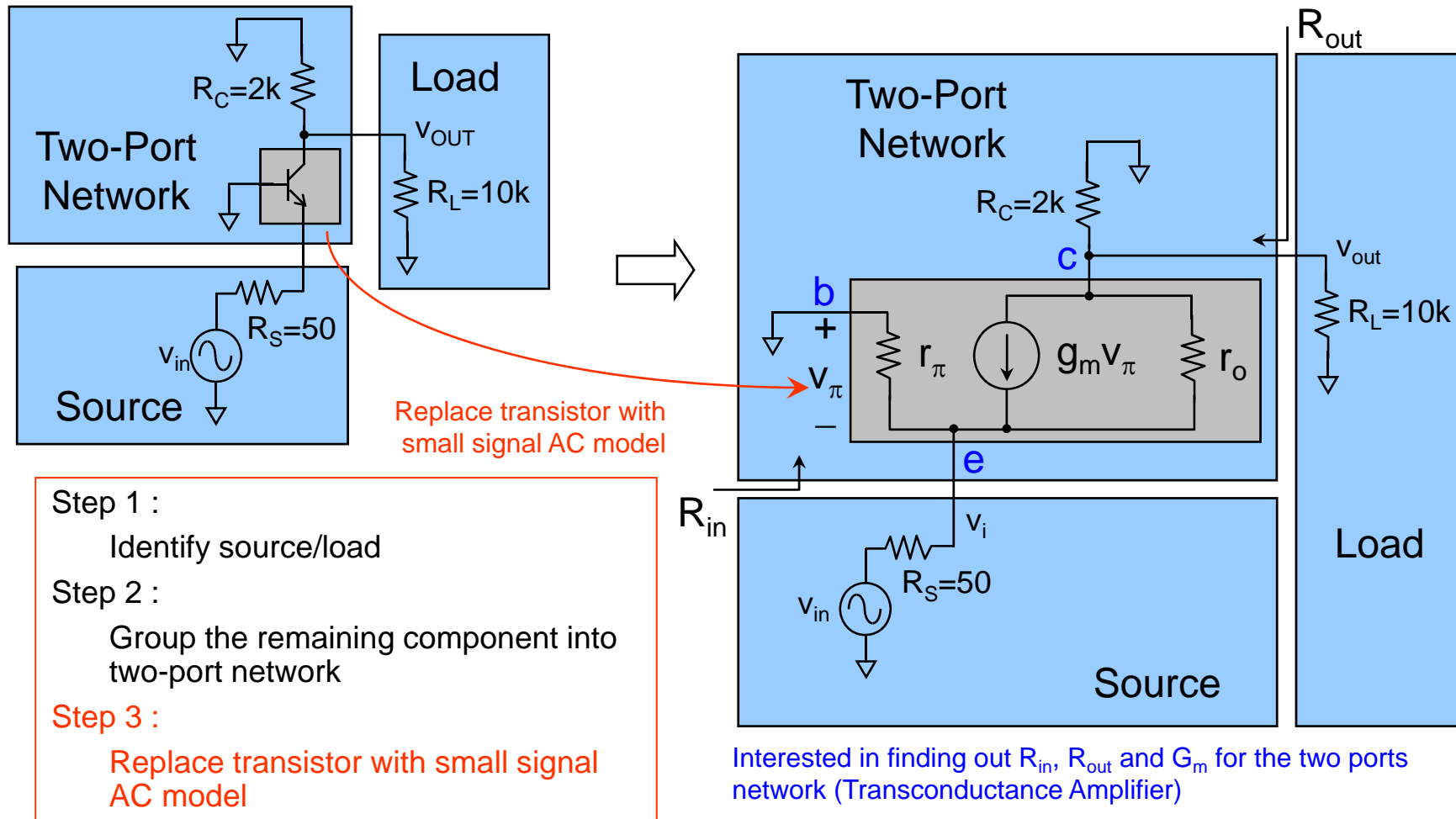



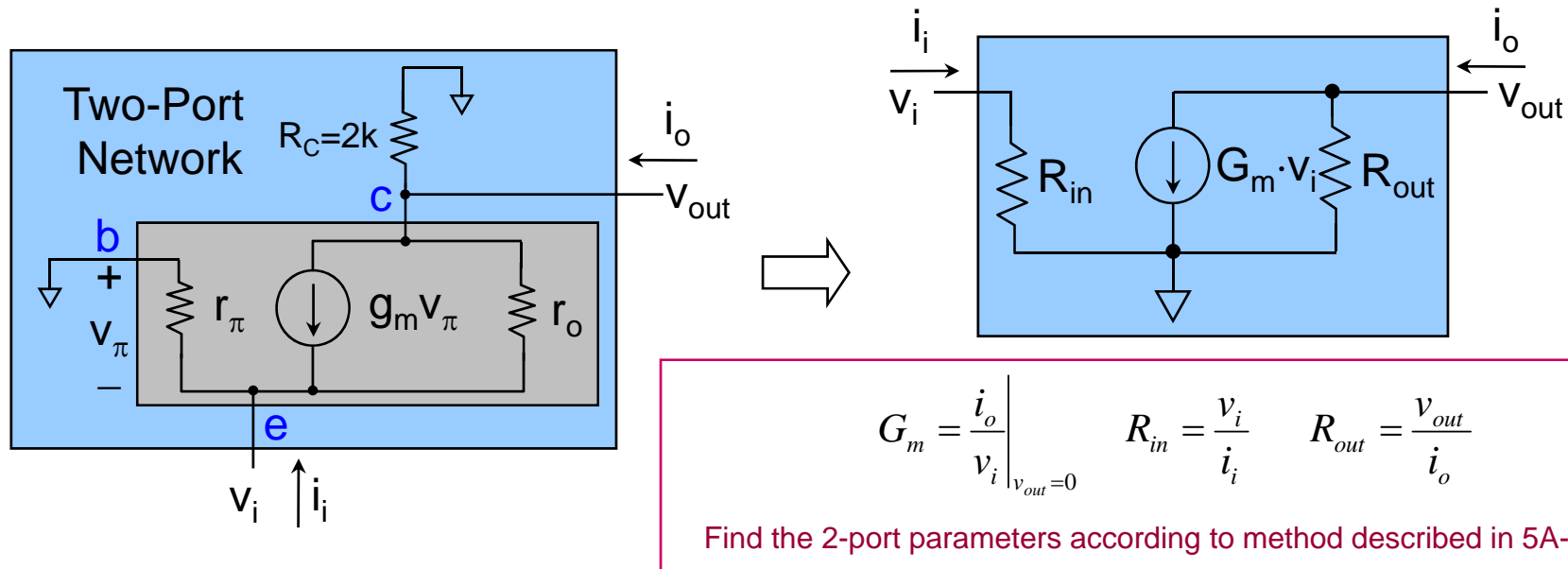
# Mapping Two-Port Network for CB (Self Reading)



- Similar concept as Thevenin equivalent
- Complicated two-port network can be represented by a two-port network characterized by only 3 parameters,  $R_{in}$ ,  $R_{out}$  and  $G_m$

# CB – Finding $G_m$ (Self Reading)

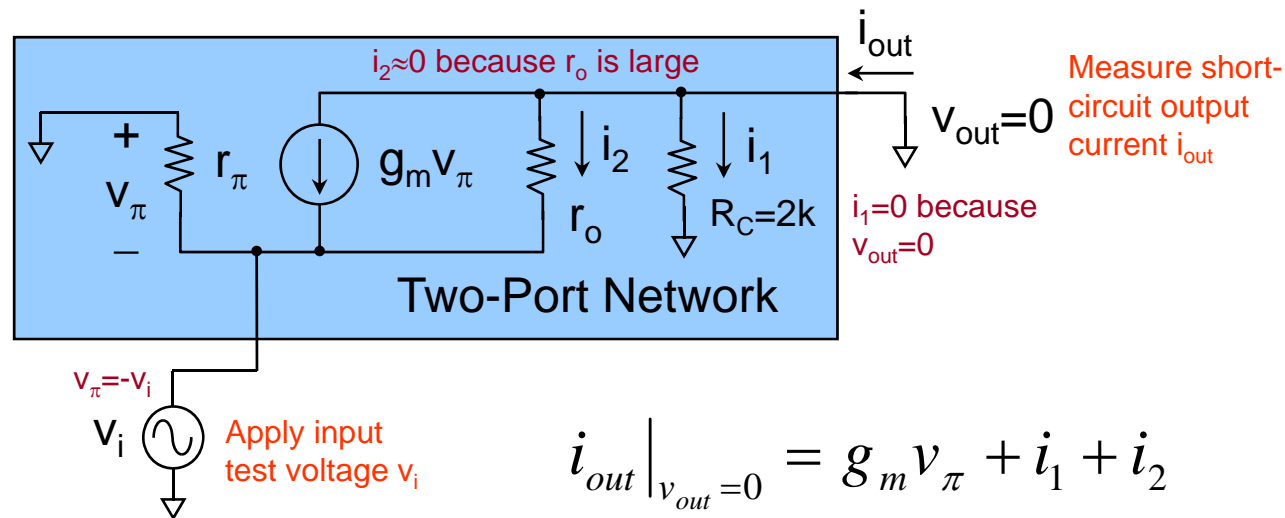


**Important Result :**  
Transconductance ( $G_m$ )  
for CB is just  $-g_m$

$$i_{out} \Big|_{v_{out}=0} = g_m v_\pi + i_1 + i_2$$

$$\approx -g_m v_i$$

$$G_m = \frac{i_{out}}{v_i} \Big|_{v_{out}=0} \approx -g_m = -19mA / V$$

# CB – Finding $R_{in}$ (Self Reading)

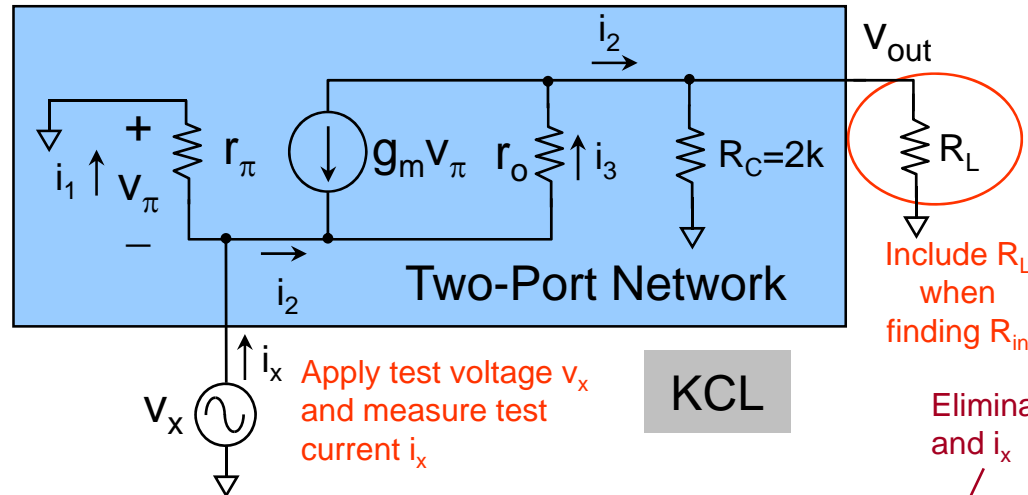

$$v_\pi = -v_x \quad i_1 = \frac{v_x}{r_\pi} \quad i_3 = \frac{v_x - v_{out}}{r_o}$$

$$i_2 = i_x - i_1 = i_x - \frac{v_x}{r_\pi}$$

Include  $R_L$   
when  
finding  $R_{in}$

Eliminate  $v_{out}$  and keep  $v_x$   
and  $i_x$

$g_m \gg 1/r_\pi$  and  $1/r_o$


$$\begin{cases} i_x = i_1 - g_m v_\pi + i_3 = \frac{v_x}{r_\pi} + g_m v_x + \frac{v_x - v_{out}}{r_o} \\ v_{out} = i_2 (R_C // R_L) = \left( i_x - \frac{v_x}{r_\pi} \right) (R_C // R_L) \end{cases}$$

$$\Rightarrow i_x = \frac{v_x}{r_\pi} + g_m v_x + \frac{v_x}{r_o} - i_x \frac{(R_C // R_L)}{r_o} + \frac{v_x (R_C // R_L)}{r_\pi r_o}$$

$$\Rightarrow R_{in} = \frac{1 + \frac{(R_C // R_L)}{r_o}}{g_m + \frac{1}{r_\pi} + \frac{1}{r_o} + \frac{(R_C // R_L)}{r_\pi r_o}}$$

$$\approx \frac{1}{g_m} \cdot \frac{r_o + (R_C // R_L)}{r_o + \frac{(R_C // R_L)}{\beta}}$$

# CB – Finding $R_{in}$ (Self Reading)

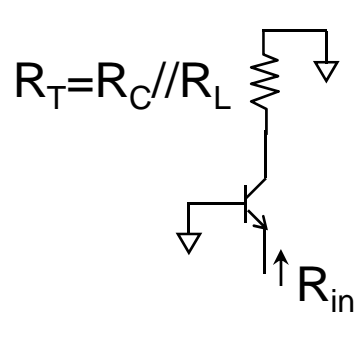
$$R_T = R_C // R_L$$
$$R_{in} \approx \frac{1}{g_m} \cdot \frac{r_o + R_T}{r_o + \frac{R_T}{\beta}}$$
$$\approx \frac{1}{g_m} \quad \left[ \text{If } R_T \ll r_o \right]$$

## Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the emitter ( $R_{in}$ ) is directly given by the formula. **No need to rederive.**

Example :


$$R_C = 2k \quad R_L = 10k \quad r_o = 202k$$

$$\Rightarrow R_T = (R_C // R_L) \ll r_o$$

$$\Rightarrow R_{in} = \frac{1}{g_m} = 53$$

- If  $R_C // R_L$  is negligible compared to  $r_o$ , the input resistance ( $R_{in}$ ) reduced to the inverse of the transconductance ( $1/g_m$ )

# CB – Finding $R_{out}$ (Self Reading)

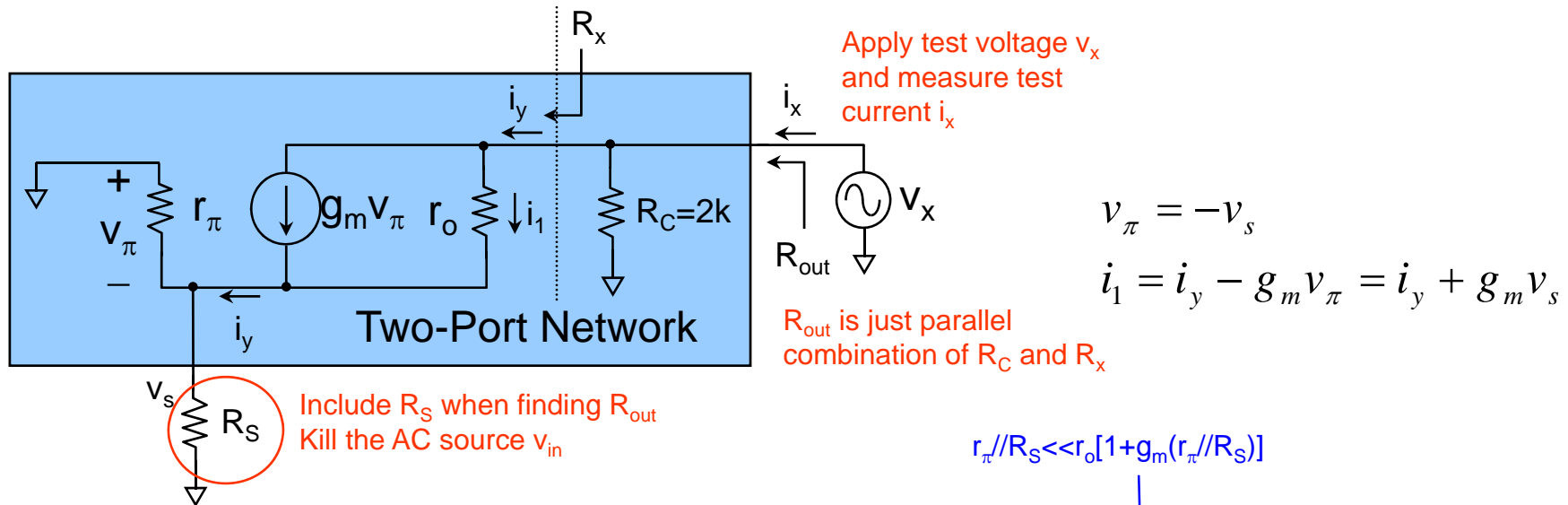

Eliminate  $v_s$  and keep  $v_x$  and  $i_y$

$$R_x = \frac{v_x}{i_y}$$

$$\begin{cases} v_s = i_y (r_\pi // R_S) \\ v_x = v_s + i_1 r_o = v_s + (i_y + g_m v_s) r_o \end{cases}$$


$$\Rightarrow v_x = i_y (r_\pi // R_S) + i_y r_o + i_y g_m (r_\pi // R_S) r_o$$

$$\Rightarrow R_x = \frac{v_x}{i_y} = (r_\pi // R_S) + r_o [1 + g_m (r_\pi // R_S)]$$

$$R_{out} = R_C // R_x \approx R_C // \{r_o [1 + g_m (r_\pi // R_S)]\} \approx R_C$$


$$r_\pi // R_S \ll r_o [1 + g_m (r_\pi // R_S)]$$

# Equivalent Resistance (Self Reading)

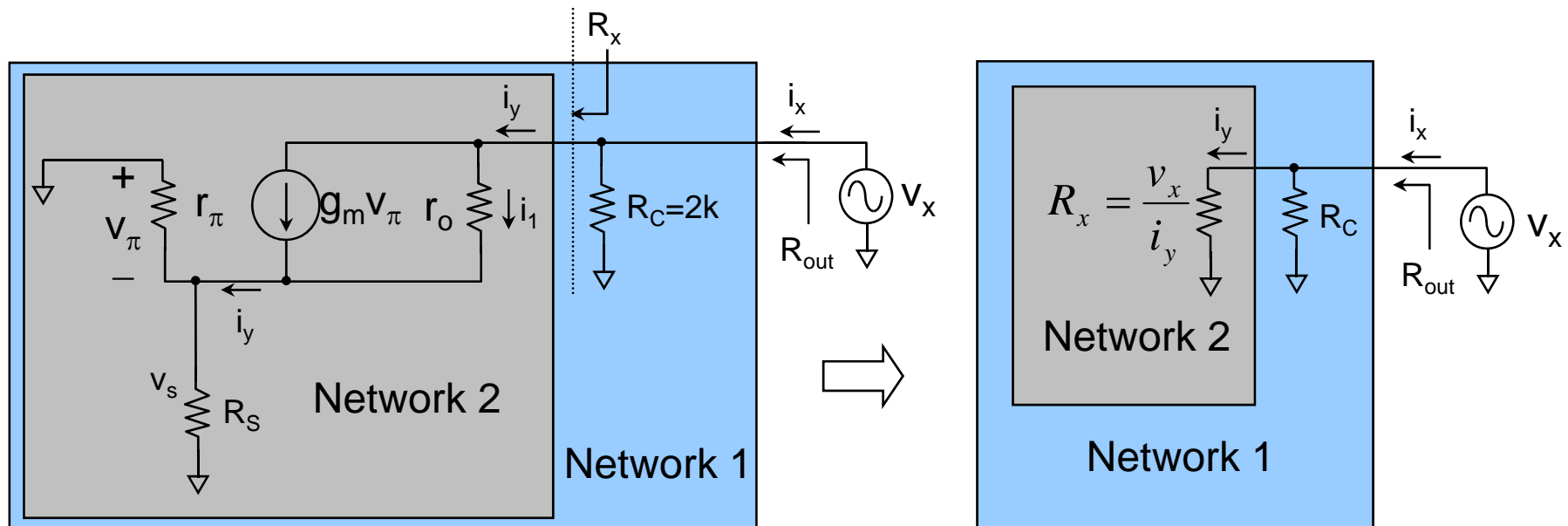

- A complicated network can be reduced to an equivalent driving point resistance

# CB – Finding $R_{out}$ (Self Reading)

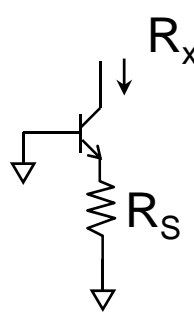
$$R_x \approx r_o [1 + g_m (r_\pi // R_S)]$$
$$\text{If } R_S \ll r_\pi \Rightarrow R_x = r_o (1 + g_m R_S)$$
$$\text{If } R_S \gg r_\pi \Rightarrow R_x = r_o (1 + g_m r_\pi) = r_o (1 + \beta)$$

## Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the collector ( $R_x$ ) is directly given by the formula. **No need to rederive.**

Example :

$$R_S = 50 \quad r_\pi = 5.26k$$
$$r_o = 202k \quad g_m = 19m$$
$$\Rightarrow R_x \approx 394k \gg R_C$$
$$\Rightarrow R_{out} \approx R_C = 2k$$


- Emitter side resistor help boost up the output resistance of the transistor ( $R_x$ )
- For BJT, the maximum achievable boost up is  $(1+\beta)r_o$

# CB – Important Results

1

**Important Result :**  
Transconductance ( $G_m$ )  
for CB is just  $-g_m$


2

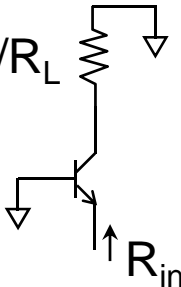

$$R_T = R_C // R_L \quad R_{in} \approx \frac{1}{g_m} \cdot \frac{r_o + R_T}{r_o + \frac{R_T}{\beta}}$$

$$\approx \frac{1}{g_m} \quad [If \quad R_T \ll r_o]$$

3

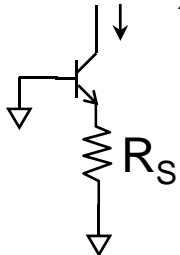


$$R_x \approx r_o [1 + g_m (r_\pi // R_S)]$$

$$If \quad R_S \ll r_\pi \Rightarrow R_x = r_o (1 + g_m R_S)$$

$$If \quad R_S \gg r_\pi \Rightarrow R_x = r_o (1 + g_m r_\pi) = r_o (1 + \beta)$$




# CB – Two-Port Network

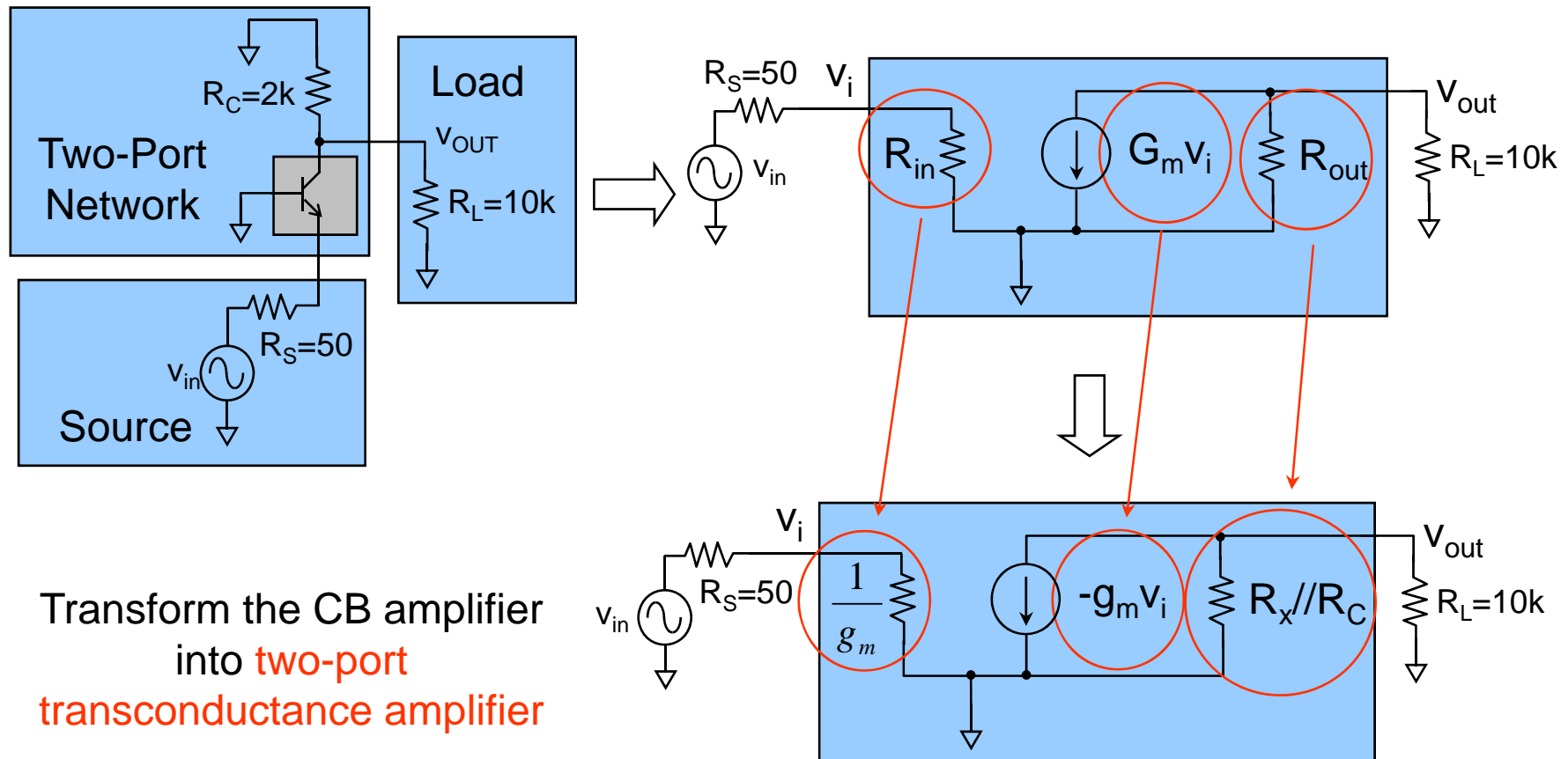

Transform the CB amplifier  
 into **two-port**  
**transconductance amplifier**

# CB – Two-Port Network ( $A_V$ )

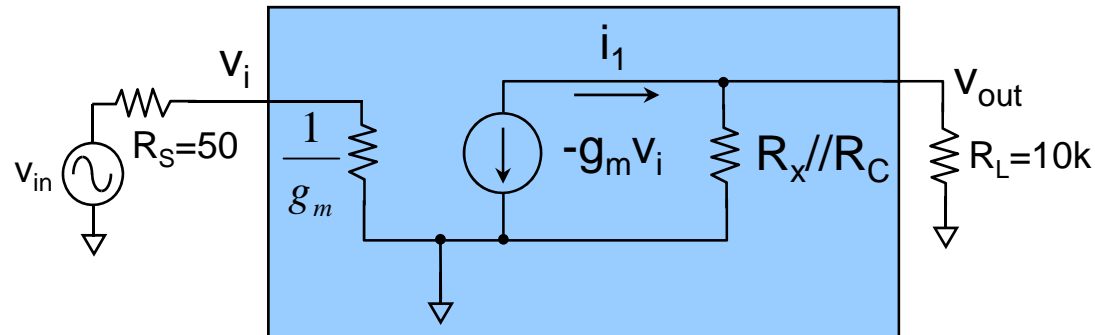

$$v_i = v_{in} \times \frac{R_{in}}{R_S + R_{in}}$$

$$R_{in} = \frac{1}{g_m}$$

$$i_1 = -(-g_m v_i) = g_m v_i$$

$$v_{out} = i_1 \times [(R_x // R_C) // R_L]$$

$$= g_m \times v_i \times [(R_x // R_C) // R_L]$$

$$\approx g_m \times \left( v_{in} \times \frac{R_{in}}{R_S + R_{in}} \right) \times (R_C // R_L)$$

$R_x$  is too big

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = \frac{R_{in}}{R_S + R_{in}} g_m (R_C // R_L)$$

# Characteristic of CB/CG

---

- Low input resistance
- High output resistance
- Medium gain
- No polarity inversion
- The higher the  $G_m$  and the total output resistance, the higher the gain ( $A_V$ )
- BJT provides larger  $g_m$  than MOS ( $g_m - g_{mb}$ )

# Lecture Summary

---

- Introduced 2-port voltage and transconductance network.
- Analyze CE/CS amplifier.
- Analyze CB/CG amplifier.

# Reading Assignment

---


- **Reading: Reference Book (Sedra & Smith)**

Chapter 1, pp. 23 – 31. (2-port networks)



Chapter 3, pp. 249 – 252, pp. 257 – 260. (CE, CB)

Chapter 4, pp. 396 – 405. (CS, CG)

# KCL

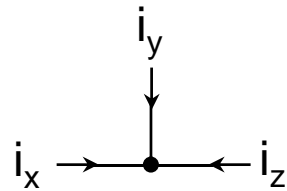

$$i_x + i_y + i_z = 0$$

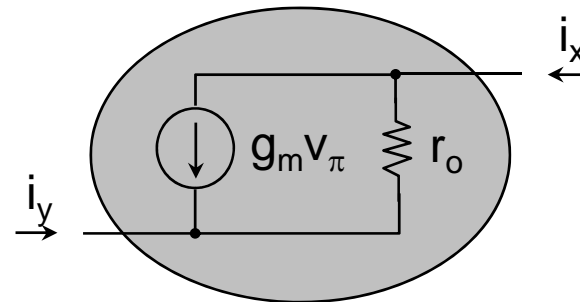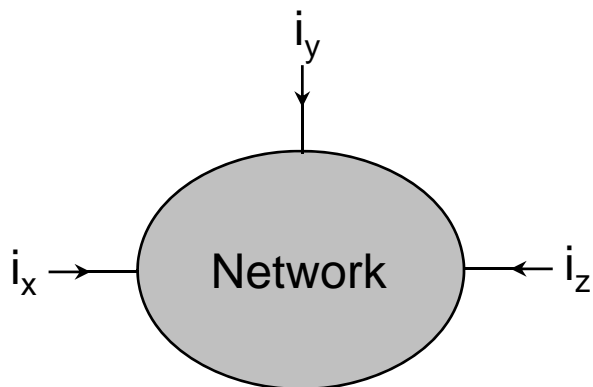

Total current going into  
the network sums to zero

$$i_x + i_y = 0$$

Back