

**NATIONAL UNIVERSITY of SINGAPORE**  
**Department of Electrical and Computer Engineering**

**EE2021 – Devices and Circuits**

**Tutorial 4 Solutions**

**Homework 3:**

**Homework 3 is Question 2 and Question 6 of Tutorial 4. You have to submit the homework assignment in hardcopy in class on Wednesday 1 April 2015.**


**Unless otherwise stated, you may use the tables of the amplifier configurations and equivalent resistances in your lecture notes in your solutions to the questions.**

- Q1. Draw the pull down network (PDN) and pull up network (PUN) of the following logic function:

$$Y = \overline{\{[(A.B) + C].D\} + (E.F)}.$$


Determine also the best case propagation delay of the above PUN,  $t_{pLH,best}$ , in terms of that of an inverter,  $t_{pLH,inv}$ . All NMOS and PMOS transistors in the above logic networks and the inverter have sizing of  $(W/L)_n = n$  and  $(W/L)_p = p$ , respectively.

 1.  $Y = \overline{\{[(A.B) + C].D\} + (E.F)}$   
 $\bar{Y} = \{[(A.B) + C].D\} + (E.F)$



Based on PDN, construct PUN using duality, or
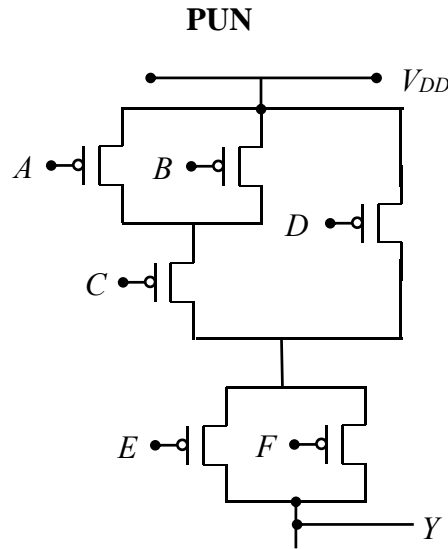
$$\begin{aligned}
 Y &= \overline{\{[(A.B) + C].D\} + (E.F)} = \overline{\{[(A.B) + C].D\}} \cdot \overline{(E.F)} \\
 &= \overline{\{[(A.B) + C] + \bar{D}\}} \cdot (\bar{E} + \bar{F}) = \overline{\{[(A.B) \cdot \bar{C}] + \bar{D}\}} \cdot (\bar{E} + \bar{F}) \\
 &= \overline{\{[(\bar{A} + \bar{B}) \cdot \bar{C}] + \bar{D}\}} \cdot (\bar{E} + \bar{F})
 \end{aligned}$$



Best case equivalent sizing of PUN (i.e., with all PMOS transistors turned on)

$$\begin{aligned}
 \left(\frac{W}{L}\right)_{eq,(\bar{A} + \bar{B})} &= 2p \\
 \left(\frac{W}{L}\right)_{eq,[(\bar{A} + \bar{B}) \cdot \bar{C}]} &= \left[\frac{1}{2p} + \frac{1}{p}\right]^{-1} = \frac{2}{3}p \\
 \left(\frac{W}{L}\right)_{eq,\{[(\bar{A} + \bar{B}) \cdot \bar{C}] + \bar{D}\}} &= \frac{2}{3}p + p = \frac{5}{3}p \\
 \left(\frac{W}{L}\right)_{eq,\{[(\bar{A} + \bar{B}) \cdot \bar{C}] + \bar{D}\} \cdot (\bar{E} + \bar{F})} &= \left[\frac{1}{\frac{5}{3}p} + \frac{1}{2p}\right]^{-1} = \frac{10}{11}p \\
 t_{pLH,best} &= \frac{11}{10} t_{pLH,inv}
 \end{aligned}$$

Q2. (i) Design the pull down network of the following logic function :

$$Y = \overline{(A + B)} \cdot C \cdot \overline{(D + E)}.$$

**[5 marks]**


(ii) Assume that all the transistors have a sizing of  $(W/L)_{min}$ . Compare the worst case  $t_{pHL}$  of the logic circuit with the  $t_{pHL}$  of an inverter with the same transistor sizing.

**[4 marks]**

(iii) Suggest one way of sizing the transistors of the logic circuit such that its worst case  $t_{pHL}$  equals the  $t_{pHL}$  of an inverter with a sizing of  $(W/L)_{min}$ .

**[3 marks]**

2. (i)

 

[5 marks]

$$(ii) \quad \left(\frac{W}{L}\right)_{eq,logic} = \left[ \left(\frac{W}{L}\right)_{min,A}^{-1} + \left(\frac{W}{L}\right)_{min,C}^{-1} + \left(\frac{W}{L}\right)_{min,D}^{-1} \right]^{-1} = \frac{1}{3} \left(\frac{W}{L}\right)_{min}$$

[2 marks]

$$\frac{t_{pHL,logic}}{t_{pHL,inverter}} = \frac{\left(\frac{W}{L}\right)_{min}}{\frac{1}{3} \left(\frac{W}{L}\right)_{min}} = 3$$

[2 marks]

(iii) Make the sizing of each of the transistors in the logic circuit equal to  $3(W/L)_{min}$ .

[3 marks]

Q3. Figure Q3 shows a pull-down network (PDN) for a logic function Y.

 


Fig. Q3

(i) Express Y in terms of A, B, C, D and E.

(ii) Draw the pull-up network (PUN) corresponding to the PDN in Fig. Q3.


- (iii) All NMOS and PMOS transistors in the above logic circuit have a sizing of  $(W/L)_{\min}$ . We shall compare the dynamic performance of the logic circuit with respect to a symmetric inverter where the sizing of NMOS transistor,  $(W/L)_{NMOS} = (W/L)_{\min}$ , and the sizing of PMOS transistor,  $(W/L)_{PMOS} = (\mu_n/\mu_p)(W/L)_{NMOS} = 2.5(W/L)_{\min}$ .

How many times is  $t_{PHL}$  of the above logic circuit compared to that of the symmetric inverter? Give the best and worst case values.

- (iv) Repeat the calculations in part (iii) for  $t_{PLH}$  of the above logic circuit.

3. (i)  $\bar{Y} = [(A.B) + D + E].C$  or  $Y = \overline{[(A.B) + D + E].C}$

(ii) PUN

 

(iii) **Best case  $t_{PHL}$ , all NMOS transistors in PDN turn on -**

$$\text{For } (A.B): \left(\frac{W}{L}\right)_{eq,AB} = \left[ \left(\frac{W}{L}\right)_{\min}^{-1} + \left(\frac{W}{L}\right)_{\min}^{-1} \right]^{-1} = \frac{1}{2} \left(\frac{W}{L}\right)_{\min}$$

$$\text{For } [(A.B) + D + E]: \left(\frac{W}{L}\right)_{eq,ABDE} = \left(\frac{W}{L}\right)_{eq,AB} + \left(\frac{W}{L}\right)_{\min} + \left(\frac{W}{L}\right)_{\min} = \frac{5}{2} \left(\frac{W}{L}\right)_{\min}$$

$$\text{For } [(A.B) + D + E].C: \left(\frac{W}{L}\right)_{eq} = \left[ \left(\frac{W}{L}\right)_{eq,ABDE}^{-1} + \left(\frac{W}{L}\right)_{\min}^{-1} \right]^{-1} = \frac{5}{7} \left(\frac{W}{L}\right)_{\min}$$

$$\frac{t_{PHL,cct}}{t_{PHL,inv}} = \frac{\left(\frac{W}{L}\right)_{NMOS}}{\frac{5}{7} \left(\frac{W}{L}\right)_{\min}} = \frac{\left(\frac{W}{L}\right)_{\min}}{\frac{5}{7} \left(\frac{W}{L}\right)_{\min}} = 1.4$$

**Worst case  $t_{PHL}$ , only A, B and C NMOS transistors in PDN turn on –**

$$\left(\frac{W}{L}\right)_{eq} = \left[ \left(\frac{W}{L}\right)_{min}^{-1} + \left(\frac{W}{L}\right)_{min}^{-1} + \left(\frac{W}{L}\right)_{min}^{-1} \right]^{-1} = \frac{1}{3} \left(\frac{W}{L}\right)_{min}$$

$$\frac{t_{PHL,cct}}{t_{PHL,inv}} = \frac{\left(\frac{W}{L}\right)_{NMOS}}{\frac{1}{3} \left(\frac{W}{L}\right)_{min}} = \frac{\left(\frac{W}{L}\right)_{min}}{\frac{1}{3} \left(\frac{W}{L}\right)_{min}} = 3$$

(iv) **Best case  $t_{PLH}$ , all PMOS transistors in PUN turn on -**

$$\text{For (A+B): } \left(\frac{W}{L}\right)_{eq,AB} = \left(\frac{W}{L}\right)_{min} + \left(\frac{W}{L}\right)_{min} = 2 \left(\frac{W}{L}\right)_{min}$$

$$\text{For [(A+B).D.E]: } \left(\frac{W}{L}\right)_{eq,ABDE} = \left[ \left(\frac{W}{L}\right)_{eq,AB}^{-1} + \left(\frac{W}{L}\right)_{min}^{-1} + \left(\frac{W}{L}\right)_{min}^{-1} \right]^{-1} = \frac{2}{5} \left(\frac{W}{L}\right)_{min}$$

$$\text{For [(A+B).D.E]+C: } \left(\frac{W}{L}\right)_{eq} = \left(\frac{W}{L}\right)_{eq,ABDE} + \left(\frac{W}{L}\right)_{min} = \frac{7}{5} \left(\frac{W}{L}\right)_{min}$$

$$\frac{t_{PLH,cct}}{t_{PLH,inv}} = \frac{\left(\frac{W}{L}\right)_{PMOS}}{\frac{7}{5} \left(\frac{W}{L}\right)_{min}} = \frac{2.5 \left(\frac{W}{L}\right)_{min}}{\frac{7}{5} \left(\frac{W}{L}\right)_{min}} = 1.79$$

**Worst case  $t_{PLH}$ , only A (or B), D and E PMOS transistors in PUN turn on –**

$$\left(\frac{W}{L}\right)_{eq} = \left[ \left(\frac{W}{L}\right)_{min}^{-1} + \left(\frac{W}{L}\right)_{min}^{-1} + \left(\frac{W}{L}\right)_{min}^{-1} \right]^{-1} = \frac{1}{3} \left(\frac{W}{L}\right)_{min}$$

$$\frac{t_{PHL,cct}}{t_{PHL,inv}} = \frac{\left(\frac{W}{L}\right)_{PMOS}}{\frac{1}{3} \left(\frac{W}{L}\right)_{min}} = \frac{2.5 \left(\frac{W}{L}\right)_{min}}{\frac{1}{3} \left(\frac{W}{L}\right)_{min}} = 7.5$$

- Q4. Assume that the AC small signal parameters of the BJTs are  $g_{m,Qi}$ ,  $r_{\pi,Qi}$ ,  $r_{o,Qi}$ , and the AC small signal parameters of the MOSFETs are  $g_{m,Mj}$ ,  $g_{mb,Mj}$ ,  $r_{i,Mj}$ ,  $r_{o,Mj}$ , where  $i$  ( $i = 1, 2$ ) and  $j$  ( $j = 1, 2, 3$ ) are the corresponding device indices. Using the equivalent resistance tables in your lecture notes, write down the expressions for the small signal AC equivalent resistances,  $R_{x1}$ ,  $R_{x2}$  and  $R_{x3}$  in the circuit in Fig. Q4.

 


Fig. Q4

---

4.  $R_{x1} = r_{\pi,Q1} \left( 1 + g_{m,Q1} \frac{1}{g_{m,M1}} \right) ;$

$$R_{x2} = R_2 + r_{\pi,Q2};$$

$$R_{x3} = r_{o,M2} // \left( R_4 + \frac{1}{g_{m,M3}} \right).$$


---

- Q5. Design a voltage amplifier that provides 0.25 W of signal output power to a 100  $\Omega$  load resistor. The signal source provides a 25 mV root-mean-square (RMS) voltage signal and has a source resistance of 0.5 M $\Omega$ .

- Using the specifications given above, calculate the required voltage gain  $v_o/v_s$ . [Hint: You need to calculate the signal voltage  $v_o$  (RMS value) across the load, and compare it with the source voltage signal  $v_s$  (RMS value)]. [Ans: 200]
- Design a multi-stage amplifier to meet the required voltage gain using chips given below. You may use a chip more than once. Please keep the number of stages in the multi-stage amplifier to a maximum of 3. The voltage gain of the multi-stage amplifier you design can be slightly higher (e.g. up to 20% higher) than the required voltage gain.

Three voltage amplifier chips are available:

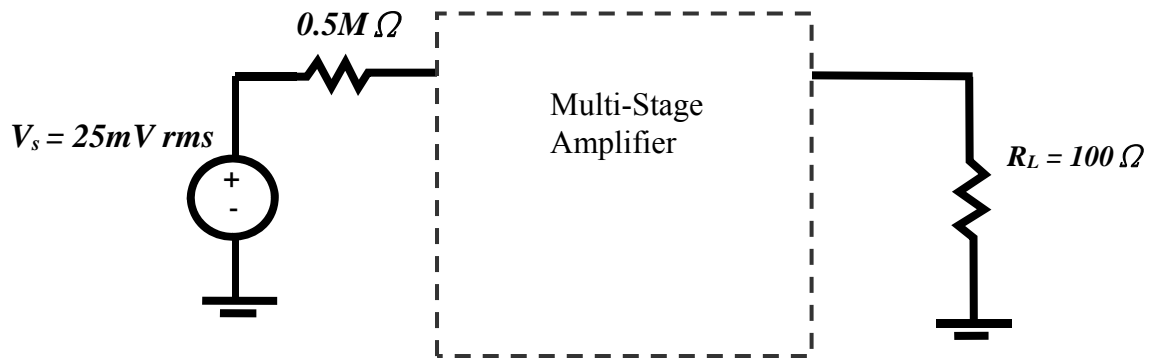
Chip 1: Input resistance  $r_{i1} = 1 \text{ M}\Omega$ ; Gain  $a_{v1} = 10$ ; Output resistance  $r_{o1} = 10 \text{ k}\Omega$ .

Chip 2: Input resistance  $r_{i2} = 10 \text{ k}\Omega$ ; Gain  $a_{v2} = 75$ ; Output resistance  $r_{o2} = 1 \text{ k}\Omega$ .

Chip 3: Input resistance  $r_{i3} = 10 \text{ k}\Omega$ ; Gain  $a_{v3} = 1$ ; Output resistance  $r_{o3} = 10 \text{ }\Omega$ .

---

5.

(i) Required power,  $P_L = 0.25 \text{ W}$ 

$$= \frac{v_o^2}{100}$$


$$v_o = 5 \text{ V r.m.s.}$$

$$\text{Therefore required overall voltage gain} = \frac{5}{0.025}$$

$$= 200$$

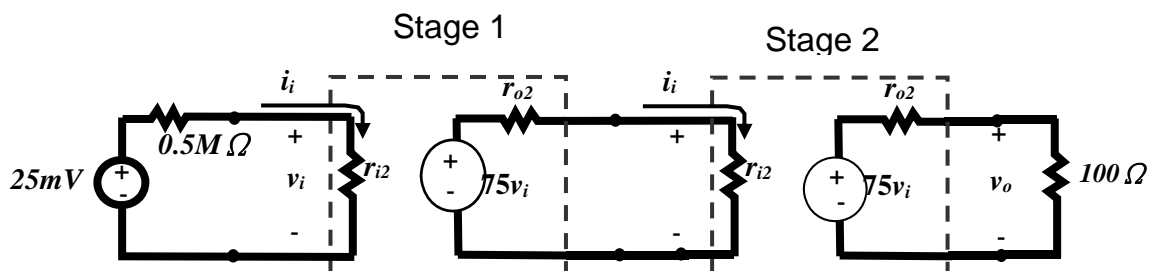(b) First Try: chip 2 + chip 2

Since chip2 has a high gain of 75, let us try to cascade 2 stages, each stage using chip2.



The overall voltage gain is

$$v_o = \left( \frac{10k}{10k + 500k} \cdot v_s \cdot 75 \right) \cdot \left( \frac{10k}{10k + 1k} \cdot 75 \right) \cdot \left( \frac{0.100k}{0.100k + 1k} \right)$$

Rearrange =>

$$\left[ \frac{v_o}{v_s} \right] = \left( \frac{10k}{10k + 500k} \cdot 75 \right) \cdot \left( \frac{10k}{10k + 1k} \cdot 75 \right) \cdot \left( \frac{0.100k}{0.100k + 1k} \right)$$

$$\begin{aligned}
 &= (1.47) \cdot (68.18) \cdot (0.09) \\
 &= 9.11 \text{ V/V}
 \end{aligned}$$

**too small, why ?**

The overall voltage gain is not high because of the factor  $\frac{0.1k}{0.1k + 1k}$  is too small. Therefore, the input resistance of the 1<sup>st</sup> stage amplifier should not be small compared to the source resistance.

Second Try: chip 2 + chip 2 + chip 2

Similarly,

$$\begin{aligned}
 \left[ \frac{v_o}{v_s} \right] &= \left( \frac{10k}{10k + 500k} \cdot 75 \right) \cdot \left( \frac{10k}{10k + 1k} \cdot 75 \right) \cdot \left( \frac{10k}{10k + 1k} \cdot 75 \right) \cdot \left( \frac{0.100k}{0.100k + 1k} \right) \\
 &= (1.47) \cdot (68.18) \cdot (68.18) \cdot (0.09) \\
 &= 615.00 \text{ V/V}
 \end{aligned}$$

**too large!**

Third Try: chip 1 + chip 2 + chip 3

Similarly,

$$\begin{aligned}
 \frac{v_o}{v_s} &= \left( \frac{1000k}{1000k + 500k} \cdot 10 \right) \cdot \left( \frac{10k}{10k + 10k} \cdot 75 \right) \cdot \left( \frac{10k}{10k + 1k} \cdot 1 \right) \cdot \left( \frac{0.1k}{0.1k + 0.01k} \right) \\
 &= (6.67) \cdot (37.5) \cdot (0.909) \cdot (0.909) \\
 &= 206.71 \text{ V/V}
 \end{aligned}$$

**OK.**



Q6. Figure Q6 below shows a single stage amplifier with current mirror biasing.

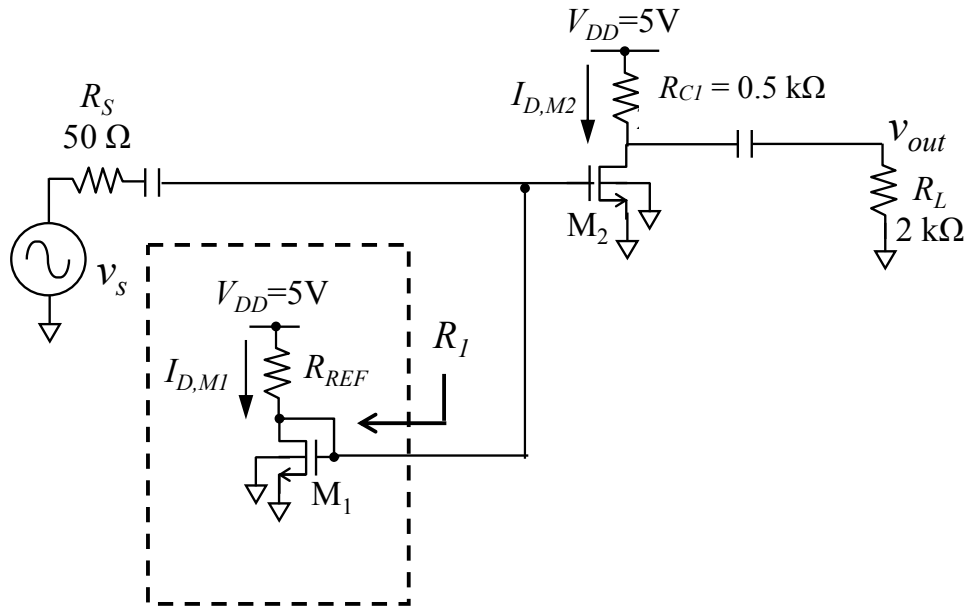


Fig. Q6

For the two n-channel MOSFETs,  $V_{THN1} = V_{THN2} = 1 \text{ V}$ ,  $\lambda_{M1} = \lambda_{M2} = 0$ ,  $K_{n,M1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_{M1} = 2 \text{ mA V}^{-2}$ ,  $K_{n,M2} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_{M2} = 4 \text{ mA V}^{-2}$ , where  $\left( \frac{W}{L} \right)_{M2} = 2 \left( \frac{W}{L} \right)_{M1}$ .

(i) Design  $R_{REF}$  such that  $I_{D,M1} = 2 \text{ mA}$ .

[5 marks]

(ii) What is the value of  $I_{D,M2}$ ?

[2 marks]

(iii) Calculate the small signal parameters of the two MOSFETs, i.e.,  $g_{m,M1}$ ,  $r_{o,M1}$ ,  $g_{m,M2}$ ,  $r_{o,M2}$ .

[4 marks]

(iv) Calculate the value of the a.c. equivalent resistance,  $R_I$ , of the circuit enclosed in the dashed box in Fig. Q6.

[3 marks]

(v) Identify the configuration of the single stage amplifier.

[1 mark]

(vi) Determine the parameters,  $G_m$ ,  $R_{in}$  and  $R_{out}$  of the two-port network of the amplifier.

[3 marks]

6. (i)  $I_{D,M1} = K_{n,M1} (V_{GS,M1} - V_{THN1})^2$

$$(V_{GS,M1} - V_{THN1}) = \sqrt{\frac{I_{D,M1}}{K_{n,M1}}} = \sqrt{\frac{2 \text{ mA}}{2 \text{ mA V}^{-2}}} = \pm 1 \text{ V} \quad (1 \text{ mark})$$

$$V_{GS,M1} = 2 \text{ V} \text{ as } V_{GS,M1} = 0 \text{ V is not applicable (MOSFET is off).} \quad (2 \text{ marks})$$

$$R_{REF} = \frac{V_{DD} - V_{GS,M1}}{I_{D,M1}} = \frac{(5-2) \text{ V}}{2 \text{ mA}} = 1.5 \text{ k}\Omega. \quad (2 \text{ marks})$$

(ii) Since  $V_{THN2} = V_{THN1}$  and  $V_{GS2} = V_{GS1}$ , but  $K_{n,M2} = 2 \times K_{n,M1}$ , therefore

$$I_{D,M2} = 2 \times I_{D,M1} = 4 \text{ mA}. \quad (2 \text{ marks})$$

(iii)  $g_{m,M1} = 2 \times \sqrt{K_{n,M1} \times I_{D,M1}} = 2 \times \sqrt{2 \text{ mA V}^{-2} \times 2 \text{ mA}} = 4 \text{ mA V}^{-1}.$

$$r_{o,M1} = \frac{1}{\lambda_{M1} \times I_{D,M1}} = \infty$$

$$g_{m,M2} = 2 \times \sqrt{K_{n,M2} \times I_{D,M2}} = 2 \times \sqrt{4 \text{ mA V}^{-2} \times 4 \text{ mA}} = 8 \text{ mA V}^{-1}.$$

$$r_{o,M2} = \frac{1}{\lambda_{M2} \times I_{D,M2}} = \infty \quad (1 \text{ mark for each answer})$$

(iv) The a.c. equivalent circuit of  $M_1$  is a diode-connected transistor, with resistance equal to  $1/g_{m,M1}$ . Hence, after setting  $V_{DD}$  to a.c. ground,

$$R_1 = R_{REF} // \left( \frac{1}{g_{m,M1}} \right) = 214.3 \Omega. \quad (3 \text{ marks})$$

(v) Common source amplifier. (1 mark)

(vi) By using the table of equivalent resistances for amplifier configurations,

$$G_m = g_{m,M2} = 8 \text{ mA V}^{-1}.$$

$$R_{in} = R_1 // \infty = 214.3 \Omega.$$

$$R_{out} = R_{C1} // \infty = 0.5 \text{ k}\Omega. \quad (1 \text{ mark for each answer})$$

Q7. [This question will not be discussed during tutorial class.]

This is a new amplifier circuit that we have not analyzed in the lectures. It is not among the amplifier configurations listed in the tables in the lecture notes. Hence, the two-port network parameters of this amplifier has to be derived from first principles.

For the amplifier circuit shown in Fig. Q7, the transistor  $Q_1$  has the following parameter values:  $I_S = 10^{-15}$  A,  $\beta = 100$ ,  $V_A = 100$  V.

(i) What are the values of the small signal parameters,  $g_{m,Q1}$ ,  $r_{\pi,Q1}$  and  $r_{o,Q1}$  of  $Q_1$ ?

[Ans. 20 mA/V, 5 k, 200 k]

(ii) Transform the circuit for AC analysis and replace the transistor with its small signal equivalent.

(iii) Assuming that the amplifier can be transformed into a 2-port transconductance amplifier, find the three parameters ( $G_m$ ,  $R_{in}$ ,  $R_{out}$ ) of the 2-port network.

[Ans. 18 mA/V, 45  $\Omega$ , 268  $\Omega$ ]

(iv) Derive the overall gain  $A_V = v_{out}/v_s$ .

[-2.6]

 


Fig. Q7


7. (i)  $I_C \approx I_E = I_{BIAS} = 0.5 \text{ mA}$ .

$$g_{m,Q1} = \frac{I_C}{V_T} = \frac{0.5 \text{ mA}}{0.025 \text{ V}} = 20 \text{ mA/V}.$$


$$r_{\pi,Q1} = \frac{\beta}{g_m} = \frac{100}{20 \times 10^{-3}} = 5 \text{ k}\Omega.$$

$$r_{o,Q1} = \frac{V_A}{I_C} = \frac{100}{0.5 \times 10^{-3}} = 200 \text{ k}\Omega.$$

(ii)

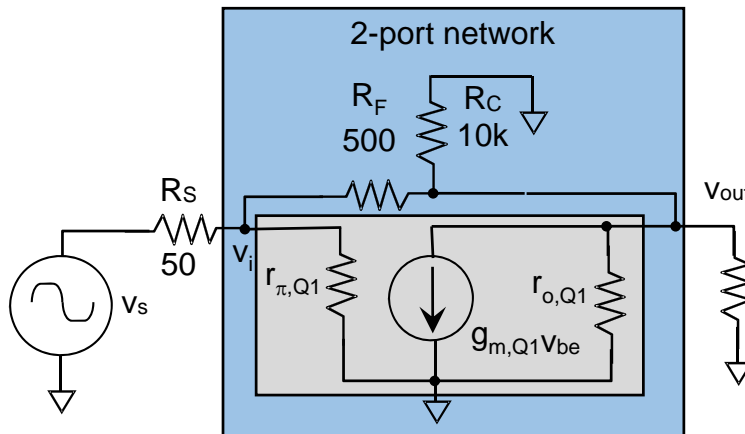

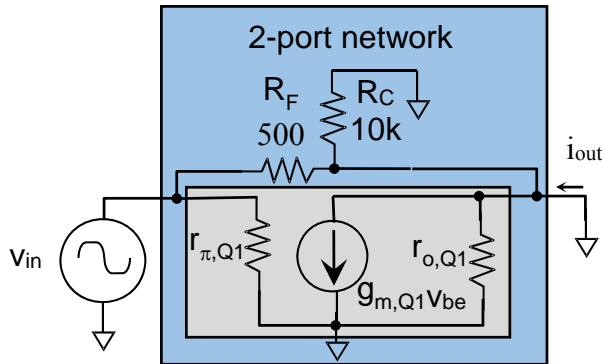(iii) To find  $G_m$  : we note that  $v_{be} = v_{in}$ .



$$i_{RC} = 0$$

$$i_{ro,Q1} \approx 0$$

$$i_{RF} = \frac{v_{in}}{R_F}$$


$$i_{out} = g_{m,Q1}v_{in} - i_{RF} = \left( g_{m,Q1} - \frac{1}{R_F} \right) v_{in}$$

$$G_m = g_{m,Q1} - \frac{1}{R_F} = 18 \text{ mA/V}^{-1}$$

or

$$\approx g_{m,Q1} (= 20 \text{ mA/V}^{-1})$$

 To find  $R_{in}$  : We note that  $v_{be} = v_x$ .



$$i_{RF} = \frac{v_{out}}{R_C // R_L // r_{o,Q1}} + g_{m,Q1}v_x \dots (1)$$

$$i_{r_{\pi,Q1}} = \frac{v_x}{r_{\pi,Q1}} \dots (2)$$

$$i_{RF} = \frac{v_x - v_{out}}{R_F} \dots (3)$$

$$i_x = i_{r_{\pi,Q1}} + i_{RF} \dots (4)$$

$$(1), (3) v_{out} \left( \frac{1}{R_C // R_L // r_{o,Q1}} + \frac{1}{R_F} \right) = v_x \left( \frac{1}{R_F} - g_{m,Q1} \right)$$


$$\because R_C, R_L, r_{o,Q1} \gg R_F \text{ and } g_{m,Q1} \gg \frac{1}{R_F}$$

$$\Rightarrow v_{out} = -v_x g_{m,Q1} R_F$$

$$\Rightarrow i_x = \frac{v_x}{r_{\pi,Q1}} + \frac{v_x + v_x g_{m,Q1} R_F}{R_F}$$

$$R_{in} = \frac{v_x}{i_x} = \frac{1}{\frac{1}{r_{\pi,Q1}} + \frac{1 + g_{m,Q1} R_F}{R_F}} = 45 \Omega \approx \frac{R_F}{1 + g_{m,Q1} R_F} \because R_F \ll r_{\pi,Q1}$$

To find  $R_{out}$  :

 

$$i_{RC} = \frac{v_x}{R_C} \quad i_{RF} = \frac{v_x}{R_F + (R_S // r_{\pi, Q1})} \approx \frac{v_x}{R_F + R_S} \quad [R_S \ll r_{\pi, Q1}]$$

$$v_{be} = v_x \frac{(R_S // r_{\pi, Q1})}{R_F + (R_S // r_{\pi, Q1})} \approx v_x \frac{R_S}{R_F + R_S}$$

$$i_{ro, Q1} \approx 0$$

$$\Rightarrow i_x = i_{RC} + i_{RF} + g_{m, Q1} v_{be} = \frac{v_x}{R_C} + \frac{v_x}{R_F + R_S} + g_{m, Q1} v_x \frac{R_S}{R_F + R_S}$$


$$i_x = v_x \left( \frac{1}{R_C} + \frac{1}{R_F + R_S} + \frac{g_{m, Q1} R_S}{R_F + R_S} \right)$$

$$R_{out} = \frac{v_x}{i_x} = \left( \frac{1}{R_C} + \frac{1}{R_F + R_S} + \frac{g_{m, Q1} R_S}{R_F + R_S} \right)^{-1} = 268 \Omega$$

or

$$R_{out} \approx \frac{1}{R_F + R_S} + \frac{g_{m, Q1} R_S}{R_F + R_S} = 275 \Omega \quad \text{since} \quad [R_F + R_S \ll R_C]$$

(iv)

 

$$R_{in} \approx \frac{R_F}{1 + g_{m, Q1} R_F} = 45 \quad G_m \approx g_{m, Q1} = 20 \text{ mA/V} \quad R_{out} \approx \frac{R_F + R_S}{2} = 275$$

$$v_i = \frac{R_{in}}{R_{in} + R_S} v_s$$

$$v_{out} = -G_m v_i (R_{out} // R_L) = -g_{m, Q1} \frac{R_{in}}{R_{in} + R_S} v_s \left( \frac{R_F + R_S}{2} // R_L \right)$$

$$A_v = \frac{v_{out}}{v_s} \approx -\frac{R_{in}}{R_{in} + R_S} g_{m, Q1} \left( \frac{R_F + R_S}{2} \right) = -2.6$$