

- Q. 1 (a) Figure 1.1 shows a two-stage amplifier circuit. Obtain an expression for the overall voltage gain v_o/v_s . (5 marks)

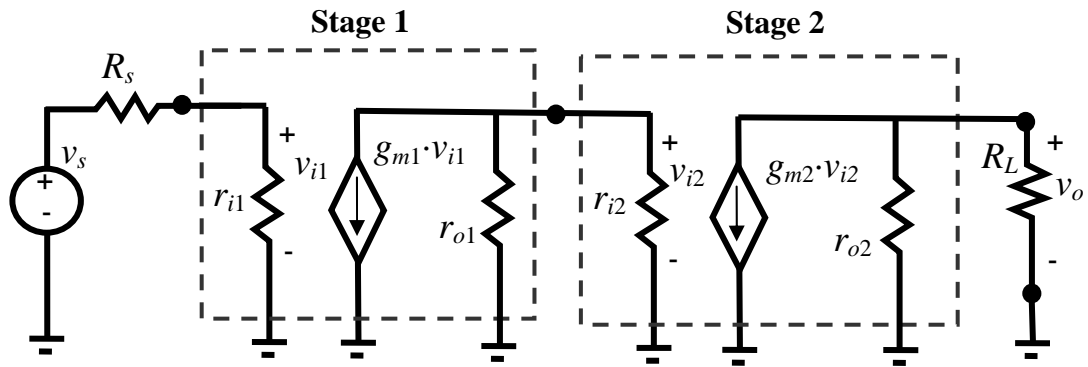


Figure 1.1.

- (b) Figure 1.2 shows a circuit which comprises a forward-biased diode at room temperature with an ideality factor $n = 1$, and three resistors R_1 , R_2 , and R_3 , where $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$. There is also one voltage source V_a . In the absence of small signal, $V_a = V_A = 2 \text{ V}$.
- Find the Thevenin's Equivalent of the circuit in the dashed box in the absence of small signal. (3 marks)
 - Assume that the voltage V_D across the diode is 0.7 V . Find the value of the DC diode current I_D . (2 marks)
Hint: Use the Thevenin's Equivalent circuit obtained in (i).
 - What is the DC voltage at node B? (2 marks)
 - What is the DC current flowing through R_1 ? (2 marks)
 - What is the DC current flowing through R_2 ? (2 marks)

Now, we consider the presence of a small signal v_a . $V_a = V_A + v_a = 2\text{V} + v_a$.

- What is the small-signal equivalent resistance r_d for the diode? (2 marks)
- Draw the small-signal equivalent circuit for Figure 1.2. (4 marks)
- Express v_d in terms of v_a , R_1 , R_2 , R_3 , and r_d . (3 marks)

 


Figure 1.2.

- Q. 2 (a) (i) State the logic function Y implemented by the circuit in Figure 2.1,
that is, express Y in terms of A, B, C, D, and E. (4 marks)
- (ii) Draw the Pull-Down Network for the logic circuit in Figure 2.1. (5 marks)
- (iii) State the logic function Y implemented by the circuit in Figure 2.2,
that is, express Y in terms of A, B, C, D, and E. (4 marks)
- (iv) Draw the Pull-Up Network for the logic circuit in Figure 2.1. (5 marks)

 


Figure 2.1

 


Figure 2.2

- (b) A three-input logic gate implementing $\overline{X} = A \cdot (B + C)$ (Figure 2.3) is constructed using minimum-sized transistors for all transistors, i.e. $(W/L)_{min}$, for all six n-channel and p-channel transistors.

We shall compare the dynamic performance of the logic gate of Figure 2.3 with that of a symmetric inverter where $(W/L)_N = (W/L)_{min}$, and $(W/L)_P = (\mu_n/\mu_p)(W/L)_N = 2.5(W/L)_{min}$. The symmetric inverter has a high-to-low propagation delay $t_{PHL(inv)}$ equal to its and low-to-high propagation delay $t_{PLH(inv)}$.

- (i) How much longer will the logic gate's high-to-low propagation delay $t_{PHL(X)}$ be compared to that of the symmetric inverter? Give the best case and worst case values if appropriate. (4 marks)
- (ii) What is the best possible low-to-high propagation delay $t_{PLH(X)}$ for this logic gate, expressed in terms of the low-to-high propagation delay $t_{PLH(inv)}$ of the symmetric inverter? (3 marks)

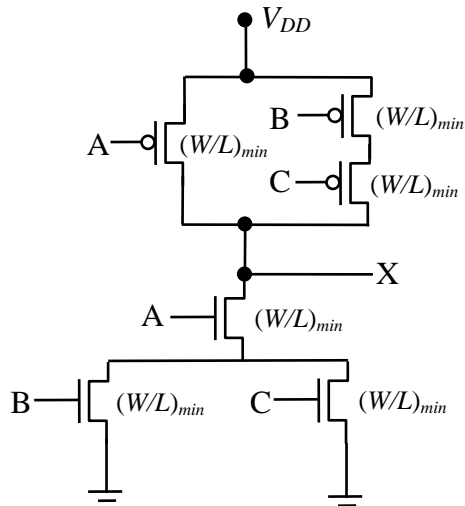


Figure 2.3


Q. 1(a)

$$\begin{aligned}
 v_{i1} &= [r_{i1}/(r_{i1} + R_s)]v_s \\
 v_{i2} &= -g_{m1} \cdot v_{i1} (r_{o1} // r_{i2}) \\
 v_o &= -g_{m2} \cdot v_{i2} \cdot (r_{o2} // R_L) \\
 &= -g_{m2} \cdot (r_{o2} // R_L) \cdot [-g_{m1} \cdot (r_{o1} // r_{i2})] \cdot [r_{i1}/(r_{i1} + R_s)]v_s
 \end{aligned}$$

$$(v_o/v_s) = g_{m1}g_{m2} \cdot [r_{o2} R_L / (r_{o2} + R_L)] \cdot [r_{o1} r_{i2} / (r_{o1} + r_{i2})] \cdot [r_{i1}/(r_{i1} + R_s)]$$

(5 marks)

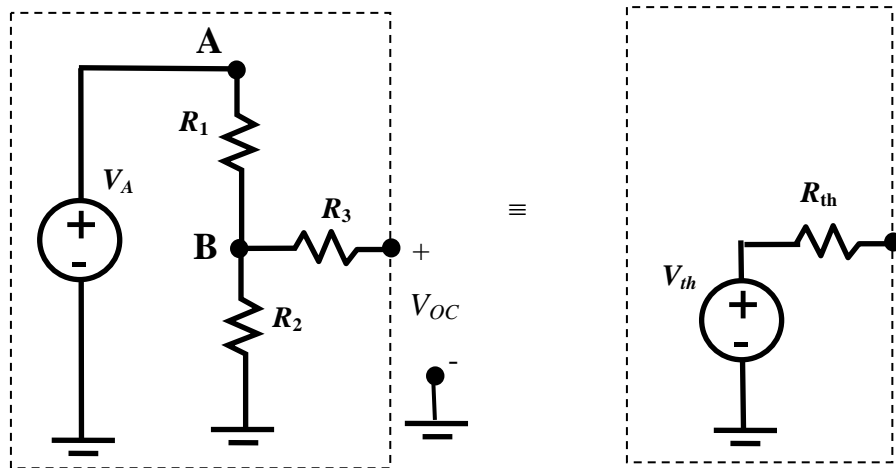Q. 1(b) (i) Thevenin's equivalent circuit is obtained as follows.




The Thevenin's voltage or open-circuit voltage is

$$V_{th} = V_{OC} = [R_2/(R_1 + R_2)] \cdot V_A = 1 \text{ V.}$$

$$R_{th} = R_3 + (R_1 // R_2) = 1.5 \text{ k}\Omega.$$

(3 marks)

(ii)

 


$$\begin{aligned} \text{Voltage across } R_{th} &= (1 - 0.7) \text{ V} \\ &= 0.3 \text{ V} \end{aligned}$$

$$I_D = 0.3 \text{ V} / 1.5 \text{ k}\Omega = 0.2 \text{ mA}$$

(2 marks)

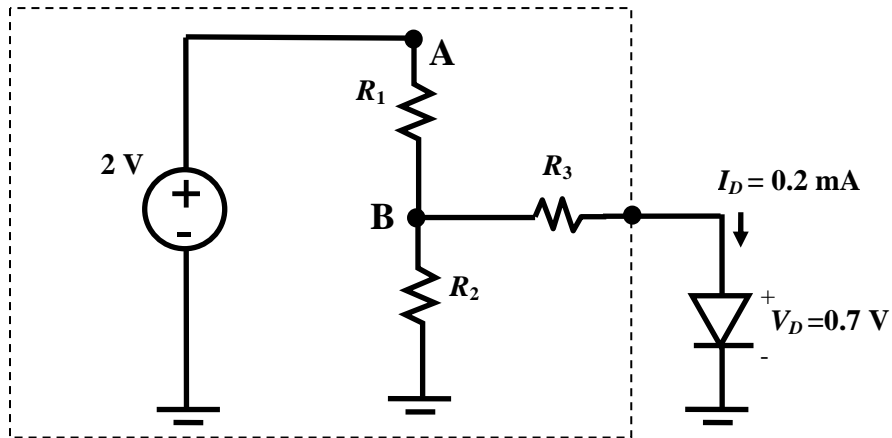(iii) The DC biasing condition for the circuit is shown here:




$$\begin{aligned} \text{DC Voltage at node B with respect to the ground } V_B &= I_D R_3 + V_D \\ &= (0.2\text{mA})(1\text{ k}\Omega) + 0.7\text{V} \\ &= 0.9\text{ V} \end{aligned} \quad (2\text{ marks})$$

$$\begin{aligned} \text{(iv) The current flowing through } R_1 &= (V_A - V_B)/R_1 = (2 - 0.9)\text{V}/1\text{ k}\Omega \\ &= 1.1\text{ mA} \end{aligned} \quad (2\text{ marks})$$

$$\begin{aligned} \text{(v) The current flowing through } R_2 &= V_B/R_2 = 0.9\text{V}/1\text{ k}\Omega \\ &= 0.9\text{ mA} \end{aligned} \quad (2\text{ marks})$$

$$\begin{aligned} \text{(vi) The small signal resistance for the diode } r_d &= V_T/I_D \\ &= 0.025\text{mV}/0.2\text{mA} \\ &= 12.5\ \Omega \end{aligned} \quad (2\text{ marks})$$

 (vii) The small signal equivalent circuit is shown here:




(viii)

$$v_d = \frac{R_2 // (R_3 + r_d)}{R_1 + [R_2 // (R_3 + r_d)]} \cdot \frac{r_d}{R_3 + r_d} v_a \quad (3\text{ marks})$$

Q. 2. (a) (i) Examining the Pull-Up Network,

$$Y = \overline{A} \cdot \overline{B} \cdot [\overline{C} + \overline{D} + \overline{E}] \quad (4 \text{ marks})$$

 (ii) The Pull-Down Network for the logic circuit in Fig. 2.1 should be:




(iii) Examining the Pull-Down Network,

$$\overline{Y} = A \cdot (B \cdot C + D \cdot E)$$

$$Y = \overline{A \cdot (B \cdot C + D \cdot E)} \quad (4 \text{ marks})$$

 (iv) The Pull-Up Network for the logic circuit in Fig. 2.2 should be:



(b)(i) Consider the high-to-low dynamic operation of the logic gate.

- In the best case, all N-MOSFETs are turned on. Transistors B and C (which are in parallel) will be turned on. The effective W/L of the parallel combination of B and C will be $2(W/L)_{min}$. This is in series with transistor A.

During the high-to-low dynamic operation,
 $(W/L)_{eq} = \{[(W/L)_{min}]^{-1} + [2(W/L)_{min}]^{-1}\}^{-1} = (2/3) (W/L)_{min}$

Therefore, we deduce that in the best case,

$$t_{PHL(X)} = (3/2) t_{PHL(inv)} \quad (2 \text{ marks})$$

- In the worst case, Transistor A is turned on, and either Transistor B or Transistor C are turned on. During the high-to-low dynamic operation,
 $(W/L)_{eq} = \{[(W/L)_{min}]^{-1} + [(W/L)_{min}]^{-1}\}^{-1} = (1/2) (W/L)_{min}$

Therefore, we deduce that in the worst case,

$$t_{PHL(X)} = 2 t_{PHL(inv)} \quad (2 \text{ marks})$$

(b)(ii) Consider the best case low-to-high dynamic operation of the logic gate.
 All P-MOSFETs with a size of $(W/L)_{min}$ are turned on.

Transistors B and C in series gives $0.5(W/L)_{min}$.

$$(W/L)_{eq} = [(W/L)_{min}] + [0.5(W/L)_{min}] = 1.5 (W/L)_{min}$$

We know that $t_{PLH} \propto 1/(W/L)_{eq}$. Thus, we have

$$t_{PLH(X)} = t_{PLH(inv)} [2.5(W/L)_{min}] / [1.5(W/L)_{min}] = 1.67 t_{PLH(inv)}. \quad (3 \text{ marks})$$