

NATIONAL UNIVERSITY of SINGAPORE

Department of Electrical and Computer Engineering

EE2021 – Devices and Circuits

Tutorial 4

Homework 3:

Homework 3 is Question 2 and Question 6 of Tutorial 4. You have to submit the homework assignment in hardcopy in class on Wednesday 1 April 2015.

Unless otherwise stated, you may use the tables of the amplifier configurations and equivalent resistances in your lecture notes in your solutions to the questions.

- Q1. Draw the pull down network (PDN) and pull up network (PUN) of the following logic function:

$$Y = \overline{\{[(A.B) + C].D\} + (E.F)}.$$

Determine also the best case propagation delay of the above PUN, $t_{pLH,best}$, in terms of that of an inverter, $t_{pLH,inv}$. All NMOS and PMOS transistors in the above logic networks and the inverter have sizing of $(W/L)_n = n$ and $(W/L)_p = p$, respectively.

- Q2. (i) Design the pull down network of the following logic function :

$$Y = \overline{(A + B) \cdot C \cdot (D + E)}.$$

[5 marks]

- (ii) Assume that all the transistors have a sizing of $(W/L)_{min}$. Compare the worst case t_{pHL} of the logic circuit with the t_{pHL} of an inverter with the same transistor sizing.

[4 marks]

- (iii) Suggest one way of sizing the transistors of the logic circuit such that its worst case t_{pHL} equals the t_{pHL} of an inverter with a sizing of $(W/L)_{min}$.

[3 marks]

Q3. Figure Q3 shows a pull-down network (PDN) for a logic function Y.

 


Fig. Q3

- (i) Express Y in terms of A, B, C, D and E.
- (ii) Draw the pull-up network (PUN) corresponding to the PDN in Fig. Q3.
- (iii) All NMOS and PMOS transistors in the above logic circuit have a sizing of $(W/L)_{\min}$. We shall compare the dynamic performance of the logic circuit with respect to a symmetric inverter where the sizing of NMOS transistor, $(W/L)_{NMOS} = (W/L)_{\min}$, and the sizing of PMOS transistor, $(W/L)_{PMOS} = (\mu_n/\mu_p)(W/L)_{NMOS} = 2.5(W/L)_{\min}$.

How many times is t_{PHL} of the above logic circuit compared to that of the symmetric inverter? Give the best and worst case values.

- (iv) Repeat the calculations in part (iii) for t_{PLH} of the above logic circuit.

[Ans. (iii) Best = 1.4, Worst = 3; (iv) Best = 1.79, Worst = 7.5]

- Q4. Assume that the AC small signal parameters of the BJTs are $g_{m,Qi}$, $r_{\pi,Qi}$, $r_{o,Qi}$, and the AC small signal parameters of the MOSFETs are $g_{m,Mj}$, $g_{mb,Mj}$, $r_{i,Mj}$, $r_{o,Mj}$, where i ($i = 1, 2$) and j ($j = 1, 2, 3$) are the corresponding device indices. Using the equivalent resistance tables in your lecture notes, write down the expressions for the small signal AC equivalent resistances, R_{x1} , R_{x2} and R_{x3} in the circuit in Fig. Q4.

 


Fig. Q4

- Q5. Design a voltage amplifier that provides 0.25 W of signal output power to a $100\ \Omega$ load resistor. The signal source provides a 25 mV root-mean-square (RMS) voltage signal and has a source resistance of $0.5\ \text{M}\Omega$.

- (i) Using the specifications given above, calculate the required voltage gain v_o/v_s . [Hint: You need to calculate the signal voltage v_o (RMS value) across the load, and compare it with the source voltage signal v_s (RMS value)].

[Ans: 200]

- (ii) Design a multi-stage amplifier to meet the required voltage gain using chips given below. You may use a chip more than once. Please keep the number of stages in the multi-stage amplifier to a maximum of 3. The voltage gain of the multi-stage amplifier you design can be slightly higher (e.g. up to 20% higher) than the required voltage gain.


Three voltage amplifier chips are available:

Chip 1: Input resistance $r_{i1} = 1\ \text{M}\Omega$; Gain $a_{v1} = 10$; Output resistance $r_{o1} = 10\ \text{k}\Omega$.

Chip 2: Input resistance $r_{i2} = 10\ \text{k}\Omega$; Gain $a_{v2} = 75$; Output resistance $r_{o2} = 1\ \text{k}\Omega$.

Chip 3: Input resistance $r_{i3} = 10\ \text{k}\Omega$; Gain $a_{v3} = 1$; Output resistance $r_{o3} = 10\ \Omega$.

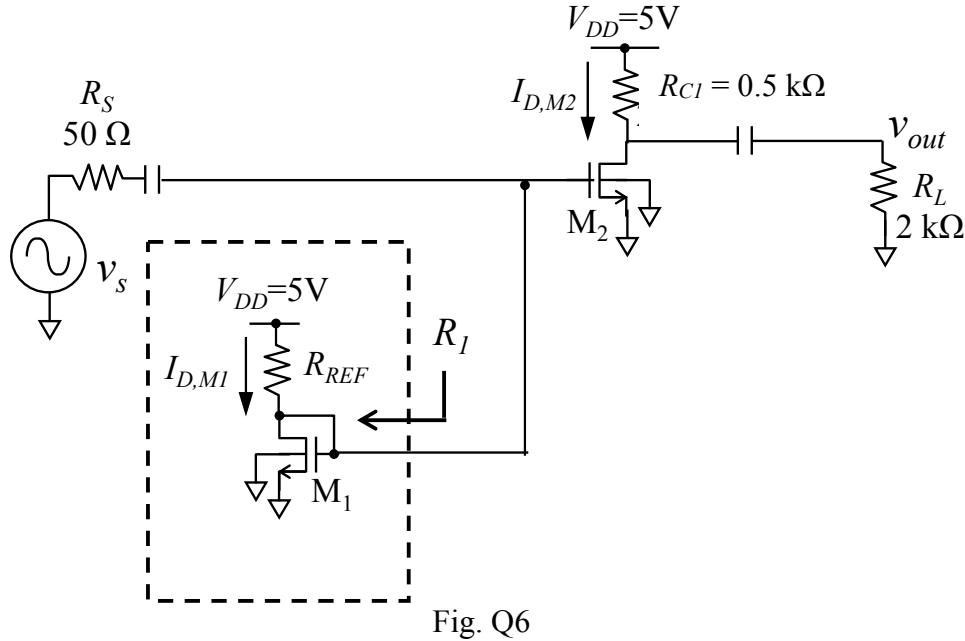Q6. Figure Q6 below shows a single stage amplifier with current mirror biasing.



For the two n-channel MOSFETs, $V_{THN1} = V_{THN2} = 1 \text{ V}$, $\lambda_{M1} = \lambda_{M2} = 0$, $K_{n,M1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_{M1} = 2 \text{ mA V}^{-2}$, $K_{n,M2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_{M2} = 4 \text{ mA V}^{-2}$, where $\left(\frac{W}{L} \right)_{M2} = 2 \left(\frac{W}{L} \right)_{M1}$.

(i) Design R_{REF} such that $I_{D,M1} = 2 \text{ mA}$.

[5 marks]

(ii) What is the value of $I_{D,M2}$?

[2 marks]

(iii) Calculate the small signal parameters of the two MOSFETs, i.e., $g_{m,M1}$, $r_{o,M1}$, $g_{m,M2}$, $r_{o,M2}$.

[4 marks]

(iv) Calculate the value of the a.c. equivalent resistance, R_I , of the circuit enclosed in the dashed box in Fig. Q6.

[3 marks]

(v) Identify the configuration of the single stage amplifier.

[1 mark]

(vi) Determine the parameters, G_m , R_{in} and R_{out} of the two-port network of the amplifier.

[3 marks]

Q7. [This question will not be discussed during tutorial class.]

This is a new amplifier circuit that we have not analyzed in the lectures. It is not among the amplifier configurations listed in the tables in the lecture notes. Hence, the two-port network parameters of this amplifier has to be derived from first principles.

For the amplifier circuit shown in Fig. Q7, the transistor Q_1 has the following parameter values: $I_S = 10^{-15}$ A, $\beta = 100$, $V_A = 100$ V.

- (i) What are the values of the small signal parameters, $g_{m,Q1}$, $r_{\pi,Q1}$ and $r_{o,Q1}$ of Q_1 ?

[Ans. 20 mA/V, 5 k, 200k]

- (ii) Transform the circuit for AC analysis and replace the transistor with its small signal equivalent.

- (iii) Assuming that the amplifier can be transformed into a 2-port transconductance amplifier, find the three parameters (G_m , R_{in} , R_{out}) of the 2-port network.

[Ans. 18 mA/V, 45 Ω , 268 Ω]

- (iv) Derive the overall gain $A_V = v_{out}/v_s$.

[-2.6]

 


Fig. Q7