EE2021 Devices and Circuits


Opamp and Opamp based circuits

Lecture Outline

Different Opamp Transfer function

Inverting amplifier, non-inverting amplifier, summer, buffer, logarithm amplifier, super-diode, SK-filter, comparator, comparator with hysterisis

Opamp Schematic

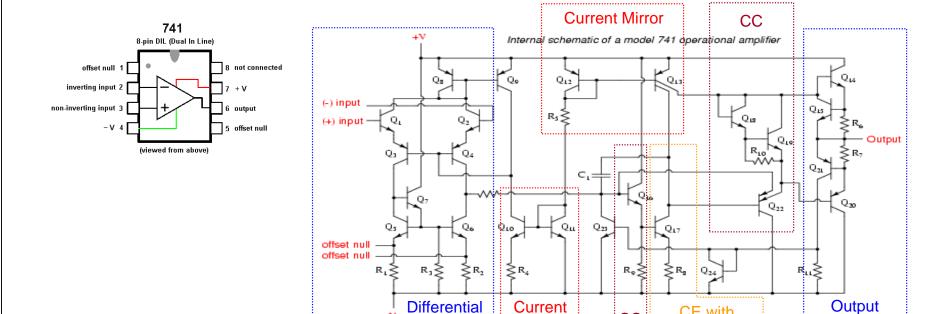

- Multistage Amplifier Analysis
- All the techniques learnt earlier in amplifier analysis will help you understand and design an opamp eventually

Amplifier

Stage


CE with

degeneration

CC

Mirror

Opamp Applications

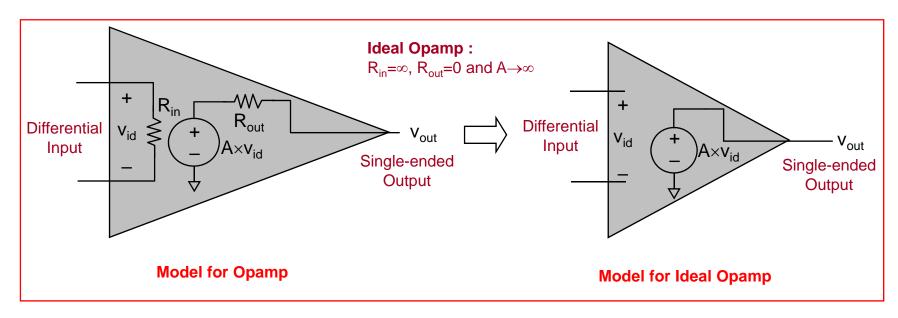


Possible Applications:

- Feedback Amplifier
- Integrator, Differentiator, Active Filter
- Simulated Inductor
- Switched-Capacitor Filter
- Oscillator
- A/D Converter

Connect some electronic components (Resistors, capacitors, transistors, diodes) surrounding the opamp will result in interesting applications

For simplicity, we always analyze opamp based circuits with ideal opamp model

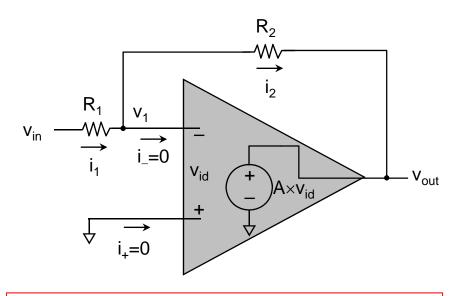How to Derive Transfer Function for Opamp Circuit?



Important Observation:

- No current flowing into the opamp, i.e. i_{_}=i_{_}=0
- If A is large and v_{out} is finite⇒v_{id}=-v₁≈0 ⇒ v+≈v-⇒Virtually short
- A real short, current can potentially flow through between two nodes. A virtual short, only the voltage appears to be zero, but there is no current flowing through between the two nodes.
- Since V+ is connected to ground, we can say v₁ is virtual ground

Transfer Function for Opamp Circuit

$$v_{id} = -v_{1}$$

$$v_{out} = Av_{id} = A(-v_{1})$$

$$\Rightarrow v_{1} = -\frac{v_{out}}{A}$$

$$\frac{v_{in} - v_{1}}{R_{1}} = \frac{v_{1} - v_{out}}{R_{2}} \quad \text{KCL:}$$


$$i_{1} = 0 \Rightarrow i_{1} = i_{2}$$

$$\Rightarrow \frac{v_{in} + \frac{v_{out}}{A}}{R_{1}} = \frac{-\frac{v_{out}}{A} - v_{out}}{R_{2}}$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = -\frac{R_{2}}{R_{1}} \frac{1}{\frac{R_{1} + R_{2}}{AR_{1}} + 1}$$

$$\approx -\frac{R_{2}}{R_{1}} \quad \text{if} \quad A \to \infty$$

Inverting Amplifier

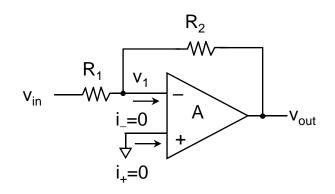

Transfer Function for Inverting Amplifier

$$v_1 = v_- \approx v_+ = 0$$
 [:: Virtually short to ground]

$$\frac{v_{in} - v_1}{R_1} = \frac{v_1 - v_{out}}{R_2}$$


$$\frac{v_{in}}{R_1} = \frac{-v_{out}}{R_2}$$


Using virtual short concept, the analysis is much simpler

$$\Rightarrow \frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1} \cdot \dots \cdot (1)$$

- The overall gain $(A_V=v_{out}/v_{in})$ is controlled by the ratio of the resistor (R_2/R_1)
- The overall gain is independent of the opamp gain (A)
- It is a feedback amplifier
- There is polarity inversion between v_{out} and v_{in}


Opamp Biasing - Old Days

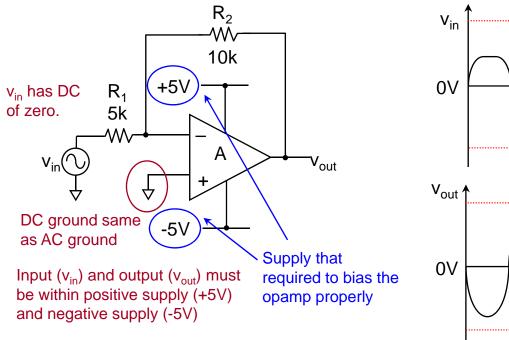

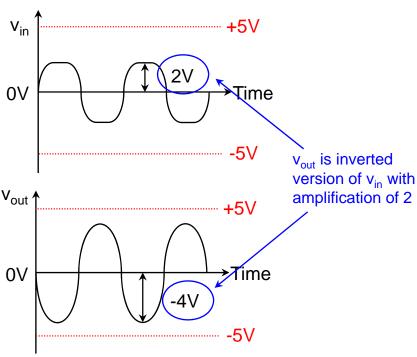


- Luxury of dual supply (+5V and -5V)
- DC ground and AC ground are the same


Opamp Biasing - Nowadays

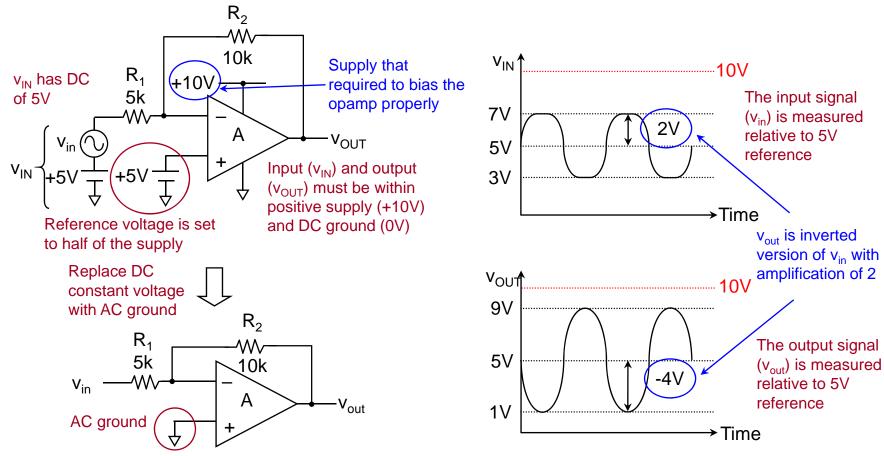

- Single supply only (+10V)
- The reference voltage is usually implemented using simple resistor divider
- DC ground and AC ground are not the same
- For analysis simplicity, we will always ignore the DC portion and perform the AC analysis.


Why Feedback Amplifier?

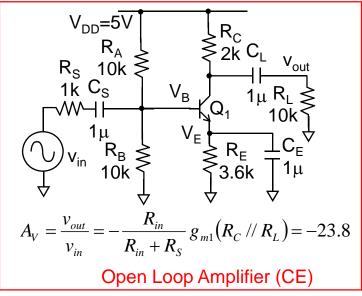

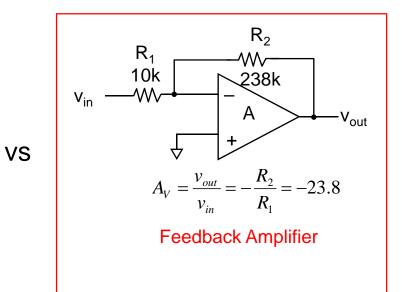


	Open Loop Amplifier	Feedback Amplifier
Gain	Not accurate (Difficult to control transistor parameters)	Accurate gain (Gain only depends on the ratio of resistors, which can be accurately controlled)
Linearity	Poor Linearity (More distortion)	High Linearity (Less distortion)
Complexity	Simple and consume less power	Opamp is complicated and consume more power

Summing Amplifier

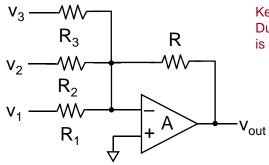

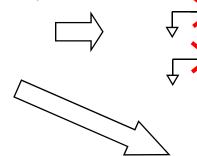- 1) Estimate output due to individual voltage source
- 2) Apply linear superposition to find the total contribution
- 3) While estimating contribution from one voltage source, kill all the other voltage source

Keep v_3 and kill v_1 , v_2 VDue to virtual ground, R_1 and R_2 is effectively removed




 $v_{-} \approx v_{+} = 0$

-v_{out}

$$\Rightarrow v_{out,v3} = -\frac{R}{R_3}v_3$$

Equation (1) from slide 8-6

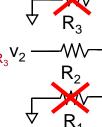
Keep v_2 and kill v_1 , v_3 Due to virtual ground, R_1 and R_3 V_2 is effectively removed



 $v_{-} \approx v_{+} = 0$

 $\Rightarrow v_{out,v2} = -\frac{R}{R_2}v_2$


Equation (1) from slide 8-6

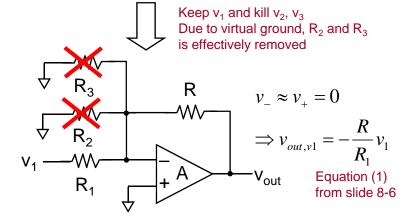


Transfer Function for Summing Amplifier
$$v_{out} = v_{out,v_1} + v_{out,v_2} + v_{out,v_3}$$
 Superposition
$$= -\left(\frac{R}{R_1}v_1 + \frac{R}{R_2}v_2 + \frac{R}{R_3}v_3\right)$$

$$= -\left(v_1 + v_2 + v_3\right) \quad if \quad R_1 = R_2 = R_3 = R$$

Steps for Opamp Circuit Analysis

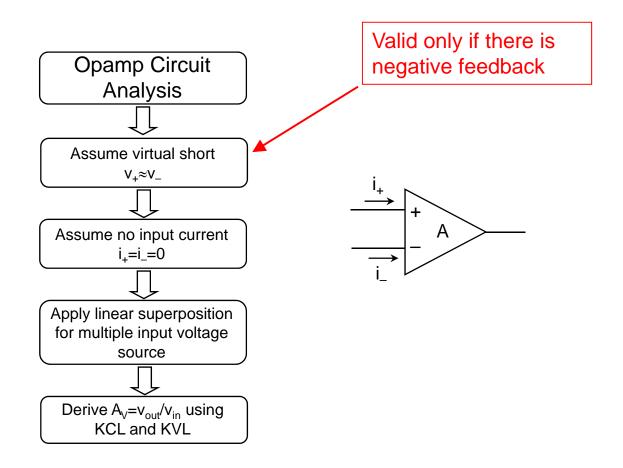

Non-Inverting Amplifier

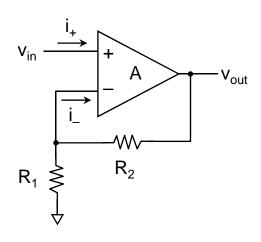

What is the limitation on the gain of non-inverting amplifier?

Transfer Function for Non-Inverting Amplifier


$$v_{-} \approx v_{+} = v_{in} \quad [\because Virtual \quad Short]$$

$$v_{-} = v_{out} \times \frac{R_{1}}{R_{1} + R_{2}} = v_{in} \quad [\because i_{+} = i_{-} = 0]$$

$$\Rightarrow \frac{v_{out}}{v_{in}} = \left(1 + \frac{R_2}{R_1}\right) \cdot \cdot \cdot \cdot \cdot (2)$$

- The overall gain $(A_V=v_{out}/v_{in})$ is controlled by the ratio of the resistor $(1+R_2/R_1)$
- The overall gain is independent of the opamp gain (A)
- It is a feedback amplifier
- There is no polarity inversion between v_{out} and v_{in}

Unity Gain Buffer (Source Follower)

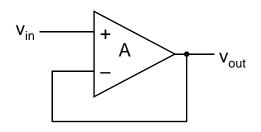


Transfer Function for Unity Gain Buffer

$$v_{out} = v_{-} \approx v_{+} = v_{in}$$
 [:: Virtual Short]
$$\Rightarrow \frac{v_{out}}{v_{in}} = 1$$


$$R_{in} = \infty$$

$$R_{out} \rightarrow 0$$

Ideal for driving low impedance load

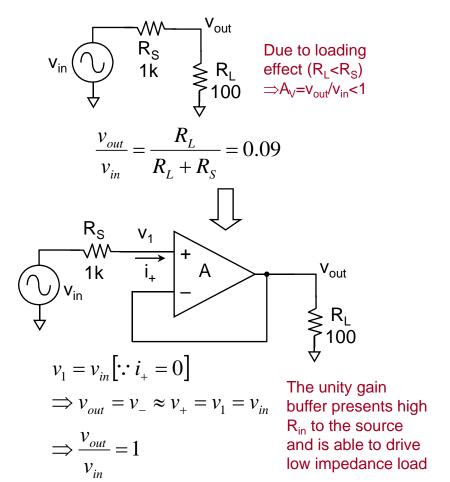

Logarithmic Amplifier

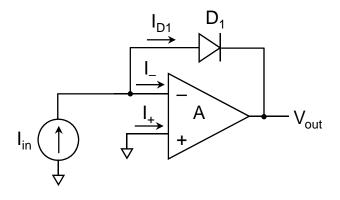

Because the signals we are dealing with consist of DC and AC components, we use upper case (V_{out} , I_{in}) rather than lower case (v_{out} , i_{in})

Transfer Function for Logarithmic Amplifier

$$V_{-} \approx V_{+} = 0 \quad \left[\because Virtual \quad Short\right]$$

$$V_{D1} = V_{-} - V_{out} \approx -V_{out}$$


$$I_{D1} = I_{S} \left(e^{V_{D1}/V_{T}} - 1 \right) \approx I_{S} e^{-V_{out}/V_{T}} \quad \text{Diode characteristic equation}$$

$$I_{D1} = I_{in} \approx I_{S} e^{-V_{out}/V_{T}} \quad \left[\because i_{+} = i_{-} = 0\right]$$

$$\Rightarrow V_{out} = -V_{T} \ln \left(\frac{I_{in}}{I_{S}} \right) \quad \text{Output is natural log of input}$$


 Suitable for application where the input has very wide dynamic range

Logarithmic Amplifier (Camera)

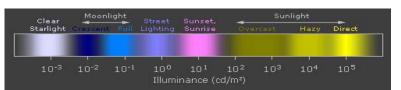

light 1pA 10pA 100pA 1nA 10nA 100n 1μΑ 10μΑ 100μΑ

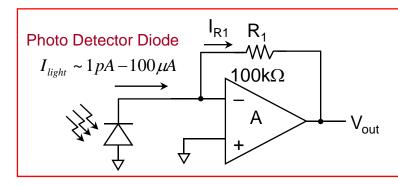
 I_{light} changes with light intensity Light intensity changes by order of magnitude \Rightarrow I_{light} also changes by order of magnitude



$$V_{out} = -I_{light} \times R_1$$
 $\sim -0.1 \mu V$ to $-10V$
Clear Direct
Starlight Sunlight

Output changes linearly with input ⇒ Difficult to detect and differentiate the input signal

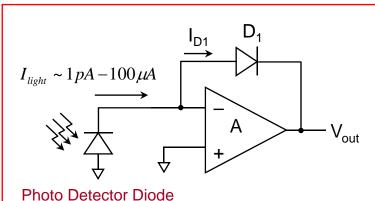V_{out}<1mV cannot be easily measured ⇒ Can only detect sunset/sunrise and above



$$I_{\rm S} = 10^{15} \quad V_{\rm T} = 25 \, {\rm mV}$$

$$I_{light} \sim 1 pA - 100 \mu A$$

Input changes by eight order of magnitude $(10^{-12} - 10^{-4})$


$$V_{out} = -V_T \ln \left(\frac{I_{light}}{I_S} \right) \sim -0.17V \ to -0.63V$$
Clear Direct
Starlight Sunlight

Output changes in log scale with input ⇒ Easy to detect and differentiate the input signal

-0.17V and -0.63V can be easily measured

⇒ All light conditions can be detected

Exponential Amplifier

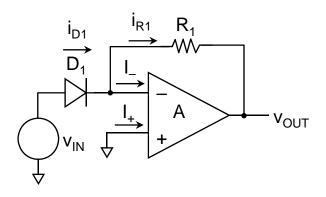

Because the signals we are dealing with consist of DC and AC components, we use lower case variable with upper case subscript (V_{OUT}, V_{IN})

Transfer Function for Exponential Amplifier

$$V_{-} \approx V_{+} = 0 \quad [\because Virtual \quad Short]$$

$$V_{D1} = V_{IN} - V_{-} \approx V_{IN}$$


$$i_{D1} = I_{S} \left(e^{V_{IN}/V_{T}} - 1 \right) \approx I_{S} e^{V_{IN}/V_{T}} \quad \text{Diode characteristic equation}$$

$$i_{D1} = i_{R1} = \frac{V_{-} - V_{OUT}}{R_{1}} \approx \frac{-V_{OUT}}{R_{1}} \quad [\because i_{+} = i_{-} = 0]$$


$$\Rightarrow V_{OUT} = -R_{1}I_{S} e^{V_{IN}/V_{T}} \quad \text{Output is exponential of input}$$

 Suitable for application where the input has very narrow dynamic range and you want to expand it for easier differentiation

Integrator

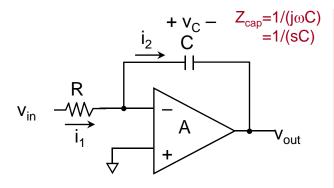

The circuit performs analog integration

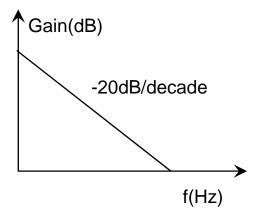

Transfer Function for Integrator

$$\begin{aligned} v_{-} &\approx v_{+} = 0 & \left[\because Virtual \ Short \right] \\ v_{C}(t) &= v_{-} - v_{out}(t) \approx -v_{out}(t) \\ i_{1}(t) &= \frac{v_{in}(t)}{R} & i_{2}(t) = C \frac{dv_{C}(t)}{dt} \approx -C \frac{dv_{out}(t)}{dt} \\ i_{1}(t) &= i_{2}(t) & \left[\because i_{+} = i_{-} = 0 \right] \\ &\Rightarrow -C \frac{dv_{out}(t)}{dt} = \frac{v_{in}(t)}{R} \\ &\Rightarrow v_{out}(t) = -\frac{1}{RC} \int_{0}^{t} v_{in}(t) dt \end{aligned}$$

Alternatively based on inverting amplifier


$$H(j\omega) = \frac{V_{out}}{V_{in}} = -\frac{Z_{cap}}{R} = -\frac{1}{j\omega CR} = -\frac{1}{sCR} = H(s)$$
 Slide 8-6 equation 1

$$\frac{1}{j\omega} = \frac{1}{s} \to \int (\cdot) dt$$


S-Transform (Learnt in EE2023, Signals and Systems)

- H(jω) reduces with increasing ω (ω=2πf)
- dB(H(jω))=20×log₁₀(|H(jω)|)
- -20dB/decade means H(jω) decreases by 20dB when the frequency (f or ω) increases by 10 times.

Differentiator

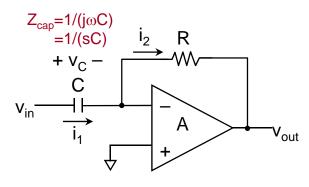

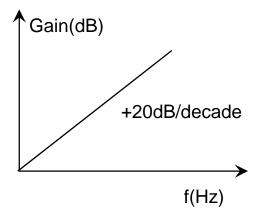The circuit performs analog differentiation



Transfer Function for Differentiator

$$v_{-} \approx v_{+} = 0 \quad [\because Virtual \; Short]$$

$$v_{C}(t) = v_{in}(t) - v_{-} \approx v_{in}(t)$$

$$i_{1}(t) = C \frac{dv_{C}(t)}{dt} \approx C \frac{dv_{in}(t)}{dt} \qquad i_{2}(t) = \frac{v_{-} - v_{out}(t)}{R} \approx -\frac{v_{out}(t)}{R}$$

$$i_{1}(t) = i_{2}(t) \quad [\because i_{+} = i_{-} = 0]$$


$$\Rightarrow -\frac{v_{out}(t)}{R} = C \frac{dv_{in}(t)}{dt}$$


$$\Rightarrow v_{out}(t) = -RC \frac{dv_{in}(t)}{dt}$$

Alternatively based on inverting amplifier

$$H(j\omega) = \frac{V_{out}}{V_{in}} = -\frac{R}{Z_{cap}} = -j\omega CR = -sCR = H(s)$$
Slide 8-6 equation 1
$$\Rightarrow j\omega = s \rightarrow \frac{d(\cdot)}{dt}$$
S-Transform (Learnt in EE2023, Signals and Systems)


- $H(j\omega)$ increases with increasing ω ($\omega=2\pi f$)
- $dB(H(j\omega))=20\times log_{10}(|H(j\omega)|)$
- +20dB/decade means H(jω) increases by 20dB when the frequency (f or ω) increases by 10 times.

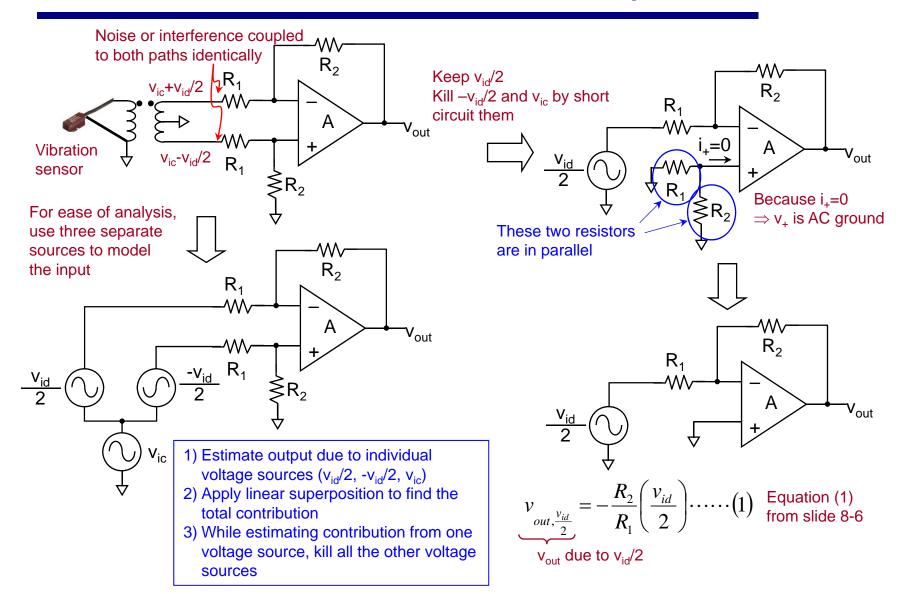

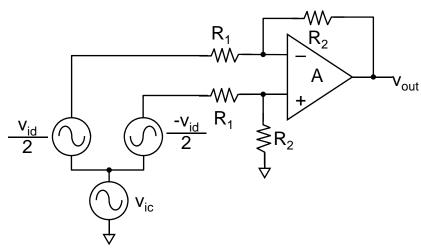

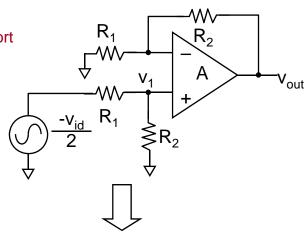Keep -v_{id}/2 Kill v_{id}/2 and v_{ic} by short circuit them






$$v_{1,-\frac{v_{id}}{2}} = \frac{R_2}{R_1 + R_2} \left(\frac{-v_{id}}{2}\right)$$


$$v_{out,-\frac{v_{id}}{2}} = \left(1 + \frac{R_2}{R_1}\right) v_{1,-\frac{v_{id}}{2}}$$
Equation (2) from slide 8-12
$$= \left(1 + \frac{R_2}{R_1}\right) \frac{R_2}{R_1 + R_2} \left(\frac{-v_{id}}{2}\right)$$

$$\Rightarrow v_{out,-\frac{v_{id}}{2}} = \frac{R_2}{R_1} \left(\frac{-v_{id}}{2}\right) \cdot \cdot \cdot \cdot \cdot (2)$$


$$v_{out} \text{ due to } -v_{id}/2$$

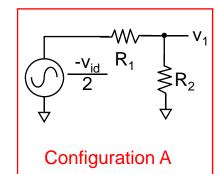


Simple resistor divider

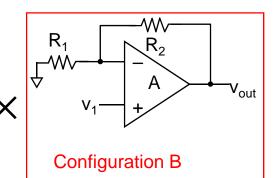

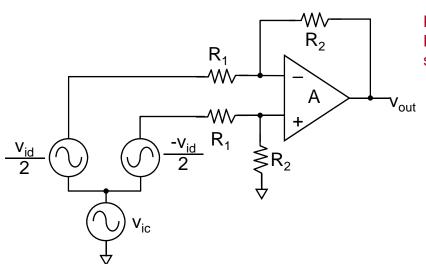Non-inverting Amplifier Equation (2) from slide 8-12



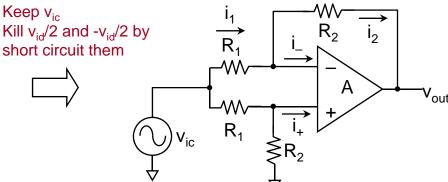

$$v_{+} = v_{ic} \times \frac{R_{2}}{R_{1} + R_{2}} \approx v_{-} [\because Virtual \ short]$$


$$i_{1} = i_{2} [\because i_{+} = i_{-} = 0]$$

$$\Rightarrow \frac{v_{ic} - v_{-}}{R_{1}} = \frac{v_{-} - v_{out, v_{ic}}}{R_{2}}$$

$$R_{2}v_{ic} - v_{ic} \times \frac{R_{2}^{2}}{R_{1} + R_{2}} = v_{ic} \times \frac{R_{1}R_{2}}{R_{1} + R_{2}} - v_{out, v_{ic}}$$

$$\Rightarrow v_{out, v_{ic}} = 0 \cdot \cdot \cdot \cdot \cdot (3)$$

$$v_{out} \text{ due to } v_{ic}$$

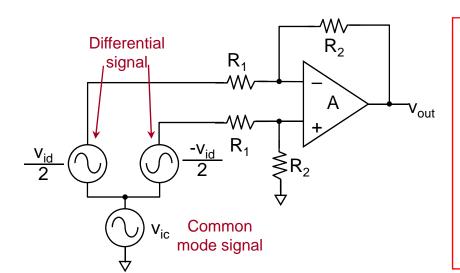


Transfer Function for Instrumentation Amplifier


$$\begin{aligned} v_{out} &= v_{out,\frac{v_{id}}{2}} + v_{out,-\frac{v_{id}}{2}} + v_{out,v_{ic}} \\ &= -\frac{R_2}{R_1} \left(\frac{v_{id}}{2}\right) + \frac{R_2}{R_1} \left(-\frac{v_{id}}{2}\right) + 0 \\ &= -\frac{R_2}{R_1} (v_{id}) \end{aligned}$$
 Superposition: Combine eqn (1), (2) and (3) from previous slides
$$= -\frac{R_2}{R_1} \left(\frac{v_{id}}{2}\right) + \frac{R_2}{R_1} \left(-\frac{v_{id}}{2}\right) + 0$$

- It rejects common mode signal and only amplifies differential signal
- Good rejection for common mode interference and noise
- Required for measurement instrument
- Limited by the matching properties of the resistors

Common Mode Interference Rejection

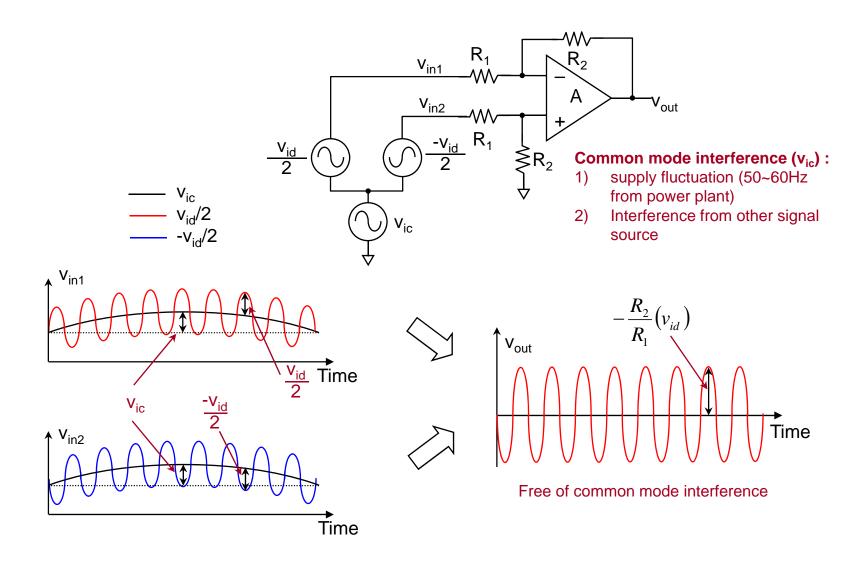


Common Mode Noise Rejection

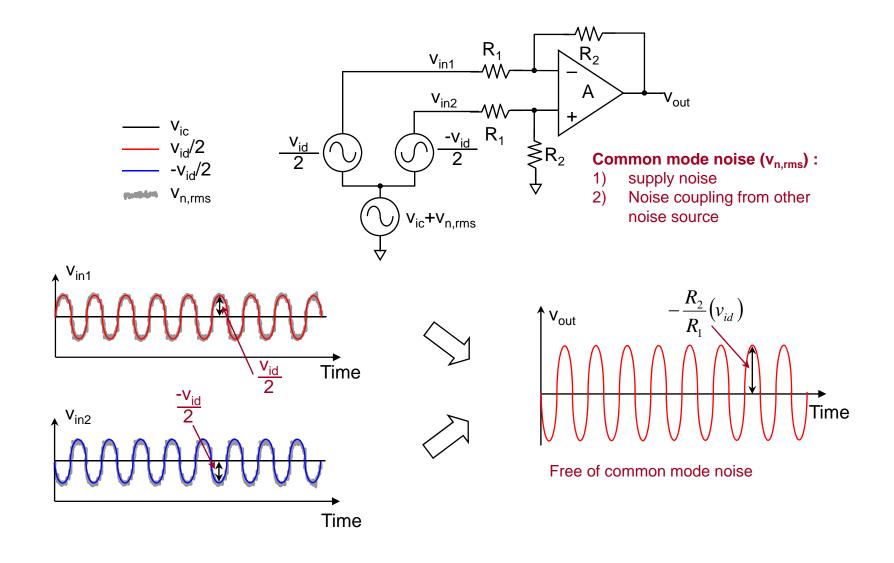

What is Filter?

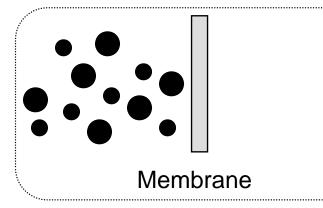Filtering consist of the following factors:
1)Filtering criteria
2)Filtering action



The membrane behaves like a filter which allows small particle to get through and block out the big particle



Selection Criteria



Action




Size



Small size goes through

What is Electronic Filter?

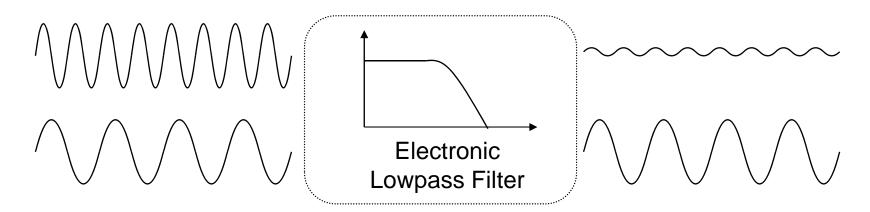



Selection Criteria



Action

The electronic lowpass filter only allows low frequency signal to go through and suppress the high frequency signal



Frequency



Pass low frequency Reject high frequency


Simple Lowpass

Passive 1st Order Lowpass Filter

Simple resistor divider

$$V_{in} \xrightarrow{\mathsf{V}_{in}} V_{out} = \frac{1}{\int_{in}^{\mathbf{V}_{out}} \mathbf{V}_{in}} = \frac{1}{\int_{i\omega} C_{1}} = \frac{$$

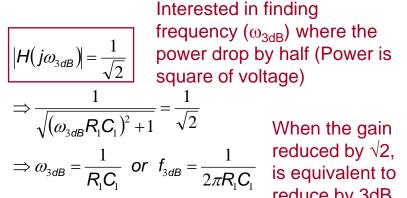
- At low frequency $(\omega \rightarrow 0)$, ignore 1st term of denominator (jωC₁R₁)⇒H(jω)≈1⇒Unity gain
- At high frequency $(\omega \rightarrow \infty)$, ignore 2^{nd} term of denominator $(1) \Rightarrow H(j\omega) \approx 1/(j\omega C_1 R_1) \Rightarrow Gain reduces$ with increasing frequency



$$\Rightarrow \frac{1}{\sqrt{(\omega_{3dB}R_{1}C_{1})^{2}+1}} = \frac{1}{\sqrt{2}}$$


$$\Rightarrow \omega_{3dB} = \frac{1}{R_{1}C_{1}} \text{ or } f_{3dB} = \frac{1}{2\pi R_{1}C_{1}}$$

reduce by 3dB

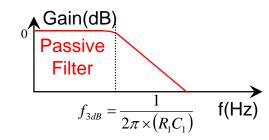



Simple Highpass

Passive 1st Order Highpass Filter

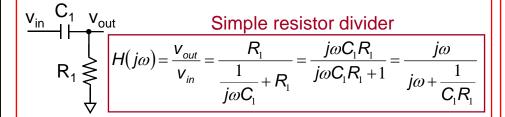


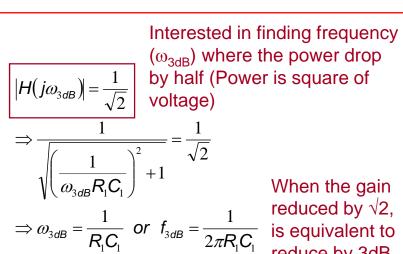
- At low frequency (ω→0), ignore 1st term of denominator
 (jω)⇒H(jω)≈jωC₁R₁⇒Gain increases with increasing frequency
- At high frequency (ω→∞), ignore 2nd term of denominator (1/(C₁R₁))
 ⇒H(jω)≈1⇒Unity gain




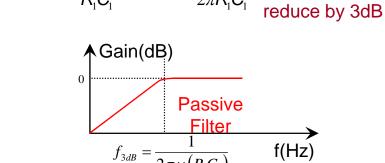

First Order Lowpass

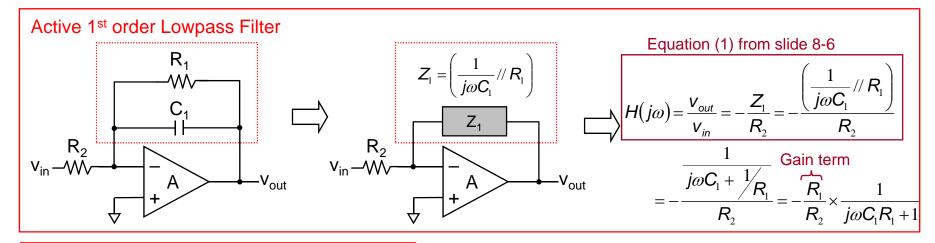


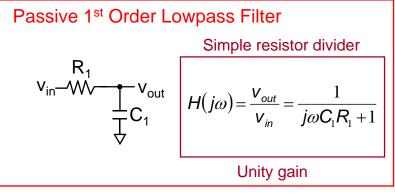


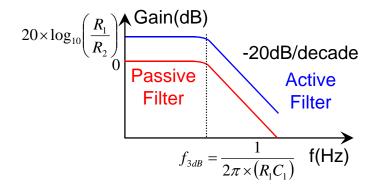


 Active 1st order lowpass has gain of R₁/R₂ versus gain of 1 for passive 1st order lowpass

First Order Highpass

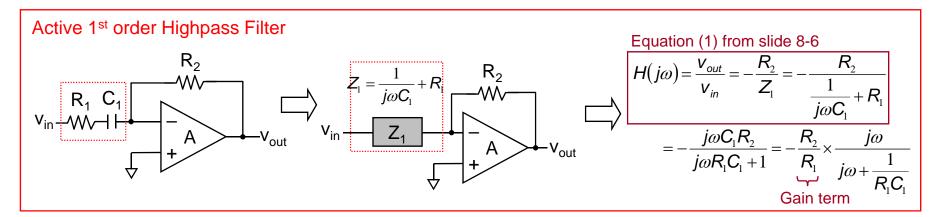


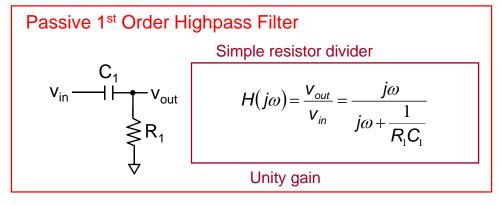

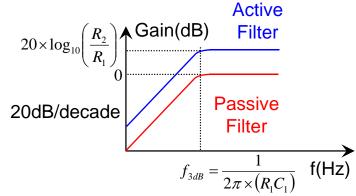


 Active 1st order highpass has gain of R₂/R₁ versus gain of 1 for passive 1st order highpass

Simplified Sallen-Key Lowpass Filter

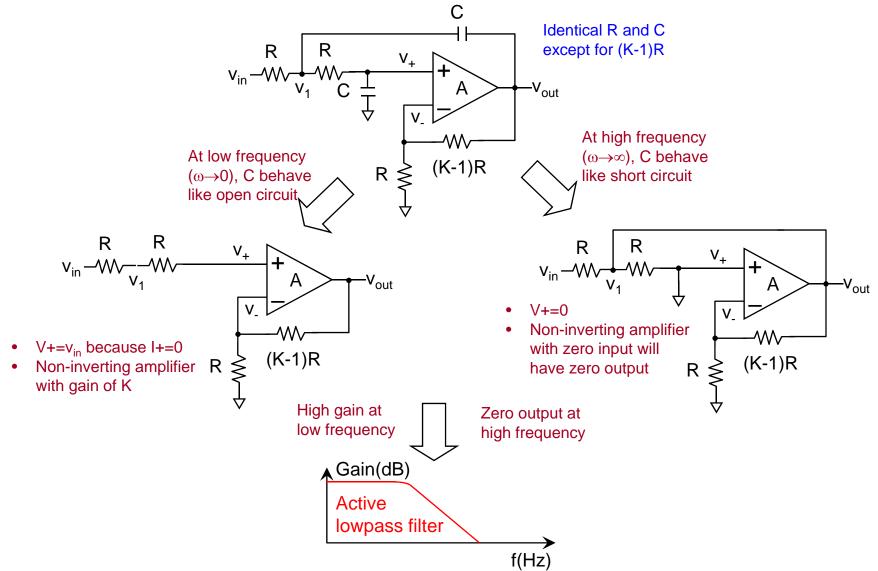

Sallen-Key Lowpass Filter

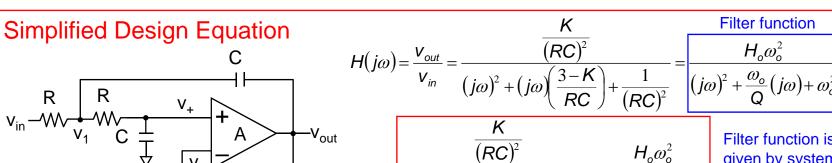

 $s^2 + s$

$$\Rightarrow \omega_o = \frac{1}{RC} \qquad \frac{1}{Q} = 3 - K \qquad H_o = K$$

Important design equation


Filter function is usually given by system designer, circuit designer only concerns about how to implement the desired filter function through opamp.

Why using 2nd order lowpass filter?

(K-1)R

Use s=iω to simplify the

notation

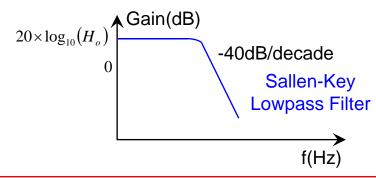

- At low frequency, ignore the 1st and 2nd terms of denominator of $H(j\omega) \Rightarrow H(j\omega) \approx H_{\alpha}$
- At high frequency, ignore the 2nd and 3rd terms of denominator of $H(j\omega) \Rightarrow H(j\omega) \approx H_0 \omega_0^2/(j\omega)^2$
- The gain reduces with ω²⇒sharper roll-off of -40dB/decade compared to 1st order lowpass filter
- It can suppress unwanted high frequency component more compared to 1st order lowpass filter

Lowpass Design Example

Design a second order lowpass filter that has Q of 0.7071 and cut-off frequency (ω_0) at 1kHz

$$\frac{\mathbf{v}_{\text{out}}}{\mathbf{v}_{\text{in}}} = \frac{H_o \omega_o^2}{(j\omega)^2 + \frac{\omega_o}{Q}(j\omega) + \omega_o^2} = \frac{H_o (2\pi \times 1k)^2}{(j\omega)^2 + \frac{2\pi \times 1k}{0.7071}(j\omega) + (2\pi \times 1k)^2}$$
Using simplified design equation
$$\frac{1}{Q} = 3 - K = \frac{1}{0.7071} \Rightarrow K = 1.59$$

$$H_o = K = 1.59$$

$$10k\Omega$$


$$v_{\text{in}} - WV$$

$$15.9nF = 0$$

$$\frac{1}{Q} = 3 - K = \frac{1}{0.7071} \Rightarrow K = 1.59$$
 $H_o = K = 1.59$

$$\omega_o = \frac{1}{RC} = 2\pi \times 1k$$

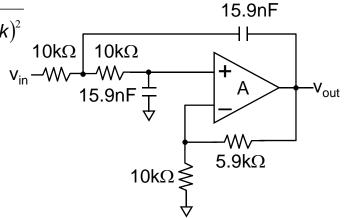
Choose $R = 10k\Omega \Rightarrow C = 15.9nF$



Important Notes on Sallen-Key Lowpass Filter:


- 1) Be able to identify the circuit topology as Sallen-Key Lowpass Filter
- 2) Be able to locate the design equations for Sallen-Key Lowpass Filter
- Be able to use the design equations to design the desired filter

Simplified Sallen-Key Highpass Filter

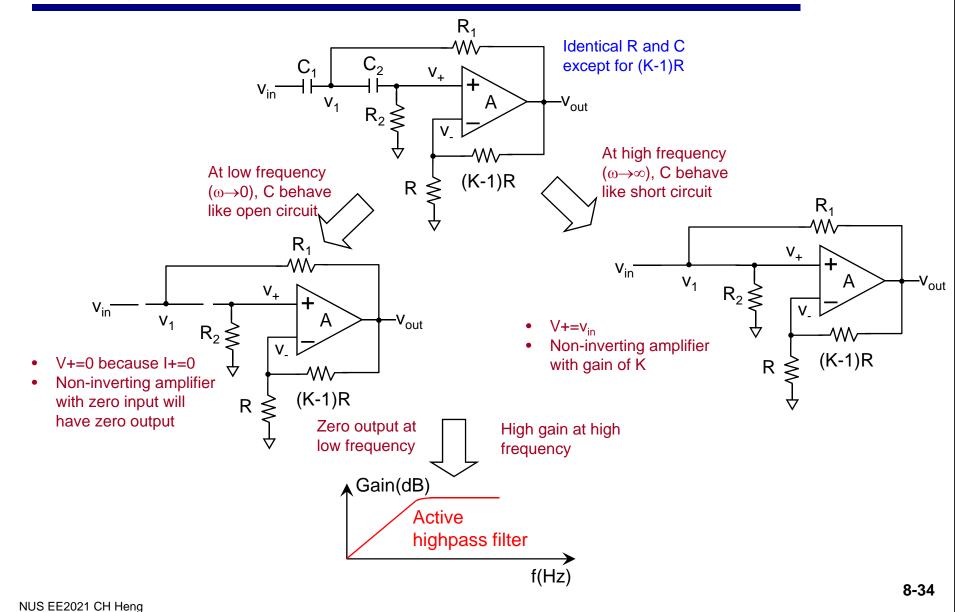

Sallen-Key Highpass Filter



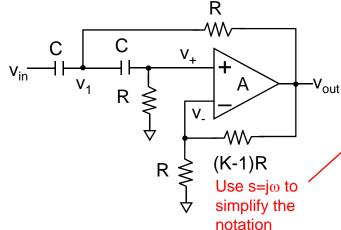

$$H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{K(j\omega)^2}{(j\omega)^2 + (j\omega)\left(\frac{3-K}{RC}\right) + \frac{1}{(RC)^2}} = \frac{I_{out}}{(j\omega)^2 + I_{out}}$$

$$= \frac{Ks^2}{s^2 + s\left(\frac{3 - K}{RC}\right) + \frac{1}{(RC)^2}} = \frac{H_o s^2}{s^2 + \frac{\omega_o}{Q}s + \omega_o^2}$$
$$= \frac{1}{RC} = \frac{1}{RC} = \frac{1}{RC} = \frac{1}{RC} = \frac{1}{RC}$$


Important design equation

Filter function

$$= \frac{H_o(j\omega)^2}{(j\omega)^2 + \frac{\omega_o}{Q}(j\omega) + \omega_o^2}$$

Filter function is usually given by system designer, circuit designer only concerns about how to implement the desired filter function through opamp.

Why using 2nd order lowpass filter?

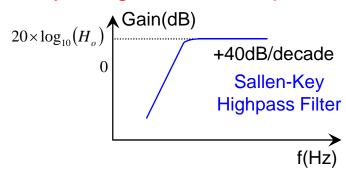

- At low frequency, ignore the 1st and 2nd terms of denominator of H(jω)⇒H(jω)≈H_o(jω)²/ω_o²
- At high frequency, ignore the 2nd and 3rd terms of denominator of H(jω)⇒H(jω)≈H_o
- The gain increases with ω²⇒sharper roll-off of +40dB/decade compared to 1st order highpass filter
- It can suppress unwanted low frequency component more compared to 1st order highpass filter

Highpass Design Example

Design a second order highpass filter that has Q of 0.7071 and cut-off frequency (ω_0) at 5kHz


$$\frac{v_{out}}{v_{in}} = \frac{H_o s^2}{s^2 + \frac{\omega_o}{Q} s + \omega_o^2} = \frac{H_o s^2}{s^2 + \frac{2\pi \times 5k}{0.7071} s + (2\pi \times 5k)^2}$$
3.2nF
$$v_{in} = \frac{V_{out}}{s^2 + \frac{\omega_o}{Q} s + \omega_o^2} = \frac{1}{s^2 + \frac{2\pi \times 5k}{0.7071} s + (2\pi \times 5k)^2}$$

Using simplified design equation

Using simplified design equation
$$\frac{1}{Q} = 3 - K = \frac{1}{0.7071} \Rightarrow K = 1.59 \qquad H_o = K = 1.59$$

$$\omega_o = \frac{1}{RC} = 2\pi \times 5k$$

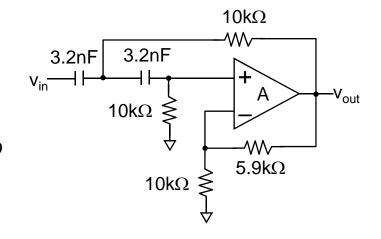Choose $R = 10k\Omega \Rightarrow C = 3.2nF$




Important Notes on Sallen-Key Highpass Filter:

- 1) Be able to identify the circuit topology as Sallen-Key Highpass Filter
- 2) Be able to locate the design equations for Sallen-Key Highpass Filter
- 3) Be able to use the design equations to design the desired filter


How to Build Higher Order Filter?

7th Order Lowpass Filter:

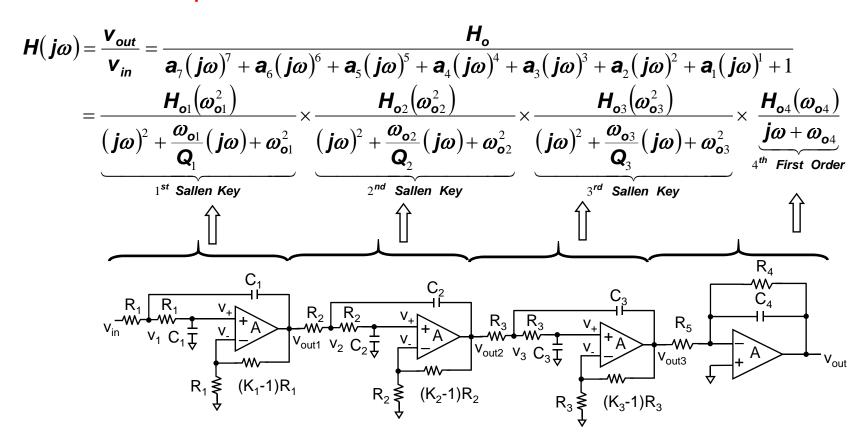


Superdiode

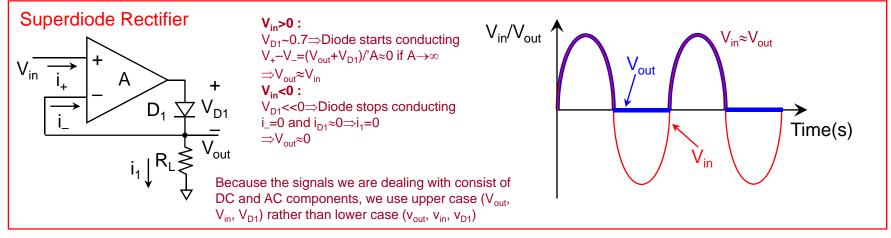Conventional Rectifier $V_{in}/V_{out} + V_{D1} - V_{out} = V_{D1} \approx 0.7$ The rectifier circuit only rectifies input when the input (V_{in}) is bigger than the diode voltage (V_{D1}) by 0.7VBecause the signals we are dealing with consist of DC and AC components, we use upper case $(V_{out}, V_{in}, V_{D1})$ rather than lower case $(V_{out}, V_{in}, V_{D1})$



- Ideal rectifier circuit should rectify input when the input (V_{in}) is bigger than zero
- Useful for AM demodulator when signal is small

Opamp Used as Comparator

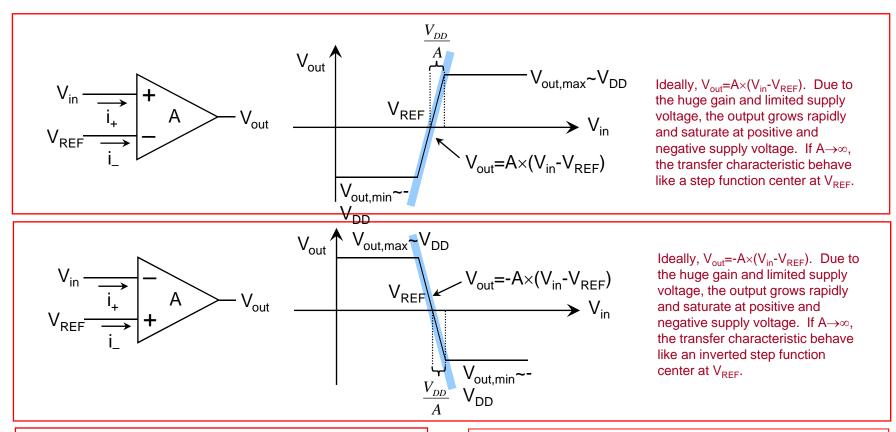

As an example, opamp with gain of 10000 and supply voltage of $\pm 10V$, when $|V_{in}-V_{ref}|>1mV$, V_{out} would saturate to $\pm 10V$.


Important Notes:


When opamp operates in open loop, virtual short (v_∗≈v_∗) no longer applies.

Applications Built using Opamp

- Now we have a library of opamp-based circuits
- We can realize more complicated functions by combining a number of opamp circuits
- This will form sub-system
- The concept will be illustrated in the following few examples

Triangular Wave

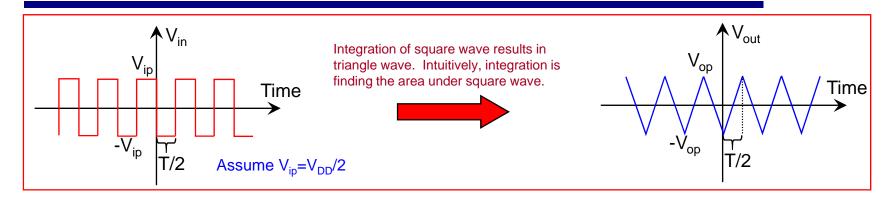

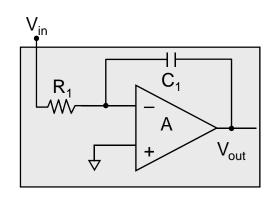

$$V_{out}(t) = -\frac{1}{R_1 C_1} \int V_{in}(t) dt$$

For
$$0 < t < \frac{T}{2}$$
:

$$V_{out}(t)|_{0}^{\frac{T}{2}} = -\frac{1}{R_{1}C_{1}} \int_{0}^{\frac{T}{2}} (-V_{ip}) dt$$

$$V_{out}(\frac{T}{2}) - V_{out}(0) = -\frac{1}{R_{1}C_{1}} \int_{0}^{\frac{T}{2}} (-\frac{V_{DD}}{2}) dt$$


$$2V_{op} = -\frac{1}{R_{1}C_{1}} \left[-\frac{V_{DD}}{2} t \right]_{t=0}^{t=\frac{T}{2}}$$

$$2V_{op} = \frac{V_{DD}T}{4R_{1}C_{1}}$$

Multiplier


■ How to create multiplier using existing opamp circuits covered so far, i.e. V_{out}=kV₁×V₂?

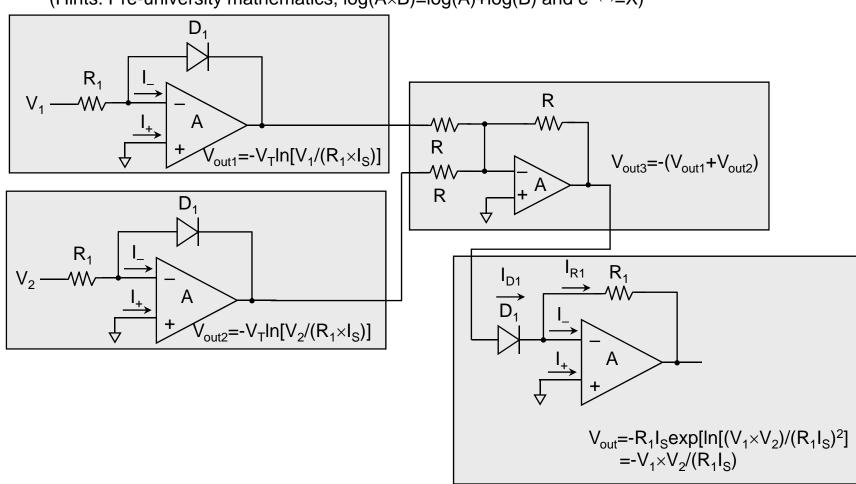(Hints: Pre-university mathematics, $log(A \times B) = log(A) + log(B)$ and $e^{ln(X)} = X$)




Bandstop Filter

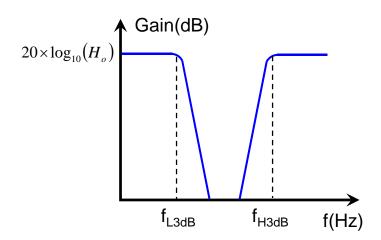
- How to create bandstop filter that has the following characteristic?
- What is the use of bandstop?
- Anti-jamming



Bandstop Filter

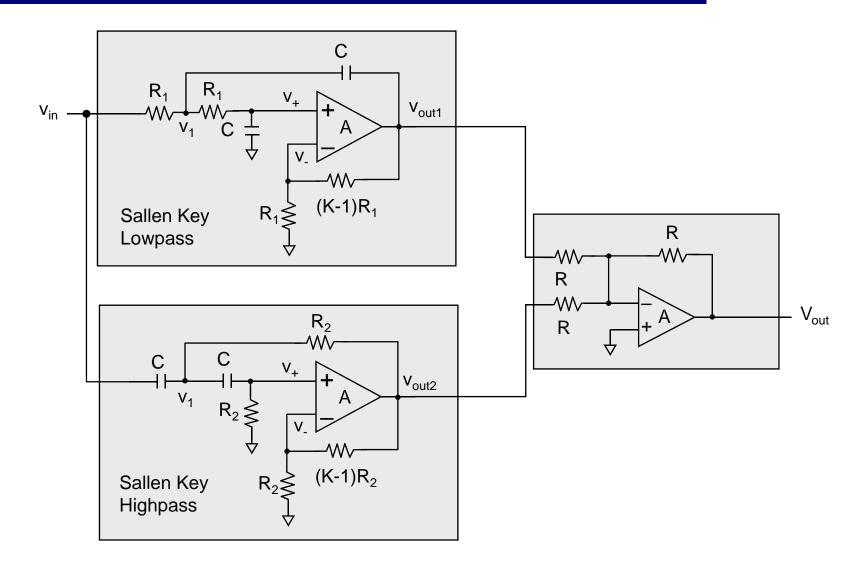

Full Wave Rectifier

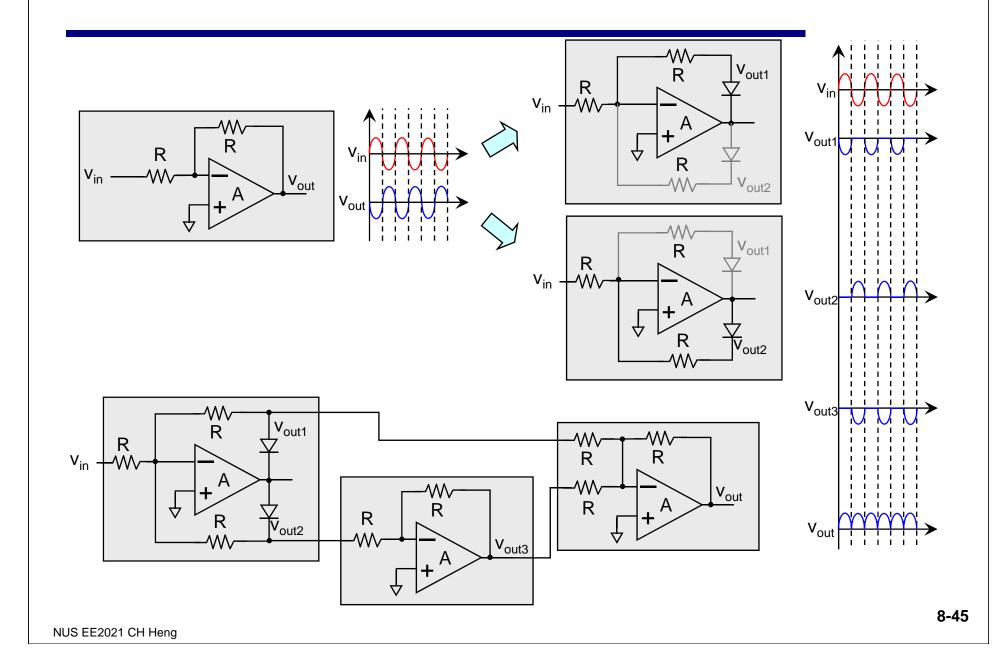

Lecture Summary

- Various opamp based circuit
- How to build sub-system using opamp based circuits

Reading Assignment

Reading: Reference Book (Sedra & Smith)
 Chapter 5, pp. 473 – 543. (Opamp)