

## NATIONAL UNIVERSITY of SINGAPORE

## Department of Electrical and Computer Engineering

## EE2021 – Devices and Circuits

## Homework 4

**Homework 4:**

You have to submit the homework assignment (Q.1) in hardcopy in class on **Wednesday 8 April 2015**.

Unless otherwise stated, you may use the tables of the amplifier configurations and equivalent resistances in your lecture notes in your solutions to the questions.

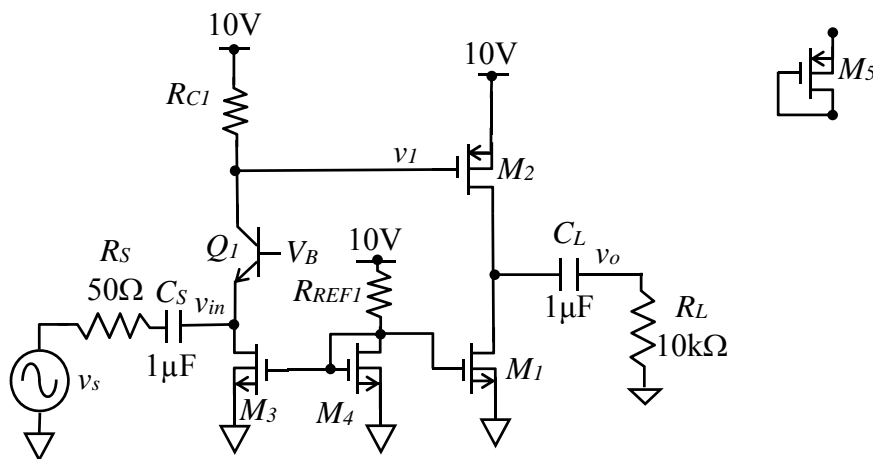
**Q.1**

Fig. Q1

In the two-stage amplifier circuit shown in Fig. Q1, assume that the npn BJT, the NMOS transistors and the PMOS transistors have the following device parameters:

- $V_A = 100 \text{ V}$  and  $\beta = 100$  for the BJT,  $Q_1$ ;
- $K_n = 2 \text{ m A/V}^2$ ,  $V_{THN} = 1 \text{ V}$ ,  $\lambda_n = 0.001 \text{ V}^{-1}$  and no body effect for the NMOS transistors,  $M_1$ ,  $M_3$  and  $M_4$ .
- $K_p = 2 \text{ m A/V}^2$ ,  $V_{THP} = -1 \text{ V}$ ,  $\lambda_p = 0.001 \text{ V}^{-1}$  and no body effect for the PMOS transistors,  $M_5$  and  $M_2$ .

Further assume that  $R_{REF1}$  is chosen such that  $M_1$ ,  $M_3$  and  $M_4$  each has a drain current of 1 mA. (You are not required to find  $R_{REF1}$ .)

- (i) Identify the configuration of each stage of the multi-stage amplifier.

[2 marks]

- (ii) Estimate the small signal parameters of  $M_2$ , i.e.  $g_{m,M2}$ , and  $r_{o,M2}$  and the small signal parameters of  $Q_1$ , i.e.,  $g_{m,Q1}$ ,  $r_{\pi,Q1}$ ,  $r_{o,Q1}$ .

[3 marks]

(iii) Design  $R_{C1}$  to ensure that  $M_2$  has the same current as  $M_1$  assuming these transistors are operating in the saturation region.

**[2 marks]**

(iv) Estimate the overall gain, i.e.,  $v_o/v_s$ .

**[6 marks]**

(v) What is the minimum  $V_B$  value allowed such that  $M_3$  is operating in the saturation region?

**[4 marks]**

(vi) If  $R_{C1}$  is replaced with  $M_5$ , would it create any biasing issue? Would the overall gain be larger or smaller?

**[3 marks]**