

EE2021

Devices and Circuits

Multi-Stage Amplifier Analysis, Speed up method

Lecture Outline

- **PMOS Multi-Stage Amplifier,**
- **BJT Multi-Stage Amplifier,**
- **NMOS Multi-Stage Amplifier,**






Not all transistors are equally important (serve different roles) in multi-stage amplifier

BJT Equivalent Resistance Summary (Table 1)

Blue: look into collector terminal

Red: look into base terminal

Green: look into emitter terminal

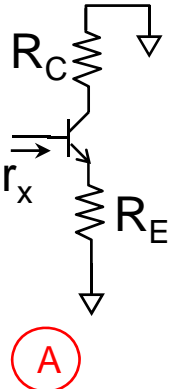
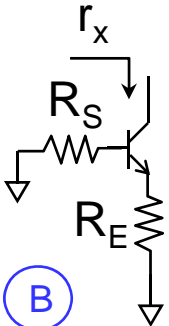
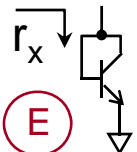
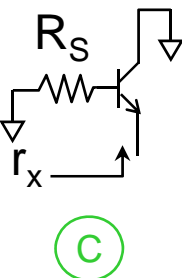
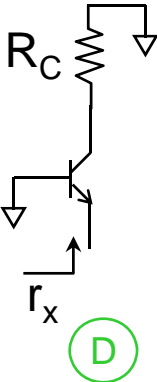
Conf	r_x	Conf	r_x	Conf	r_x
	$r_\pi + (1 + \beta)R_E$ $\approx r_\pi (1 + g_m R_E)$		$r_o \left\{ 1 + g_m \left[(r_\pi + R_S) \parallel R_E \right] \left(\frac{r_\pi}{r_\pi + R_S} \right) \right\}$ <p>If $R_S = 0$ and $r_\pi \ll R_E$ $\Rightarrow r_{x,\max} = r_o (\beta + 1)$</p>		$\frac{1}{g_m}$
	$\frac{R_S + r_\pi}{1 + \beta} \parallel r_o$ $\approx \frac{R_S}{1 + \beta} + \frac{1}{g_m}$		$\frac{1}{g_m} \times \frac{r_o + R_C}{r_o + \frac{R_C}{\beta}}$		

MOS Equivalent Resistance Summary (Table 2)

Blue: look into drain terminal


Red: look into gate terminal

Green: look into source terminal

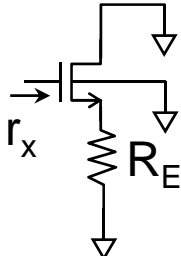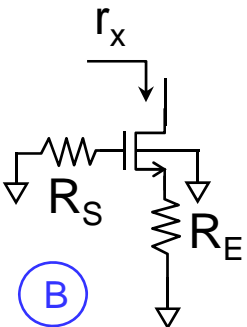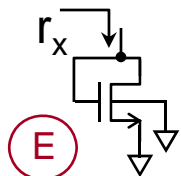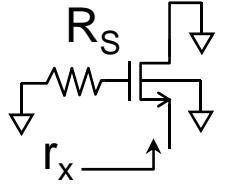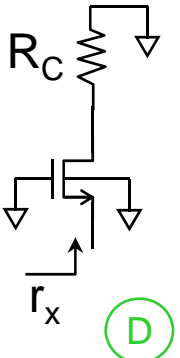Conf	r_x	Conf	r_x	Conf	r_x
 (A)	∞	 (B)	$r_o [1 + (g_m - g_{mb}) R_E]$	 (E)	$\frac{1}{g_m}$
 (C)	$\frac{1}{g_m - g_{mb}}$	 (D)	$\frac{1}{g_m - g_{mb}} \times \frac{r_o + R_C}{r_o}$		


BJT Amplifier Configurations

(Table 3)

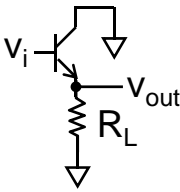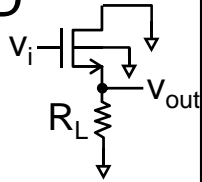BJT	G_m	A_v
CE (A)	g_m	Derive Based on 2-port Network
CB (B)	$-g_m$	Derive Based on 2-port Network
CC (C) 	Too Complex To Be Useful	$\frac{g_m R_L}{1 + g_m R_L}$
CE with Emitter Degeneration (D)	$\frac{g_m}{1 + g_m R_E}$	Derive Based on 2-port Network

MOS Amplifier Configurations

(Table 4)

MOS	G_m	A_v
CS (A)	g_m	Derive Based on 2-port Network
CG (B)	$-(g_m - g_{mb})$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network
CD (C) 	Too Complex To Be Useful	$\frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} \approx \frac{g_m}{g_m - g_{mb}}$ <i>Drop g_{mb} if no body effect</i>
CS with R_E (D)	$\frac{g_m}{1 + (g_m - g_{mb}) R_E}$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network

Similarity of Circuit AC Analysis to Differentiation

$$\frac{\partial(x^2)}{\partial x} = \lim_{\Delta x \rightarrow 0} \frac{(x + \Delta x)^2 - x^2}{\Delta x}$$

$$= 2x$$

$$\frac{\partial(e^x)}{\partial x} = \lim_{\Delta x \rightarrow 0} \frac{e^{x+\Delta x} - e^x}{\Delta x}$$

$$= e^x$$

$$\frac{\partial(\sin x)}{\partial x} = \lim_{\Delta x \rightarrow 0} \frac{\sin(x + \Delta x) - \sin x}{\Delta x}$$

$$= \cos x$$

$$f(x) = x^2 + e^x + \sin x$$

$$f'(x) = 2x + e^x + \cos x$$

Find out the derivative directly
using differentiation table


Differentiation Table

f(x)	f'(x)
x^n	$n \cdot x^{n-1}$
$\sin(x)$	$\cos(x)$
e^x	e^x

Differentiation

- Find derivative for important functions
- Group all these derivatives into a so-called differentiation table
- To derive derivative for more complex function, use the table to write down the individual derivatives directly

AC Analysis of Complicated Circuit

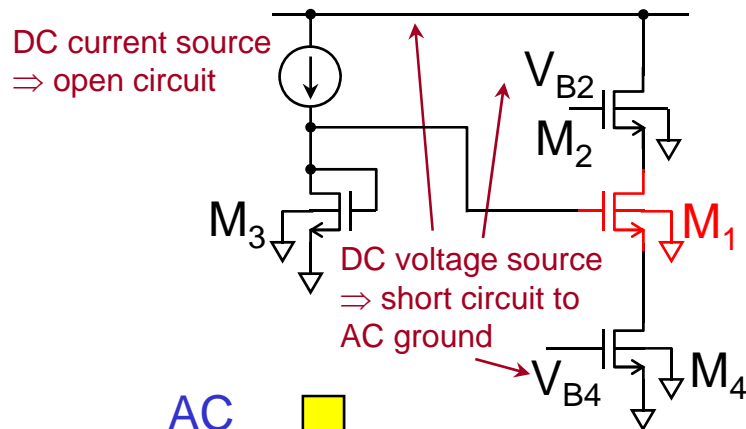

AC Circuit

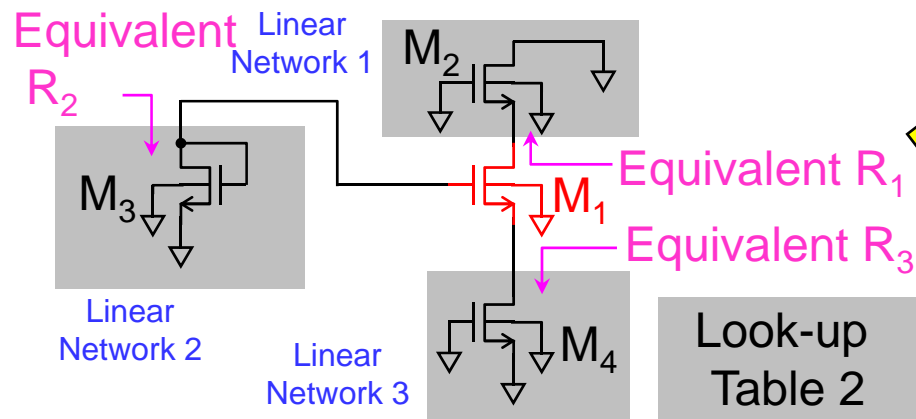



Table 2
configuration C
with $R_S=0$
⇒ $1/(g_{m2}-g_{mb2})$

Table 2
configuration E
⇒ $1/g_{m3}$

Table 2
configuration B
with $R_E=0$
⇒ $1/(\lambda I_{D4})$

Identify familiar transistor configurations and apply formula directly for the equivalent resistance


Multi-Stage Amplifier

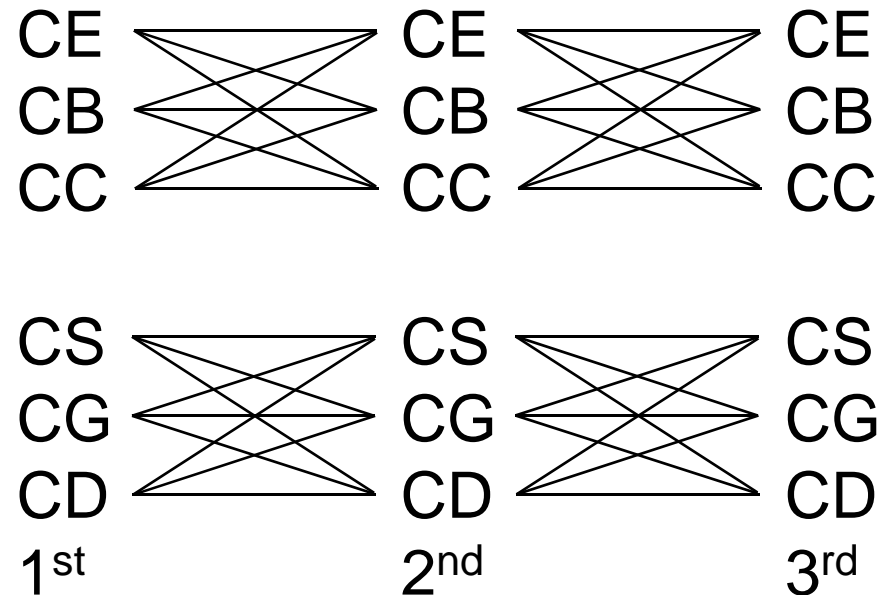

Why multi-stage?


- To modify R_{in} , R_{out} or the overall gain

Steps for Multi-stage Amplifier Analysis

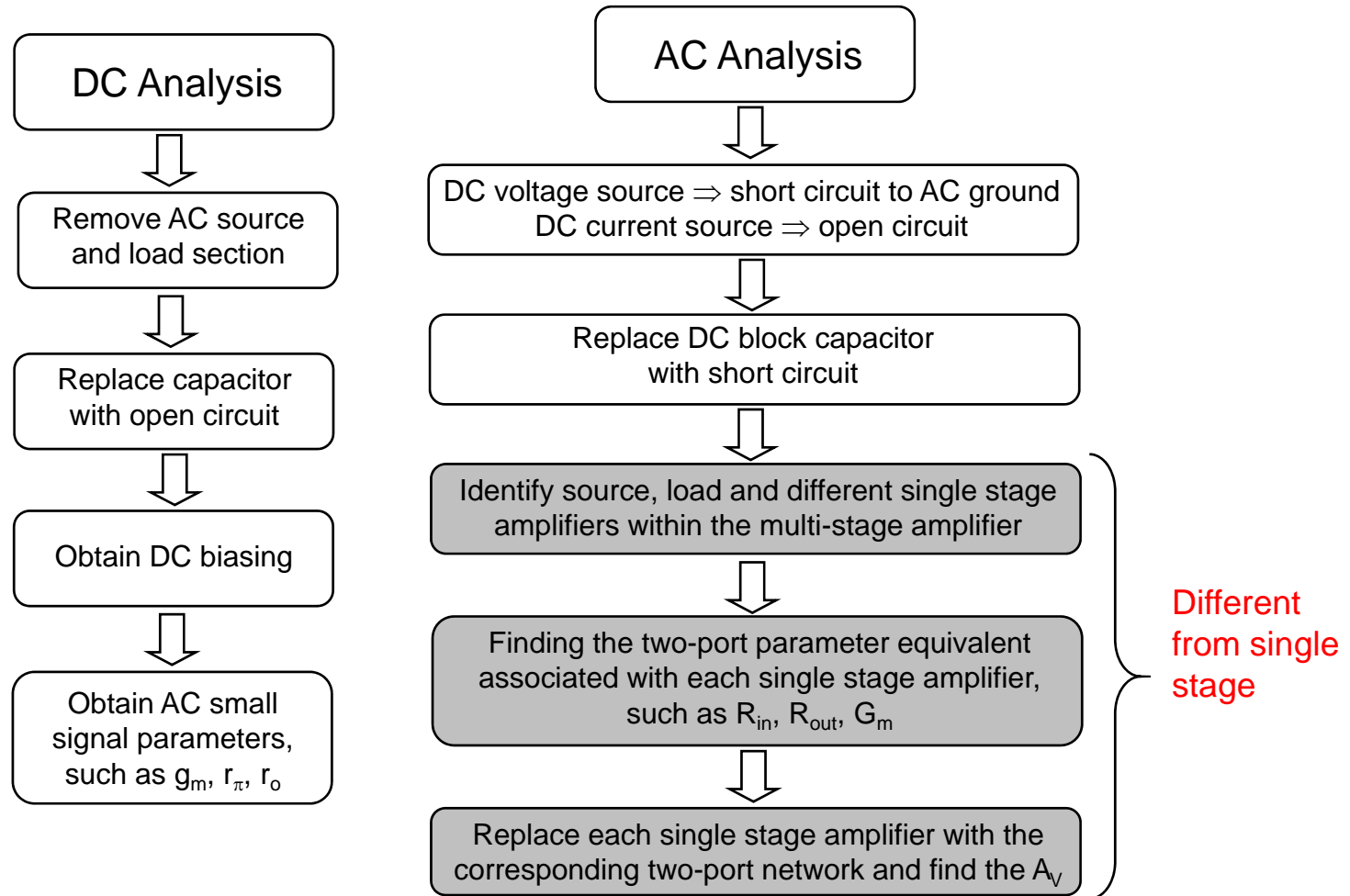

PMOS Example (DC Analysis)

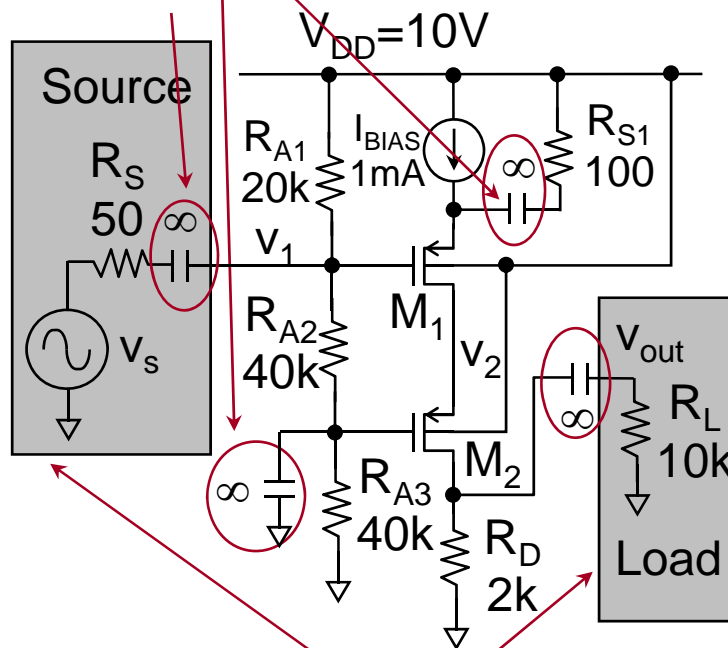Replace DC block capacitor with open circuit for DC analysis




Remove AC source and load section for DC analysis

$$\begin{aligned} K_p &= 2\text{mA/V}^2 \\ V_{\text{THP}} &= -1\text{V} \\ \lambda_p &= 0.01\text{V}^{-1} \end{aligned}$$

$$\begin{aligned} V_{G,M1} &= \text{Gate voltage of } M_1 \\ V_{S,M1} &= \text{Source voltage of } M_1 \\ V_{G,M2} &= \text{Gate voltage of } M_2 \\ V_{S,M2} &= \text{Source voltage of } M_2 \end{aligned}$$

- Identify Source and Load

PMOS Example (DC Analysis)

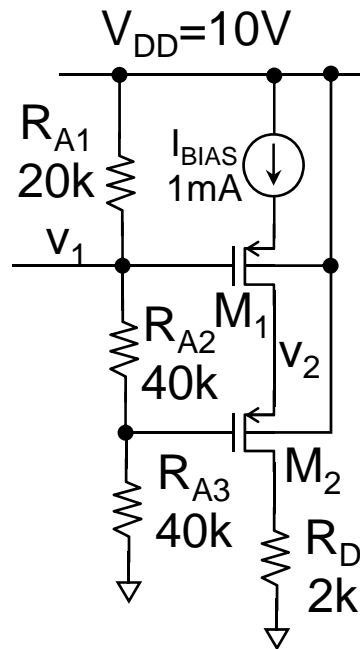

$$\begin{aligned} K_p &= 2\text{mA/V}^2 \\ V_{THP} &= -1\text{V} \\ \lambda_p &= 0.01\text{V}^{-1} \end{aligned}$$

Determine DC biasing

$$I_{D,M2} = I_{D,M1} = I_{S,M1} = I_{BIAS} = 1\text{mA}$$

Determine AC small signal parameter

$$\begin{aligned} g_{m,M1} &= g_{m,M2} = \sqrt{4K_p I_{D,M1}} \\ &= 2.8\text{mA/V} \end{aligned}$$


$$g_{mb} \approx -\frac{g_m}{4} = -0.71\text{mA/V}$$

$$r_i = \infty$$


$$r_o = \frac{1}{\lambda_p I_D} = 100\text{k}\Omega$$

Good approximation, no need to go through detailed calculations

PMOS Example (AC Analysis)

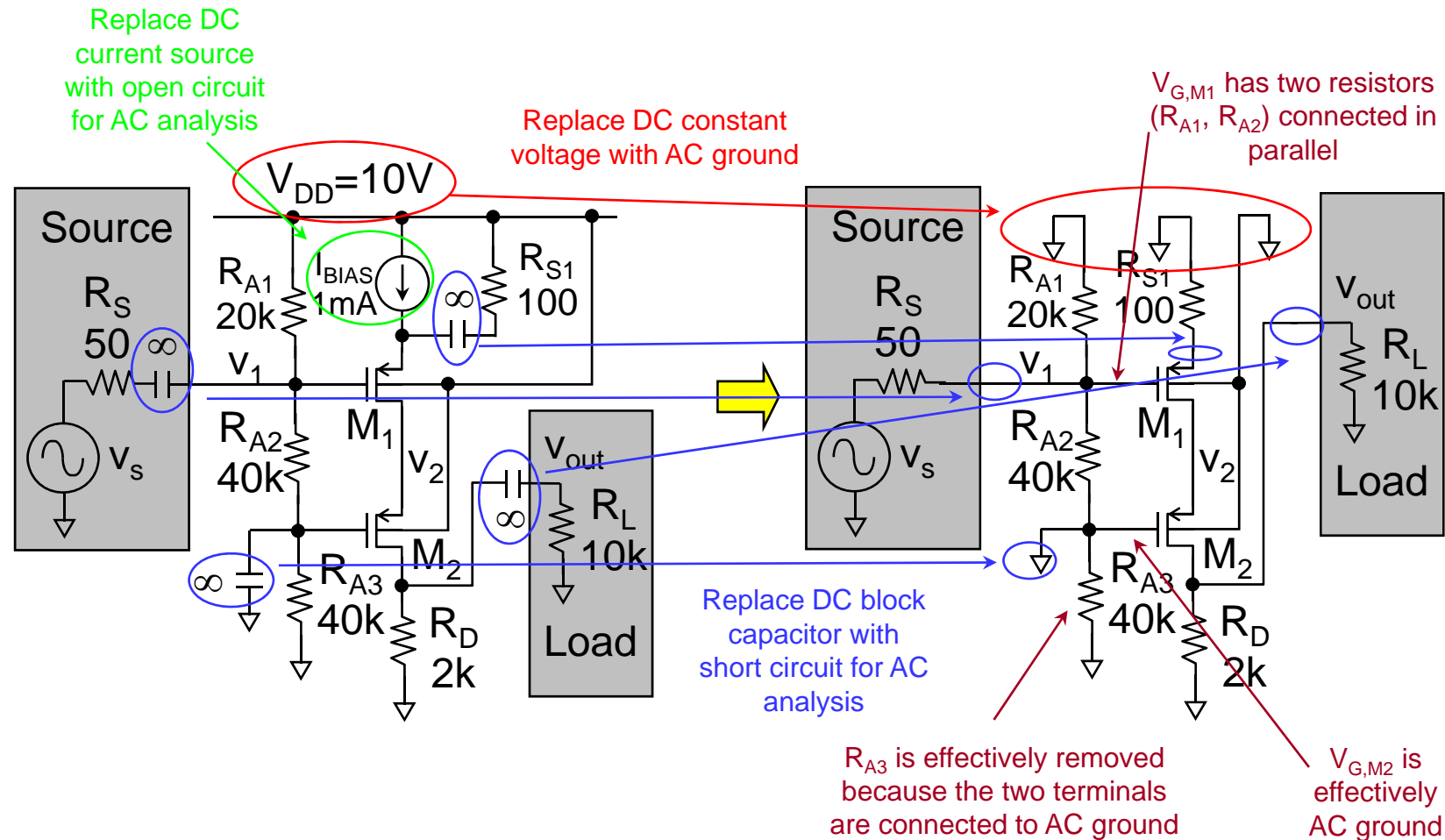


PMOS Example (Identify Single Stage)

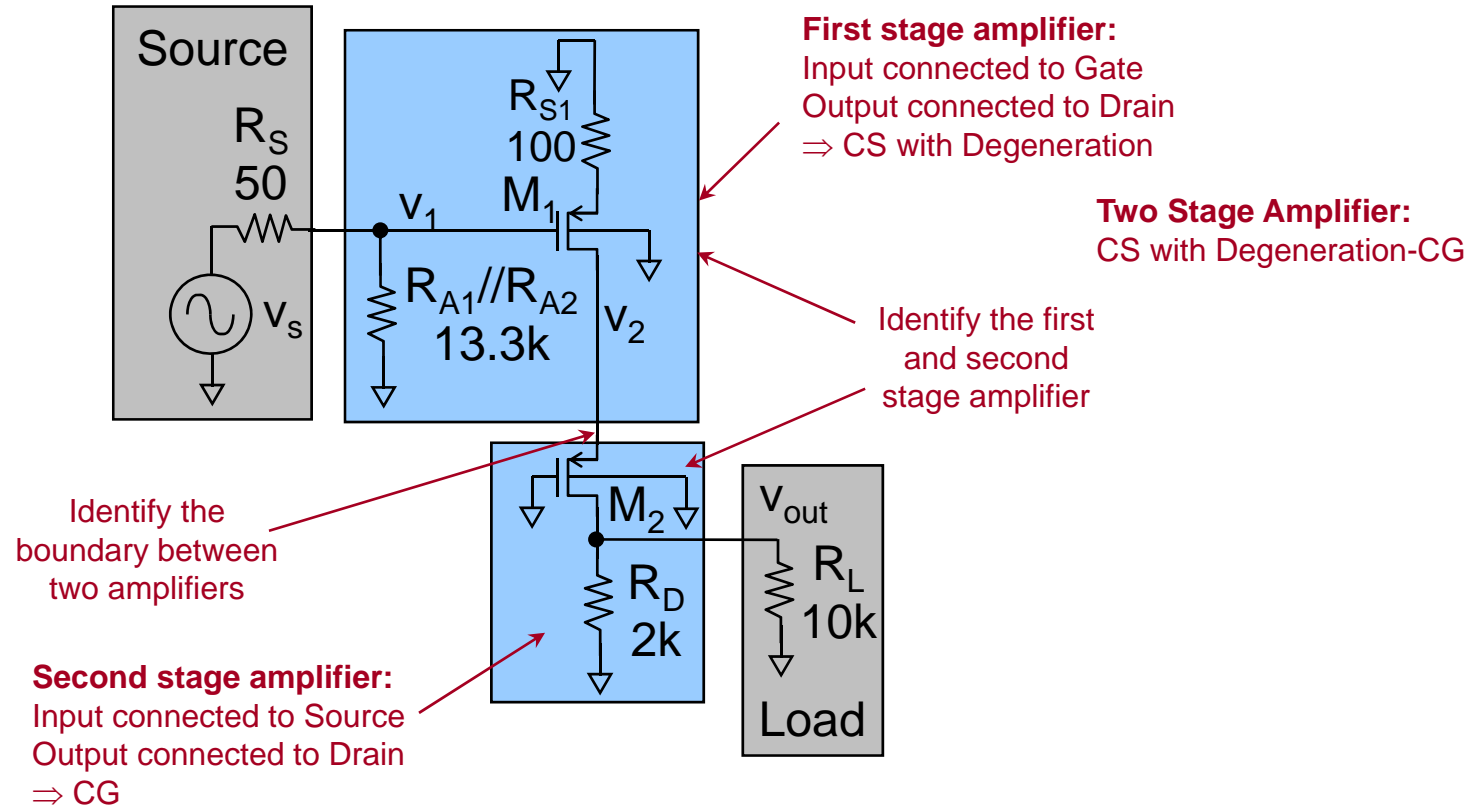


- Each single stage amplifier can be replaced with its two-port network equivalent consisting of R_{in} , R_{out} and G_m

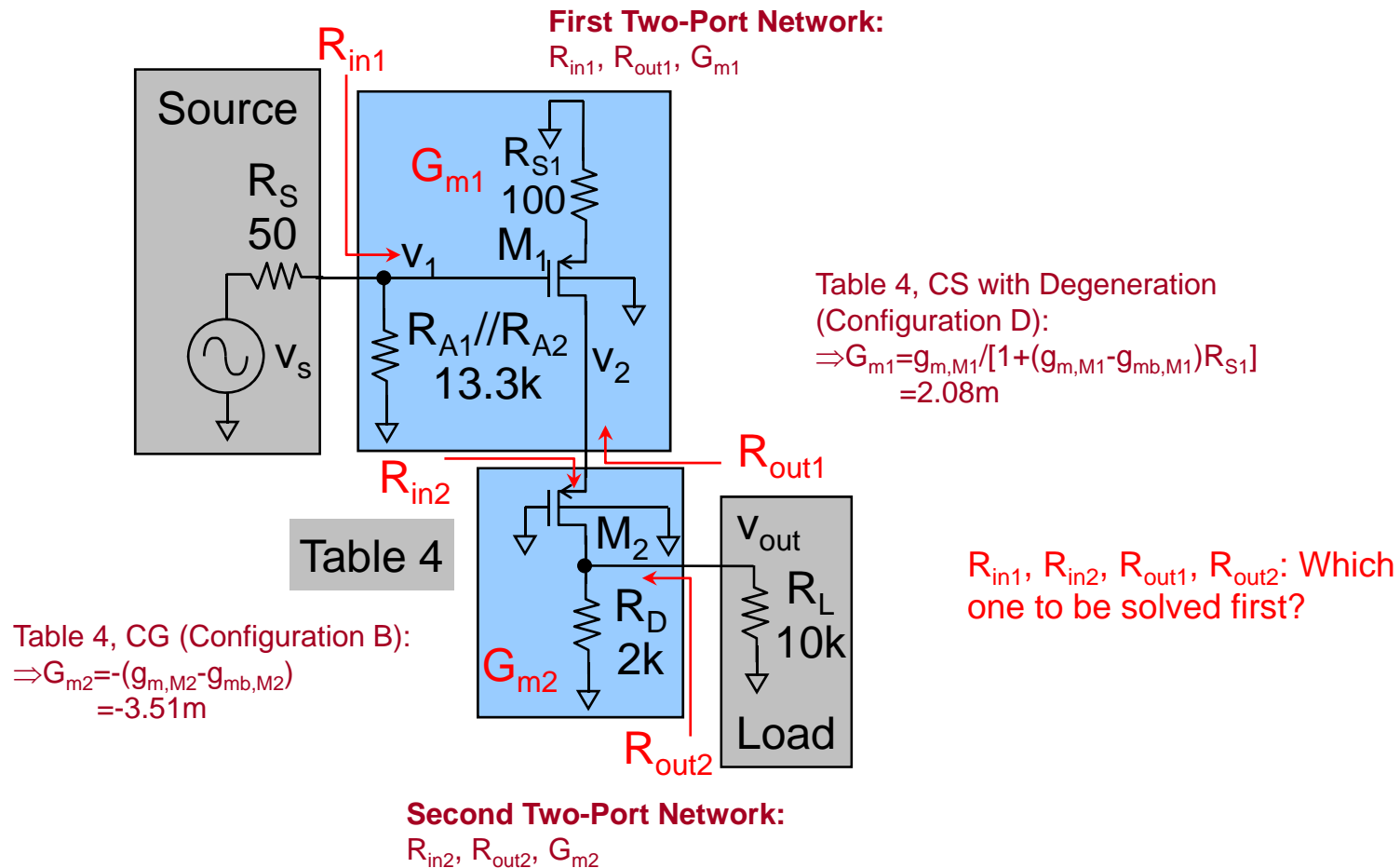PMOS Example (Identify 2-Port Parameters)



- Identify the 2-port network and the corresponding R_{in} , R_{out} and G_m


PMOS Example (Finding R_{in2})

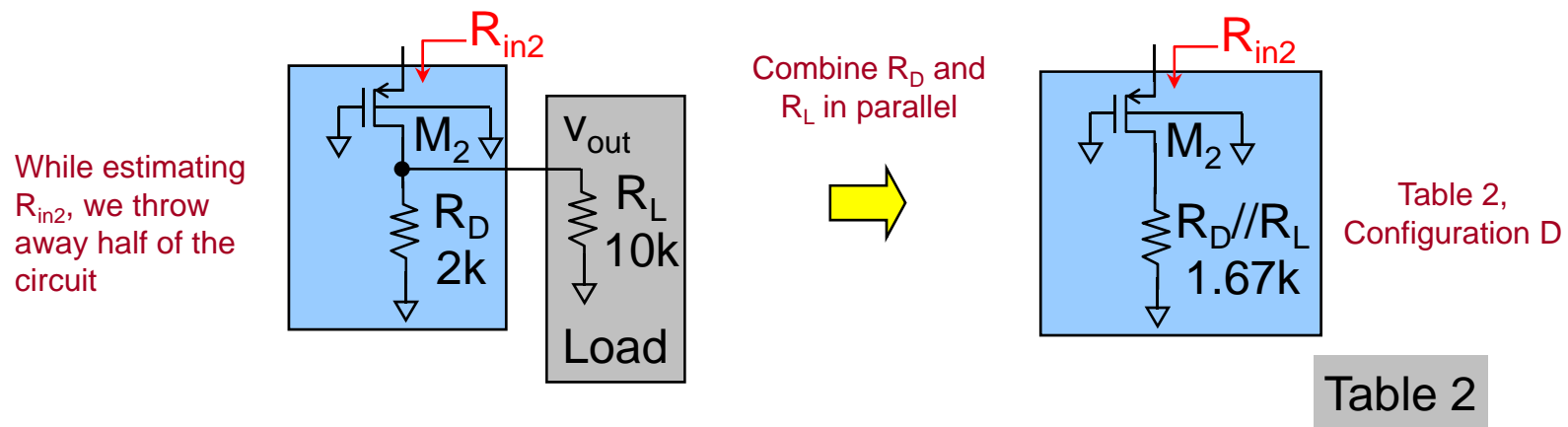

Configuration D

$$\Rightarrow R_{in2} = \frac{1}{g_{m,M2} - g_{mb,M2}} \frac{r_{o,M2} + (R_L // R_D)}{r_{o,M2}} \approx \frac{1}{g_{m,M2} - g_{mb,M2}} = 285$$

PMOS Example (Finding R_{out1})

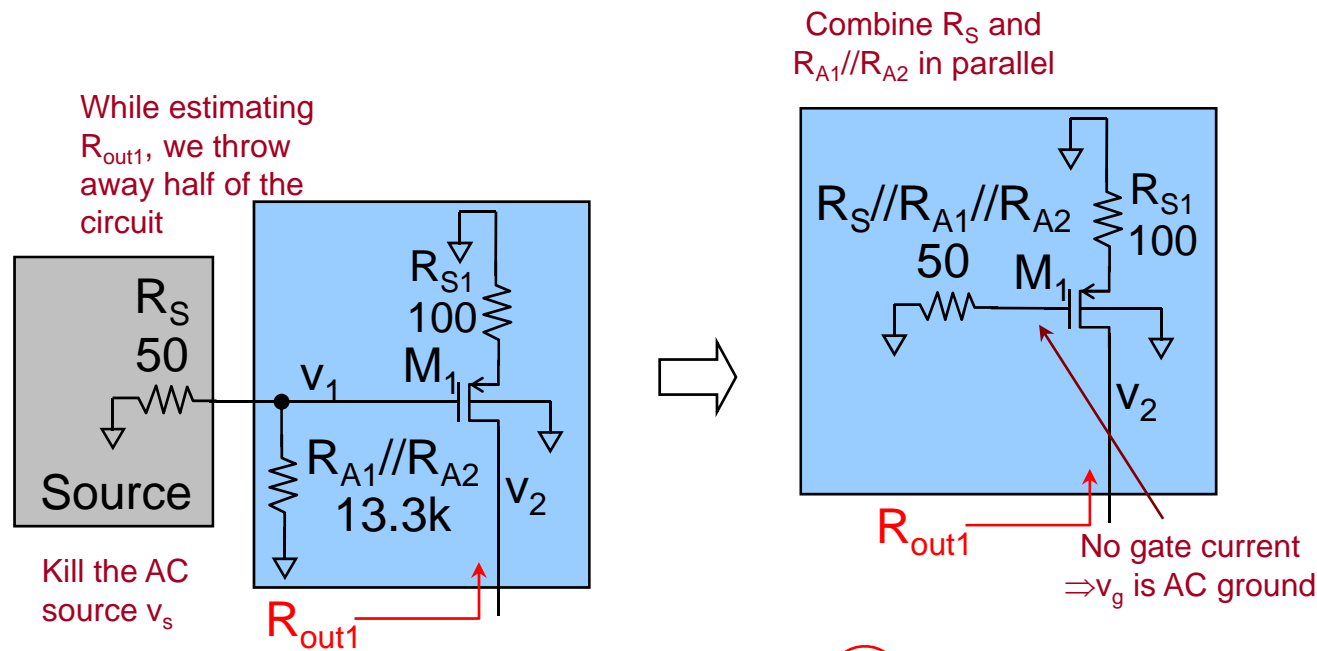


Configuration **(B)**

$$\Rightarrow R_{out1} = r_{o,M1} [1 + (g_{m,M1} - g_{mb,M1}) R_{S1}] = 135k$$

Table 2


PMOS Example (Finding R_{in1})

Table 2, Configuration A:
The resistance looking into the
gate of M_1 is ∞

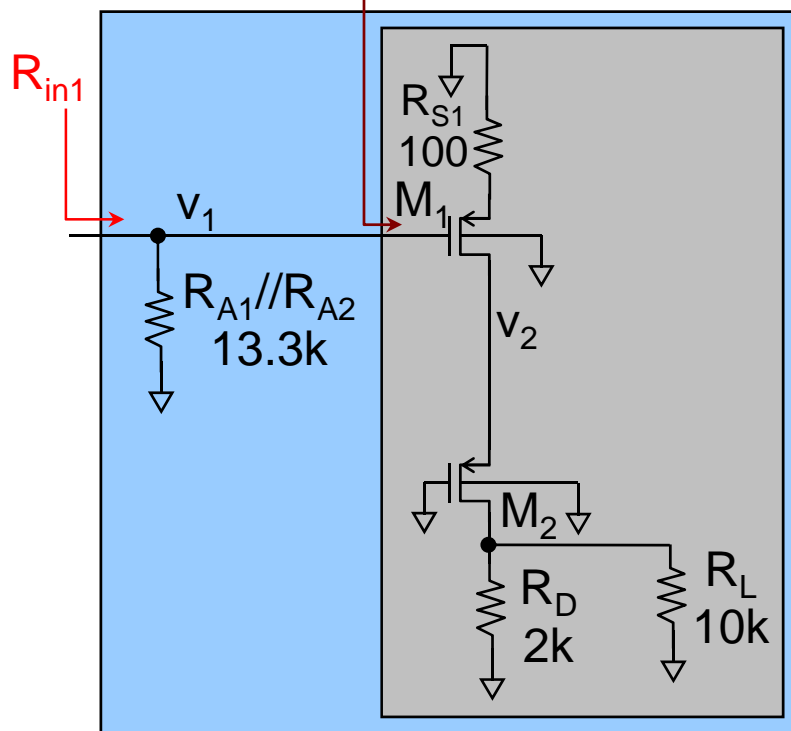


$$\begin{aligned} R_{in1} &= R_{A1} // R_{A2} \\ &= 13.3k \end{aligned}$$

PMOS Example (Finding R_{out2})

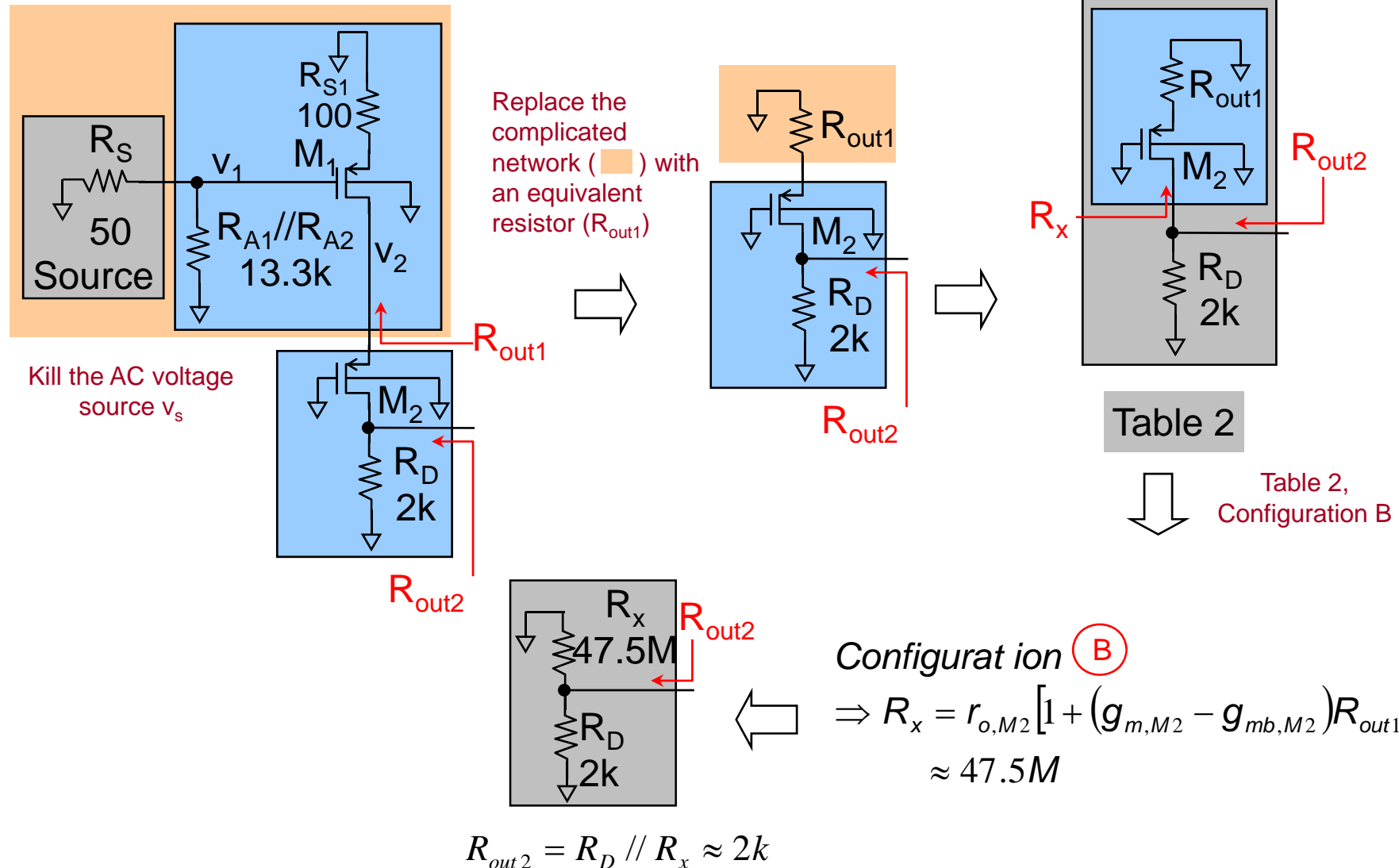

PMOS Example (2-Port)

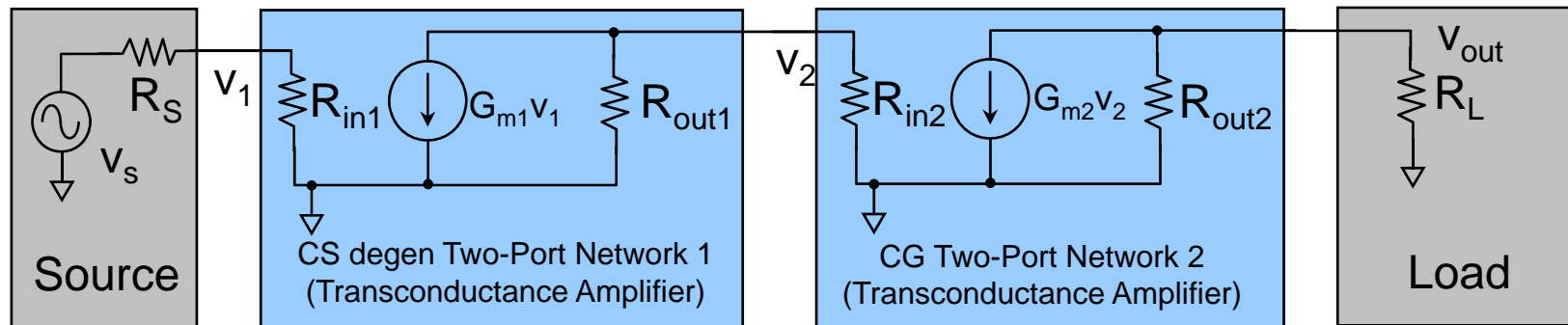


Replace each single stage amplifier with their two-port network equivalent

$$\begin{aligned}
 R_{in1} &= R_{A1} // R_{A2} \\
 &= 13.3k \\
 R_{out1} &= r_{o,M1} [1 + (g_{m,M1} - g_{mb,M1}) R_{S1}] \\
 &= 135k \\
 G_{m1} &= \frac{g_{m,M1}}{1 + (g_{m,M1} - g_{mb,M1}) R_{S1}} \\
 &= 2.08m
 \end{aligned}$$

$$\begin{aligned}
 R_{in2} &= \frac{1}{g_{m,M2} - g_{mb,M2}} \frac{r_{o,M2} + R_D // R_L}{r_{o,M2}} \\
 &\approx 285 \\
 R_{out2} &= R_D // \{ r_{o,M2} [1 + (g_{m,M2} - g_{mb,M2}) R_{out1}] \} \\
 &\approx 2k \\
 G_{m2} &= -(g_{m,M2} - g_{mb,M2}) \\
 &= -3.51m
 \end{aligned}$$

PMOS Example (2-Port)

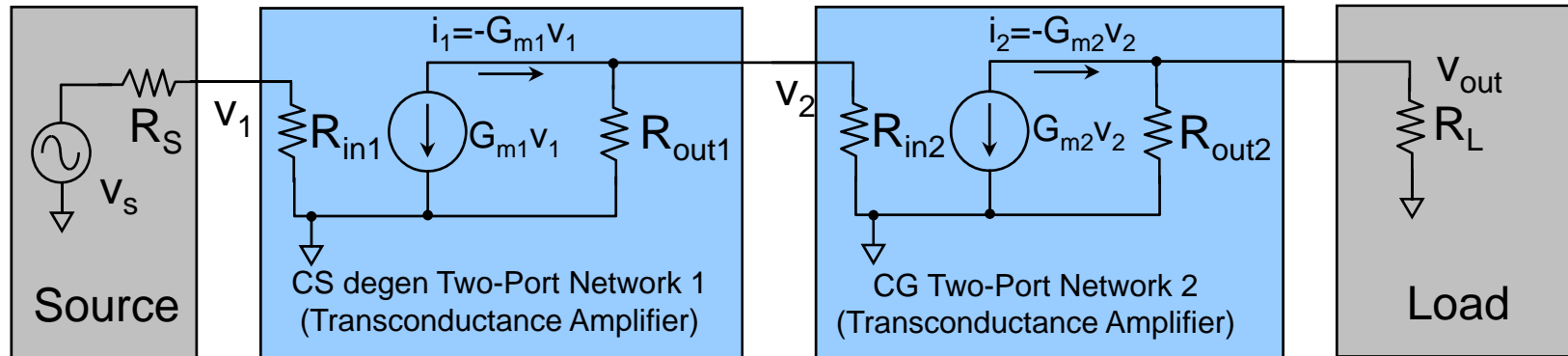


$$\begin{aligned}
 V_1 &= V_s \times \frac{R_{in1}}{R_{in1} + R_S} \\
 &\approx V_s \\
 V_2 &= i_1 \times (R_{out1} \parallel R_{in2}) \\
 &= -G_{m1} V_1 (R_{out1} \parallel R_{in2}) \\
 &\approx -0.59 V_1 \approx -0.59 V_s
 \end{aligned}$$

$$\begin{aligned}
 V_{out} &= i_2 \times (R_{out2} \parallel R_L) \\
 &= -G_{m2} V_2 (R_{out2} \parallel R_L) \\
 &\approx 5.86 V_2 \\
 &= -3.46 V_s
 \end{aligned}$$


$$A_V = \frac{V_{out}}{V_s} = -3.46$$

PMOS Example (2-Port)

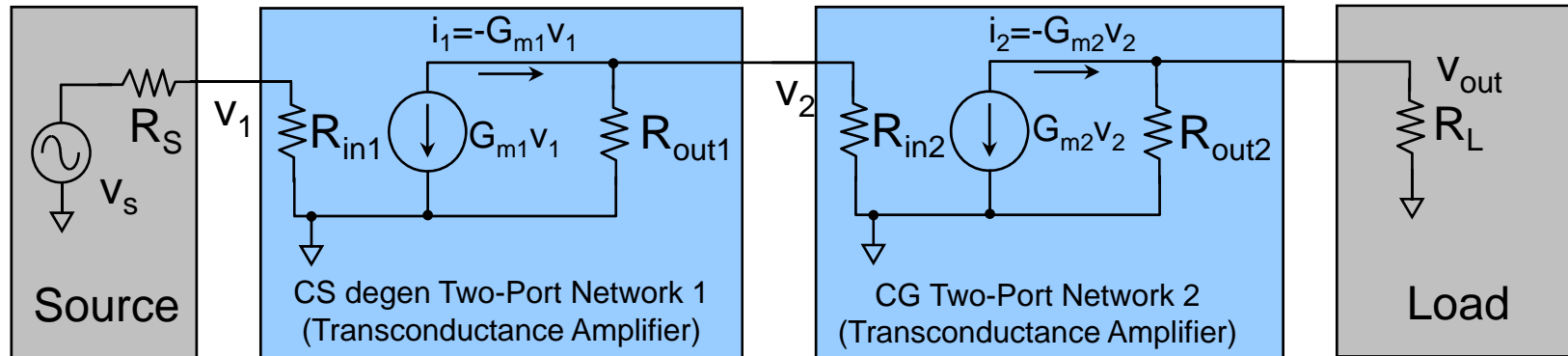

$$\begin{aligned}
 A_V &= \frac{V_{out}}{V_s} = \frac{V_1}{V_s} \times \frac{V_2}{V_1} \times \frac{V_{out}}{V_2} \\
 &= \underbrace{\frac{(R_{A1} // R_{A2})}{R_S + (R_{A1} // R_{A2})}}_{\text{Resistor Divider}} \times \underbrace{\left[-G_{m1} (R_{out1} // R_{in2}) \right]}_{\text{1st Stage CS with Degeneration}} \underbrace{\left[-G_{m2} (R_{out2} // R_L) \right]}_{\text{2nd Stage CG}} \\
 &= \underbrace{\frac{(R_{A1} // R_{A2})}{R_S + (R_{A1} // R_{A2})}}_{\text{Resistor Divider}} \times \underbrace{\frac{-g_{m,M1}}{1 + (g_{m,M1} - g_{mb,M1})R_{S1}}}_{\text{1st Stage CS with Degeneration}} \underbrace{\frac{1}{g_{m,M2} - g_{mb,M2}} (g_{m,M2} - g_{mb,M2})(R_D // R_L)}_{\text{2nd Stage CG}} \\
 &= -3.46
 \end{aligned}$$

BJT Example (DC Analysis)

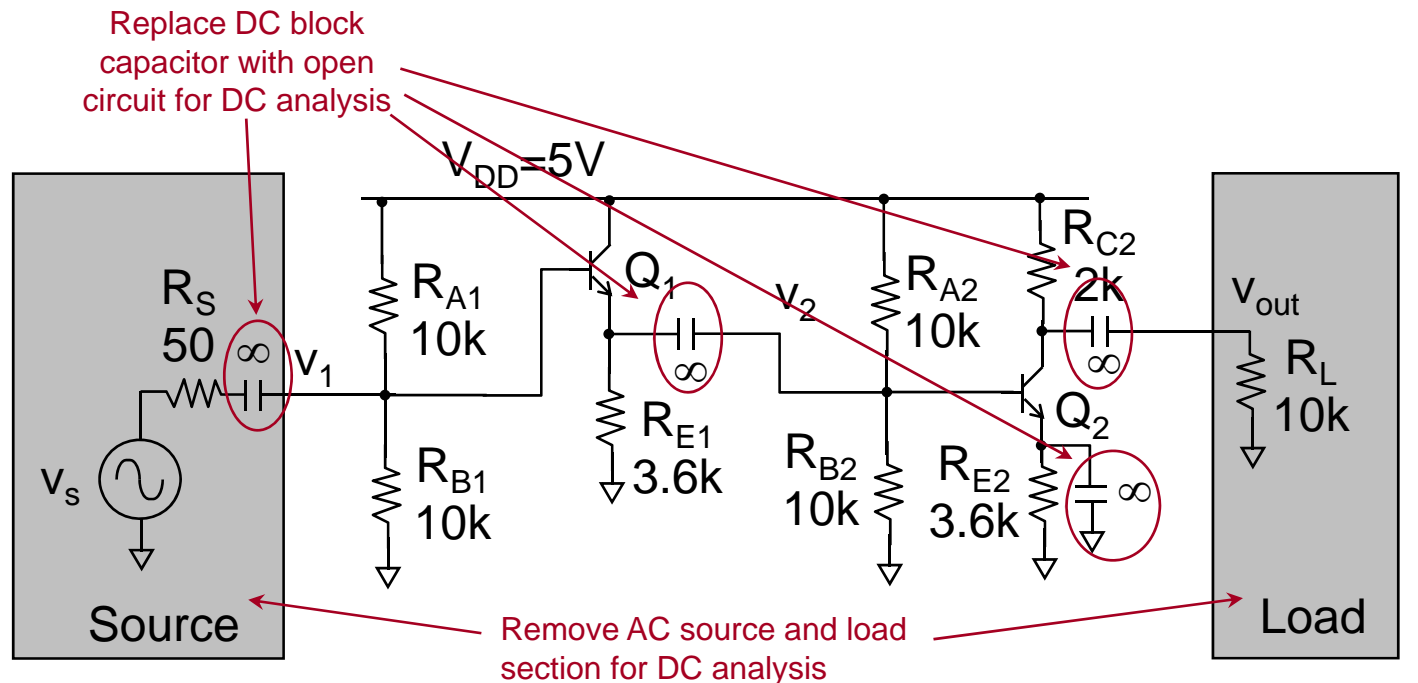


$V_{B,Q1}$ = Base voltage of Q_1
 $V_{E,Q1}$ = Emitter voltage of Q_1
 $V_{B,Q2}$ = Base voltage of Q_2
 $V_{C,Q2}$ = Collector voltage of Q_2

$I_S = 10^{-15} \text{ A}$
 $\beta = 100$
 $V_A = 100 \text{ V}$

- Identify Source and Load

BJT Example (DC Analysis)

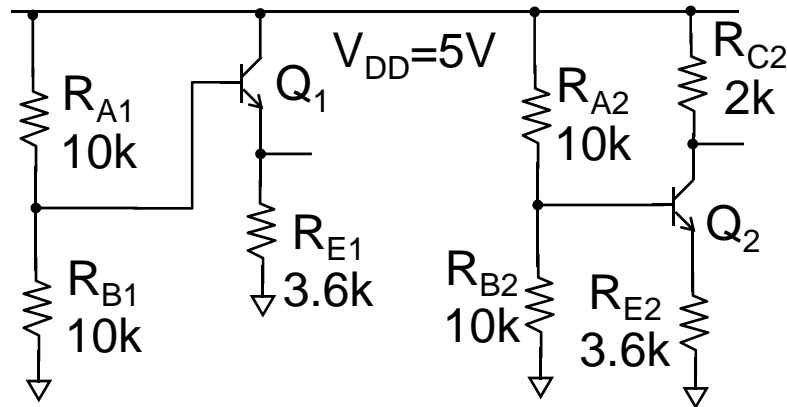

$$I_S = 10^{-15} \text{ A}$$

$$\beta = 100$$

$$V_A = 100 \text{ V}$$

The goal of DC analysis is to find the collector current flowing through Q_1 and Q_2 (I_{C1} , I_{C2}). To find the collector current, we can assume $V_{BE,Q1}$ and $V_{BE,Q2}$ equal to 0.7V, and obtain the current through KCL and KVL.

Never do the following:

~~$$\because V_{BE,Q1} = V_{BE,Q2} \approx 0.7$$

$$\Rightarrow I_{C1} \approx I_{C2} \approx I_S e^{\frac{V_{BE,Q1}}{V_T}}$$~~

Determine DC Biasing

$$V_{B,Q1} = \frac{R_{B1}}{R_{A1} + R_{B1}} \times V_{DD} = 2.5 \text{ V}$$

Simple resistor divider

$$V_{E,Q1} = V_{B,Q1} - 0.7 = 1.8 \text{ V}$$

Using the approximation $V_{BE,Q1} = 0.7 \text{ V}$

$$\Rightarrow I_{C,Q1} \approx I_{E,Q1} = \frac{V_{E,Q1}}{R_{E1}} = 500 \mu\text{A}$$

$$\Rightarrow I_{B,Q1} = \frac{I_{C,Q1}}{\beta} = 5 \mu\text{A}$$

$$V_{B,Q2} = \frac{R_{B2}}{R_{A2} + R_{B2}} \times V_{DD} = 2.5 \text{ V}$$

Simple resistor divider


$$V_{E,Q2} = V_{B,Q2} - 0.7 = 1.8 \text{ V}$$

Using the approximation $V_{BE,Q2} = 0.7 \text{ V}$

$$\Rightarrow I_{C,Q2} \approx I_{E,Q2} = \frac{V_{E,Q2}}{R_{E2}} = 500 \mu\text{A}$$

$$\Rightarrow I_{B,Q2} = \frac{I_{C,Q2}}{\beta} = 5 \mu\text{A}$$

BJT Example (Small Signal AC Equivalent)

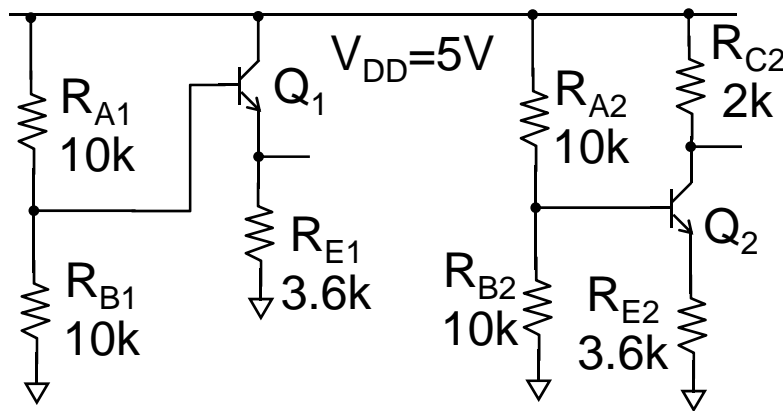

Determine AC small signal parameter

$$\because I_{C,Q1} = I_{C,Q2} = 500 \mu \text{ and } V_T = 25mV$$

$$\Rightarrow g_{m,Q1} = g_{m,Q2} = \frac{I_{C,Q1}}{V_T} = 20mA/V$$


$$\Rightarrow r_{\pi,Q1} = r_{\pi,Q2} = \frac{\beta}{g_{m,Q1}} = 5k$$

$$r_{o,Q1} = r_{o,Q2} = \frac{V_A}{I_{C,Q1}} \approx 200k$$


Notice that all AC small signal parameters depend on collector current

Find g_m , r_{π} and r_o

BJT Example (AC Analysis)

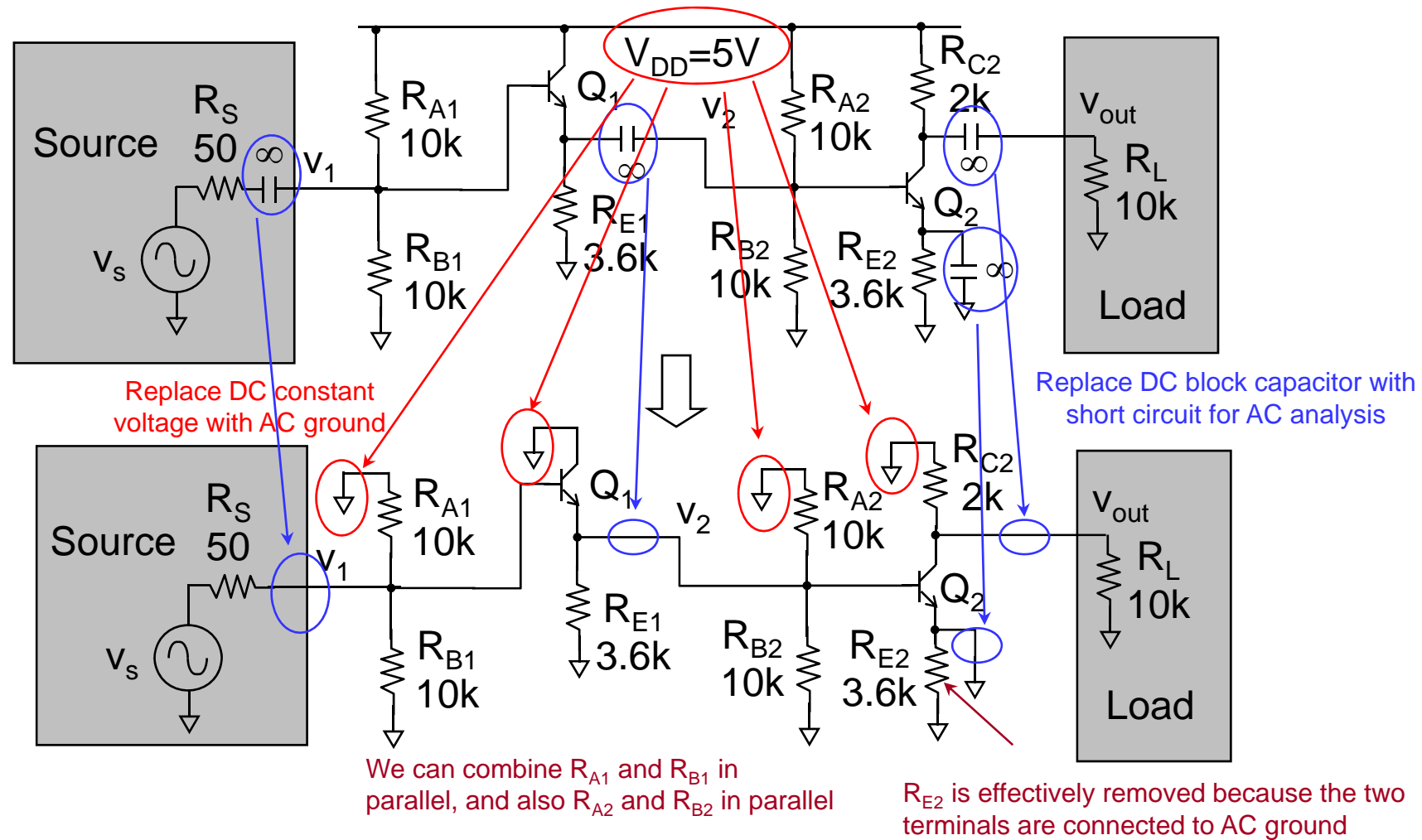


BJT Example (Identify Single Stage)

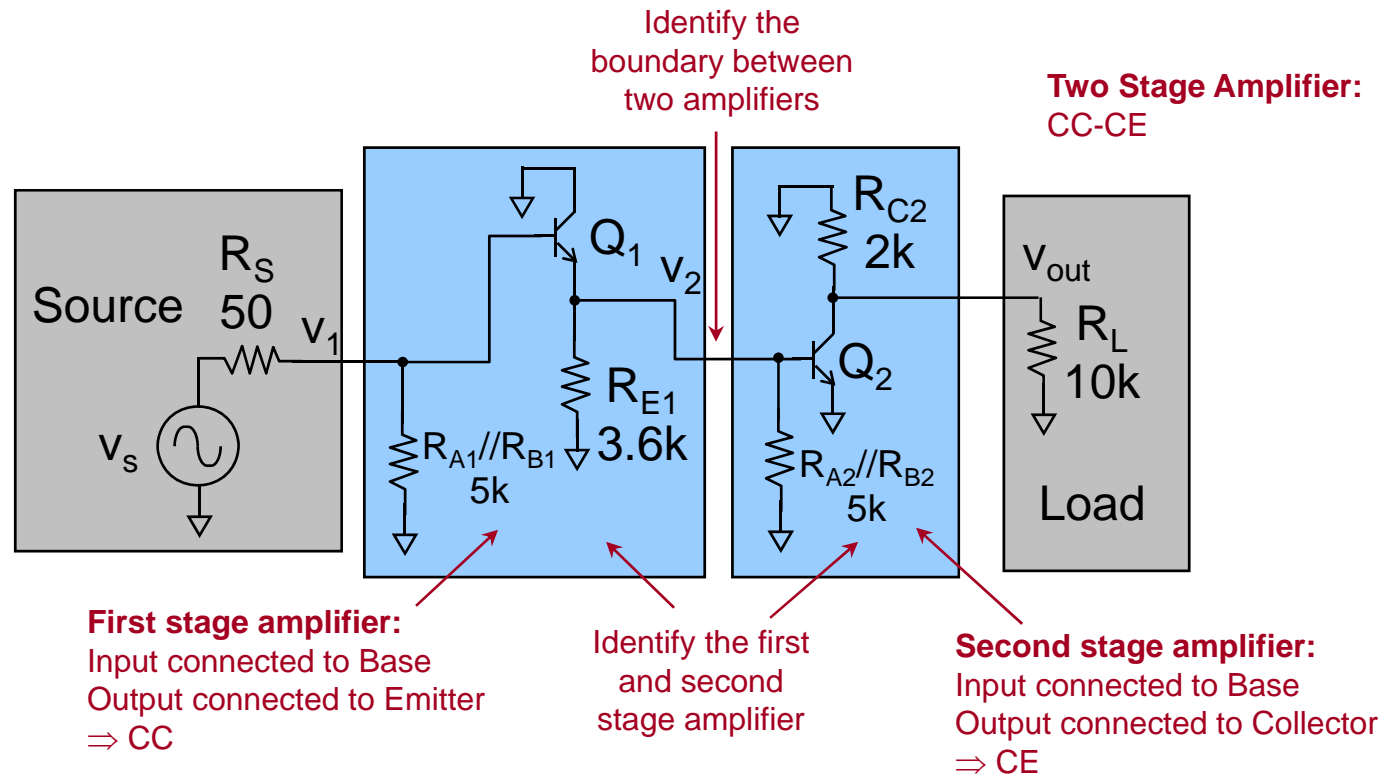

- Each single stage amplifier can be replaced with its two-port network equivalent consists of R_{in} , R_{out} and G_m


BJT Example (Identify 2-Port Parameters)

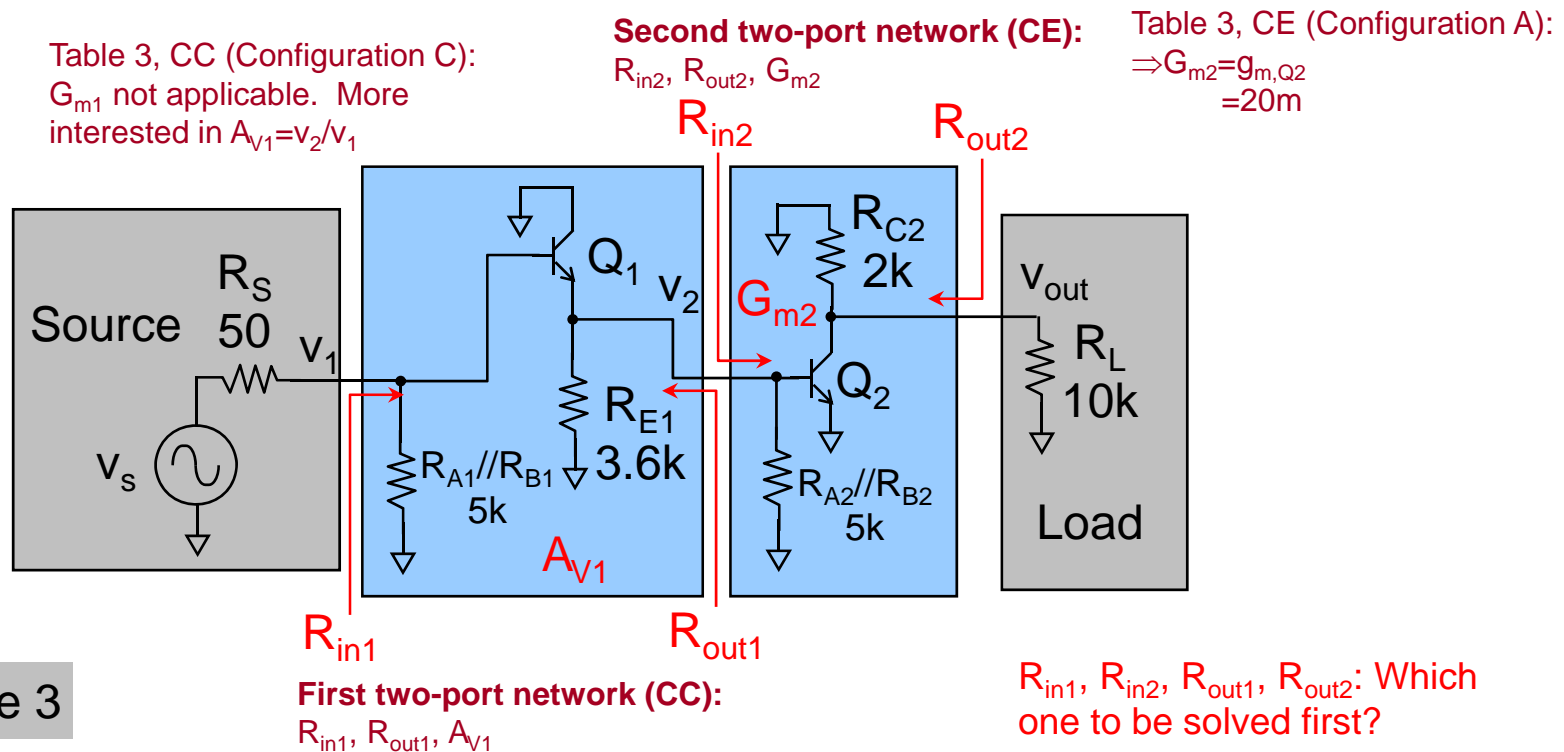

- Identify the 2-port network and the corresponding R_{in} , R_{out} , G_m , and A_V

BJT Example (Finding R_{in2})

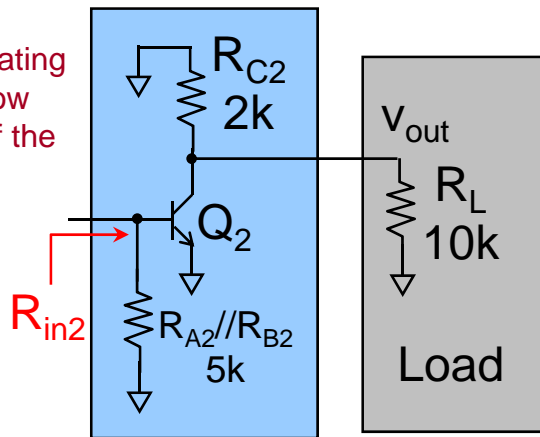While estimating R_{in2} , we throw away half of the circuit



Combine R_{C2} and R_L in parallel

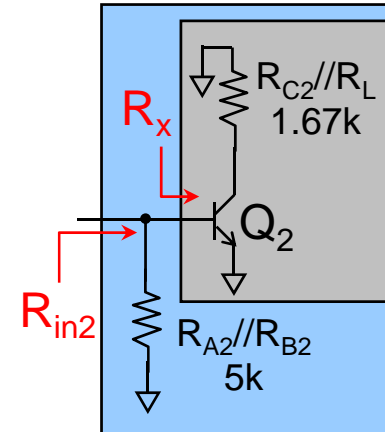



Table 1



Table 1,
Configuration A
with $R_E = 0$


Configuration **A**
 $\Rightarrow R_x = r_{\pi, Q2} = 5k$
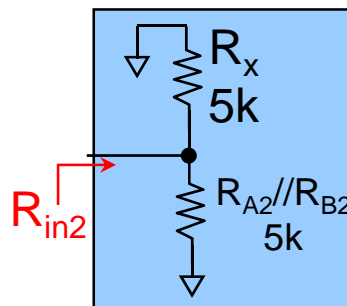
$$\begin{aligned} \Rightarrow R_{in2} &= R_{A2} // R_{B2} // R_x \\ &= R_{A2} // R_{B2} // r_{\pi, Q2} \\ &= 2.5k \end{aligned}$$



BJT Example (Finding R_{out1})

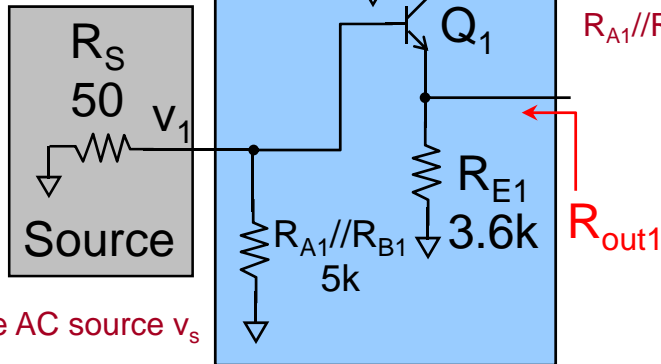While estimating R_{out1} , we throw away half of the circuit



Kill the AC source v_s

Combine R_S and $R_{A1} // R_{B1}$ in parallel

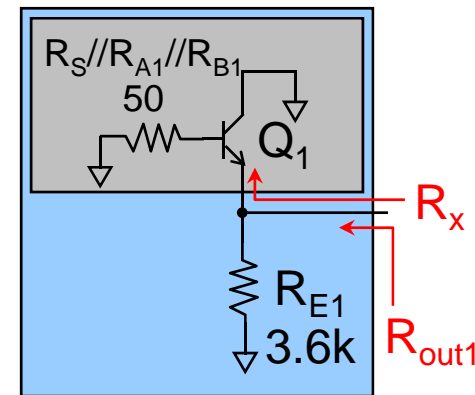



Table 1

Table 1, Configuration C


Configuration **C**

$$\Rightarrow R_x = \frac{R_S // R_{A1} // R_{B1}}{\beta + 1} + \frac{1}{g_{m,Q1}} \approx 50$$

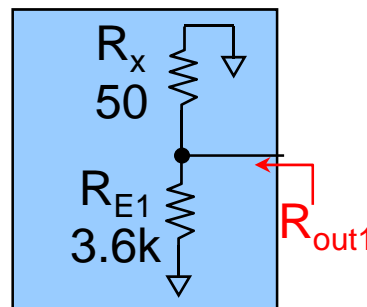
$$\Rightarrow R_{out1} = R_x // R_{E1} \approx 50$$




BJT Example (Finding R_{in1})

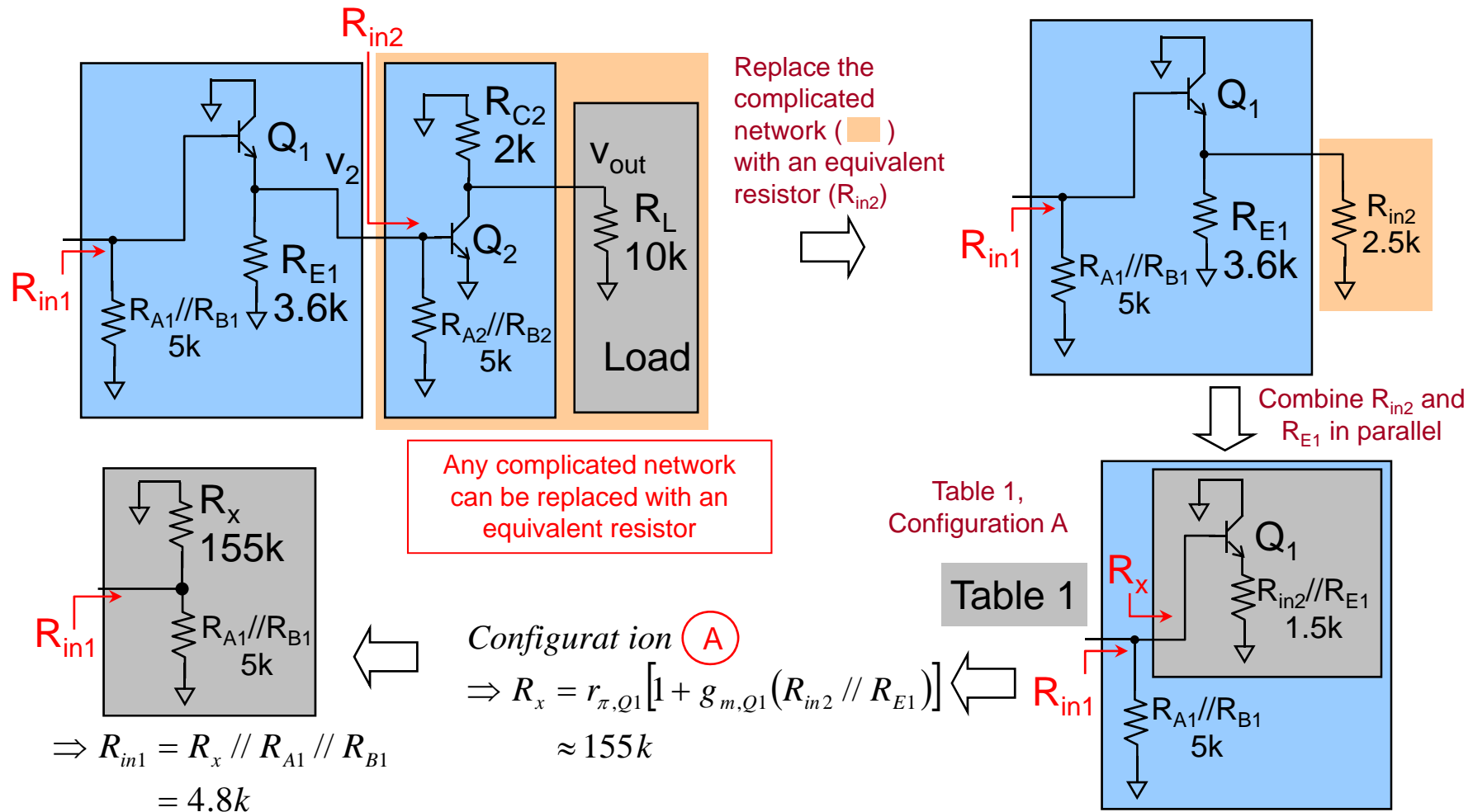


BJT Example (Finding R_{out2})

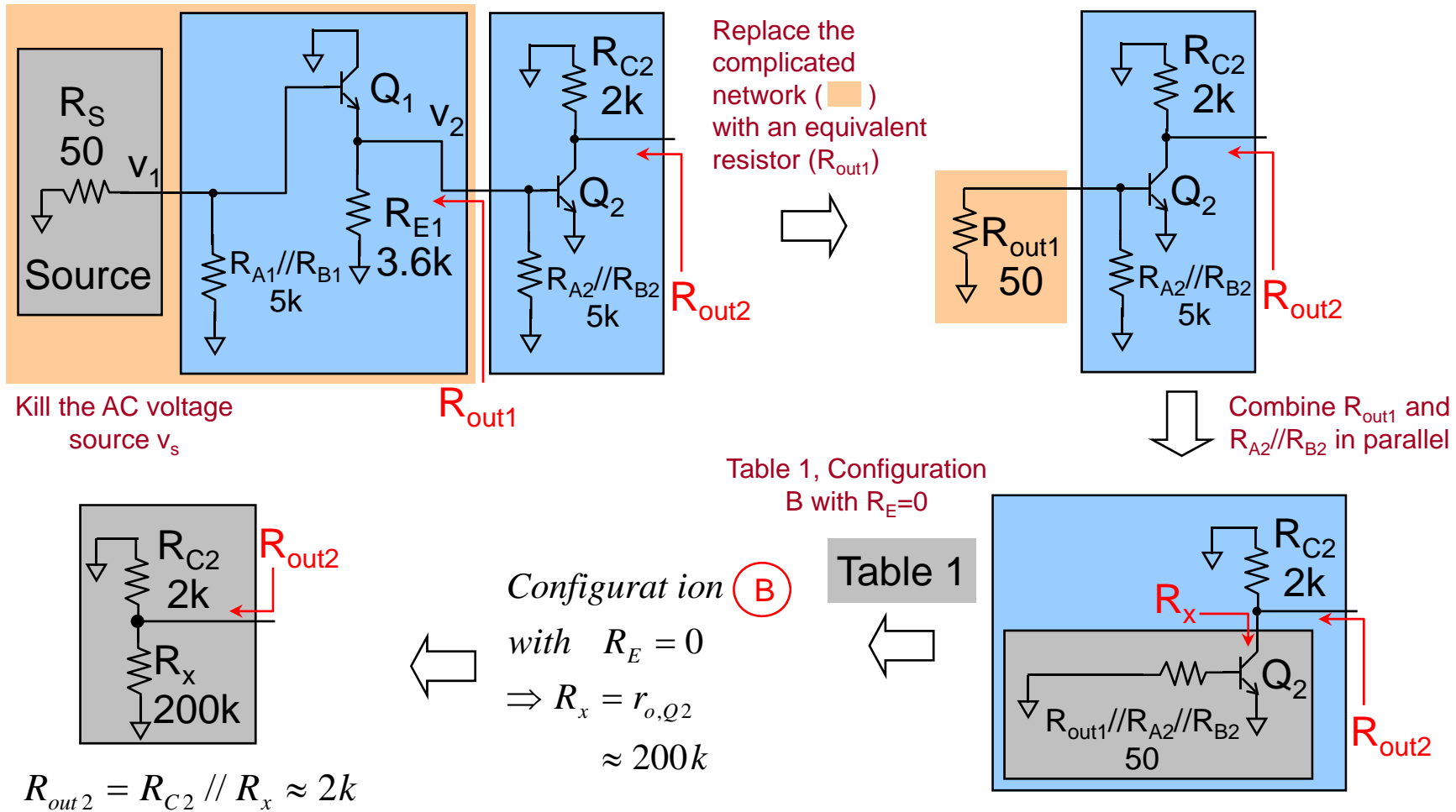

BJT Example (Finding $A_{V1} = v_2/v_1$)

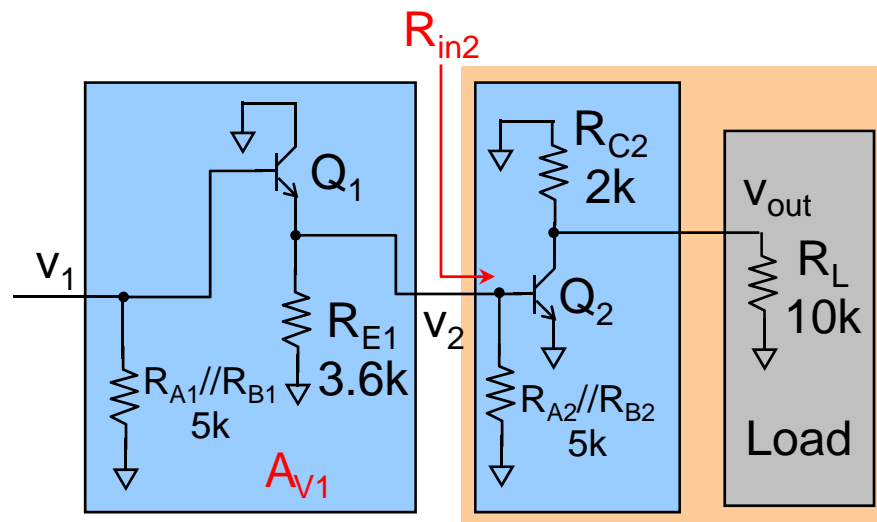

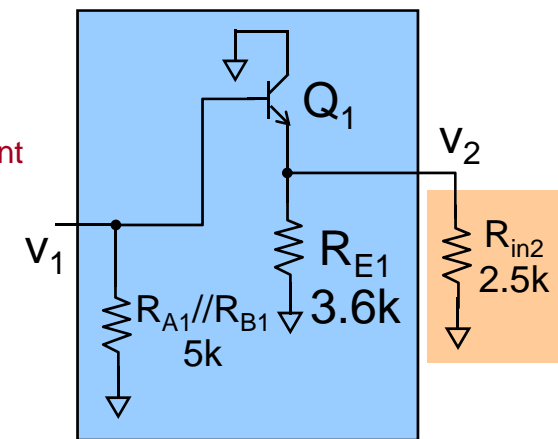Replace the complicated network (orange box) with an equivalent resistor (R_{in2})



Combine R_{in2} and R_{E1} in parallel

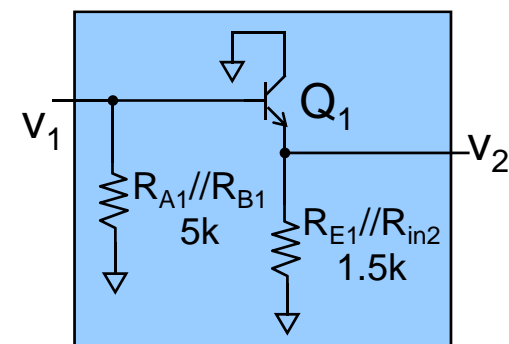


Table 3

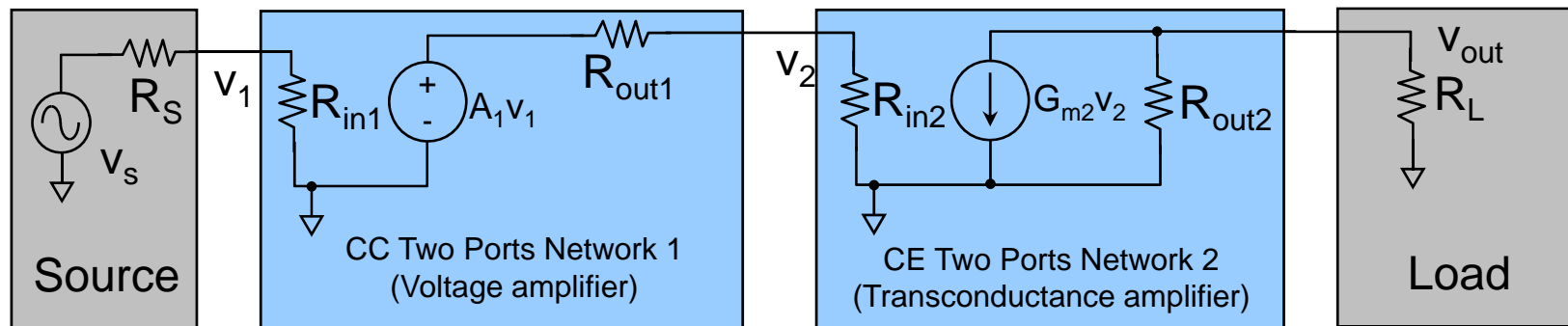


Table 3,
Configuration C

Configuration (C)

$$A_{V1} = \frac{v_2}{v_1} = \frac{g_{m,Q1}(R_{E1} // R_{in2})}{1 + g_{m,Q1}(R_{E1} // R_{in2})} \approx 1$$

BJT Example (2-Port)



Replace each single stage amplifier with their two-port network equivalent

$$R_{in1} = R_{A1} // R_{B1} // \{r_{\pi,Q1} [1 + g_{m,Q1} (R_{E1} // R_{in2})]\}$$

$$= 4.8k$$

$$R_{out1} = R_{E1} // \left[\frac{R_s // R_{A1} // R_{B1}}{\beta + 1} + \frac{1}{g_{m,Q1}} \right]$$

$$= 50$$

$$A_{v1} = \frac{v_2}{v_1} = \frac{g_{m,Q1} (R_{E1} // R_{in2})}{1 + g_{m,Q1} (R_{E1} // R_{in2})}$$

$$\approx 1$$

$$R_{in2} = R_{A2} // R_{B2} // r_{\pi,Q2}$$

$$= 2.5k$$


$$R_{out2} = R_{C2} // r_{o,Q2}$$

$$\approx 2k$$

$$G_{m2} = g_{m,Q2}$$

$$= 20m$$

BJT Example (2-Port)

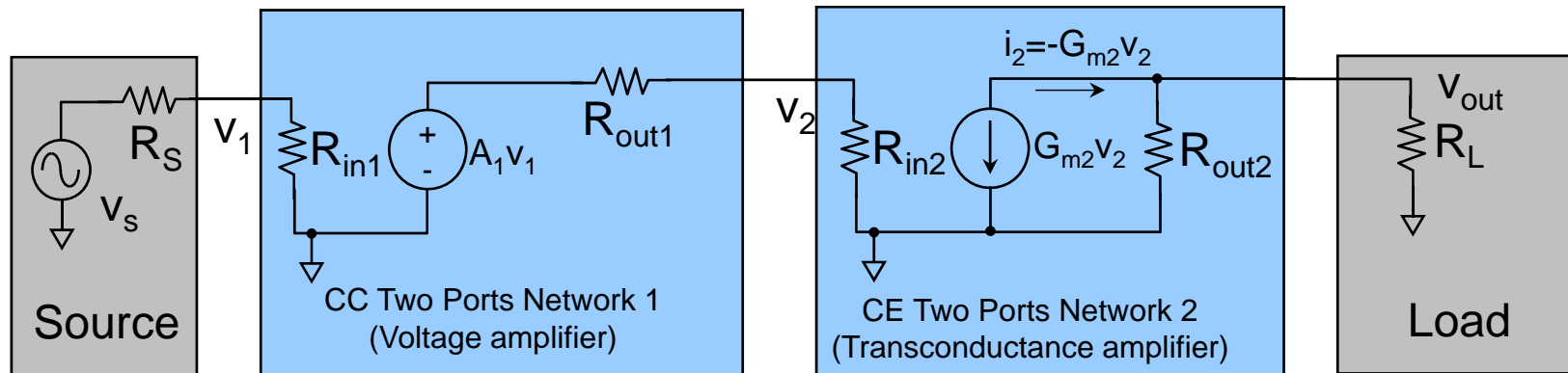

$$v_1 = v_s \times \frac{R_{in1}}{R_{in1} + R_s}$$

$$\approx v_s$$

$$v_2 = v_1 \times \frac{g_{m,Q1}(R_{E1} // R_{in2})}{1 + g_{m,Q1}(R_{E1} // R_{in2})}$$

$$\approx v_1$$

$$v_{out} = i_2 \times (R_{out2} // R_L)$$


$$= -G_{m2} v_2 (R_{out2} // R_L)$$

$$\approx -33 v_2$$

$$= -33 v_s$$


$$A_V = \frac{v_{out}}{v_s} = -33$$

BJT Example (2-Port)

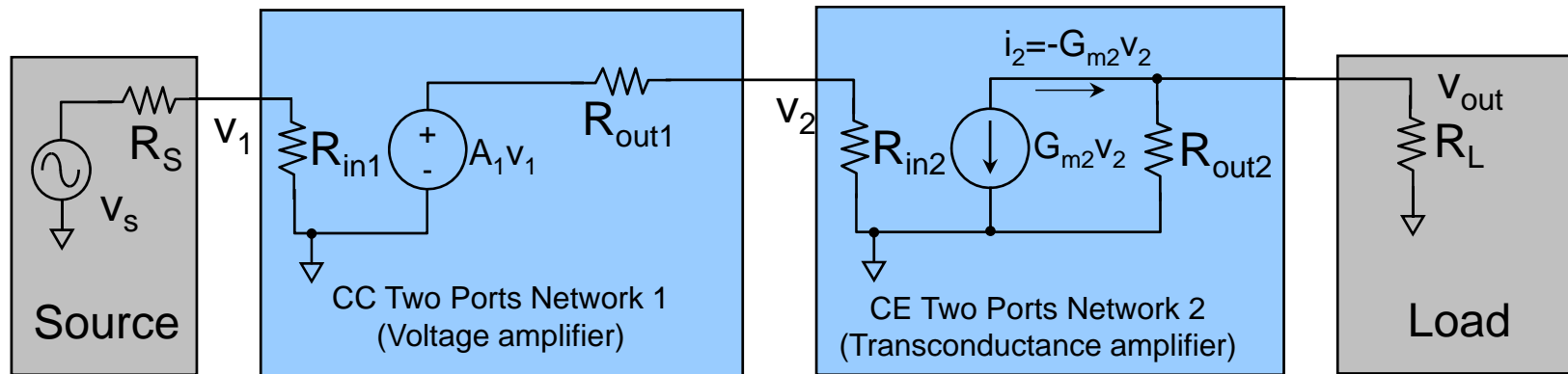


$$\begin{aligned}
 A_V &= \frac{V_{out}}{V_s} = \frac{V_1}{V_s} \times \frac{V_2}{V_1} \times \frac{V_{out}}{V_2} \\
 &= \underbrace{\frac{R_{in1}}{R_S + R_{in1}}}_{\text{Resistor Divider}} \underbrace{A_{V1}}_{\text{1st Stage CC}} \underbrace{\left[-G_{m2} (R_{out2} \parallel R_L) \right]}_{\text{2nd Stage CE}} \\
 &= \underbrace{\frac{R_{in1}}{R_S + R_{in1}}}_{\text{Resistor Divider}} \underbrace{\frac{g_{m,Q1} (R_{E1} \parallel R_{in2})}{1 + g_{m,Q1} (R_{E1} \parallel R_{in2})}}_{\text{1st Stage CC}} \underbrace{\left(-g_{m,Q2} \right) (R_{C2} \parallel r_{o,Q2} \parallel R_L)}_{\text{2nd Stage CE}} \\
 &= -33.33
 \end{aligned}$$

Current Source

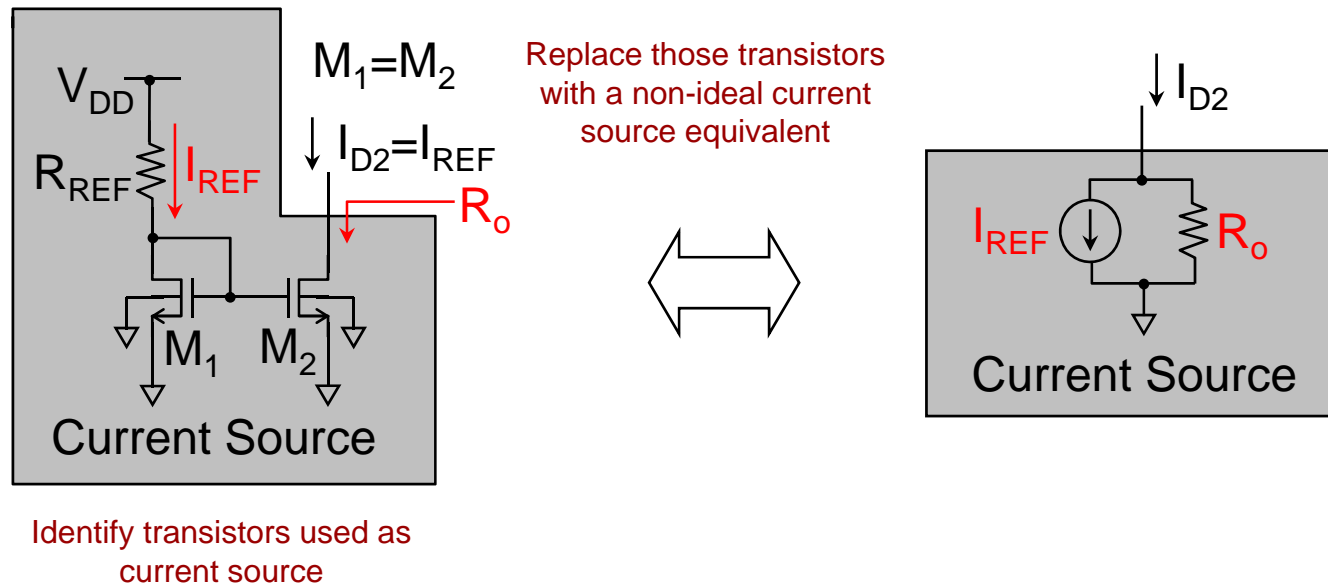


- Not all transistors are amplifiers
- Some transistors are used as non-ideal current source

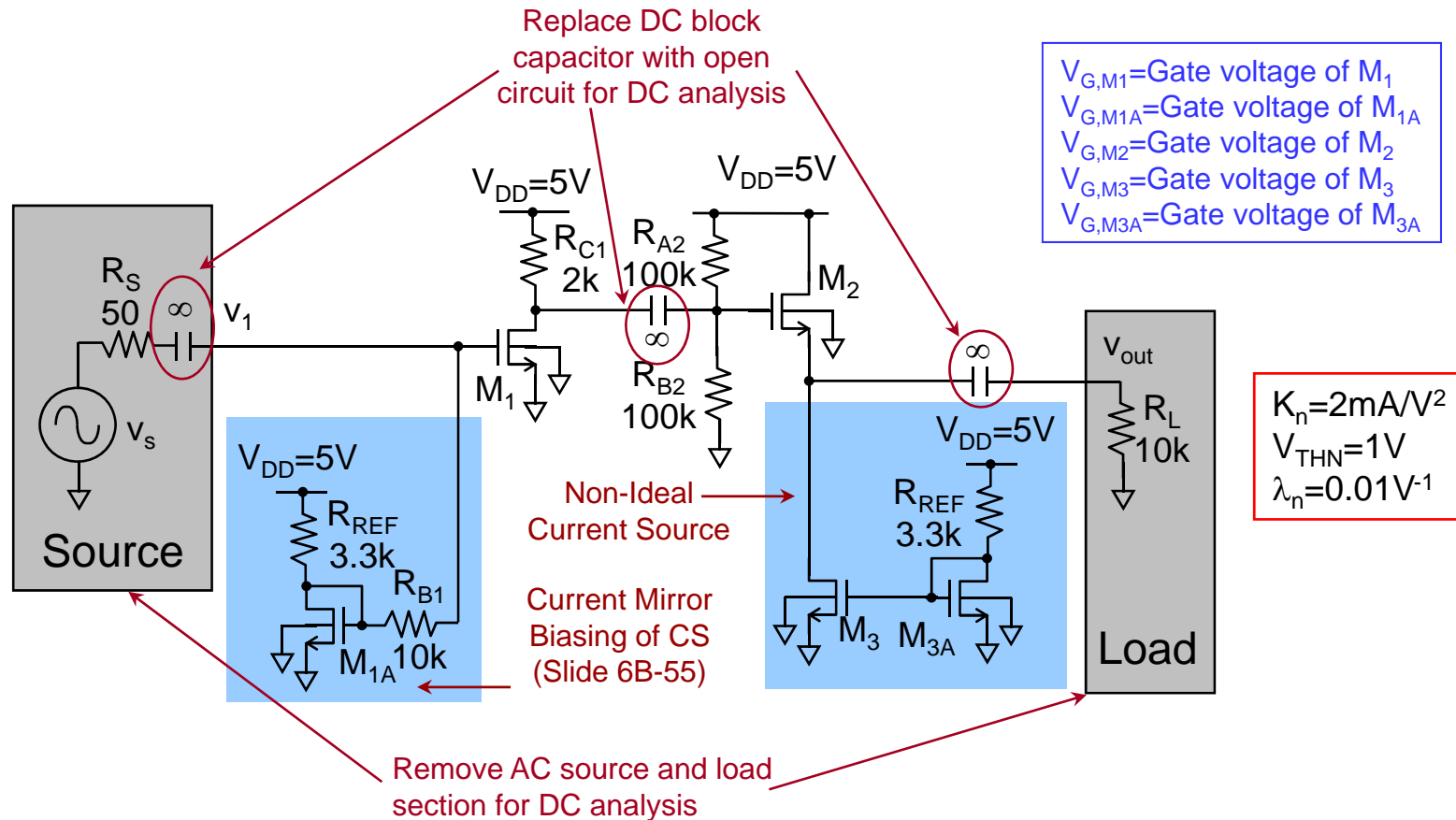Two Stage Amplifier Example (DC Analysis)



- Identify Source and Load

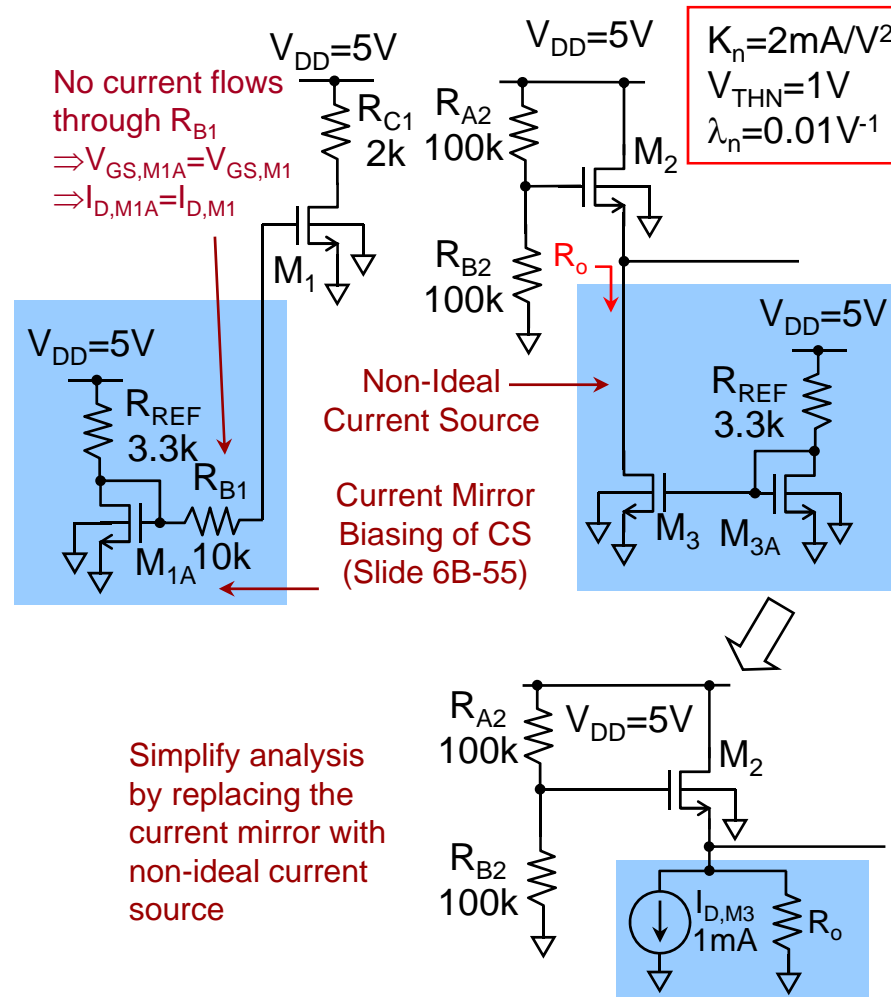Two Stage Amplifier Example (Current Mirror Biasing)



Determine DC Biasing

$$I_{D,M1A} = K_n (V_{GS,M1A} - V_{THN})^2 \dots\dots (1)$$

$$I_{D,M1A} = \frac{V_{DD} - V_{GS,M1A}}{R_{REF}} \dots\dots (2)$$

$$\Rightarrow 6.6V_{GS,M1A}^2 - 13.2V_{GS,M1A} + 6.6 = 5 - V_{GS,M1A}$$

$$\Rightarrow 6.6V_{GS,M1A}^2 - 12.2V_{GS,M1A} + 1.6 = 0$$

$$\Rightarrow V_{GS,M1A} = \frac{-(-12.2) \pm \sqrt{(12.2)^2 - 4(6.6)(1.6)}}{2(6.6)}$$

$$= 1.71 \text{ or } 0.142$$

$$\because V_{GS,M1A} = 0.142 \Rightarrow M_{1A} \text{ turns off}$$


$$\Rightarrow V_{GS,M1A} = 1.71$$

$$\Rightarrow I_{D,M1A} = I_{D,M1} = 1mA$$

Similarly

$$I_{D,M2} = I_{D,M3} = I_{D,M3A} = 1mA$$

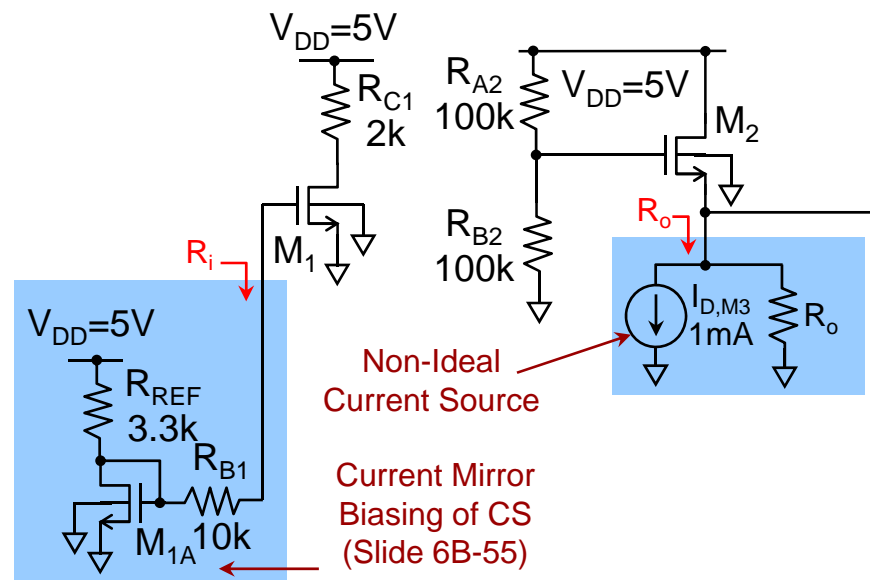Two Stage Amplifier Example (Small Signal AC Equivalent)



Notice that all AC small signal parameters depend on drain current

Find g_m , r_π and r_o

Determine AC small signal parameters

$$\because I_{D,M1A} = I_{D,M1} = I_{D,M2} = 1mA$$

$$\Rightarrow g_{m,M1A} = g_{m,M1} = g_{m,M2} = \sqrt{4K_n I_{D,M1A}} = 2.83mA/V$$

$$\Rightarrow g_{mb,M1A} = g_{mb,M1} = 0$$

$$\Rightarrow g_{mb,M2} = -\frac{g_{m,M1A}}{4} = -0.71m$$

$$r_{o,M1} = r_{o,M2} = \frac{1}{\lambda_n I_{D,M1}} \approx 100k$$


$$R_o = r_{o,M3} = \frac{1}{\lambda_n I_{D,M3}} \approx 100k$$

Table 2,
Configuration B


$$R_i = R_{B1} + \left(R_{REF} // \frac{1}{g_{m,M1A}} \right) = 10.3k$$

Slide
6B-55

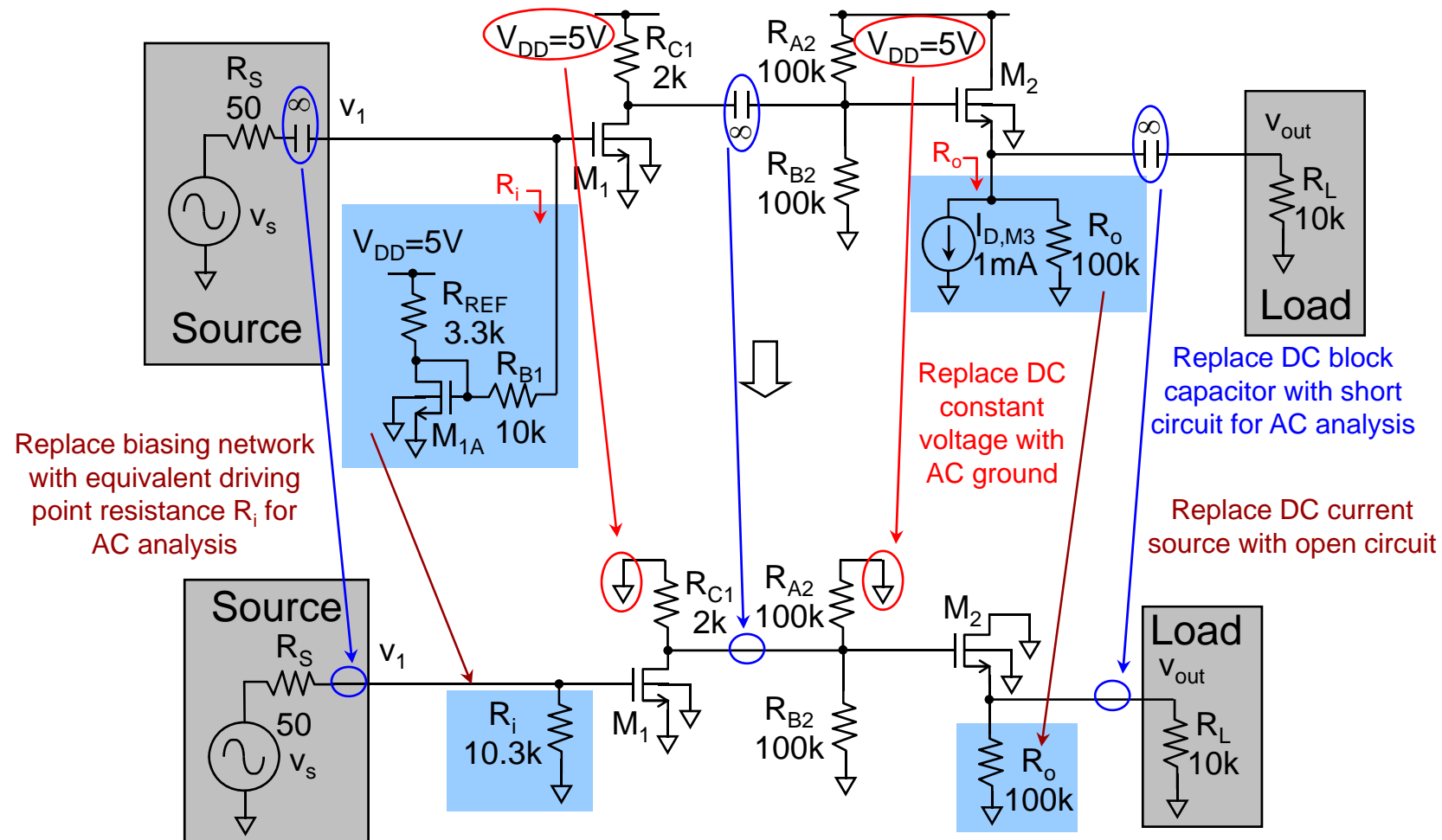Two Stage Amplifier Example (AC Analysis)




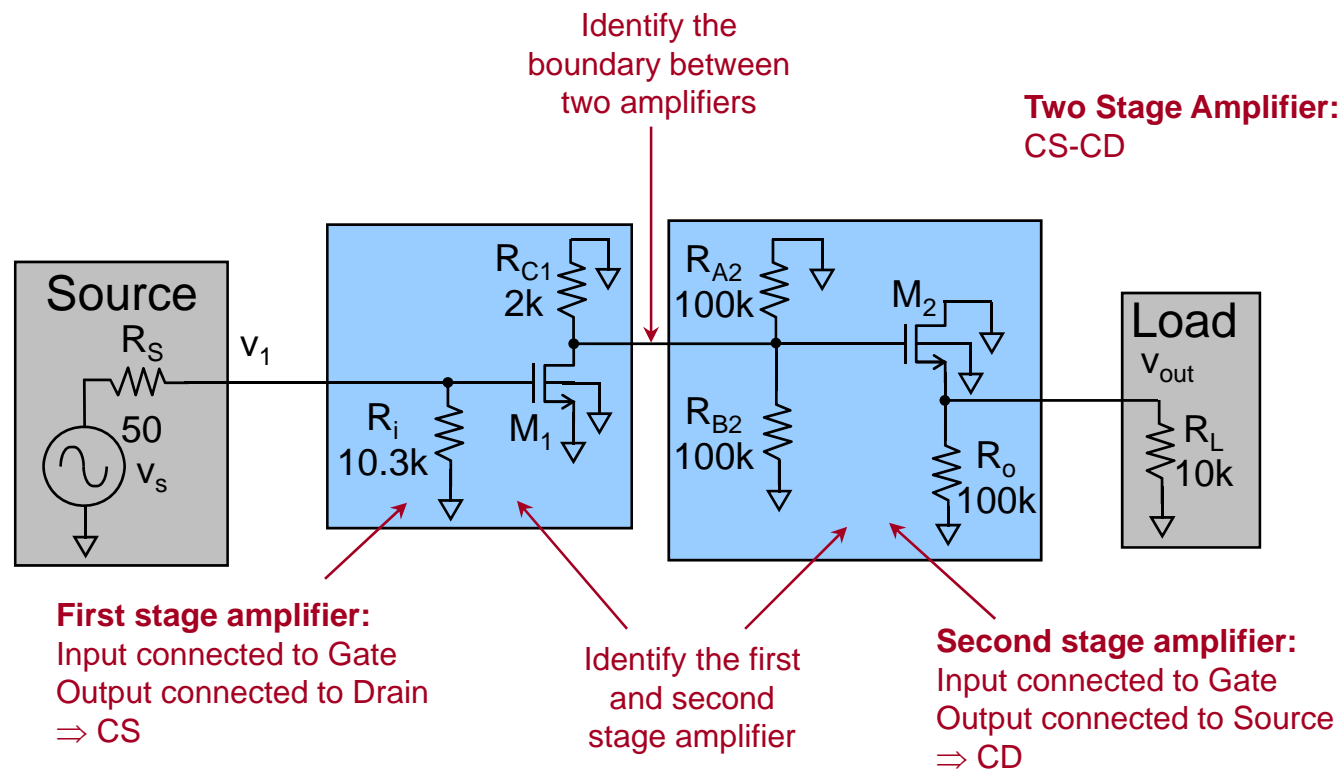Two Stage Amplifier Example (Identify Single Stage)



- Each single stage amplifier can be replaced with its two-port network equivalent consists of R_{in} , R_{out} and G_m

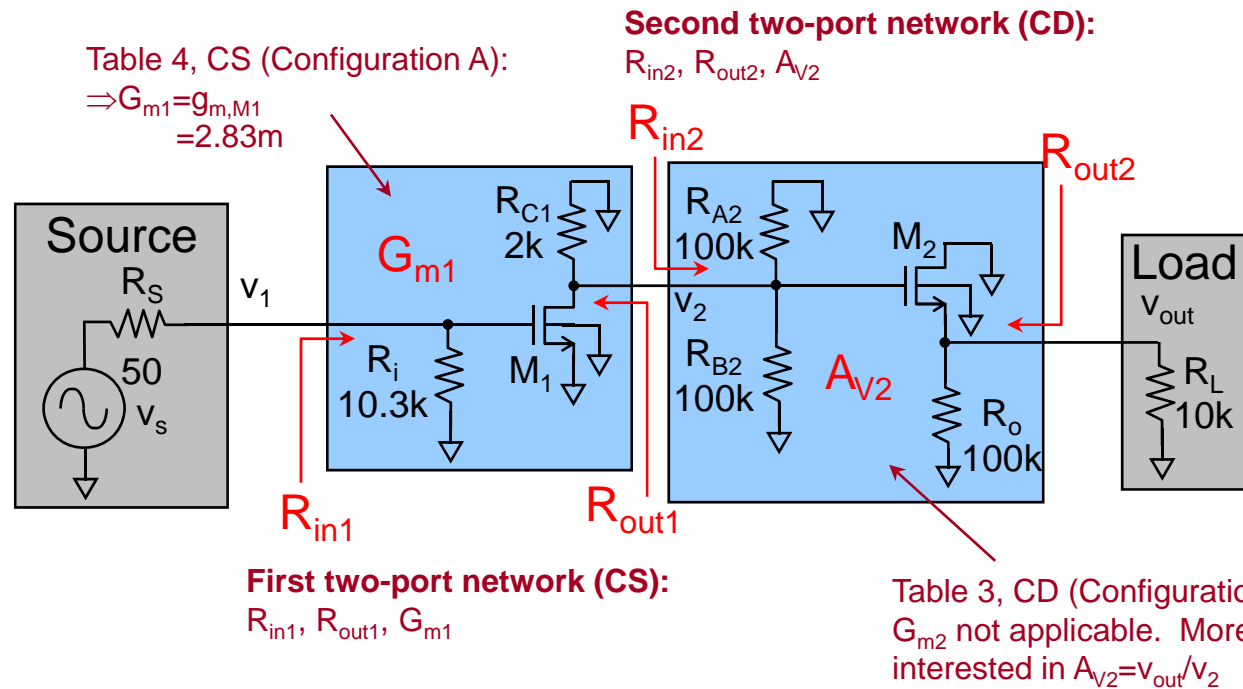Two Stage Amplifier Example (Identify 2-Port Parameters)





$R_{in1}, R_{in2}, R_{out1}, R_{out2}$: Which one to be solve first?

Table 4


- Identify the 2-port network and the corresponding R_{in} , R_{out} , G_m , and A_v

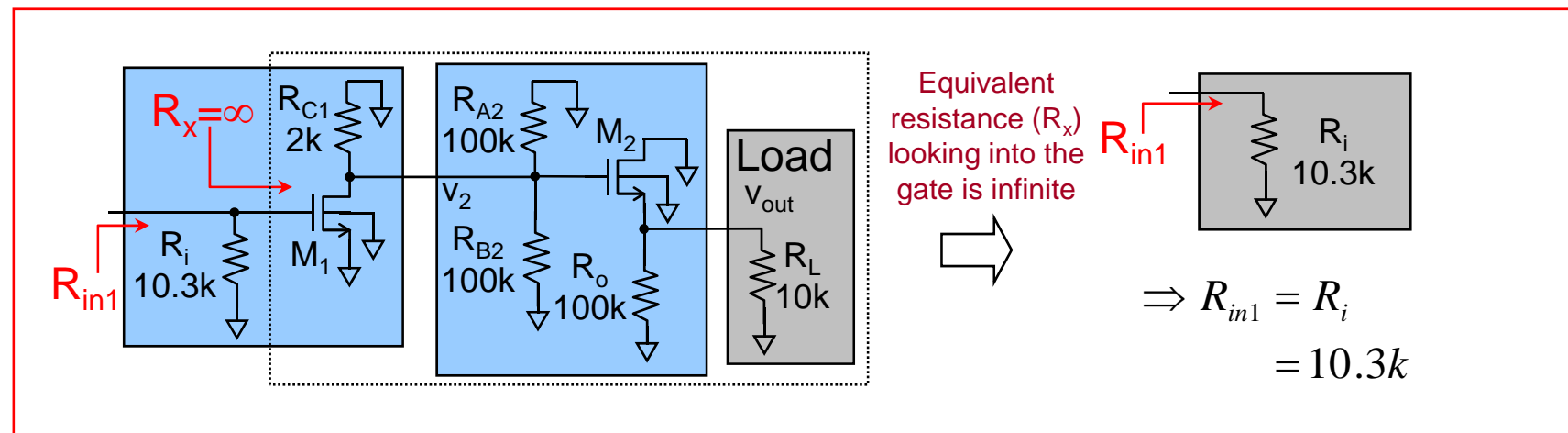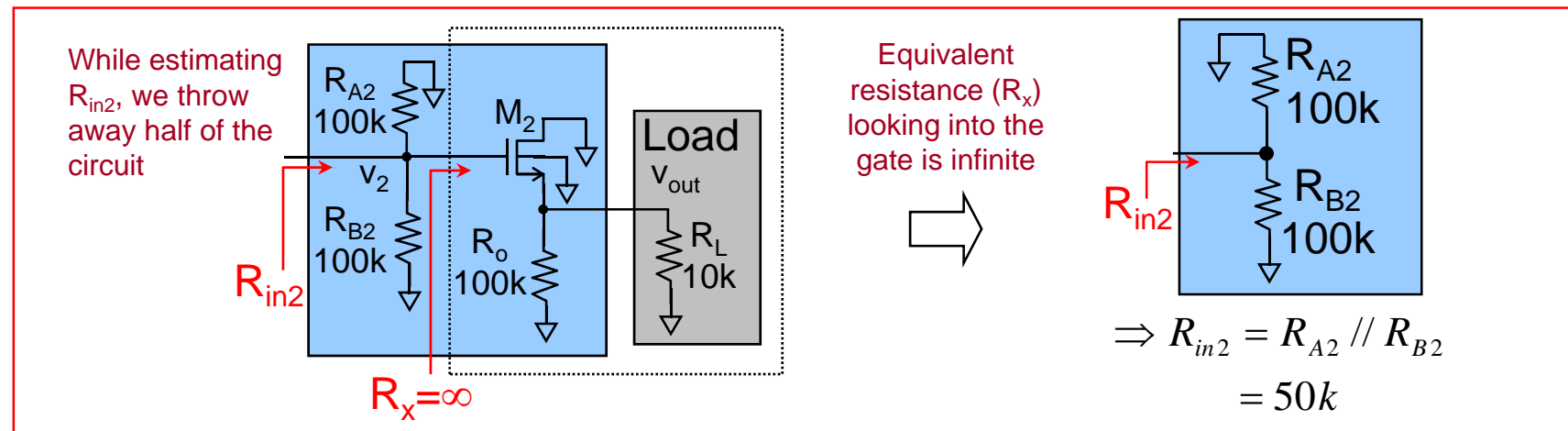Two Stage Amplifier Example (Finding R_{in2} and R_{in1})



Two Stage Amplifier Example (Finding R_{out1})

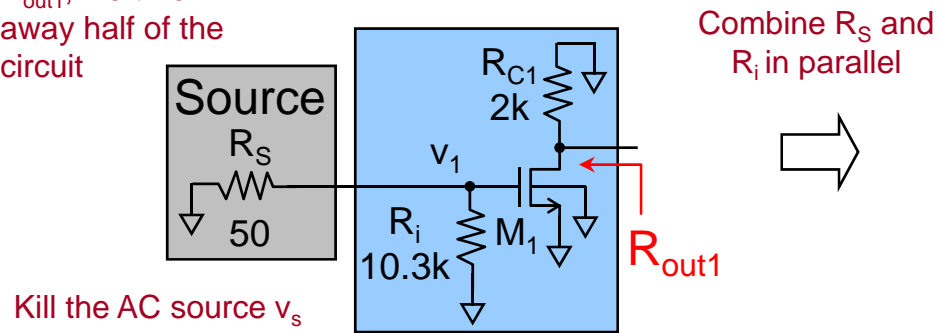While estimating R_{out1} , we throw away half of the circuit



No current flows through the gate
 $\Rightarrow v_1 = 0$


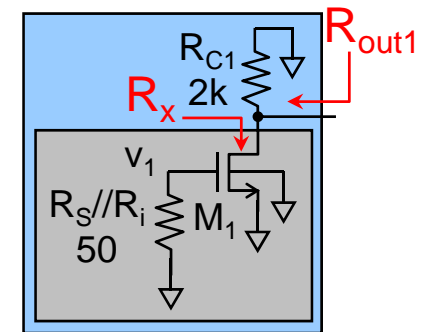


Table 2

Table 2,
Configuration B
with $R_E = 0$

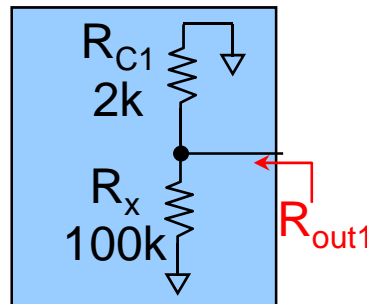
$$\Rightarrow R_{out1} = R_x // R_{C1} \approx 2k$$



Configuration **(B)**


$$\Rightarrow R_x = r_{o,M1} = 100k$$

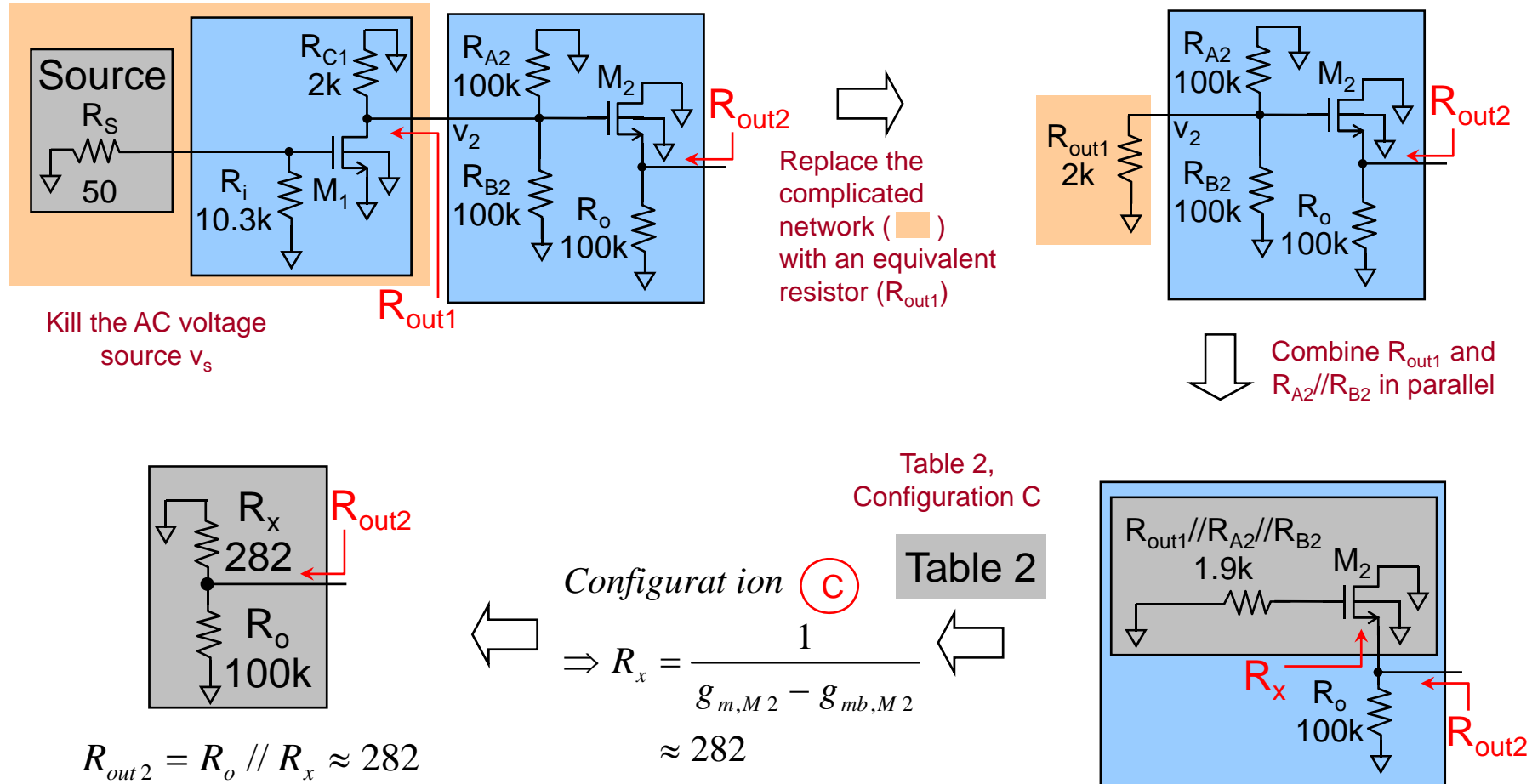Two Stage Amplifier Example (Finding R_{out2})



Two Stage Amplifier Example

(Finding $A_{V2} = v_{out}/v_2$)

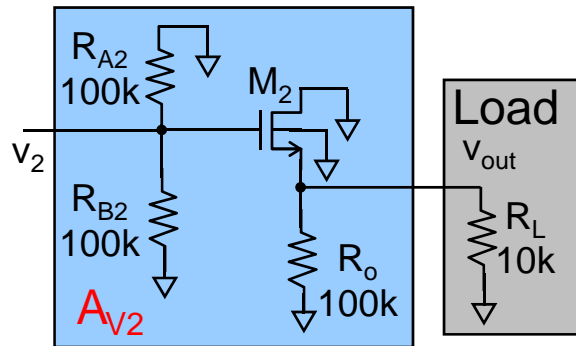

Combine R_L and R_o in parallel



Combine R_{A2} and R_{B2} in parallel

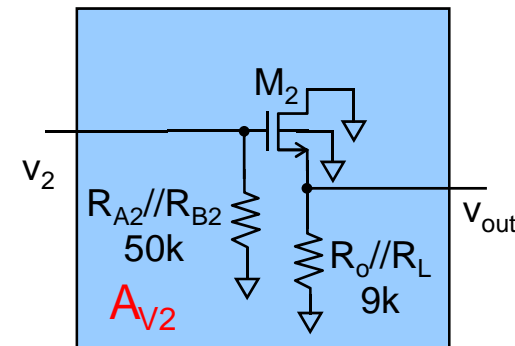


Table 4

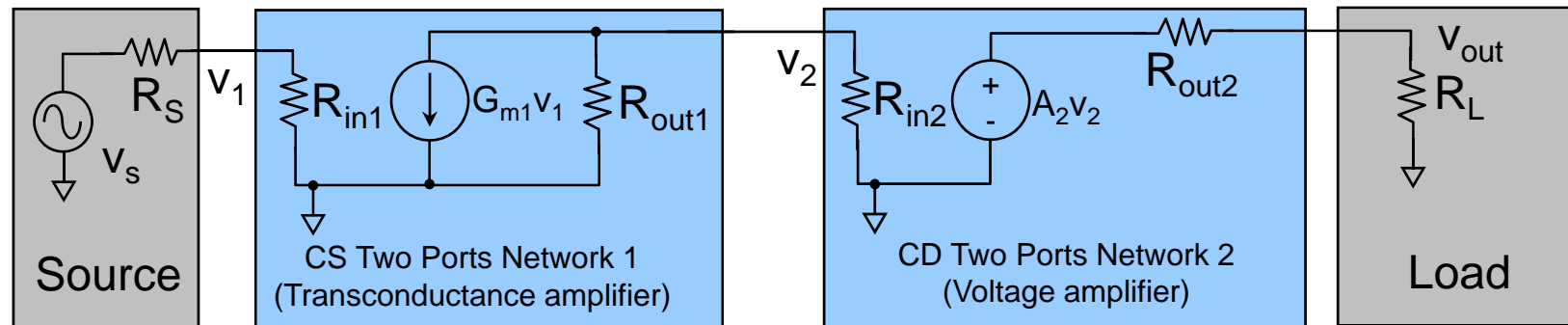


Table 3,
Configuration C

Configuration **C**

$$A_{V2} = \frac{v_{out}}{v_2} = \frac{g_{m,M2}(R_o // R_L)}{1 + (g_{m,M2} - g_{mb,M2})(R_o // R_L)} \approx 0.78$$

Two Stage Amplifier Example (2-Port)



Replace each single stage amplifier with their two-port network equivalent

$$R_{in1} = R_i = R_{B1} + \left(R_{REF} // \frac{1}{g_{m,M1A}} \right)$$

$$= 10.3k$$

$$R_{out1} = R_{C1} // r_{o,M1}$$

$$\approx 2k$$

$$G_{m1} = g_{m,M1}$$

$$= 2.83mA/V$$

$$R_{in2} = R_{A2} // R_{B2}$$

$$= 50k$$

$$R_{out2} = \frac{1}{g_{m,M2} - g_{mb,M2}} // R_o$$


$$\approx 282$$

$$A_{V2} = \frac{v_{out}}{v_2} = \frac{g_{m,M2}(R_o // R_L)}{1 + (g_{m,M2} - g_{mb,M2})(R_o // R_L)}$$

$$= 0.78$$

Two Stage Amplifier

Example (2-Port)

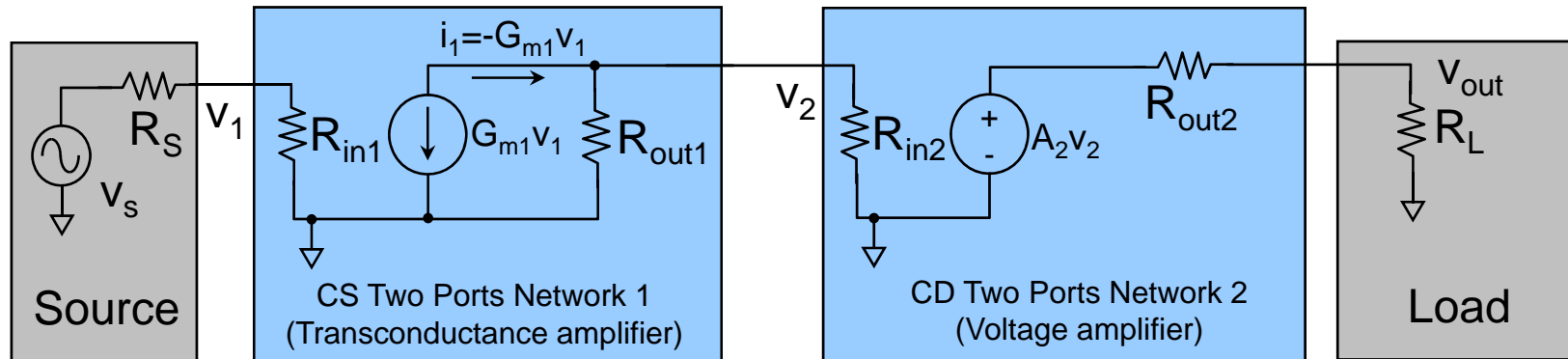

$$v_1 = v_s \times \frac{R_{in1}}{R_{in1} + R_S}$$

$$\approx v_s$$

$$\begin{aligned} v_2 &= i_1 \times (R_{out1} // R_{in2}) \\ &= -G_{m1}v_1 \times (R_{out1} // R_{in2}) \\ &\approx -5.4v_s \end{aligned}$$

$$v_{out} = v_2 \times \frac{g_{m,M2}(R_o // R_L)}{1 + (g_{m,M2} - g_{mb,M2})(R_o // R_L)}$$


$$= 0.78v_2$$

$$\approx -4.2v_s$$

$$A_V = \frac{v_{out}}{v_s} = -4.2$$

Two Stage Amplifier

Example (2-Port)

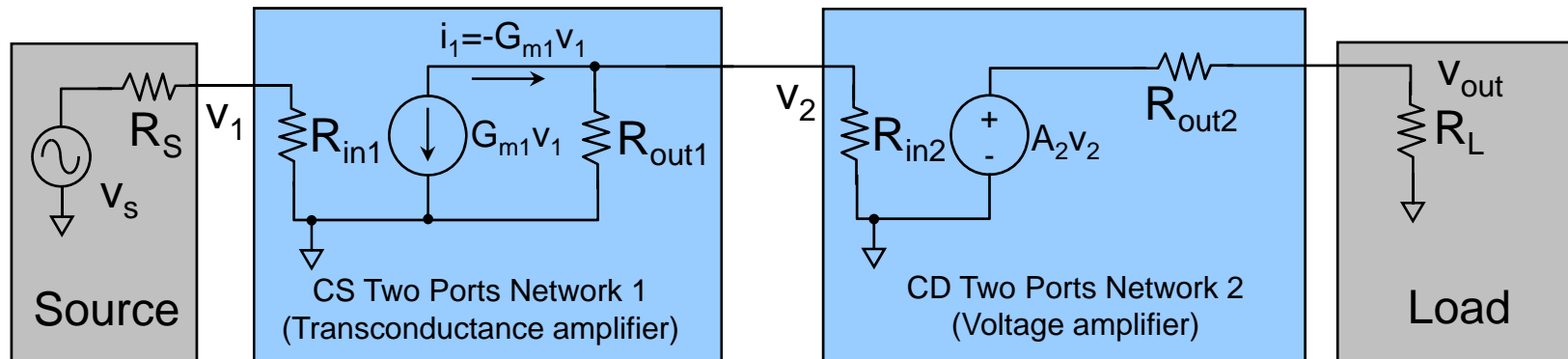


$$A_V = \frac{V_{out}}{V_s} = \frac{V_1}{V_s} \times \frac{V_2}{V_1} \times \frac{V_{out}}{V_2}$$

$$= \underbrace{\frac{R_{in1}}{R_S + R_{in1}}}_{\text{Resistor Divider}} \underbrace{\left[-G_{m1} (R_{out1} // R_{in2}) \right]}_{\text{1st Stage CS}} \underbrace{A_{V2}}_{\text{2nd Stage CD}}$$

$$= \underbrace{\frac{R_{in1}}{R_S + R_{in1}}}_{\text{Resistor Divider}} \underbrace{\left(-g_{m,M1} \right) (R_{C1} // R_{in2})}_{\text{1st Stage CS}} \underbrace{\frac{g_{m,M2} (R_L // r_{o,M3})}{1 + (g_{m,M2} - g_{mb,M2}) (R_L // r_{o,M3})}}_{\text{2nd Stage CD}}$$

$$= -4.2$$

How about Amplifier Design?

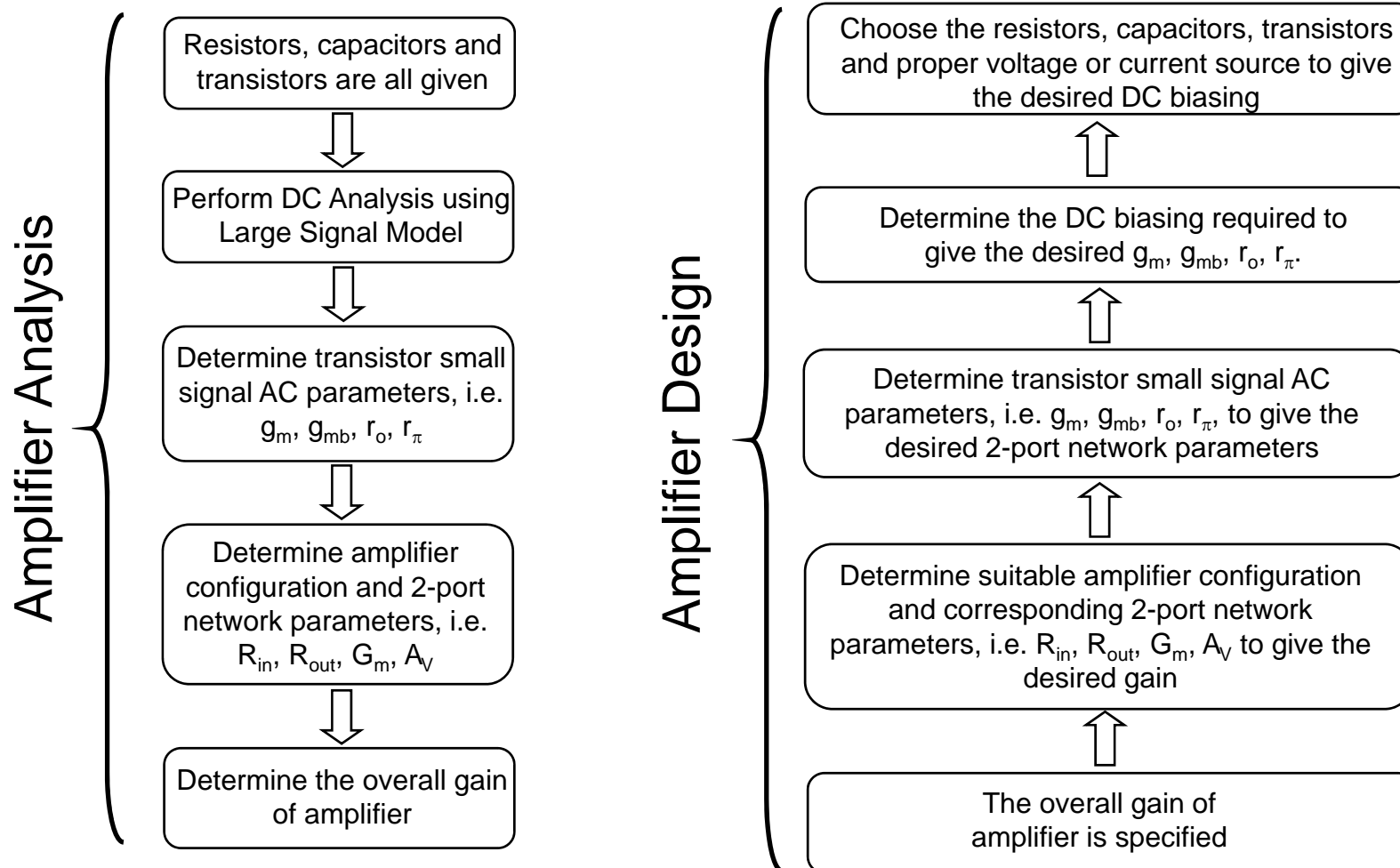

Lecture Summary

- Conceptually explain the analysis of multi-stage amplifier.
- Multi-stage amplifier analysis for 2-stage PMOS amplifiers.
- Multi-stage amplifier analysis for 2-stage BJT amplifiers.
- Multi-stage amplifier analysis for 2-stage NMOS amplifiers.

Reading Assignment






- **Reading: Reference Book (Sedra & Smith)**
Chapter 6, pp. 666 – 673. (Multi-stage amplifier)

BJT Equivalent Resistance Summary (Table 1)

Blue: look into collector terminal

Red: look into base terminal

Green: look into emitter terminal

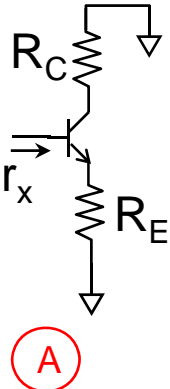
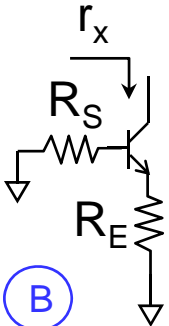
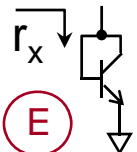
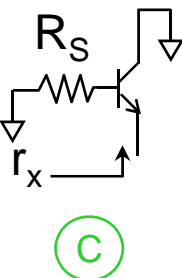
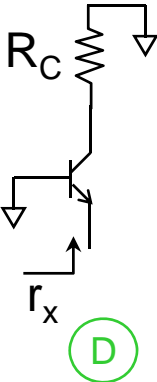
Conf	r_x	Conf	r_x	Conf	r_x
	$r_\pi + (1 + \beta)R_E$ $\approx r_\pi (1 + g_m R_E)$		$r_o \left\{ 1 + g_m \left[(r_\pi + R_S) \parallel R_E \right] \left(\frac{r_\pi}{r_\pi + R_S} \right) \right\}$ <p>If $R_S = 0$ and $r_\pi \ll R_E$ $\Rightarrow r_{x,\max} = r_o (\beta + 1)$</p>		$\frac{1}{g_m}$
	$\frac{R_S + r_\pi}{1 + \beta} \parallel r_o$ $\approx \frac{R_S}{1 + \beta} + \frac{1}{g_m}$		$\frac{1}{g_m} \times \frac{r_o + R_C}{r_o + \frac{R_C}{\beta}}$		

MOS Equivalent Resistance Summary (Table 2)

Blue: look into drain terminal


Red: look into gate terminal

Green: look into source terminal

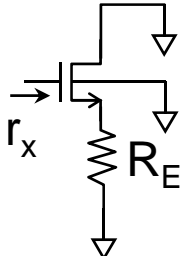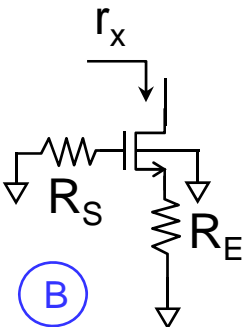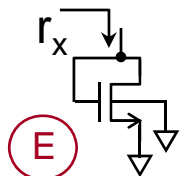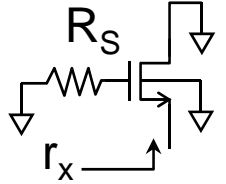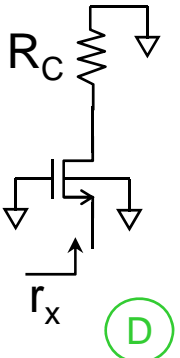Conf	r_x	Conf	r_x	Conf	r_x
 <p>(A)</p>	∞	 <p>(B)</p>	$r_o [1 + (g_m - g_{mb}) R_E]$	 <p>(E)</p>	$\frac{1}{g_m}$
 <p>(C)</p>	$\frac{1}{g_m - g_{mb}}$	 <p>(D)</p>	$\frac{1}{g_m - g_{mb}} \times \frac{r_o + R_C}{r_o}$		


BJT Amplifier Configurations

(Table 3)

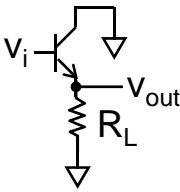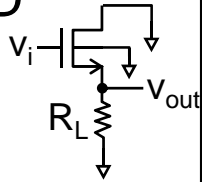BJT	G_m	A_v
CE (A)	g_m	Derive Based on 2-port Network
CB (B)	$-g_m$	Derive Based on 2-port Network
CC (C) 	Too Complex To Be Useful	$\frac{g_m R_L}{1 + g_m R_L}$
CE with Emitter Degeneration (D)	$\frac{g_m}{1 + g_m R_E}$	Derive Based on 2-port Network

MOS Amplifier Configurations

(Table 4)

MOS	G_m	A_v
CS (A)	g_m	Derive Based on 2-port Network
CG (B)	$-(g_m - g_{mb})$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network
CD (C) 	Too Complex To Be Useful	$\frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} \approx \frac{g_m}{g_m - g_{mb}}$ <i>Drop g_{mb} if no body effect</i>
CS with R_E (D)	$\frac{g_m}{1 + (g_m - g_{mb}) R_E}$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network