

EE2021

Devices and Circuits

**Single Transistor Amplifier –
CC/CD, CE/CS with
Degeneration, Current Mirror**



Lecture Outline

- **Single Transistor Amplifiers,**
CC/CD, CE/CS with degeneration
- **Current Mirror**

Common Drain (CD)

$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A/V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$

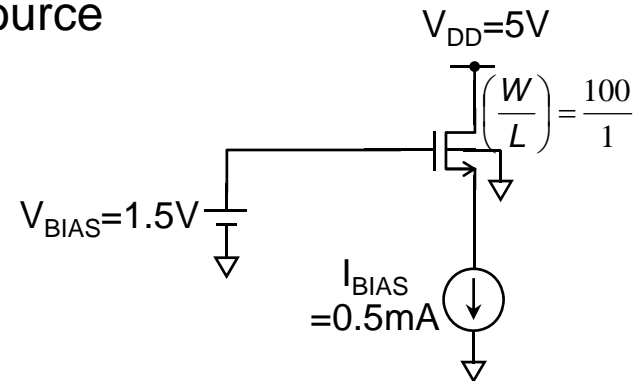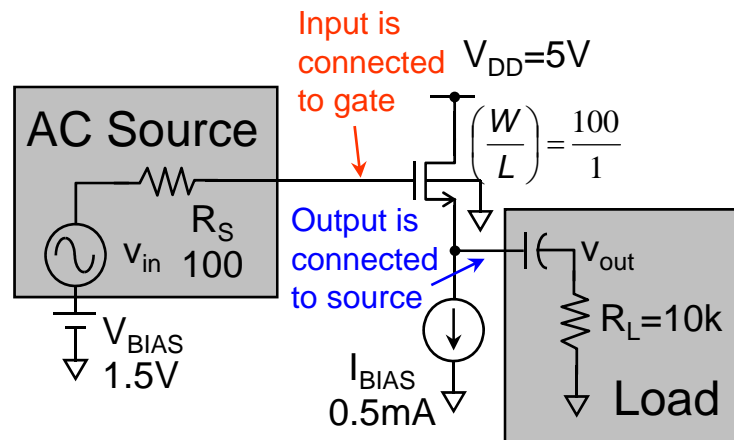
For DC analysis,
remove AC source
and load



- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- Input** connected to **Gate**, **output** connected to **Source**, **Drain** connected to neither input nor output \Rightarrow **Common Drain (CD)**

DC Analysis

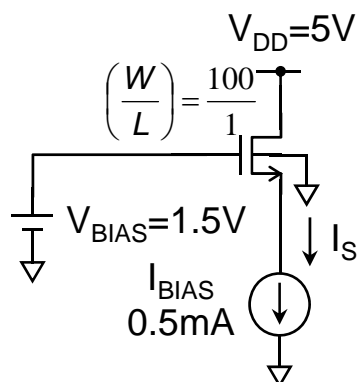- Remove source/load section when doing DC analysis



$$\begin{aligned}\mu_n C_{ox} &= 80 \mu A/V^2 \\ V_{THN} &= 0.7V \\ \lambda_n &= 0.02 V^{-1}\end{aligned}$$

Determine DC biasing

$$I_D = I_S = I_{BIAS} = 0.5mA$$

Determine AC
small signal parameter

$$\left(\frac{W}{L}\right) = \frac{100}{1}$$


$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} = 2.83mA/V$$

$$g_{mb} \approx -\frac{g_m}{4} = -0.71mA/V$$

$$r_i = \infty$$

$$r_o = \frac{1}{\lambda_n I_D} = 100k\Omega$$

AC Analysis

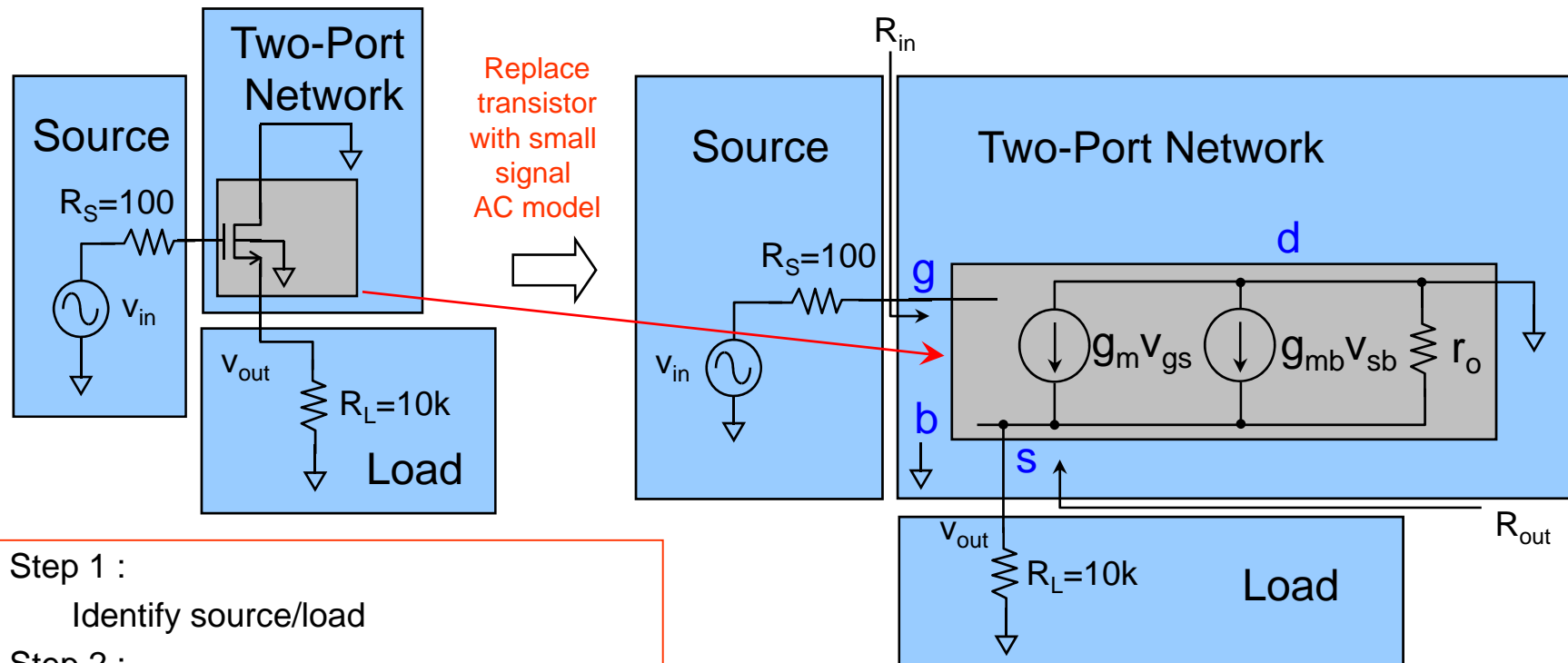

Step 1 :

Identify source/load

Step 2 :

Group the remaining component into two-port network


Step 3 :

Replace transistor with small signal AC model

Interested in finding out R_{in} , R_{out} and A for the two ports network (Voltage Amplifier)

$$R_{in} = \infty$$

CD – Two-Port Network (R_{out})

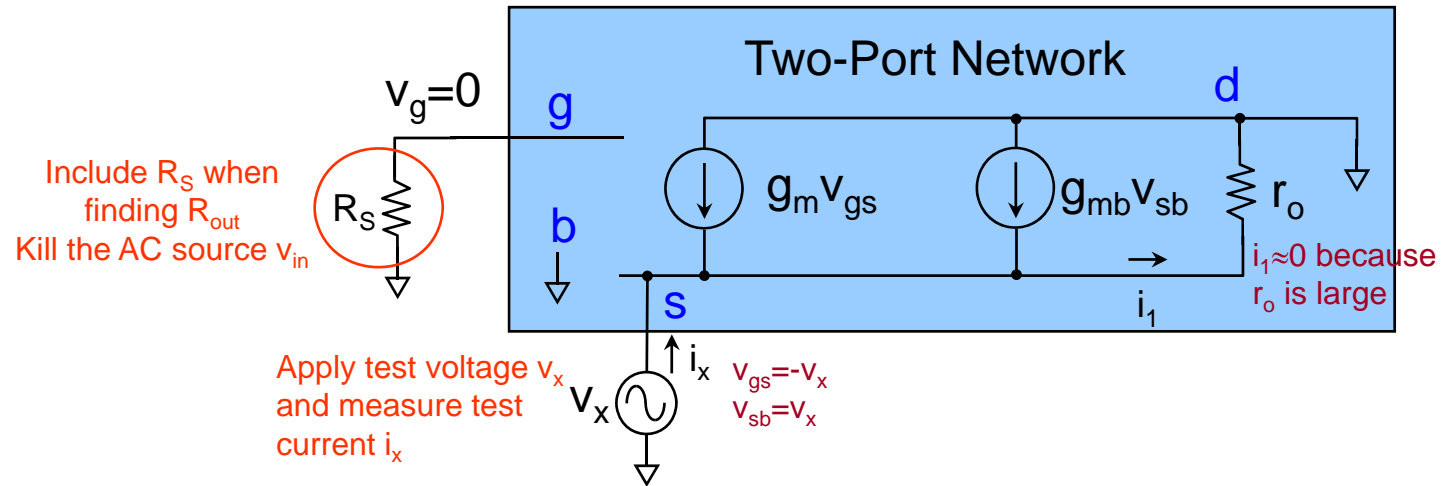


$$i_x \approx -g_m v_{gs} - g_{mb} v_{sb} = (g_m - g_{mb}) v_x$$

$$\Rightarrow R_{out} \approx \frac{1}{g_m - g_{mb}}$$

CD – Two-Port Network (R_{out})

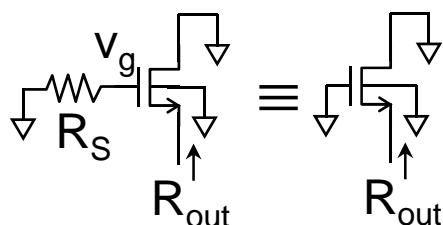Since no current flow through R_S , v_g is same as AC ground



$$R_{out} \approx \frac{1}{g_m - g_{mb}}$$

Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the source (R_{out}) is directly given by the formula. **No need to rederive.**

Example :



$$R_S = 100 \quad r_o = 100k$$

$$g_m = 2.83m \quad g_{mb} = -0.71m$$

$$\Rightarrow R_{out} \approx 283$$

- The output impedance does not depend on R_S


MOS -Equivalent Resistance

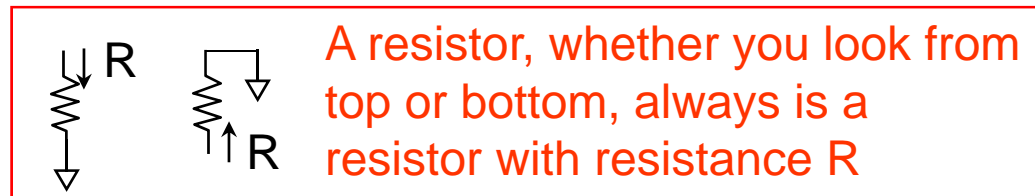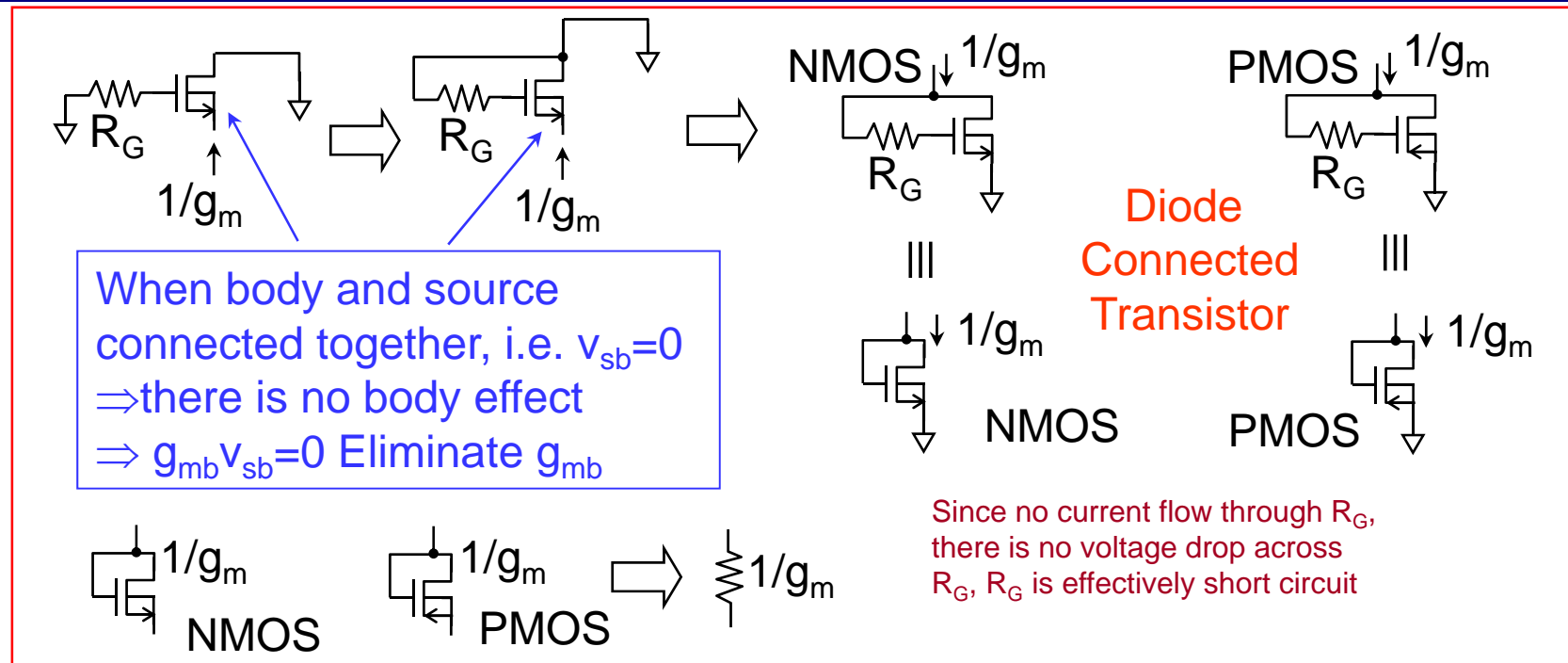

Only
APPLICABLE for
 AC analysis

- When the **drain** and **gate** are connected together, the transistor is called **diode connected transistor**
- Diode connected transistor** has equivalent resistance of $1/g_m$ if there is no body effect

CD – Two-Port Network (A_V)

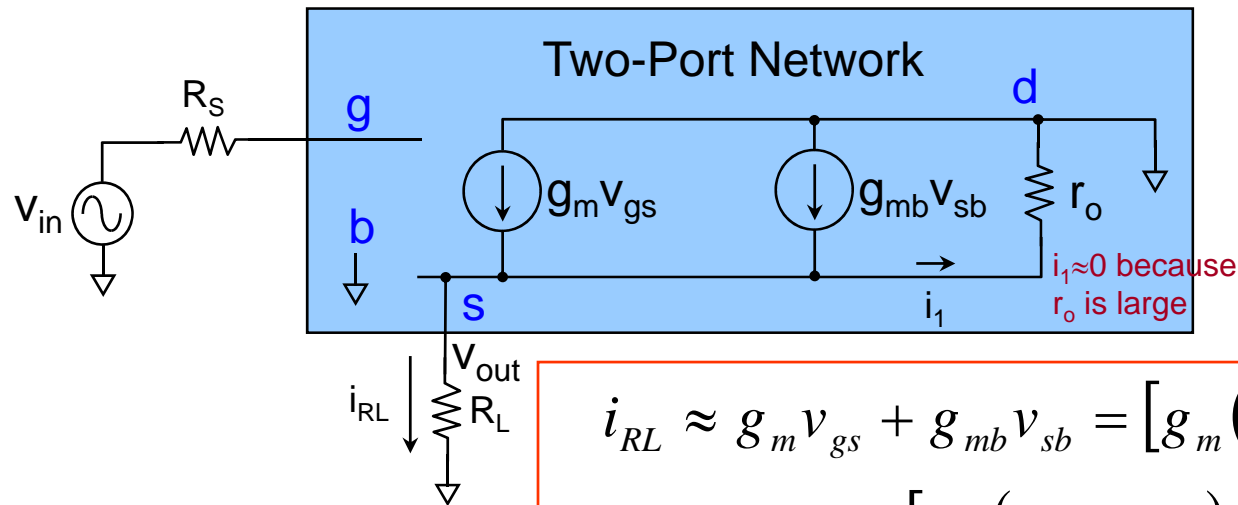

$$v_{gs} = v_{in} - v_{out}$$

$$v_{sb} = v_{out}$$

No body effect means
source and body are
connected together
 $\Rightarrow g_{mb}$ can be eliminated in
the equation

$$i_{RL} \approx g_m v_{gs} + g_{mb} v_{sb} = [g_m (v_{in} - v_{out}) + g_{mb} v_{out}]$$

$$v_{out} = i_{RL} R_L \approx [g_m (v_{in} - v_{out}) + g_{mb} v_{out}] R_L$$

$$\Rightarrow [1 + (g_m - g_{mb}) R_L] v_{out} = g_m R_L v_{in}$$

$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} \approx \frac{g_m}{g_m - g_{mb}} \approx 0.8$$


If $(g_m - g_{mb}) R_L \gg 1$

- Without body effect, $g_{mb} v_{sb} = 0 \Rightarrow A_V \approx 1$

CD – Important Results

1

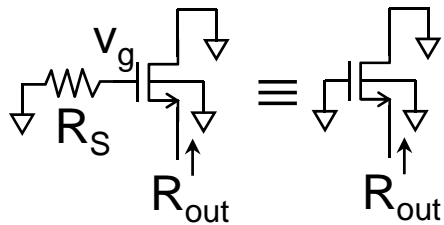
Since no current flow through R_S , v_g is same as AC ground



$$R_{out} \approx \frac{1}{g_m - g_{mb}}$$

2

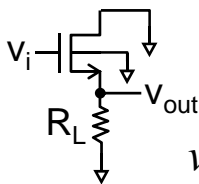
Relationship between v_{in} and v_{out} is defined as follows:




$$v_{out} = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} v_i$$

3

Diode Connected Transistor

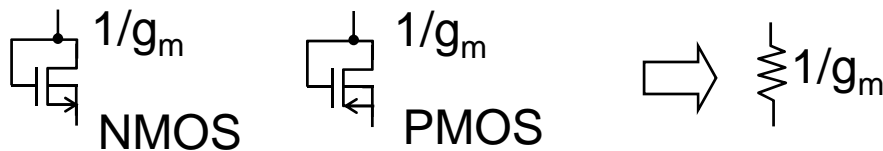


CD – Two-Port Network


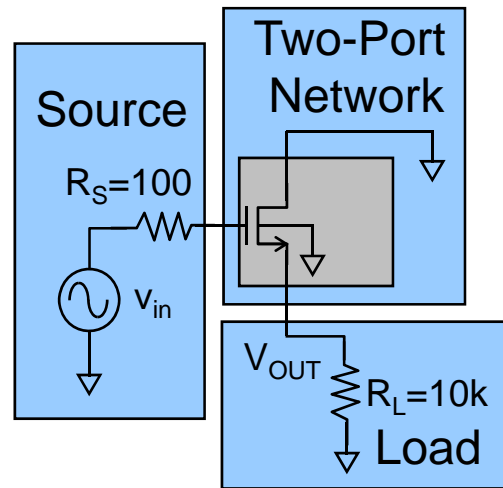


Transform the CD amplifier into **two-port voltage amplifier**

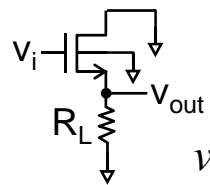Relationship between v_{in} and v_{out} is defined as follows:



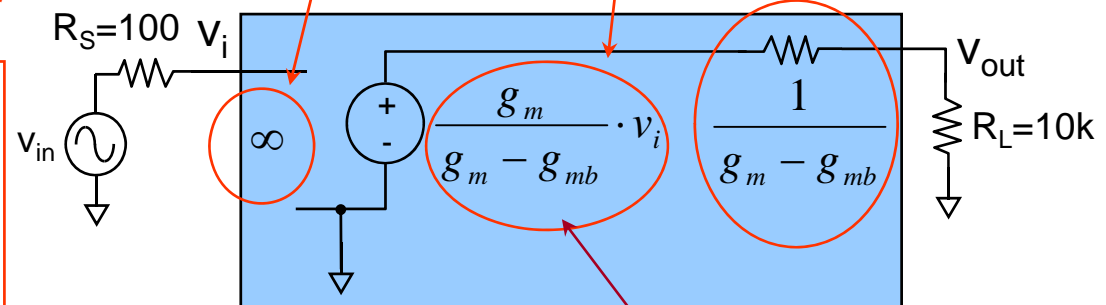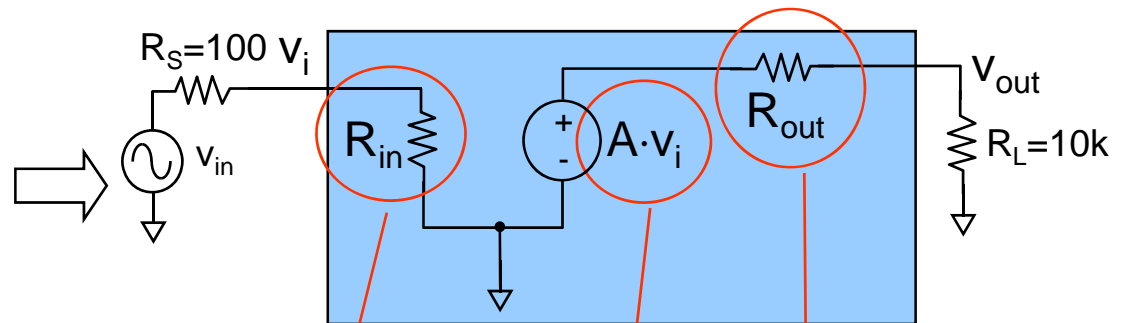
$$v_{out} = \frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} v_i$$



It is simpler to remember A_v rather than A

A can be found based on the A_v .


Common Collector (CC)

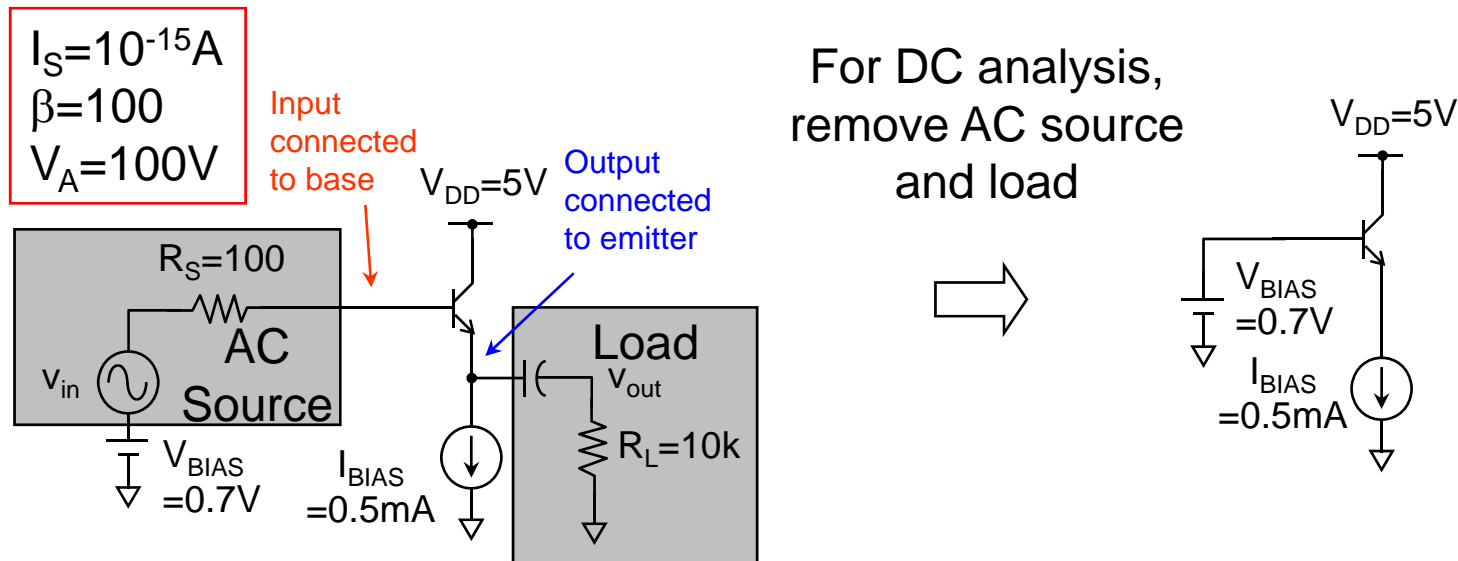

- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- **Input** connected to **Base**, **output** connected to **Emitter**, **Collector** connected to neither input nor output \Rightarrow **Common Collector (CC)**

DC Analysis (Self Reading)

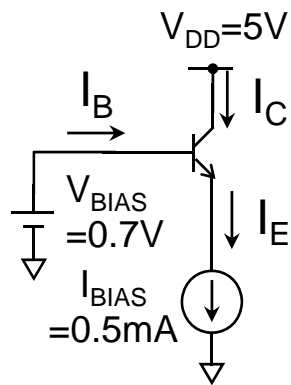- Remove source/load section when doing DC analysis



$$\begin{aligned} I_S &= 10^{-15}A \\ \beta &= 100 \\ V_A &= 100V \end{aligned}$$

Determine DC biasing

$$V_T = 26mV$$

$$I_E = I_{BIAS} = 0.5mA$$

$$I_C = \frac{\beta}{\beta + 1} I_E = 0.495mA$$

$$I_B = 4.95\mu A$$


Determine AC small signal parameter

$$g_m = \frac{I_C}{V_T} = 19mA/V$$

$$r_\pi = \frac{\beta}{g_m} = 5.26k\Omega$$

$$r_o = \frac{V_A}{I_C} = 202k\Omega$$

AC Analysis (Self Reading)

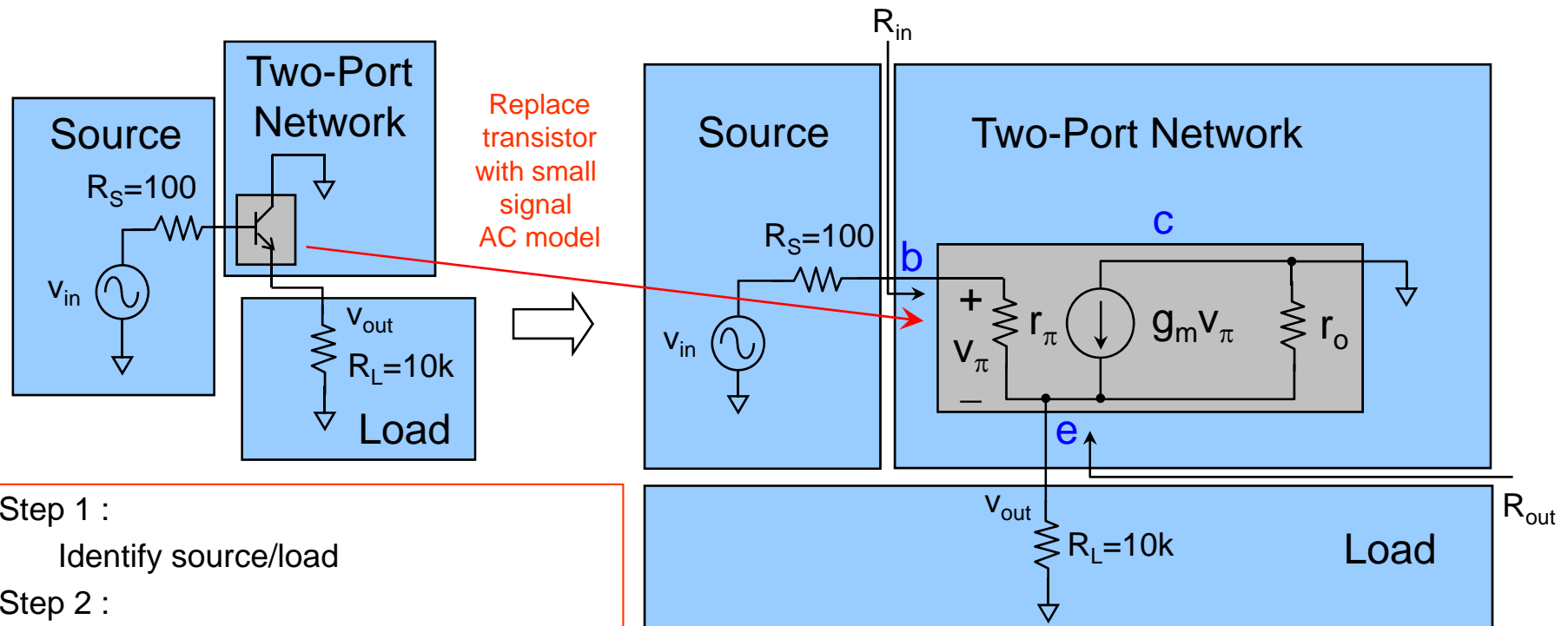

Step 1 :

Identify source/load

Step 2 :


Group the remaining component into two-port network

Step 3 :

Replace transistor with small signal AC model

Interested in finding out R_{in} , R_{out} and A for the two ports network (Voltage Amplifier)

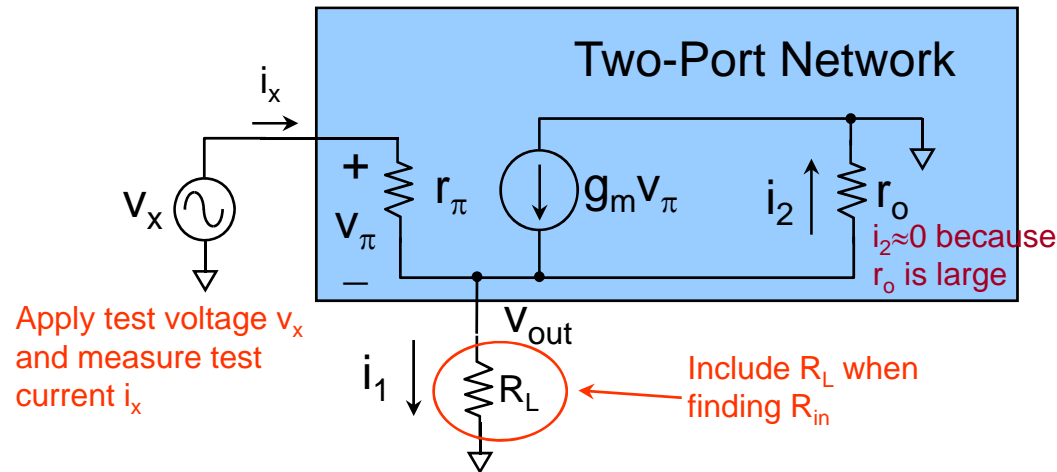CC – Two-Port Network (R_{in}) (Self Reading)



$$v_{\pi} = v_x - v_{out}$$

$$i_1 = \frac{v_{out}}{R_L}$$


$$\begin{cases} v_x - v_{out} = i_x r_{\pi} \\ i_x = i_1 + i_2 - g_m v_{\pi} \\ = \frac{v_{out}}{R_L} - g_m (v_x - v_{out}) \end{cases}$$

$$\Rightarrow i_x = \frac{v_x - i_x r_{\pi}}{R_L} - g_m i_x r_{\pi}$$

Eliminate v_{out} and keep v_x and i_x

$$\begin{aligned} \Rightarrow R_{in} &= r_{\pi} + g_m r_{\pi} R_L + R_L \\ &= r_{\pi} + (\beta + 1) R_L \\ &\approx r_{\pi} (1 + g_m R_L) \end{aligned}$$

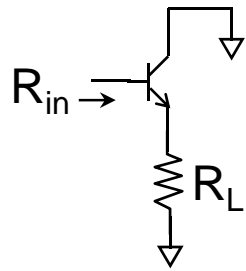CC – Two-Port Network (R_{in}) (Self Reading)



$$\begin{aligned} R_{in} &\approx r_{\pi} + (\beta + 1)R_L \\ &\approx r_{\pi} \left[1 + \frac{(\beta + 1)}{r_{\pi}} R_L \right] \\ &\approx r_{\pi} [1 + g_m R_L] \end{aligned}$$

Important Result:


If you see the transistor connected in the similar fashion, the resistance looking into the base (R_{in}) is directly given by the formula. **No need to rederive.**

Example :

$$\begin{aligned} R_L &= 10k \quad r_o = 202k \\ \Rightarrow R_{in} &= r_{\pi} + (\beta + 1)R_L \\ &= 1.01M \end{aligned}$$

- Emitter side resistor helps boost up the input resistance looking into the base

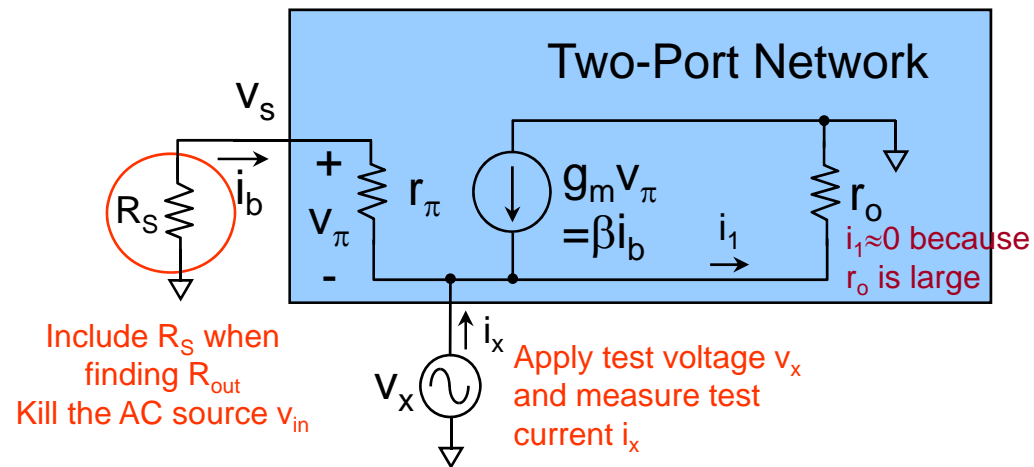CC – Two-Port Network (R_{out}) (Self Reading)




Eliminate i_b and keep v_x and i_x

$$\Rightarrow \begin{cases} i_x \approx -(\beta + 1)i_b \\ i_b = -\frac{v_x}{R_s + r_\pi} \end{cases}$$

$$\Rightarrow R_{out} = \frac{R_s + r_\pi}{\beta + 1} \approx \frac{R_s}{\beta + 1} + \frac{1}{g_m}$$

CC – Two-Port Network (R_{out}) (Self Reading)

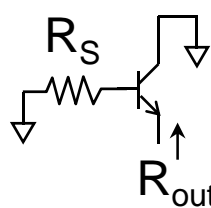
$$R_{out} \approx \frac{R_S}{\beta + 1} + \frac{1}{g_m}$$
$$\approx \frac{1}{g_m} \quad [if \ R_S \text{ is small}]$$

Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the emitter (R_{out}) is directly given by the formula. **No need to rederive.**

Example :



$$R_S = 100 \quad r_\pi = 5.26k$$

$$r_o = 202k \quad g_m = 19m$$

$$\Rightarrow R_{out} \approx 54$$

- If R_S is small, the output impedance is just the inverse of the transconductance

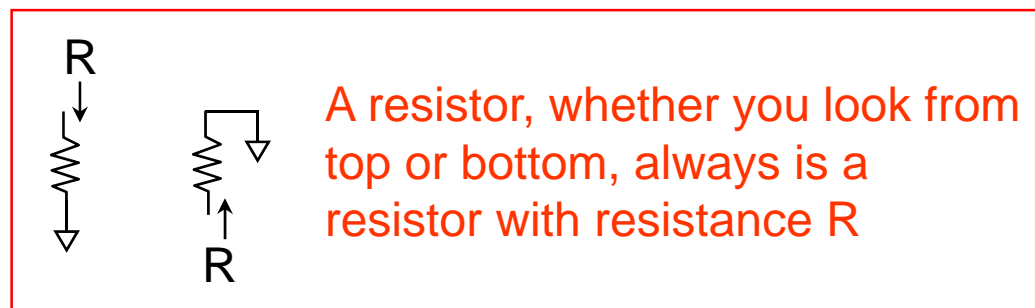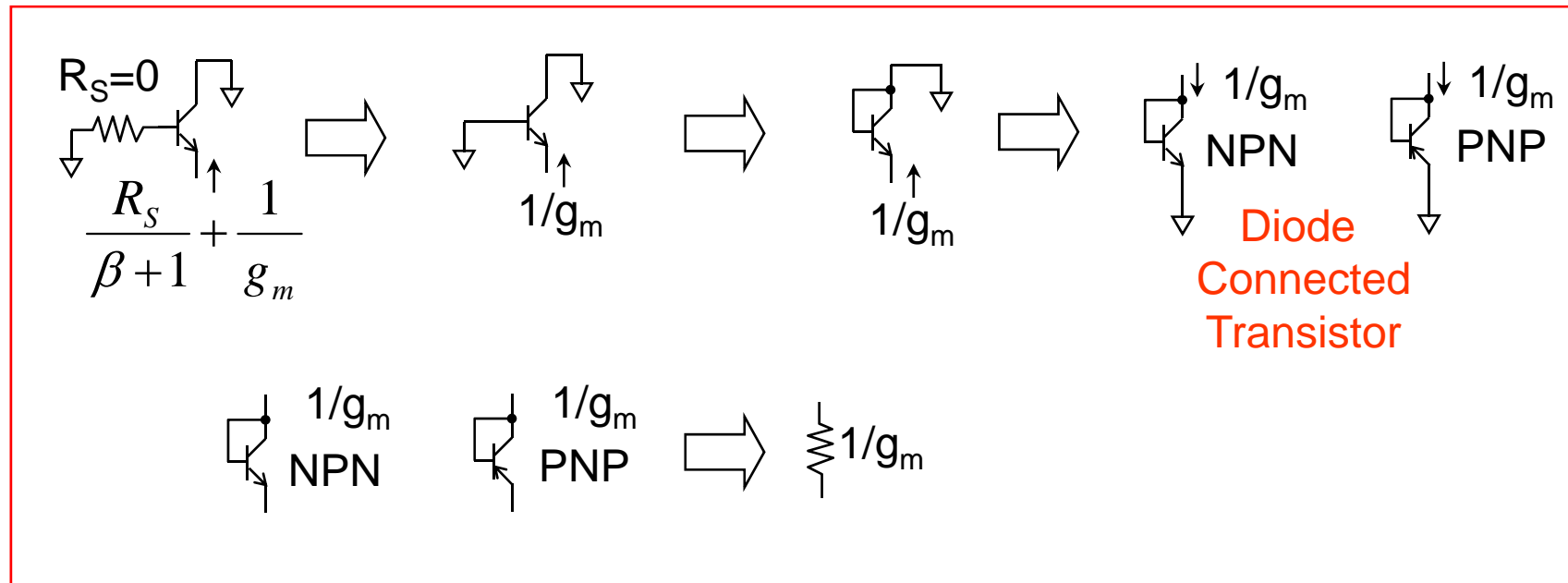
BJT – Diode Connected Transistor Equivalent Resistance (Self Reading)




Only
APPLICABLE for
AC analysis

- When the **collector** and **base** are connected together, the transistor is called **diode connected transistor**
- Diode connected transistor** has equivalent resistance of $1/g_m$

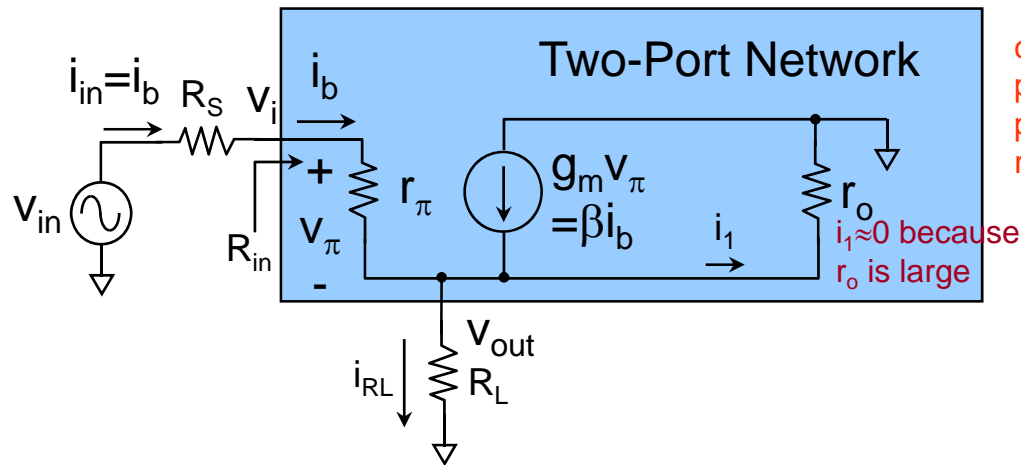CC – Two-Port Network (A_V) (Self Reading)



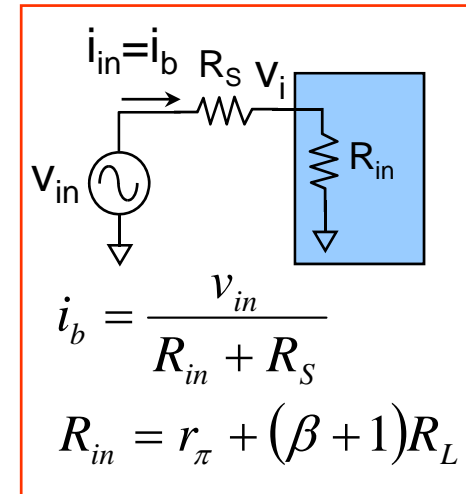To determine i_b , we can assume the two ports network present an input resistance R_{in}



Eliminate i_b and keep v_{out} and v_{in}

$$i_{RL} = (\beta + 1)i_b - i_1$$

$$v_{out} = i_{RL} \times R_L$$

$$= (\beta + 1)i_b \times R_L$$


$$\Rightarrow A_V = \frac{v_{out}}{v_{in}} = \frac{(\beta + 1)i_b \times R_L}{[R_S + r_{\pi} + (\beta + 1)R_L]i_b}$$

$$= \frac{(\beta + 1)R_L}{R_S + r_{\pi} + (\beta + 1)R_L}$$

$$= \frac{g_m R_L}{1 + g_m R_L} \approx 1 \quad [If \quad g_m R_L \gg 1]$$

CC – Important Results

1

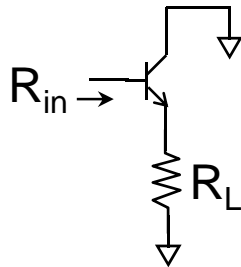


$$R_{in} \approx r_{\pi} + (\beta + 1)R_L$$

$$\approx r_{\pi} \left[1 + \frac{(\beta + 1)}{r_{\pi}} R_L \right]$$

$$\approx r_{\pi} [1 + g_m R_L]$$


2

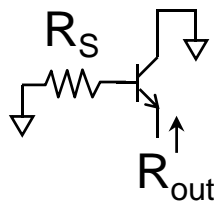

$$R_{out} \approx \frac{R_S}{\beta + 1} + \frac{1}{g_m}$$

$$\approx \frac{1}{g_m} \quad [\text{if } R_S \text{ is small}]$$

3

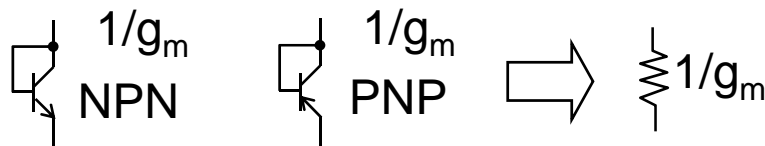


4

Relationship between v_i and v_{out} is defined as follows:




$$v_{out} = \frac{g_m R_L}{1 + g_m R_L} v_i$$

CC – Two-Port Network

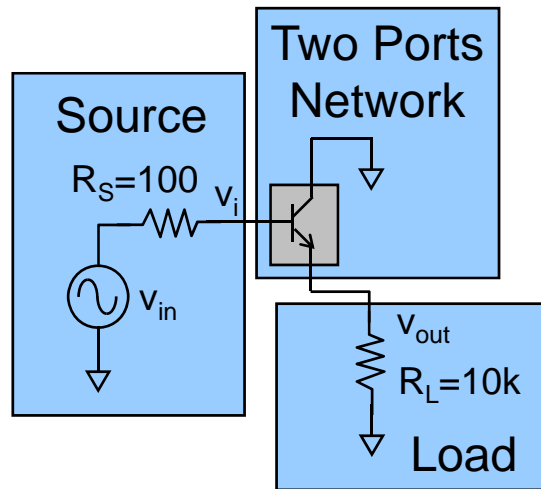

Transform the CC amplifier into **two-port voltage amplifier**

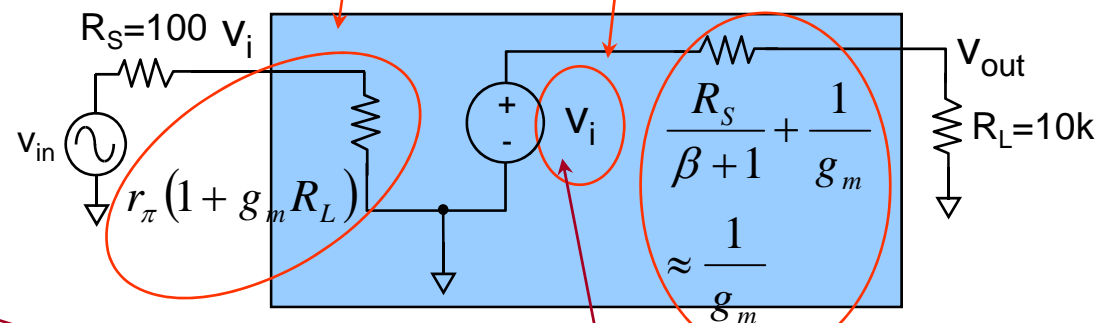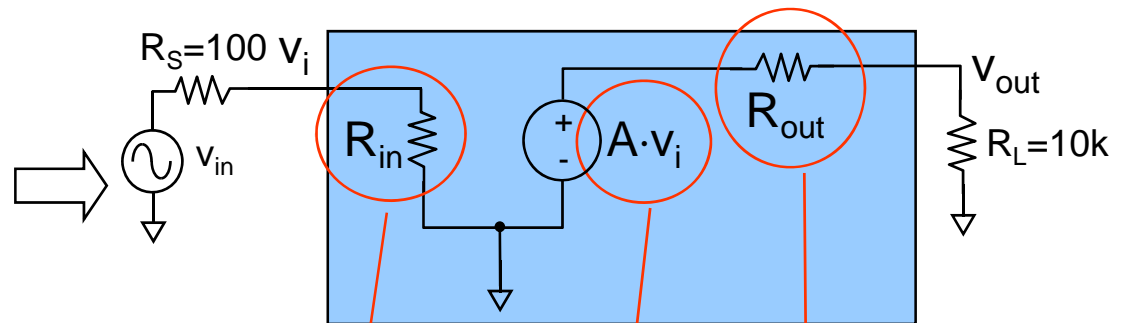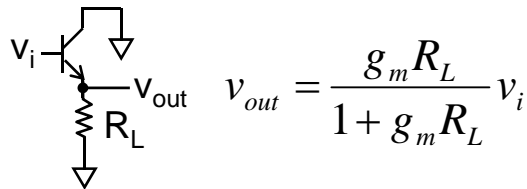Relationship between v_i and v_{out} is defined as follows:




It is simpler to remember A_v rather than A

A can be found based on A_v

Characteristic of CC/CD

- High input resistance
- Low output resistance
- Close to unity gain
- No polarity inversion
- Ideal buffer (Emitter/Source follower)
- BJT provides larger g_m than MOS ($g_m - g_{mb}$)
 - ⇒ Lower output resistance
 - ⇒ Better buffer


CE with Emitter Degeneration

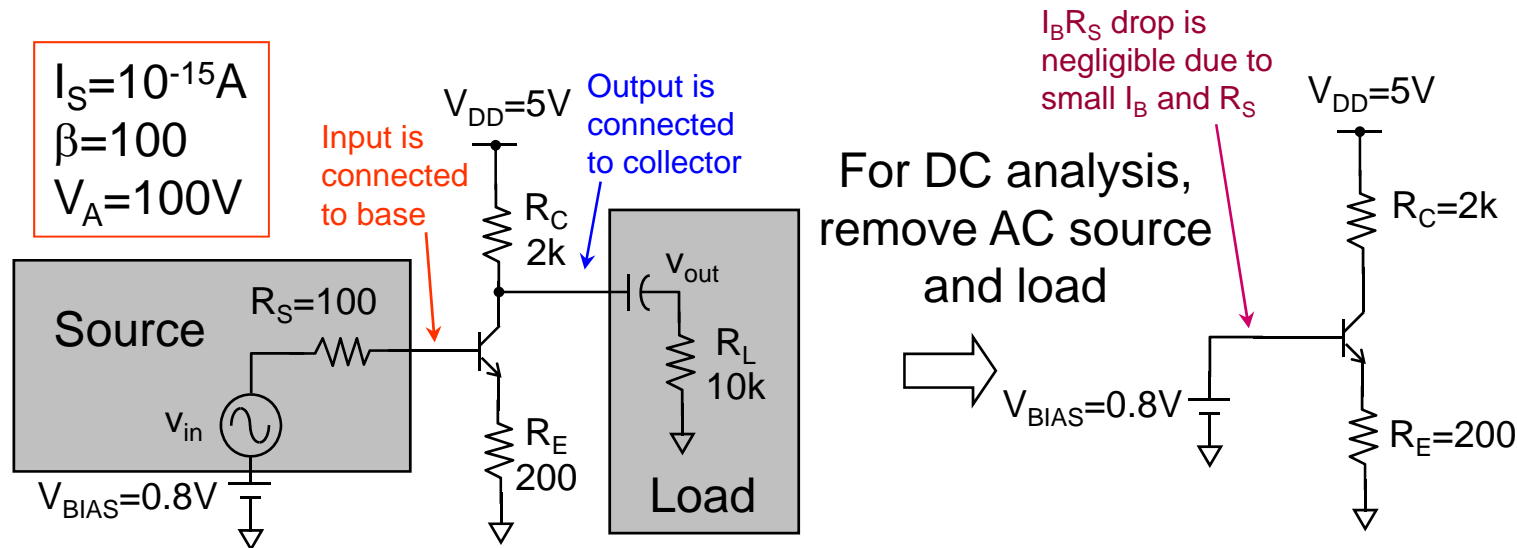

- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- Input connected to Base, output connected to Collector, Emitter connected to neither input nor output and is connected to a resistor
 \Rightarrow CE with Emitter Degeneration

DC Analysis

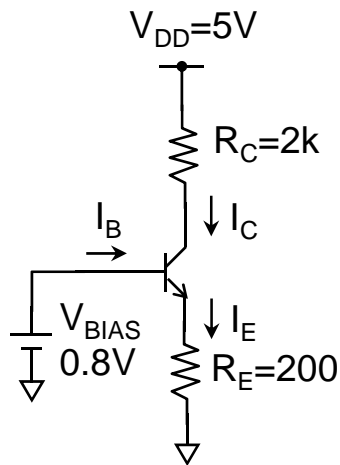- Remove source/load section when doing DC analysis



$$\begin{aligned} I_S &= 10^{-15} \text{ A} \\ \beta &= 100 \\ V_A &= 100 \text{ V} \end{aligned}$$

Determine DC biasing

$$V_T = 26 \text{ mV}$$

Assume $V_{BE} \approx 0.7 \text{ V}$

$$I_E = \frac{V_{BIAS} - V_{BE}}{R_E} = 0.5 \text{ mA}$$

$$I_C = \frac{\beta}{\beta + 1} I_E = 0.495 \text{ mA}$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) \approx 0.7001$$

\therefore Valid Assumption

$$I_B = 4.95 \mu\text{A}$$

Determine AC small signal parameter


$$g_m = \frac{I_C}{V_T} = 19 \text{ mA/V}$$

$$r_\pi = \frac{\beta}{g_m} = 5.26 \text{ k}\Omega$$

$$r_o = \frac{V_A}{I_C} = 202 \text{ k}\Omega$$

If the assumption is invalid, use the updated V_{BE} , re-estimate I_C , a few iterations might be needed

AC Analysis

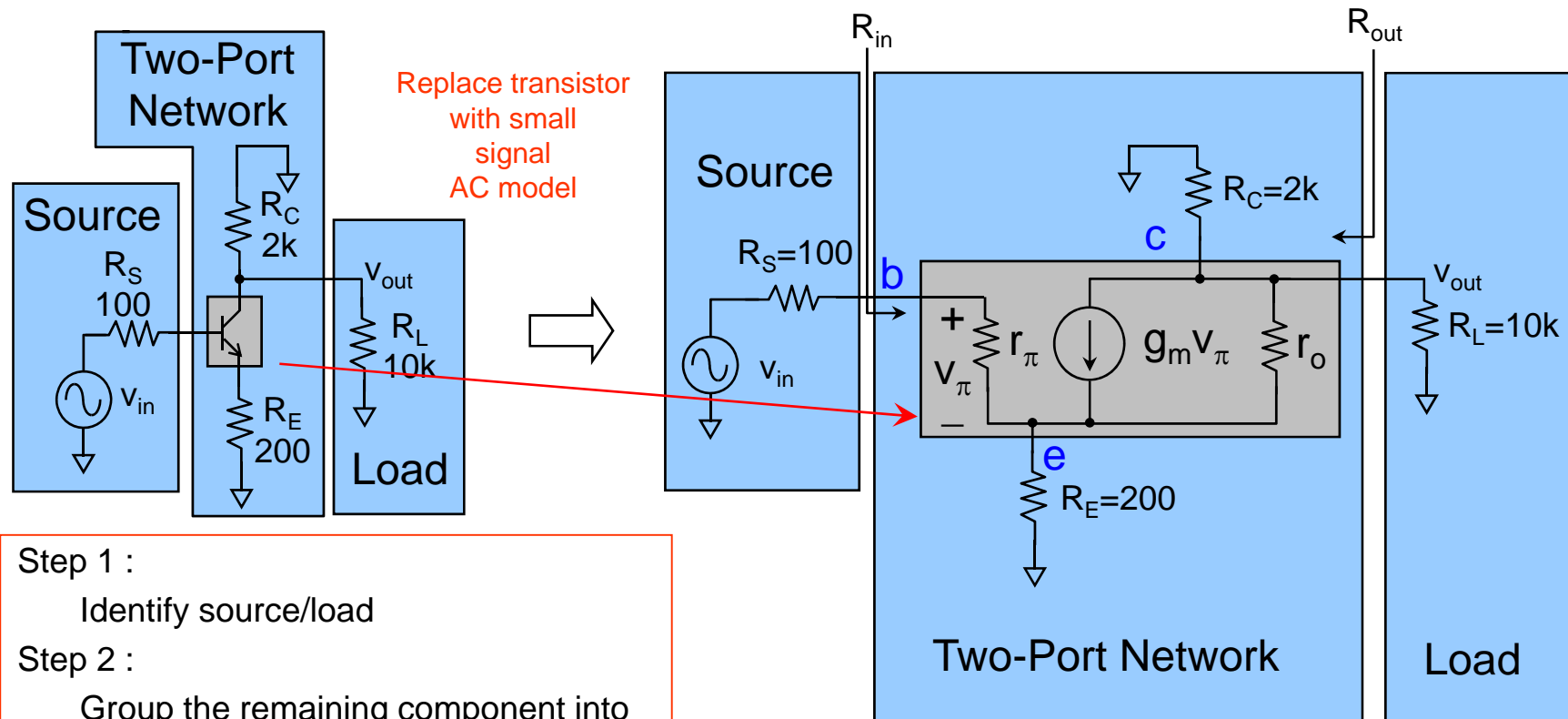

Step 1 :

Identify source/load


Step 2 :

Group the remaining component into two-port network

Step 3 :

Replace transistor with small signal AC model

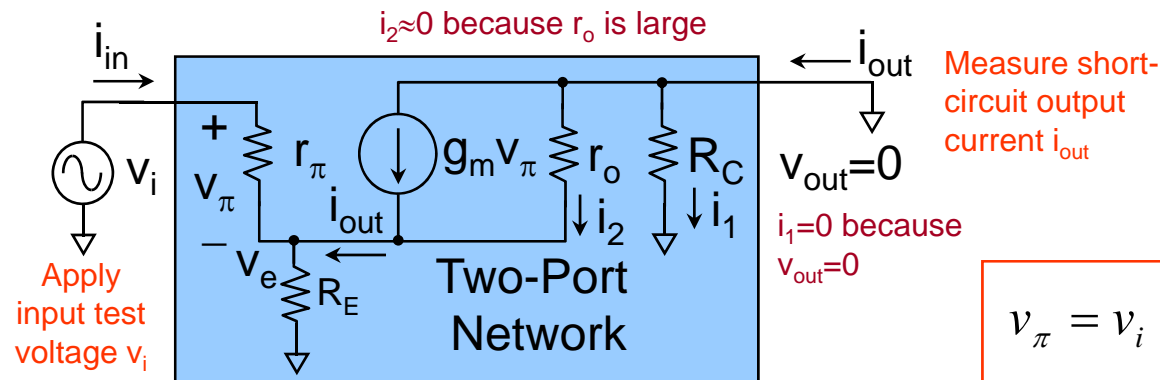CE with Emitter Degeneration – Two-Port Network (G_m)



Important Result :
Transconductance (G_m) is just $g_m/(1+g_m R_E)$

$$v_\pi = v_i - v_e \quad i_{in} = \frac{v_i - v_e}{r_\pi}$$

$$\begin{cases} i_{in} + i_{out} \big|_{v_{out}=0} = v_e / R_E \\ i_{out} \big|_{v_{out}=0} \approx g_m v_\pi = g_m (v_i - v_e) \end{cases}$$


$$\Rightarrow v_e = v_i - \frac{i_{out} \big|_{v_{out}=0}}{g_m}$$

Eliminate i_{in} , v_e and keep v_i and i_{out}

$$\frac{i_{out} \big|_{v_{out}=0}}{g_m r_\pi} + i_{out} \big|_{v_{out}=0} = \frac{v_i}{R_E} - \frac{i_{out} \big|_{v_{out}=0}}{g_m R_E}$$

$$\begin{aligned} \Rightarrow G_m &= \frac{i_{out}}{v_i} \bigg|_{v_{out}=0} = \frac{g_m r_\pi}{r_\pi + (1 + g_m r_\pi) R_E} \\ &\approx \frac{g_m}{1 + g_m R_E} = 4 \text{ mA/V} \end{aligned}$$

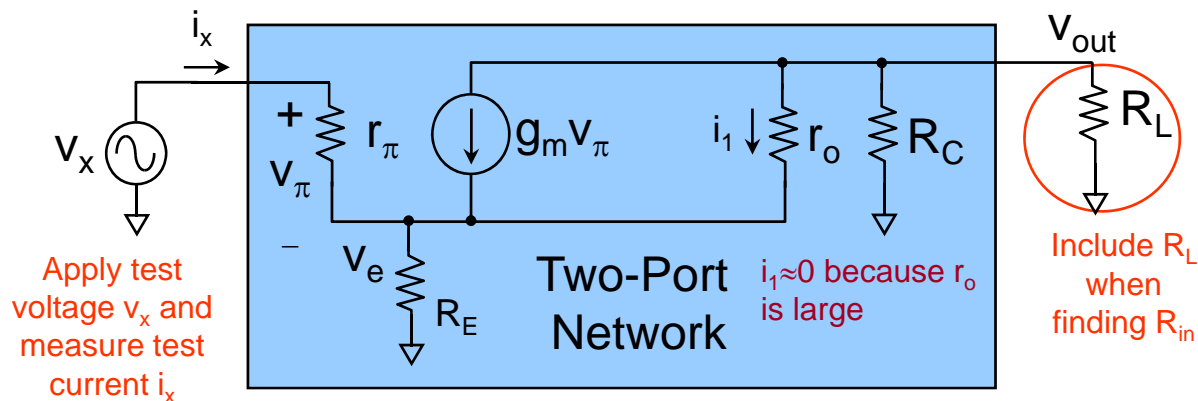CE with Emitter Degeneration – Two-Port Network (R_{in})



$$\begin{aligned} v_\pi &= v_x - v_e \\ &= i_x r_\pi \end{aligned}$$


$$\begin{cases} i_x = \frac{v_e}{R_E} - g_m v_\pi = \frac{v_e}{R_E} - g_m (v_x - v_e) \\ v_e = v_x - i_x r_\pi \end{cases}$$

Eliminate v_e and keep v_x and i_x

$$\Rightarrow i_x = \frac{v_x}{R_E} - \frac{i_x r_\pi}{R_E} - g_m i_x r_\pi$$

$$\begin{aligned} \Rightarrow R_{in} &= r_\pi + g_m r_\pi R_E + R_E \\ &\approx r_\pi + (\beta + 1) R_E \\ &\approx r_\pi [1 + g_m R_E] \end{aligned}$$

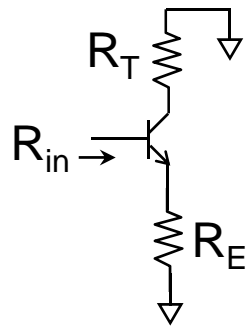CE with Emitter Degeneration – Two-Port Network (R_{in})



$$R_{in} \approx r_{\pi} + (\beta + 1)R_E$$
$$\approx r_{\pi} [1 + g_m R_E]$$

Important Result:


If you see the transistor connected in the similar fashion, the resistance looking into the base (R_{in}) is directly given by the formula. **No need to rederive.**

Example :

$$R_E = 200 \quad r_o = 202k$$
$$\Rightarrow R_{in} = r_{\pi} + (\beta + 1)R_E$$
$$= 25.5k$$

- Emitter side resistor helps boost up the input resistance looking into the base, **same formula as CC**

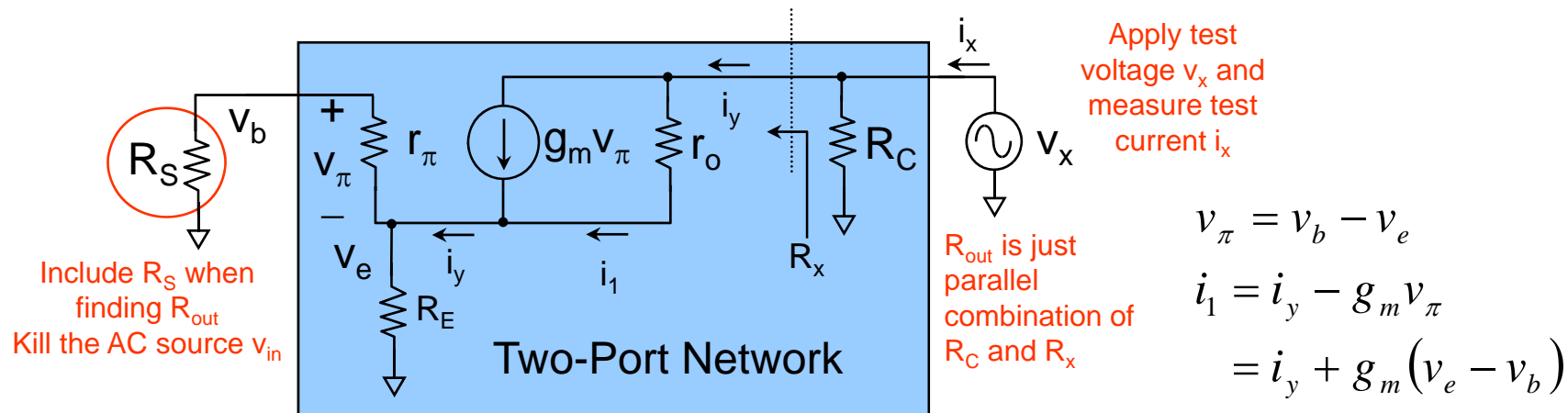CE with Emitter Degeneration – Two-Port Network (R_{out})



$$\Rightarrow \begin{cases} v_x \approx v_e + i_1 r_o = v_e + [i_y + g_m (v_e - v_b)] r_o \\ v_e = i_y [(R_S + r_\pi) // R_E] \\ v_e - v_b = \frac{r_\pi}{R_S + r_\pi} v_e \end{cases}$$


Eliminate v_e , v_b and keep v_x and i_y

$$\Rightarrow R_x \approx r_o \left\{ 1 + g_m [(R_S + r_\pi) // R_E] \left(\frac{r_\pi}{R_S + r_\pi} \right) \right\}$$

$$R_{out} = R_x // R_C \approx R_C$$

$$\Rightarrow v_x \approx i_y [(R_S + r_\pi) // R_E] + i_y r_o + g_m i_y [(R_S + r_\pi) // R_E] \left(\frac{r_\pi}{R_S + r_\pi} \right) r_o$$

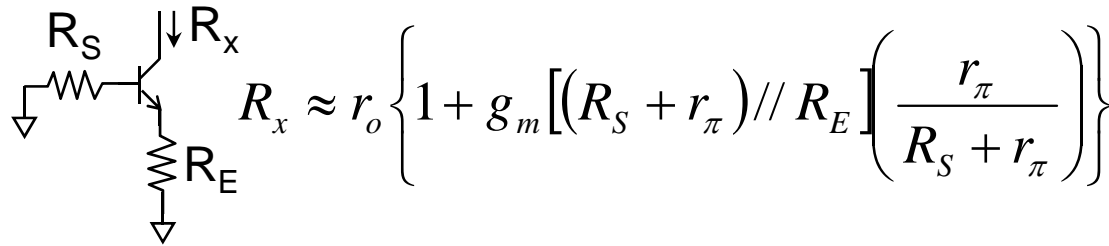CE with Emitter Degeneration – Two-Port Network (R_{out})



Important Result:

If you see the transistor connected in the similar fashion, the resistance looking into the collector (R_x) is directly given by the formula.

No need to rederive.

Example :

$$R_S = 100 \quad r_\pi = 5.26k$$

$$R_E = 200 \quad r_o = 202k$$

$$g_m = 19m$$

$$\Rightarrow R_x \approx 928k$$

$$\Rightarrow R_{out} \approx R_C = 2k$$


- Emitter side resistor helps boost up the transistor output resistance (R_x)
- Very similar to CB configuration. **Same formula as CB if $R_S=0$.**

CE with Degeneration – Important Results

1


Important Result :
Transconductance (G_m) is just $g_m/(1+g_m R_E)$

2

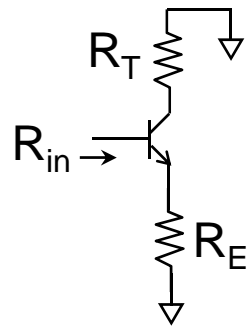


$$R_{in} \approx r_{\pi} + (\beta + 1)R_E \\ \approx r_{\pi} [1 + g_m R_E]$$

3

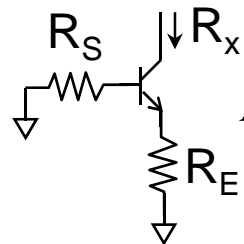


$$R_x \approx r_o \left\{ 1 + g_m \left[(R_S + r_{\pi}) // R_E \right] \left(\frac{r_{\pi}}{R_S + r_{\pi}} \right) \right\}$$

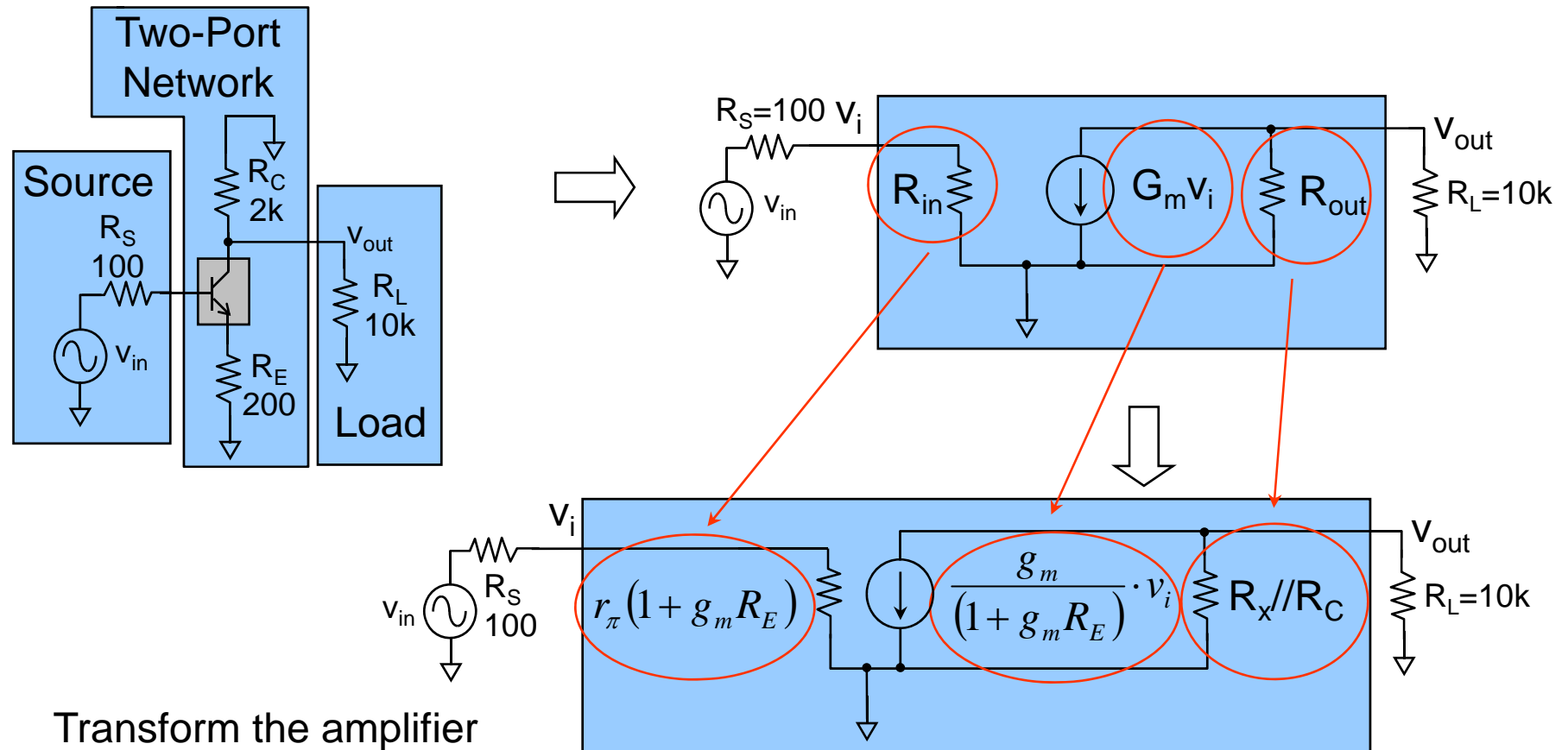CE with Emitter Degeneration – Two-Port Network



Transform the amplifier
into **two-port**
transconductance amplifier

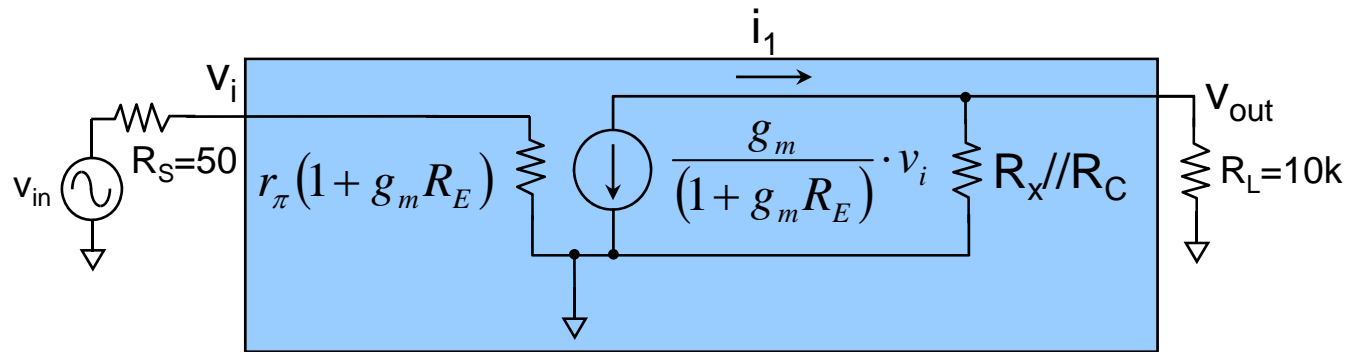CE with Emitter Degeneration – Two-Port Network (A_V)



$$v_i = \frac{r_\pi (1 + g_m R_E)}{R_S + r_\pi (1 + g_m R_E)} v_{in} \quad i_1 = -\frac{g_m}{1 + g_m R_E} v_i$$

$$v_{out} = i_1 \times [(R_x // R_C) // R_L]$$


$$= -\frac{g_m}{1 + g_m R_E} v_i \times [(R_x // R_C) // R_L]$$

$$A_V = \frac{v_{out}}{v_{in}} = -\frac{r_\pi (1 + g_m R_E)}{R_S + r_\pi (1 + g_m R_E)} \times \frac{g_m}{1 + g_m R_E} \times [(R_x // R_C) // R_L]$$



CS with Source Degeneration

$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A/V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$
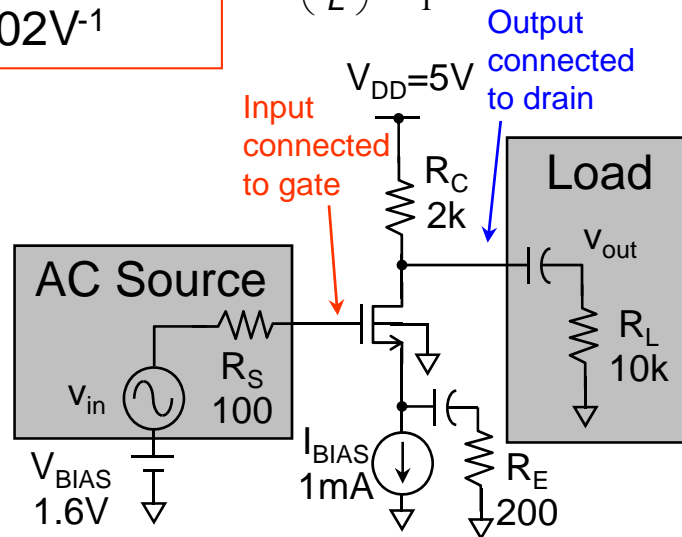
$$\left(\frac{W}{L}\right) = \frac{100}{1}$$



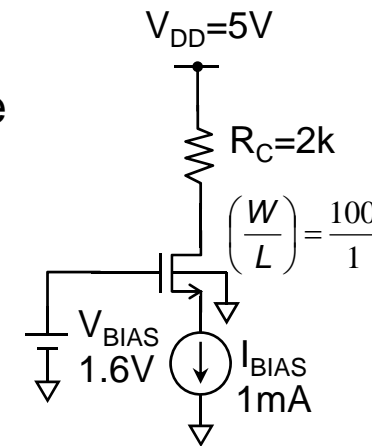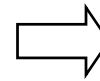
For DC analysis,
remove AC source
and load



- Identify Source and Load
- To identify amplifier configuration, we need to consider AC equivalent circuits, i.e. short circuit capacitors
- Input connected to Gate, output connected to Drain, Source connected to neither input nor output and is connected to a resistor
⇒ CS with Source Degeneration

DC Analysis (Self Reading)

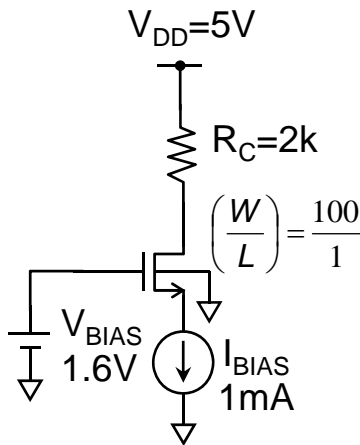- Remove source/load section when doing DC analysis



$$\begin{aligned}\mu_n C_{ox} &= 80 \mu\text{A}/\text{V}^2 \\ V_{THN} &= 0.7\text{V} \\ \lambda_n &= 0.02\text{V}^{-1}\end{aligned}$$

Determine DC biasing

$$\begin{aligned}I_D &= I_S = I_{BIAS} = 1\text{mA} \\ \left(\frac{W}{L}\right) &= \frac{100}{1}\end{aligned}$$

Good approximation, no need to go through detailed calculations

Determine AC small signal parameter


$$\begin{aligned}g_m &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_D} \\ &= 4\text{mA}/\text{V}\end{aligned}$$

$$g_{mb} \approx -\frac{g_m}{4} = -1\text{mA}/\text{V}$$

$$r_i = \infty$$


$$r_o = \frac{1}{\lambda_n I_D} = 50\text{k}\Omega$$

AC Analysis (Self Reading)

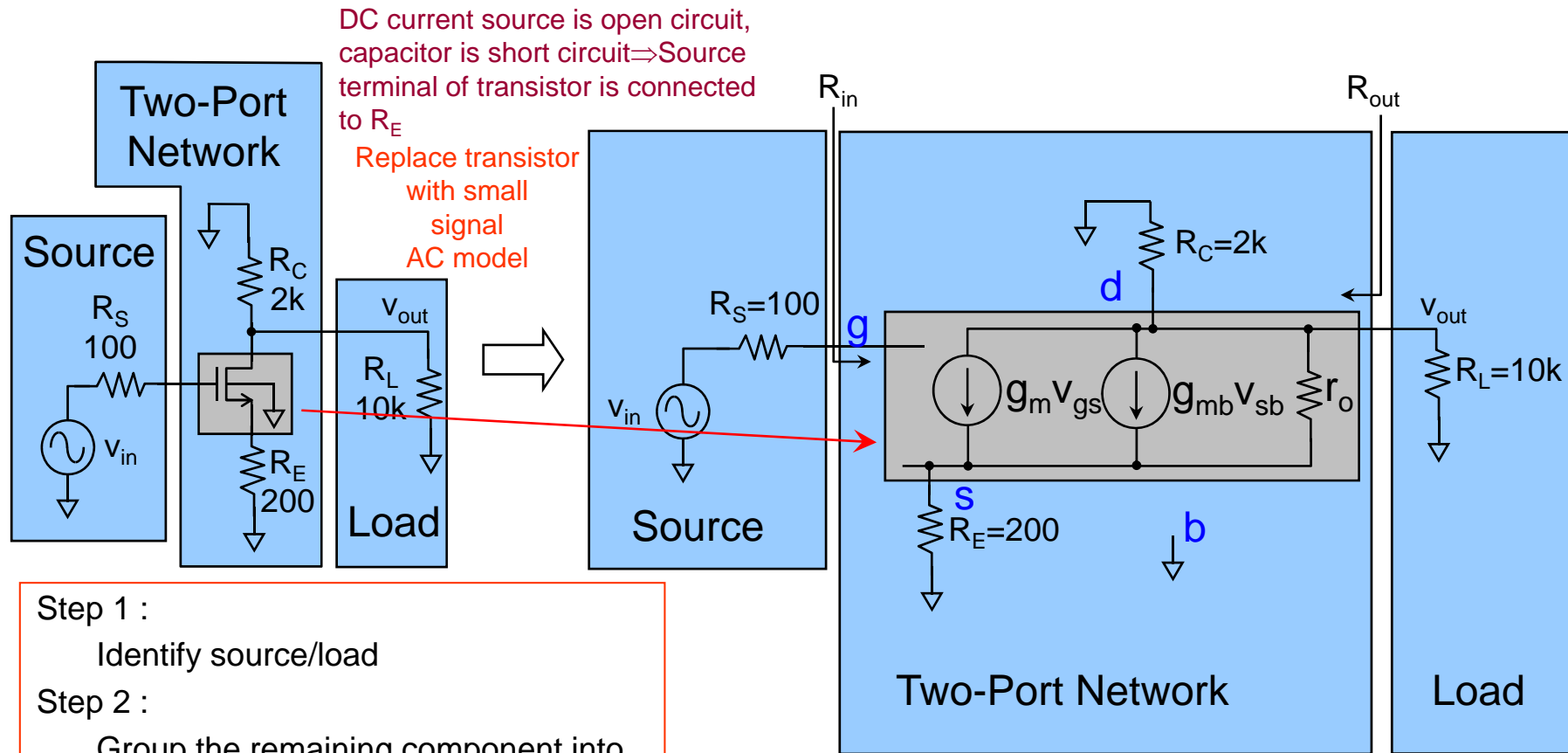

$$R_{in} = \infty$$

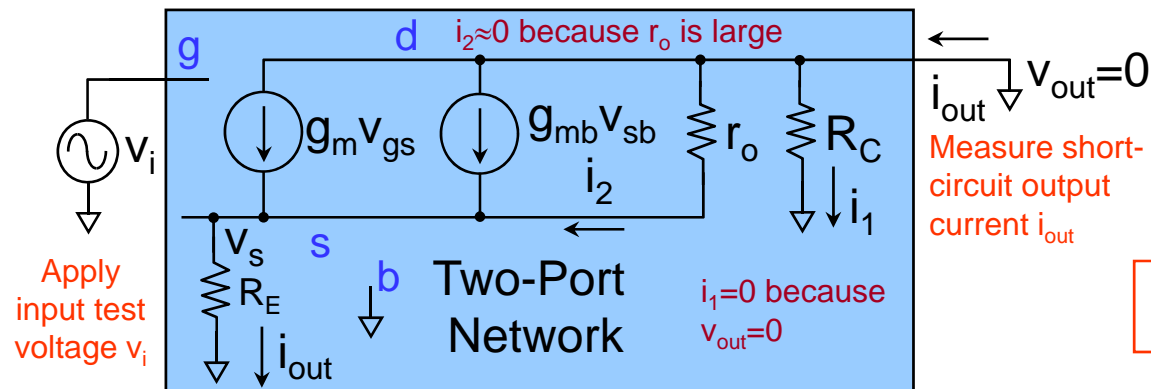CS with Source Degeneration – Two-Port Network (G_m) (Self Reading)




Important Result :
Transconductance (G_m) is just
 $g_m / [1 + (g_m - g_{mb}) R_E]$

$$v_{gs} = v_i - v_s \quad v_{sb} = v_s$$

$$\begin{aligned} & \left\{ \begin{aligned} v_s &\approx i_{out} \big|_{v_{out}=0} \times R_E \\ i_{out} \big|_{v_{out}=0} &\approx g_m v_{gs} + g_{mb} v_{sb} \\ &\approx g_m (v_i - v_s) + g_{mb} v_s \end{aligned} \right. \quad \begin{aligned} & \text{Eliminate } v_s \text{ and keep } v_i \\ & \text{and } i_{out} \end{aligned} \Rightarrow G_m = \frac{i_{out}}{v_i} \bigg|_{v_{out}=0} \\ & \Rightarrow i_{out} \big|_{v_{out}=0} \approx g_m v_i - (g_m - g_{mb}) i_{out} \big|_{v_{out}=0} \times R_E \end{aligned}$$

$$\begin{aligned} G_m &= \frac{g_m}{1 + (g_m - g_{mb}) R_E} \\ &= 2 \text{ mA/V} \end{aligned}$$

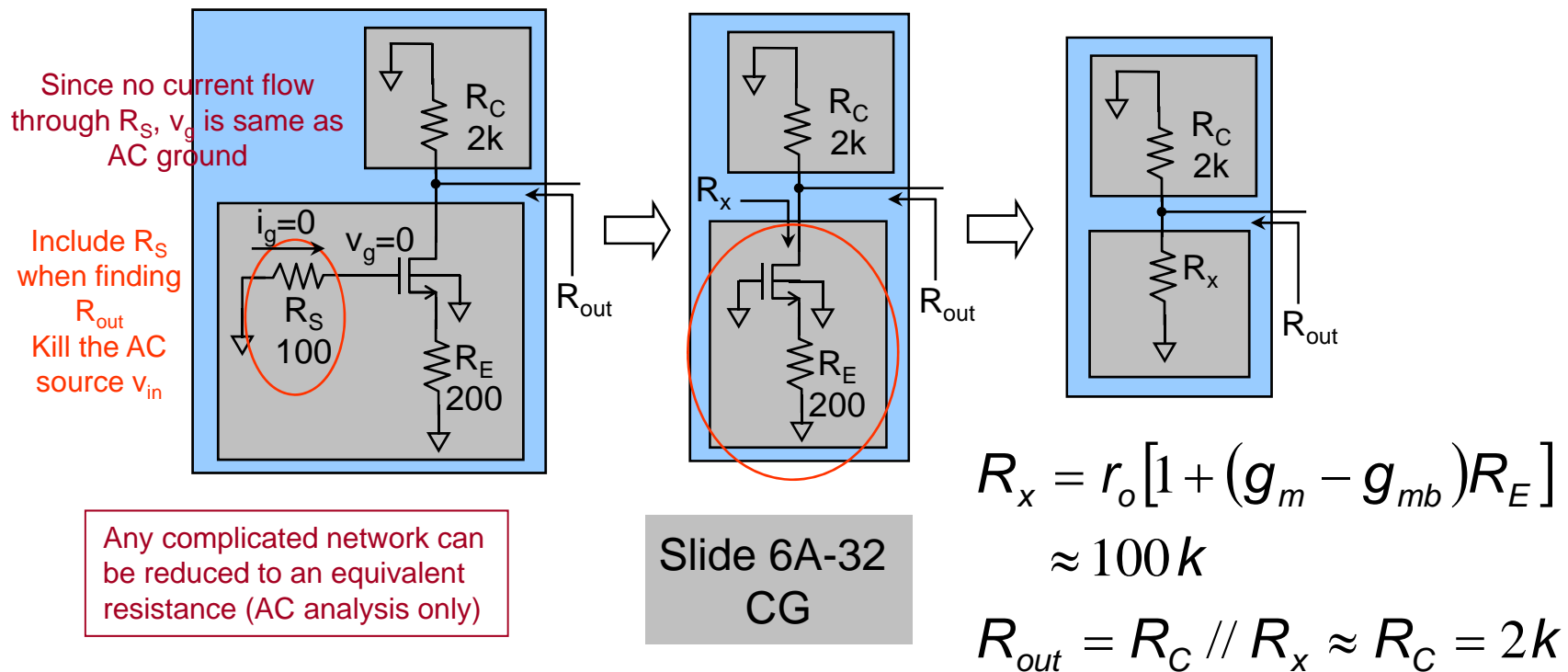CS with Source Degeneration – Two-Port Network (R_{out}) (Self Reading)



- Source side resistance helps boost up the transistor output resistance (R_x)
- Same as CG


CS with Degeneration – Important Results

1

Important Result :

Transconductance (G_m) is just $g_m/[1+(g_m-g_{mb})R_E]$


2

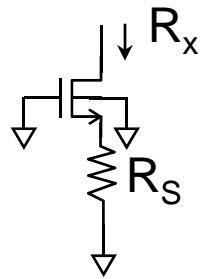

$$R_x \approx r_o [1 + (g_m - g_{mb})R_S]$$


Same result as CG

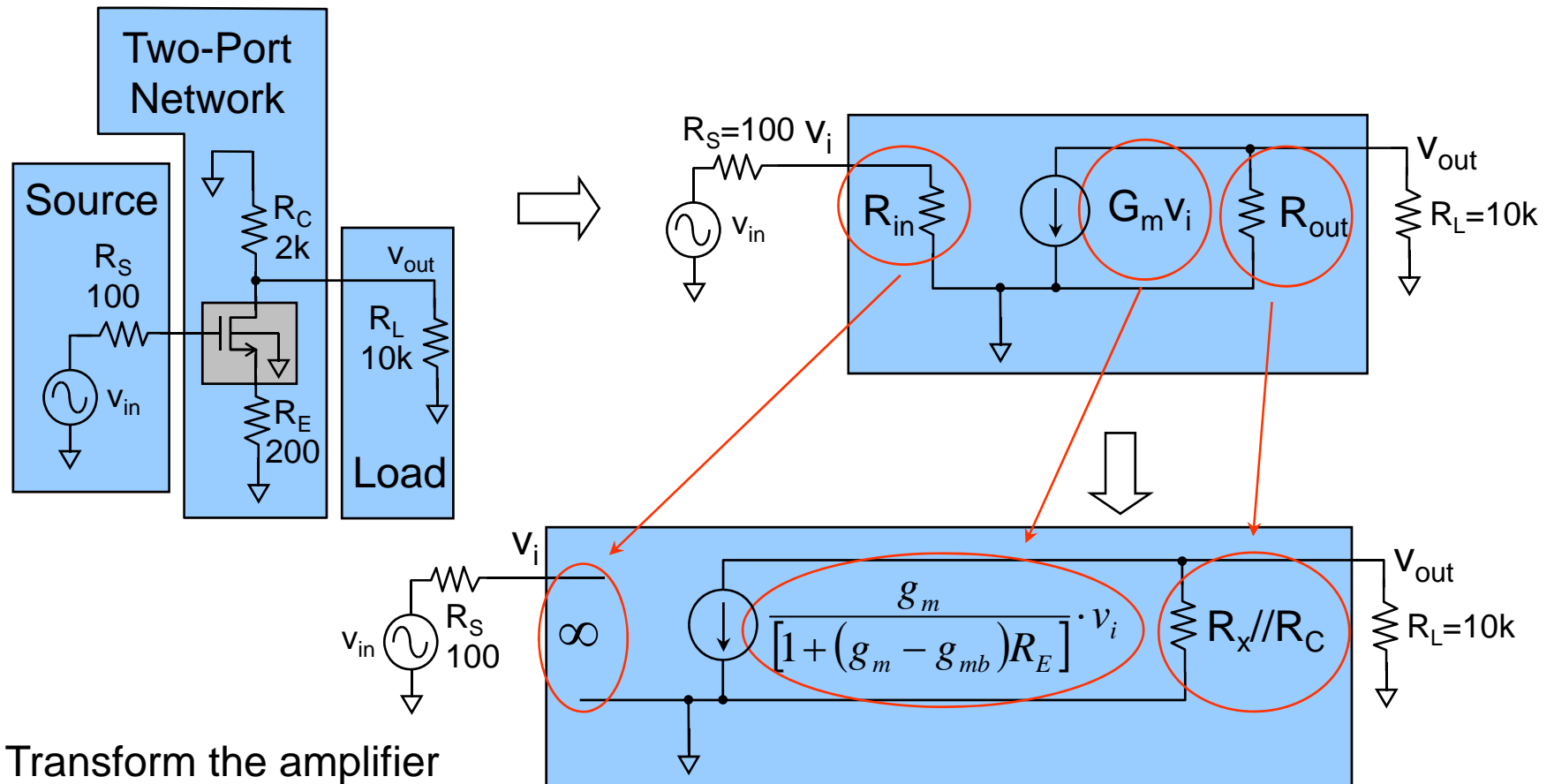CS with Source Degeneration – Two-Port Network



Transform the amplifier
into **two-port**
transconductance amplifier

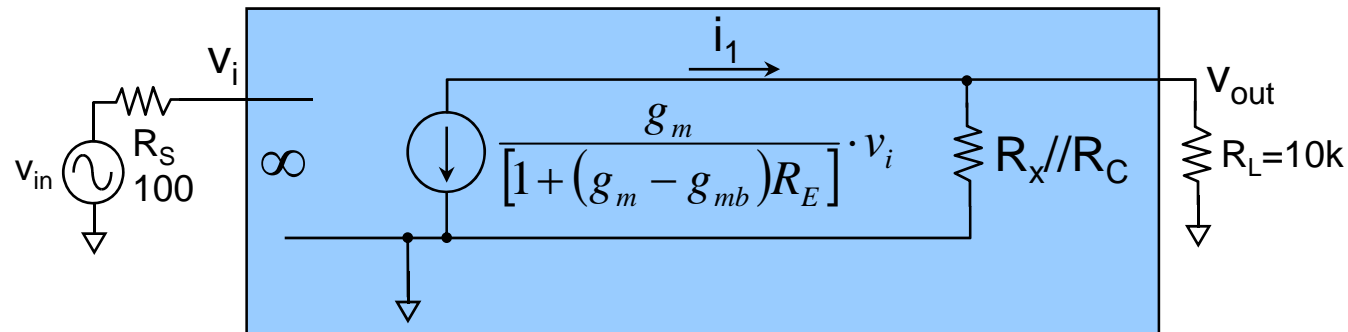CS with Source Degeneration – Two-Port Network (A_V)



$$v_i = v_{in} \quad i_1 = -\frac{g_m}{1 + (g_m - g_{mb})R_E} \times v_i$$

$$v_{out} = i_1 \times (R_{out} // R_L) = -\frac{g_m}{1 + (g_m - g_{mb})R_E} \times v_i \times (R_{out} // R_L)$$

$$\approx -v_{in} \times \frac{g_m}{1 + (g_m - g_{mb})R_E} \times [(R_C // R_x) // R_L]$$

$$\Rightarrow A_V \approx -\frac{g_m}{1 + (g_m - g_{mb})R_E} \times (R_C // R_L)$$


Characteristic of CE/CS with Emitter/Source Degeneration

- High input resistance
- High output resistance
- Lower Gain than CE and CS
- Polarity inversion

Effect of Capacitors

Consider CB amplifier example (Slide 6A-49):

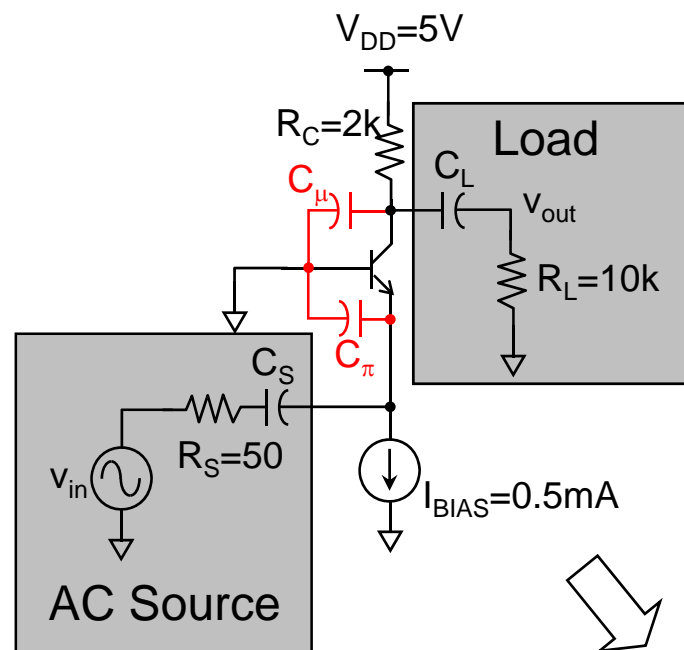- C_L and C_S are external capacitors added to the circuit, it is usually large ($\sim \mu\text{F}$ range)
- C_μ and C_π are **parasitic** capacitor inherent to the BJT device, it is usually small ($\sim \text{pF}$ range)




	Low freq ($\rightarrow \text{DC}$)	Mid freq	High freq
C_S, C_L	Open	Short	Short
C_μ, C_π	Open	Open	Short


Audio : $< 20\text{kHz}$

Video : $< 6\text{MHz}$

RF : $\sim \text{GHz}$

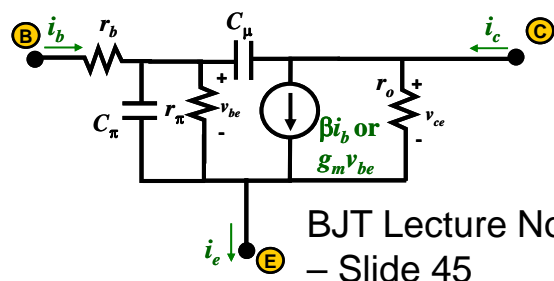


BJT Lecture Notes
– Slide 45

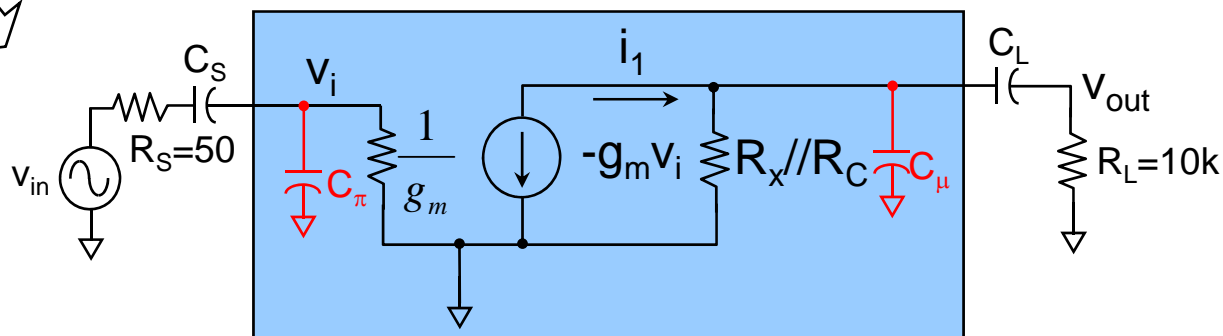


6B-44

Effect of Capacitors

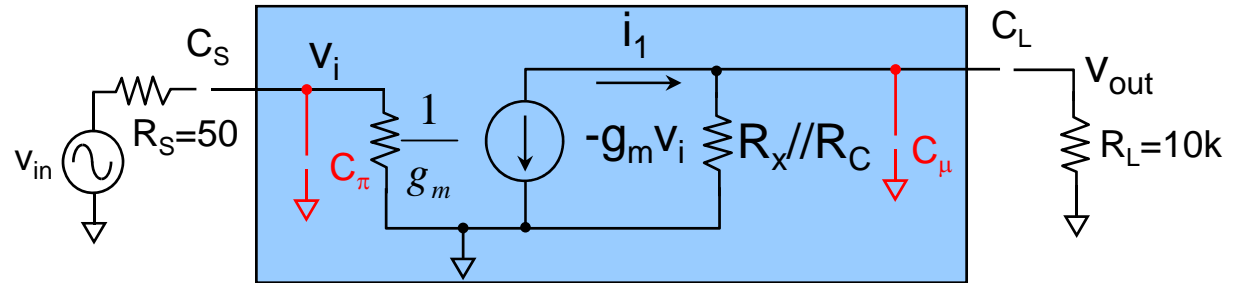
At low frequency,
 $C_S, C_L, C_\mu, C_\pi \rightarrow$ open circuit
 v_{out} isolated from $v_{in} \Rightarrow v_{out}=0$



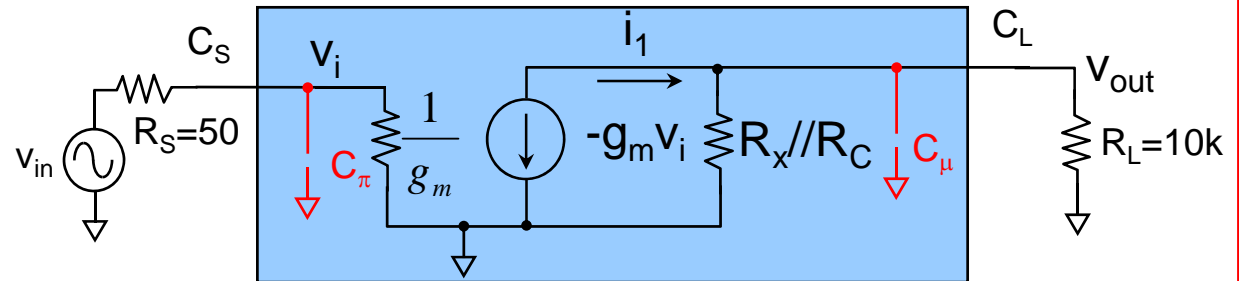
At middle frequency,
 $C_S, C_L \rightarrow$ short circuit
 $C_\mu, C_\pi \rightarrow$ open circuit
 2-port network $\Rightarrow v_{out} = A_v \times v_{in}$



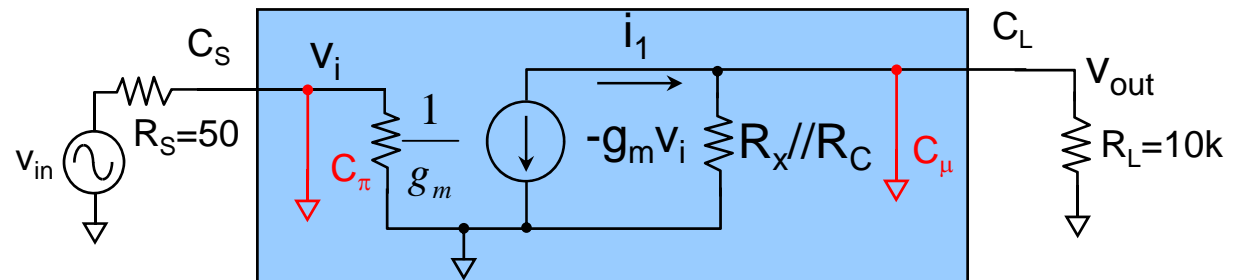At high frequency,
 $C_S, C_L \rightarrow$ short circuit
 $C_\mu, C_\pi \rightarrow$ short circuit
 v_{in} and v_{out} short to ground
 $\Rightarrow v_{out}=0$




Effect of Capacitors

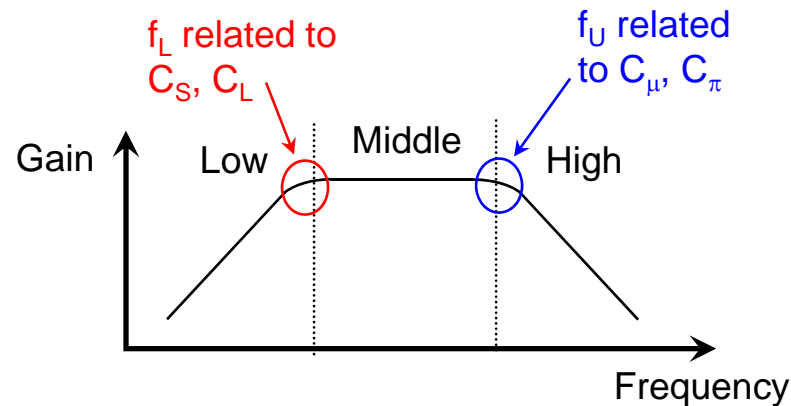


- C_S and C_L cause the gain to drop at low frequency due to open circuit at low frequency.
- C_μ and C_π cause the gain to drop at high frequency due to short circuit at high frequency.
- At the middle frequency, C_S and C_L are short circuit whereas C_μ and C_π are open circuit. The amplifier behaves like 2-port network with gain.
- The lower cut-off point (f_L), i.e. the frequency below which the gain starts to drop are related to RC time constant related to C_S and C_L .
- The upper cut-off point (f_U), i.e. the frequency above which the gain starts to drop are related to RC time constant related to C_μ and C_π .

Ideal versus Non-ideal Current Source


Ideal Current Source

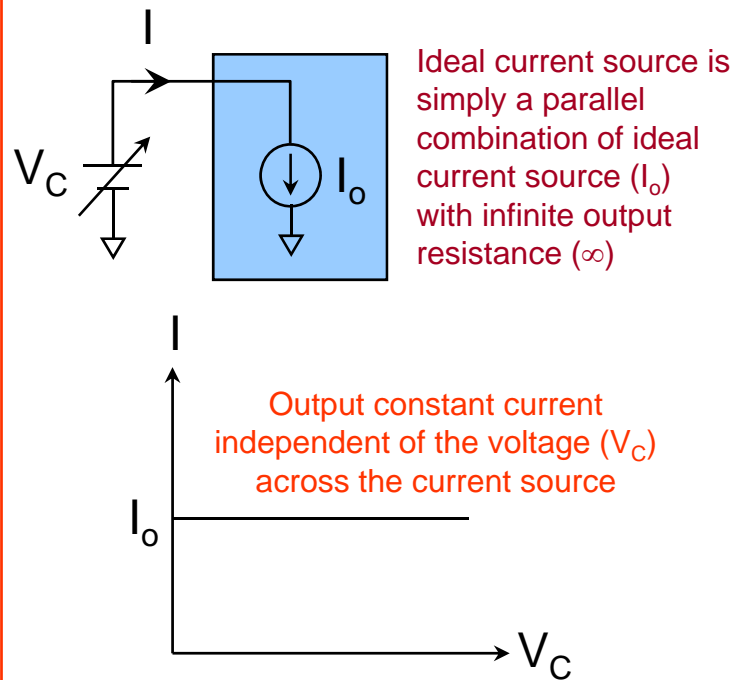


Non-ideal Current Source

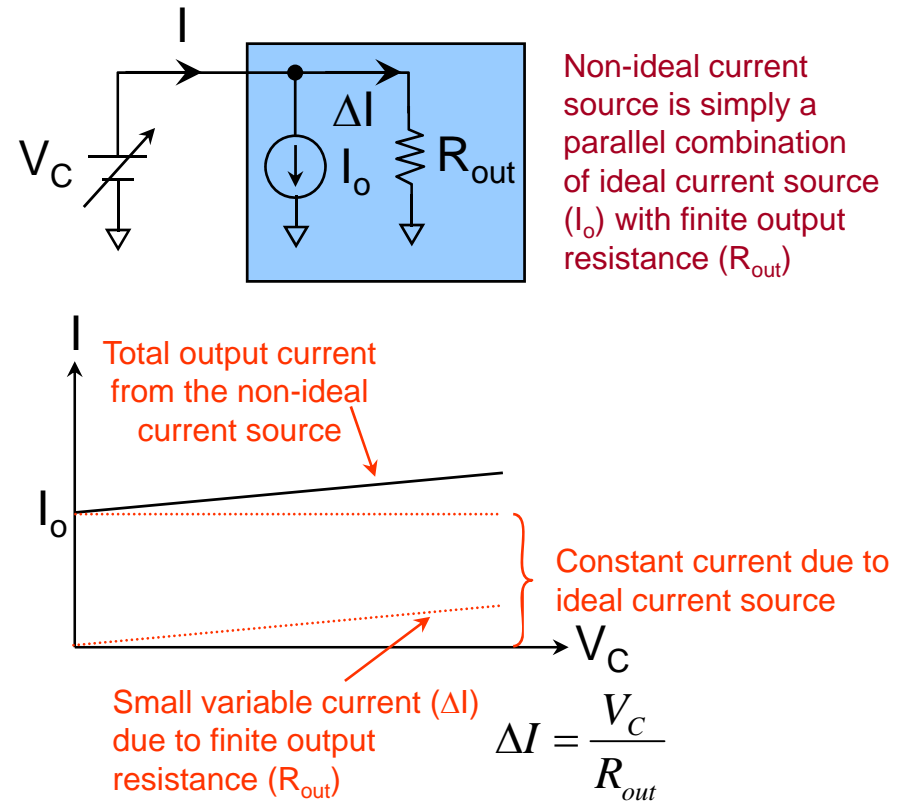


Transistor as Current Source

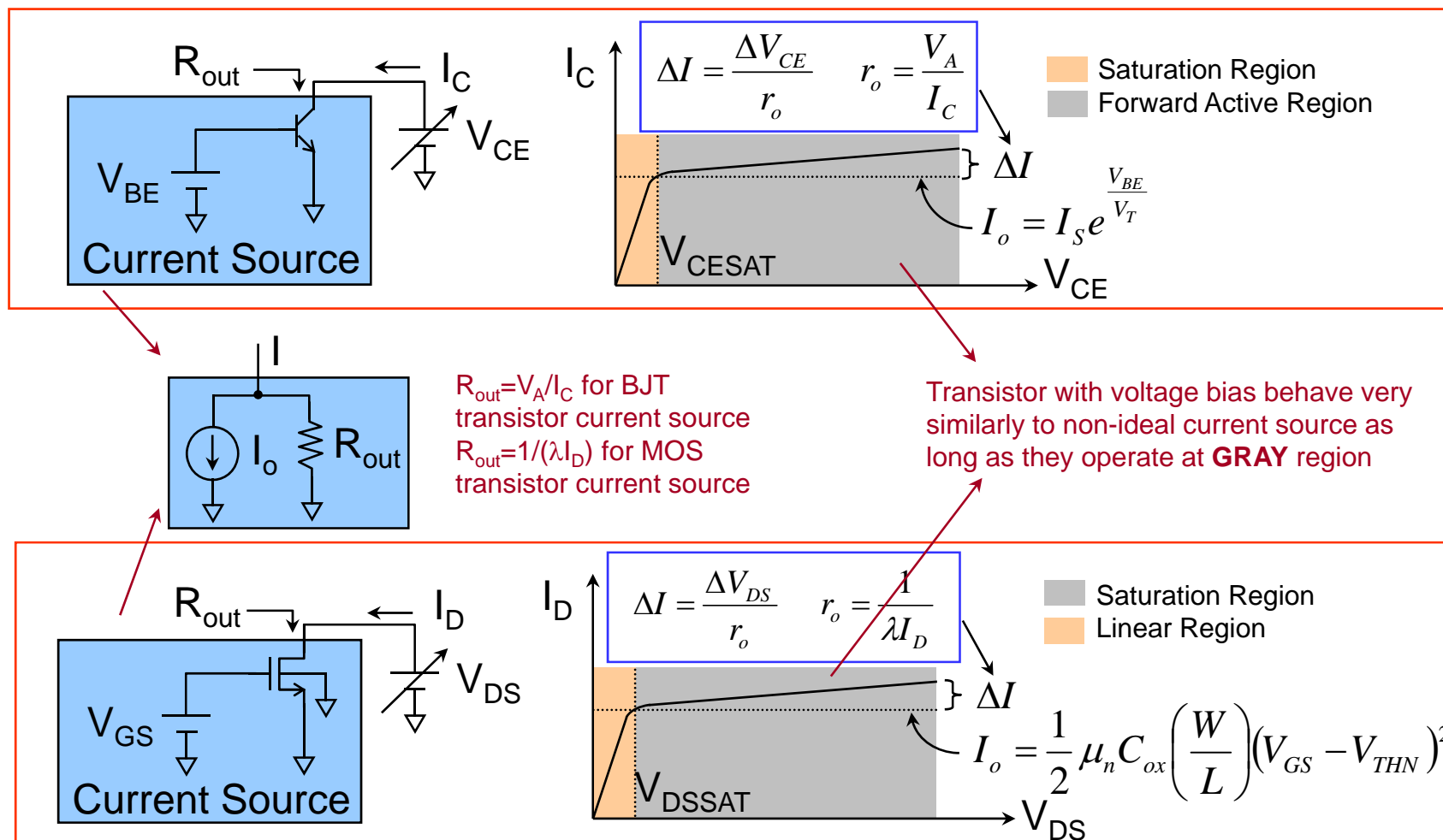

BJT Current Mirror

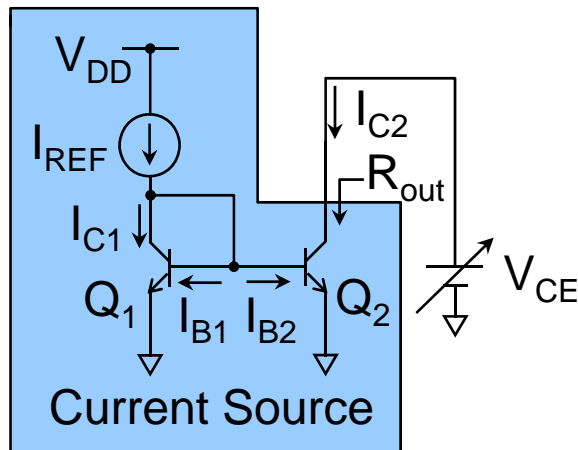

AC Analysis

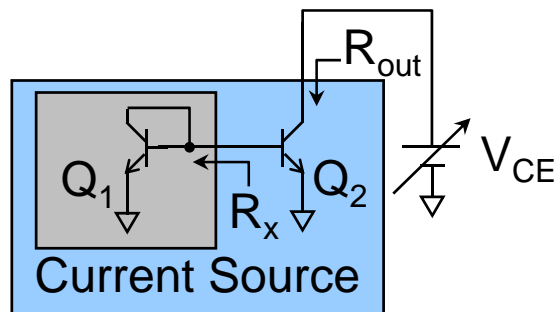

Determine DC Biasing

$$I_{REF} = I_{C1} + I_{B1} + I_{B2}$$

$$\because V_{BE1} = V_{BE2}$$

$$\Rightarrow I_{B1} = I_{B2} = \frac{I_{C1}}{\beta}$$

$$\Rightarrow I_{C2} \approx I_{C1} \approx \frac{\beta}{\beta + 2} I_{REF}$$

Determine AC small signal parameter


$$g_{m1} = g_{m2} = \frac{I_C}{V_T}$$

$$R_{out} = r_o = \frac{V_A}{I_C}$$

I_{C2} not exactly equal to I_{REF} due to finite current gain β


Look-up Table 1

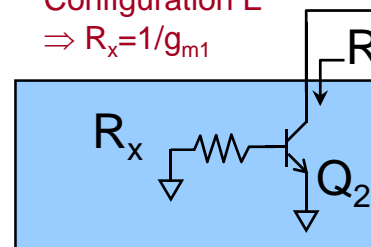Configuration E
 $\Rightarrow R_x = 1/g_{m1}$



Configuration B
with $R_E = 0$
 $\Rightarrow R_{out} = V_A/I_{C2}$

BJT Current Mirror

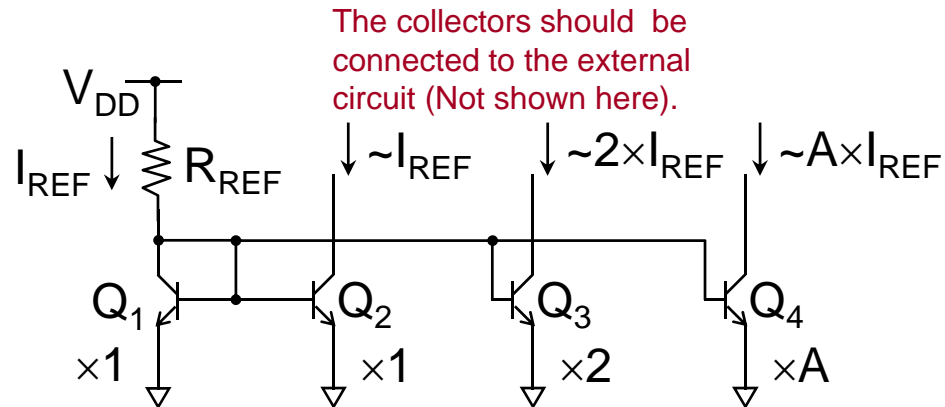

Because all BJTs share the same V_{BE} , the transistor currents are proportional to their corresponding area ratio

$$I_{REF} = \frac{V_{DD} - V_{BE}}{R_{REF}} \quad I_{REF} \text{ can be obtained easily through a resistor}$$


$$I_{C1} \approx I_{REF} = J_S e^{\frac{V_{BE}}{V_T}} \times \text{Area}$$

$$I_{C2} \approx I_{C1} \quad I_{C3} \approx 2 \times I_{C1}$$

$$I_{C4} \approx A \times I_{C1}$$

- Using same V_{BE} created from the reference branch, different current source can be created by laying out different area of BJT
- The current source is not identical to I_{REF} due to :
 - Finite current gain β
 - Finite output resistance r_o and different V_{CE} from the reference branch

MOS Current Mirror

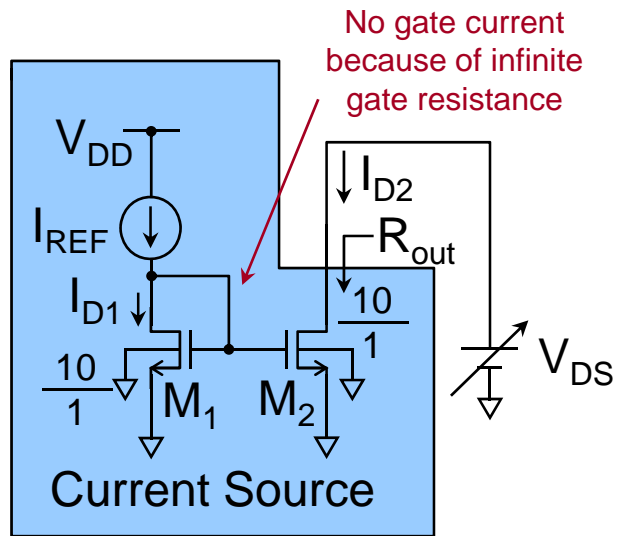

Determine DC Biasing

$$I_{REF} = I_{D1}$$

$$\therefore V_{GS1} = V_{GS2}$$

$$\Rightarrow I_{D1} = I_{D2} = I_{REF}$$



Determine AC small signal parameter

$$g_{m1} = g_{m2}$$


$$= \sqrt{2\mu_n C_{ox} \left(\frac{10}{1}\right) I_{D1}}$$

$$R_{out} = r_o = \frac{1}{\lambda I_{D2}}$$

AC Analysis

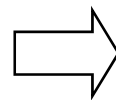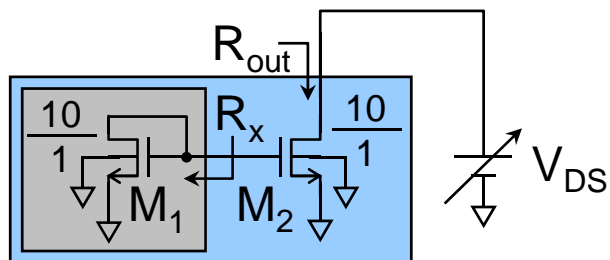

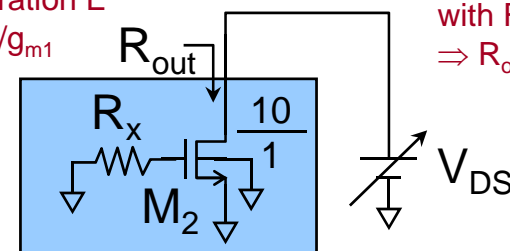Configuration E
 $\Rightarrow R_x = 1/g_{m1}$




Configuration B
with $R_E = 0$
 $\Rightarrow R_{out} = 1/\lambda I_{D2}$

Look-up
Table 2

MOS Current Mirror

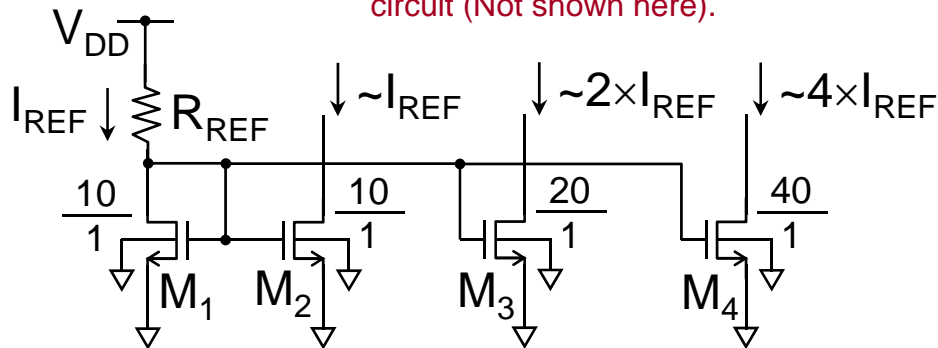The drain should be connected to the external circuit (Not shown here).



Because all MOSFETs share the same V_{GS} , the transistor currents are proportional to their corresponding sizing ratio


$$I_{REF} = \frac{V_{DD} - V_{GS}}{R_{REF}} \quad I_{REF} \text{ can be obtained easily through a resistor}$$

$$I_{D1} = I_{REF} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L} \right)_{M1} (V_{GS} - V_{THN})^2$$

$$I_{D2} = I_{D1} \quad I_{D3} = 2 \times I_{D1} \quad I_{D4} = 4 \times I_{D1}$$

- Using same V_{GS} created from the reference branch, different current source can be created by laying out different size of MOS transistors
- The current source is not identical to I_{REF} due to finite output resistance r_o and different V_{DS} from the reference branch

Conventional Resistor Biasing for CS

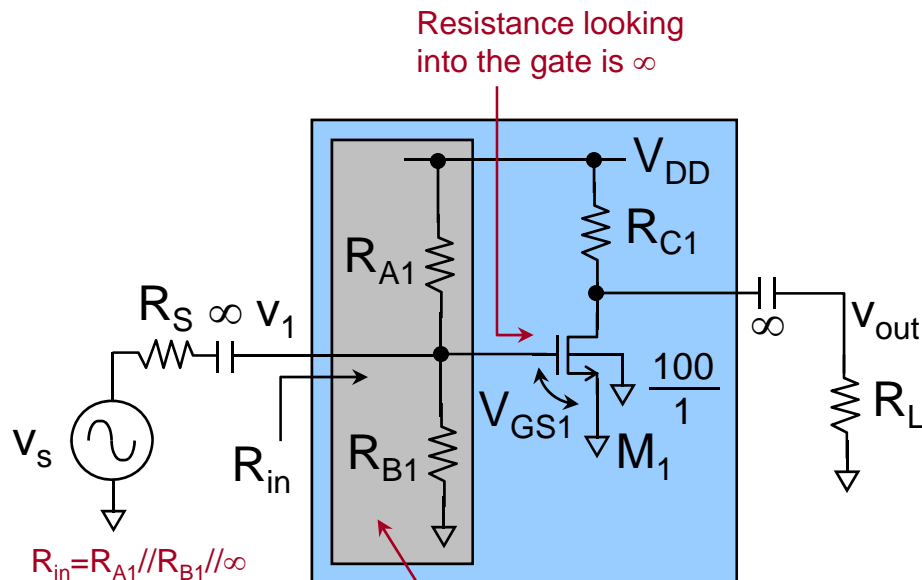

Commonly used technique for discrete circuit design. Difficult to gauge the M_1 current due to device parameters variation.

Biasing Network:

The resistors (R_{A1} , R_{B1}) determine the V_{GS} biasing and the V_{GS} biasing in turns determines the drain current (I_{D1}) of the transistor (M_1). All AC small signal parameters are related to the drain current of the transistor (I_{D1}).

Determine DC Biasing

$$I_{D1} = K(V_{GS1} - V_{THN})^2$$

In the design, the desired I_{D1} is usually given

$\Rightarrow V_{GS1}$ can be determined

$$\therefore V_{GS1} = V_{DD} \times \frac{R_{B1}}{R_{A1} + R_{B1}}$$

R_{A1} and R_{B1} can be determined

Determine AC Small Signal Parameter

$$g_{m1} = \sqrt{4KI_{D1}}$$

$$r_{o1} = \frac{1}{\lambda I_{D1}}$$

Current Mirror Biasing for CS

Determine DC Biasing

$$\because V_{GS1} = V_{GS2} \quad \text{and} \quad M_1 = M_2$$

$$\Rightarrow I_{D1} = I_{D2} = I_{REF}$$

$$I_{REF} = I_{D2} = K(V_{GS2} - V_{THN})^2$$


$$\Rightarrow V_{GS2} \text{ can be determined}$$

$$\because I_{REF} = \frac{V_{DD} - V_{GS2}}{R_{REF}}$$

$$\Rightarrow R_{REF} \text{ can be determined}$$

In the design, the desired I_{D1} is usually given

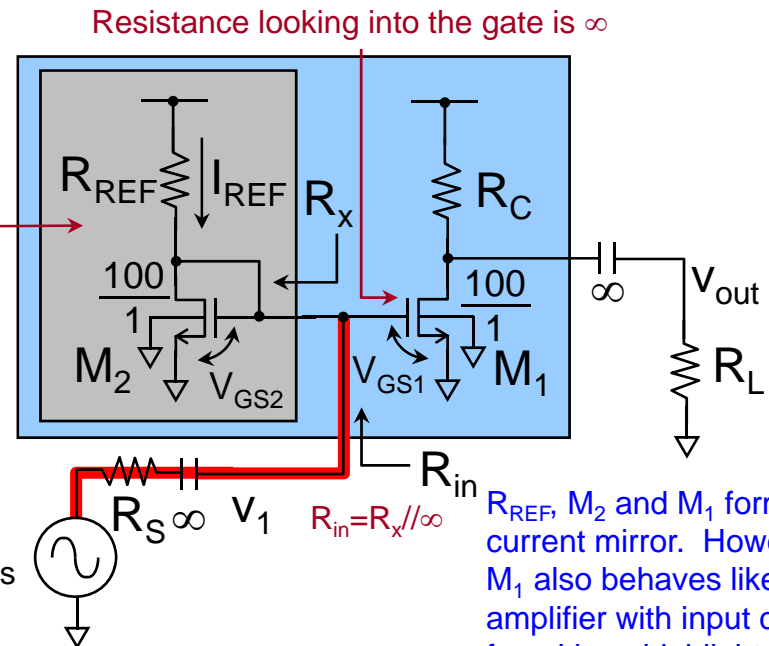Biasing Network:
The current mirror configuration ensure M_1 and M_2 has the same current ($I_{D1}=I_{D2}$). The current flow through M_2 ($I_{D2}=I_{REF}$) is determined by R_{REF} .



R_{REF} , M_2 and M_1 form a current mirror. However, M_1 also behaves like CS amplifier with input coming from V_s as highlighted in red.


Determine AC Small Signal Parameter

$$g_{m1} = \sqrt{4KI_{D1}}$$

$$r_{o1} = 1/(\lambda I_{D1})$$

Replace the DC voltage with AC ground

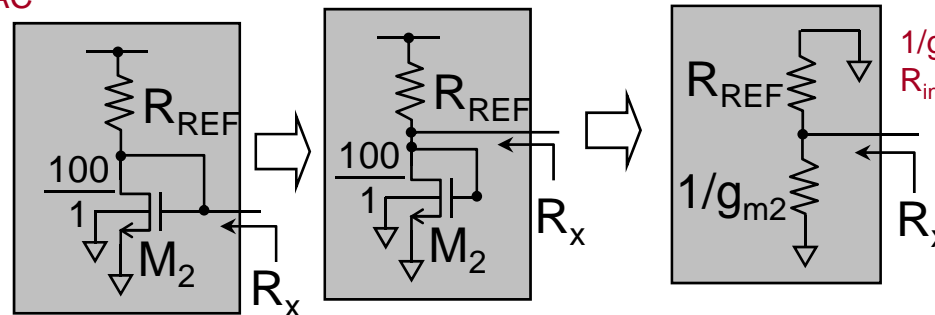Replace the diode-connected transistor M_2 with the equivalent resistor $1/g_{m2}$




R_{in} too small

Current Mirror Biasing for CS



Because there is no current flowing through R_B ($I_{RB}=0$)
 $\Rightarrow V_{GS1}=V_{GS2}$, i.e. there is no change in DC biasing condition by adding additional R_B

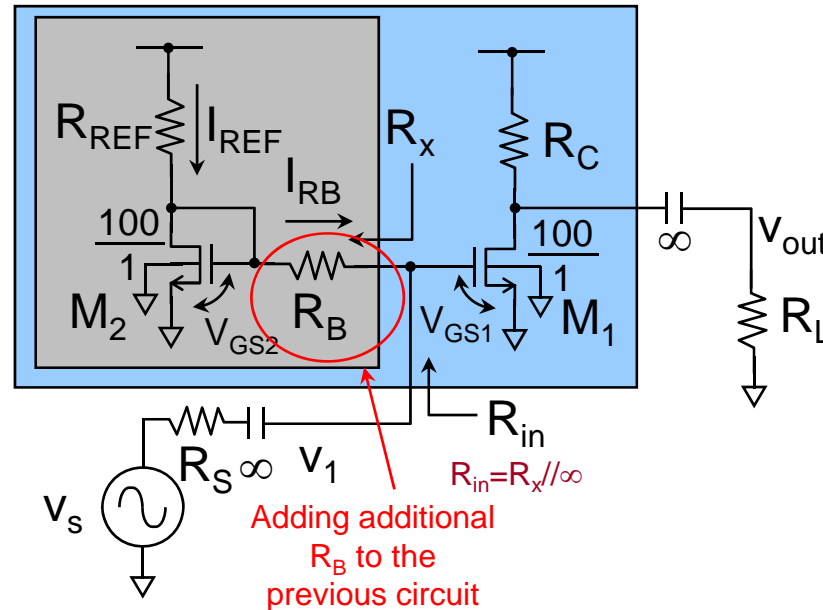Commonly used technique for integrated circuit design as R_{REF} is externally adjustable to give the desired current



Replace the DC voltage with AC ground

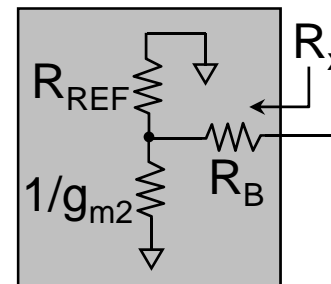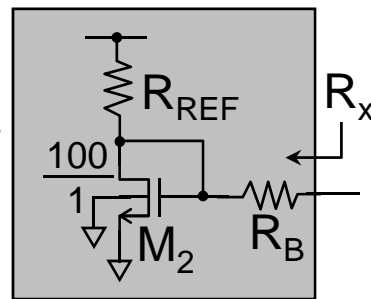Replace the diode-connected transistor M_2 with the equivalent resistor $1/g_{m2}$



$$R_x = R_B + (1/g_{m2}) // R_{REF}$$

$$\approx R_B + 1/g_{m2}$$

$$1/g_{m2} \ll R_{REF}$$

$$R_{in} = R_x$$

R_{in} can be made large by choosing large R_B

BJT Equivalent Resistance Summary (Table 1)

Blue: look into collector terminal

Red: look into base terminal

Green: look into emitter terminal






Conf	r_x	Conf	r_x	Conf	r_x
	$r_\pi + (1 + \beta)R_E$ $\approx r_\pi (1 + g_m R_E)$		$r_o \left\{ 1 + g_m \left[(r_\pi + R_S) \parallel R_E \right] \left(\frac{r_\pi}{r_\pi + R_S} \right) \right\}$ <p>If $R_S = 0$ and $r_\pi \ll R_E$ $\Rightarrow r_{x,\max} = r_o (\beta + 1)$</p>		$\frac{1}{g_m}$
	$\frac{R_S + r_\pi}{1 + \beta} \parallel r_o$ $\approx \frac{R_S}{1 + \beta} + \frac{1}{g_m}$		$\frac{1}{g_m} \times \frac{r_o + R_C}{r_o + \frac{R_C}{\beta}}$		

MOS Equivalent Resistance Summary (Table 2)

Blue: look into drain terminal

Red: look into gate terminal


Green: look into source terminal

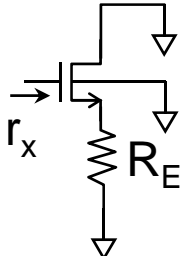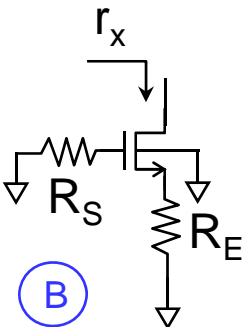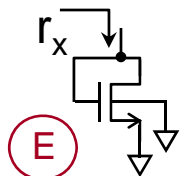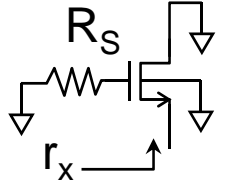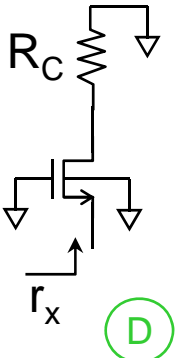Conf	r_x	Conf	r_x	Conf	r_x
 (A)	∞	 (B)	$r_o [1 + (g_m - g_{mb}) R_E]$	 (E)	$\frac{1}{g_m}$
 (C)	$\frac{1}{g_m - g_{mb}}$	 (D)	$\frac{1}{g_m - g_{mb}} \times \frac{r_o + R_C}{r_o}$		

BJT Amplifier Configurations


(Table 3)

BJT	G_m	A_v
CE (A)	g_m	Derive Based on 2-port Network
CB (B)	$-g_m$	Derive Based on 2-port Network
CC (C)	Too Complex To Be Useful	$\frac{g_m R_L}{1 + g_m R_L}$
CE with Emitter Degeneration (D)	$\frac{g_m}{1 + g_m R_E}$	Derive Based on 2-port Network

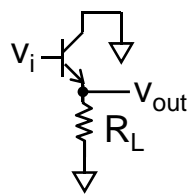

MOS Amplifier Configurations

(Table 4)

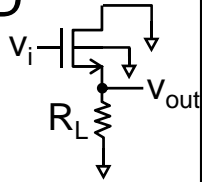MOS	G_m	A_v
CS (A)	g_m	Derive Based on 2-port Network
CG (B)	$-(g_m - g_{mb})$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network
CD (C) 	Too Complex To Be Useful	$\frac{g_m R_L}{1 + (g_m - g_{mb}) R_L} \approx \frac{g_m}{g_m - g_{mb}}$ <i>Drop g_{mb} if no body effect</i>
CS with R_E (D)	$\frac{g_m}{1 + (g_m - g_{mb}) R_E}$ <i>Drop g_{mb} if no body effect</i>	Derive Based on 2-port Network

Lecture Summary

- Analyze CC/CD, CS/CE with degeneration amplifiers.
- Analyze MOSFET/BJT current mirror

Reading Assignment

- **Reading: Reference Book (Sedra & Smith)**

Chapter 4, pp. 401 – 405, pp. 405 – 408. (CD)

Chapter 3, pp. 260 – 265. (CC)

Chapter 3, pp. 252 – 257. (CE with degeneration)

Chapter 4, pp. 399 – 401. (CS with degeneration)

Chapter 6, pp. 587 – 595. (BJT and MOS current mirror)